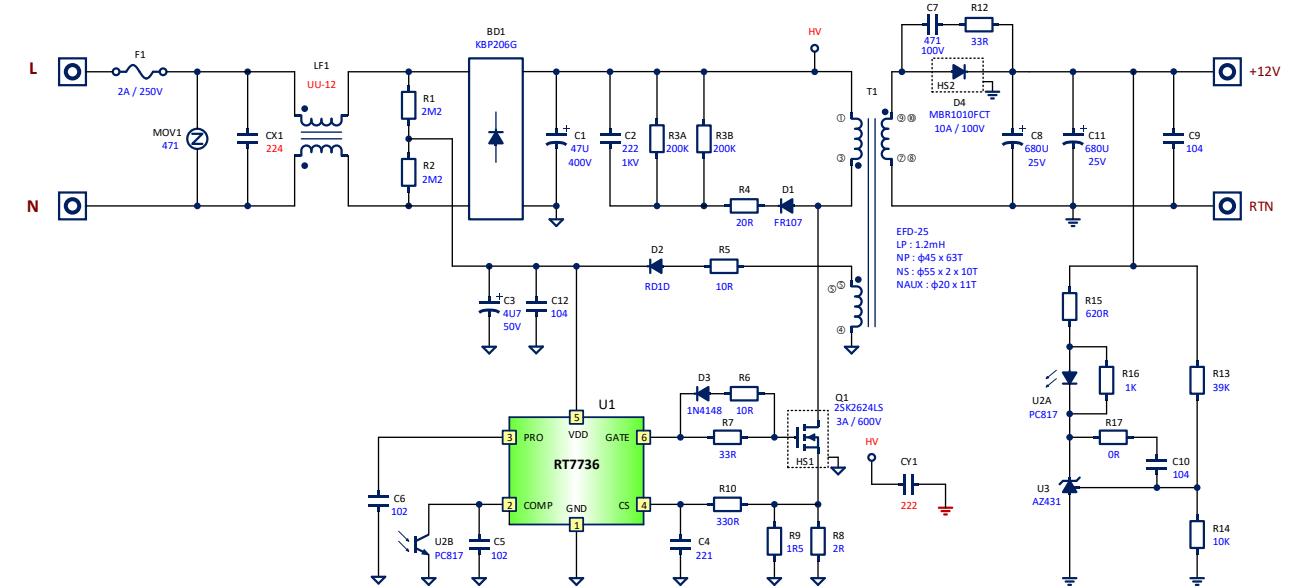


# 結合光耦和分路穩壓器的返馳電源回授設計

## Off-line Flyback Feedback Design with Optocoupler and Shunt Regulator

王信雄  
April, 2022



# Outline

---

- DC Steady-State Analysis of a Flyback Converter
- Peak Current Mode Control (PCMC) and Compensation
- Small-Signal Modeling of Flyback Converters
- Type II ( $2P_1Z$ ) Compensator Implemented by Optocoupler and Shunt Regulator
- Stray capacitance of Optocoupler

# Prerequisites

---

- Flyback Power Circuit Design
- Small-Signal Modeling of Switching Regulators
- Peak Current Model Control of Switching Converters

## References

1. [AN035\\_TW](#) “離線返馳轉換器設計重點”, 立錡科技
2. [AN017\\_TW](#) “離線返馳轉換器回授設計”, 立錡科技
3. “開關轉換器控制理論與設計實務”, 王信雄 / 立錡科技 · 城邦出版社

# Performance Related Technologies

---


## Power Processing Related

- Load Power
- Conversion Efficiency
- Output Voltage Ripple
- Weight and Volume
- Electromagnetic Interference (EMI)


## Control Related

- DC Regulation
- Line Rejection (Audio-Susceptibility)
- Load Rejection (Output Impedance)
- Response to a Step Load Change (Dynamic)
- Stability (Phase / Gain Margin)

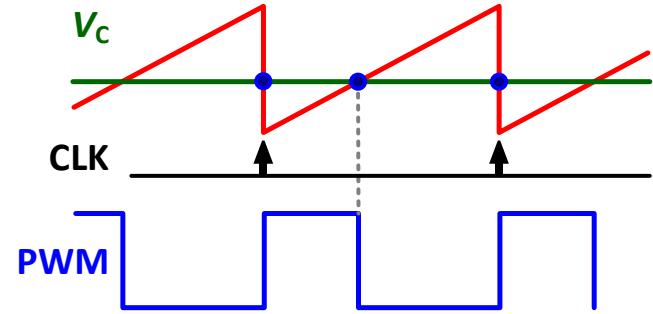
# Control Schemes of Switching Converters




Voltage Mode Control

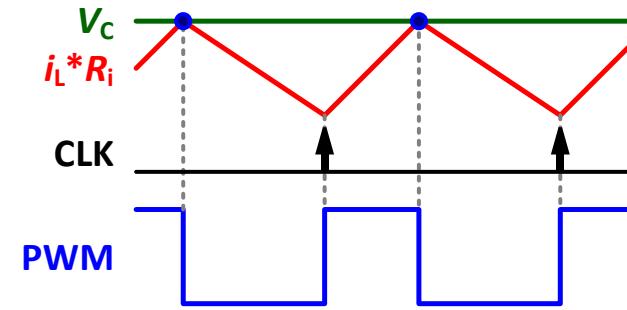


Peak Current Control

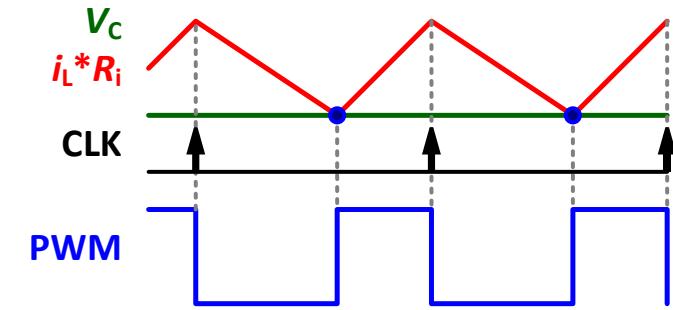


Valley Current Control

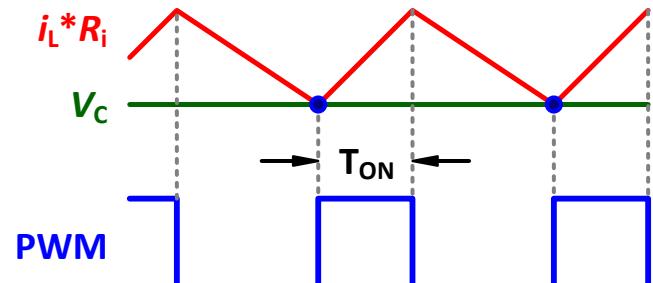

Constant ON Time Control

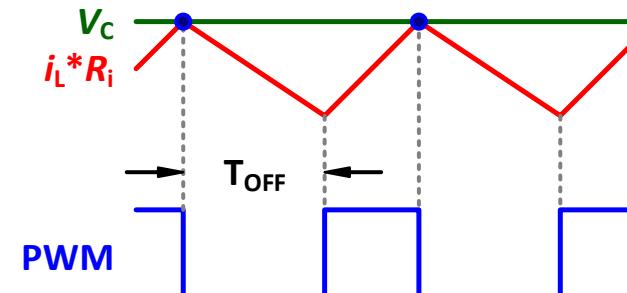


Constant OFF Time Control

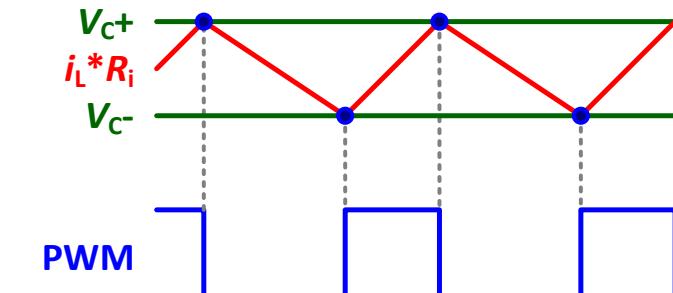


Hysteric Control

# Voltage-Mode-Control vs. Peak-Current-Mode Control


VMC

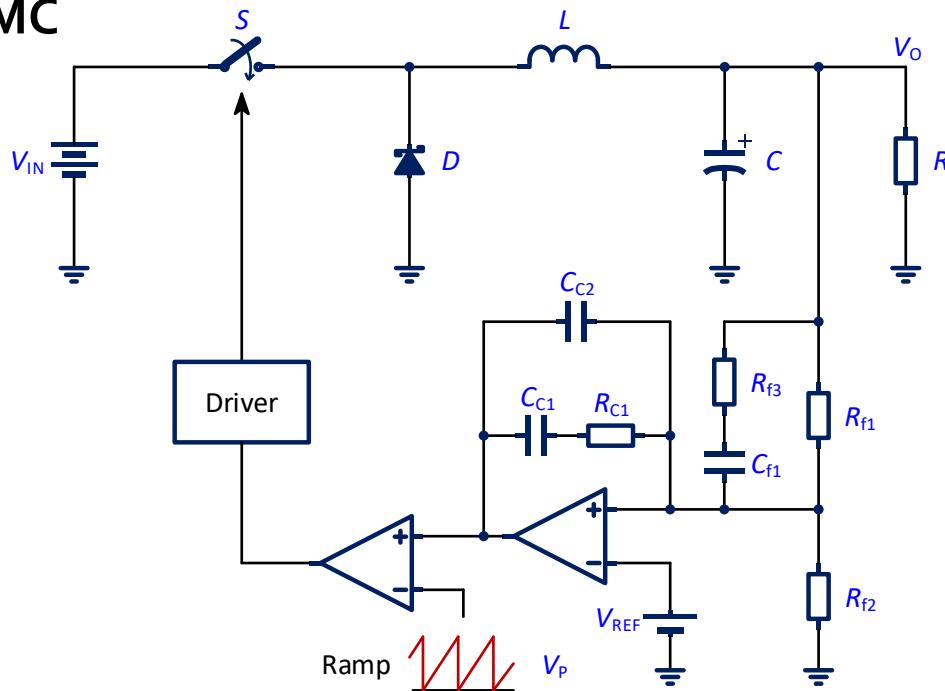

PCMC

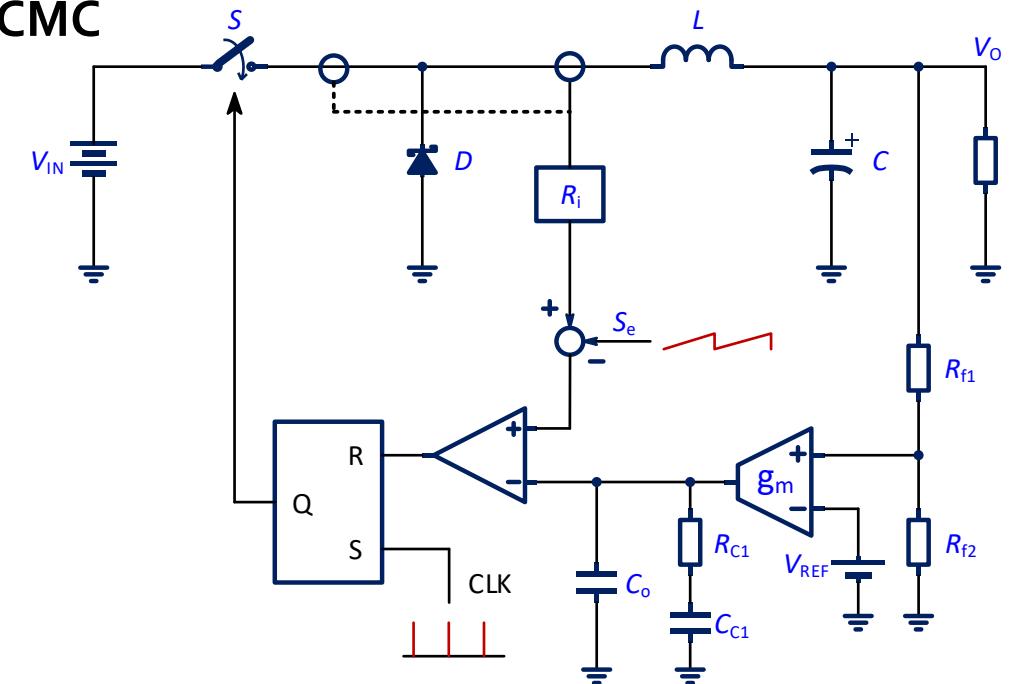


Clock

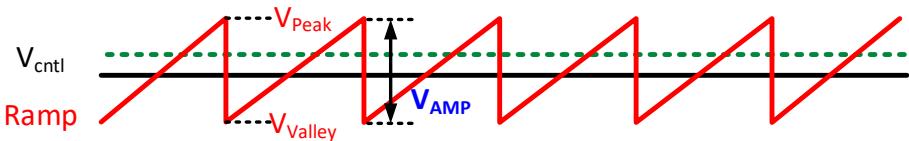

Latch Output

Clock

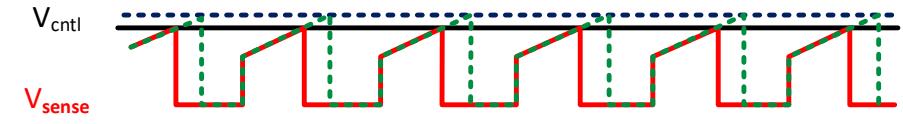

Latch Output

# Voltage-Mode-Control vs. Peak-Current-Mode Control

---


## Features of VMC

- Feedback from output voltage to ensure voltage regulation.
- Switching frequency is pre-defined by sawtooth wave.
- Right-Half-Plane Zero limits the crossover bandwidth in boost, buck-boost converters and their derived, such as flyback.
- **High noise immunity.**

## Features of PCMC

- Input voltage feed-forward, good open-loop line regulation
- Optimal large-signal behavior
- No conditional loop stability issues
- Automatic pulse-by-pulse current limiting
- Less complexity / cost
- Subharmonic instability (slope compensation needed)
- Accurate current sensing circuit is needed
- Noise immunity is worse when light load



# Flyback Converter (I)

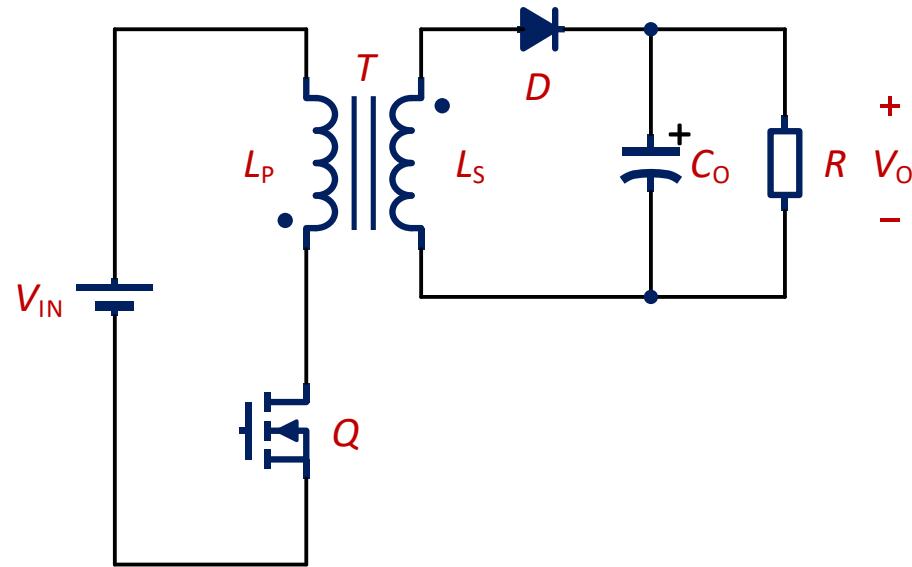


- Derived from Buck-Boost Converter with Coupled Inductor.
- Pulsating Currents in both Input and Output Sides.
- Right-Half-Plane-Zero Exists in Control to Output Transfer Function.
- Peak-Current-Mode-Control is usually Applied.
- Transformer (Coupled-Inductor) Design is similar with Power Inductor.

# Flyback Converter (II)


C.C.M.

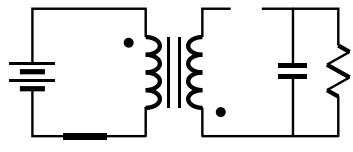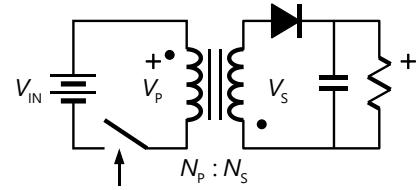



Switch "ON" period

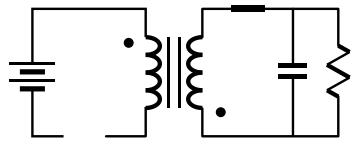


Switch "OFF" period

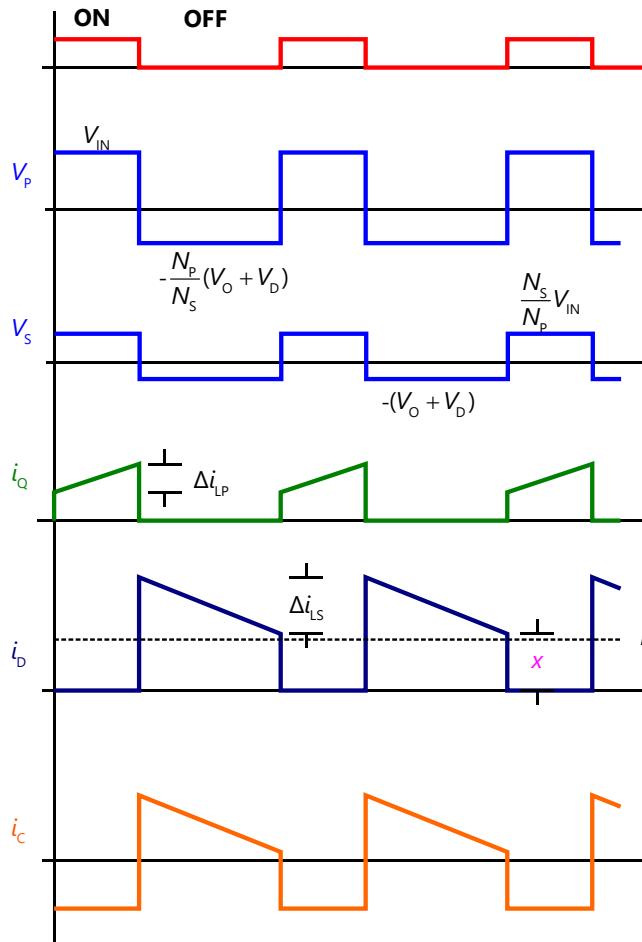


D.C.M.

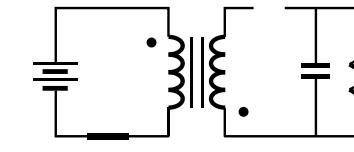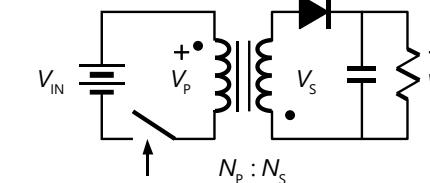

Switch "ON" period

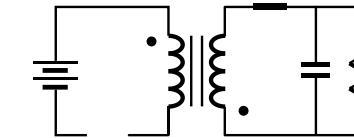

Switch "OFF" period

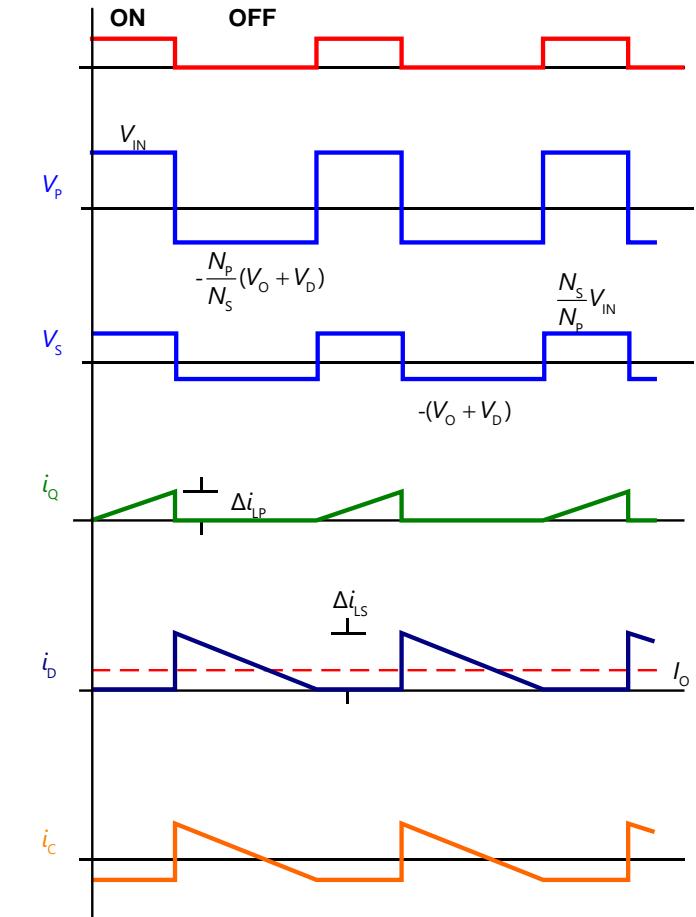


# Flyback Converter (III)

Volt-Sec Balance :

$$\frac{N_p}{N_s} \cdot \frac{(V_o + V_d)}{V_{IN}} = \frac{D}{1-D}$$

or

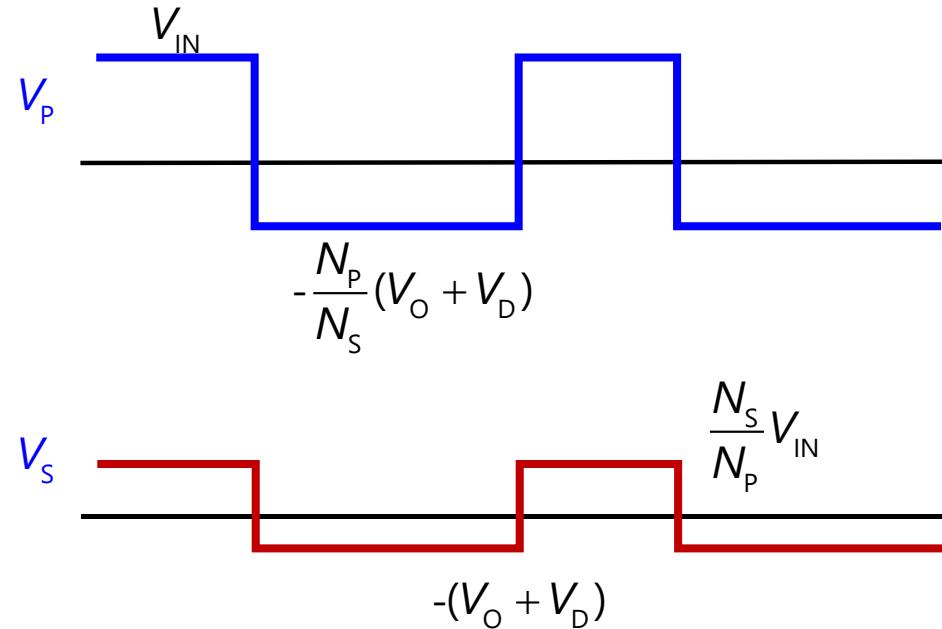
$$D = \frac{\frac{N_p}{N_s} \cdot (V_o + V_d)}{V_{IN} + \frac{N_p}{N_s} \cdot (V_o + V_d)}$$



- Duty Cycle depends on input and output voltage only.
- Duty Cycle can be adjusted by transformer turns ratio.
- For minimum input voltage, once turns ratio is fixed, the maximum duty cycle is defined.

# Flyback Converter (IV)

## Primary Current

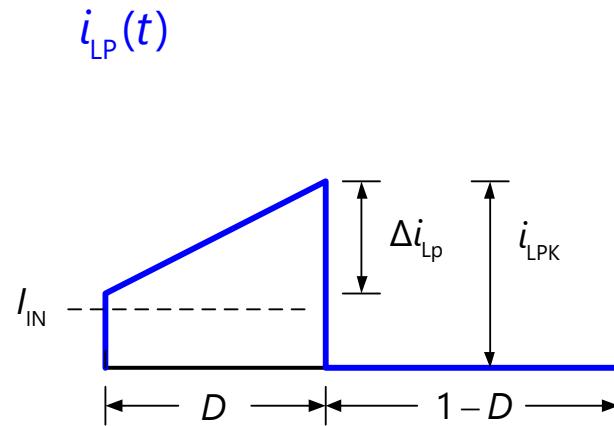

$$\Delta i_{LP} = \frac{V_{IN}}{L_P} \cdot D T_S$$


$$I_Q = I_{IN} = \frac{1}{2} D \cdot (2i_{LPK} - \Delta i_{LP})$$

$$i_{LPK} = \frac{N_s}{N_p} i_{LSK}$$

$$\Delta i_{LP} = \frac{N_s}{N_p} \Delta i_{LS}$$

$$i_{LP,\text{rms}} = \sqrt{D \cdot \left[ i_{LPK} \cdot (i_{LPK} - \Delta i_{LP}) + \frac{1}{3} \Delta i_{LP}^2 \right]}$$

## Secondary Current

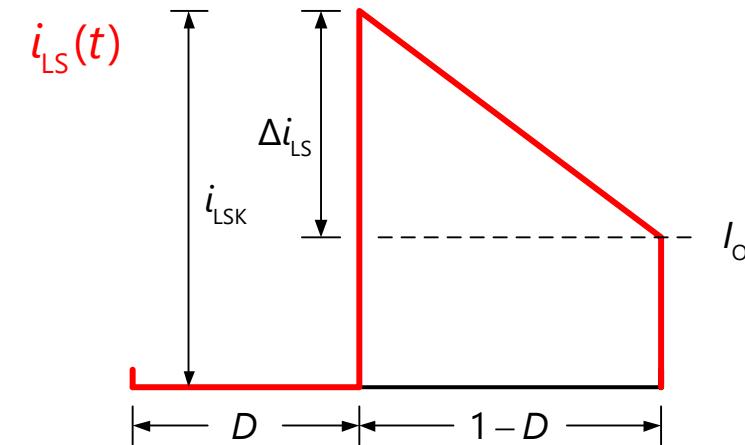

$$\Delta i_{LS} = \frac{(V_o + V_d)}{L_s} \cdot (1 - D) T_S$$

$$I_D = I_O = \frac{1}{2} (1 - D) \cdot (2i_{LSK} - \Delta i_{LS})$$

$$I_{IN} = \left( \frac{D}{1 - D} \right) \cdot \frac{N_s}{N_p} I_O$$


$$i_{LS,\text{rms}} = \sqrt{(1 - D) \cdot \left[ i_{LSK} \cdot (i_{LSK} - \Delta i_{LS}) + \frac{1}{3} \Delta i_{LS}^2 \right]}$$

# DC Analysis (PCMC Flyback)

$f_s = 100\text{kHz}$ ,  $Q$  &  $D$  are ideal.

CTR of PC817C = 50%

Find  $V_O$ ,  $V_C$  and  $V_{FB}$

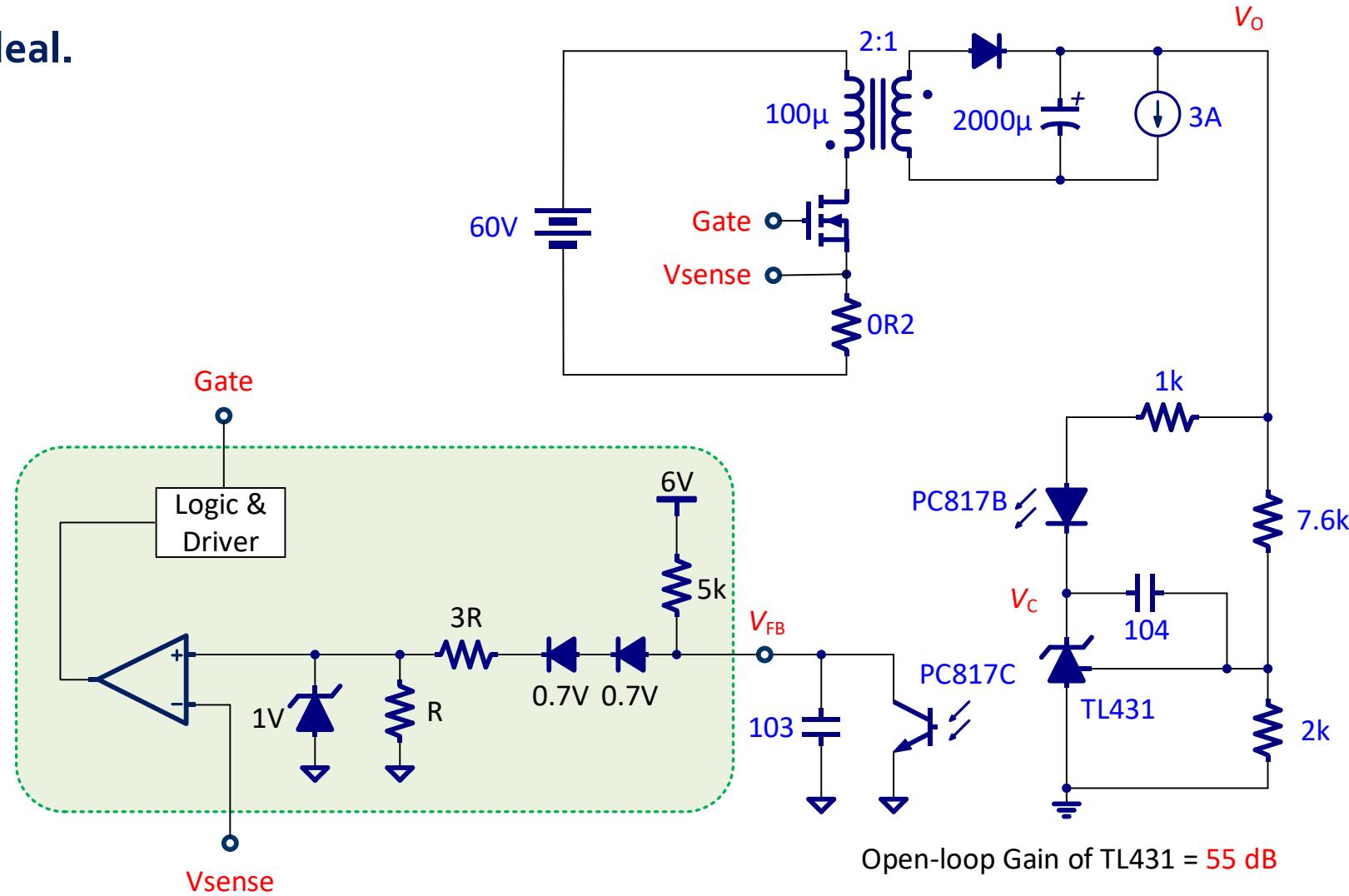

# Operating Point Calculation (I)

$$L_s = \frac{100\mu}{2^2} = 25\mu(\text{H}) \quad V_o \approx 2.5 \cdot \frac{7.6k + 2k}{2k} = 12(\text{V})$$

Assume C.C.M. operation, calculate duty cycle,


$$D = \frac{nV_o}{(V_{IN} + nV_o)} = \frac{2 \cdot 12}{(60 + 2 \cdot 12)} = 0.286$$

From secondary current,

$$I_o = (2 \cdot I_x + \Delta i_{LS}) \cdot \frac{(1-D)}{2} \quad \text{and} \quad \Delta i_{LS} = \frac{V_o}{L_s} \cdot (1-D) T_s$$

$$\Delta i_{LS} = 3.429(\text{A}) \quad I_x = 2.486(\text{A}) \quad (\text{C.C.M. is ensured})$$
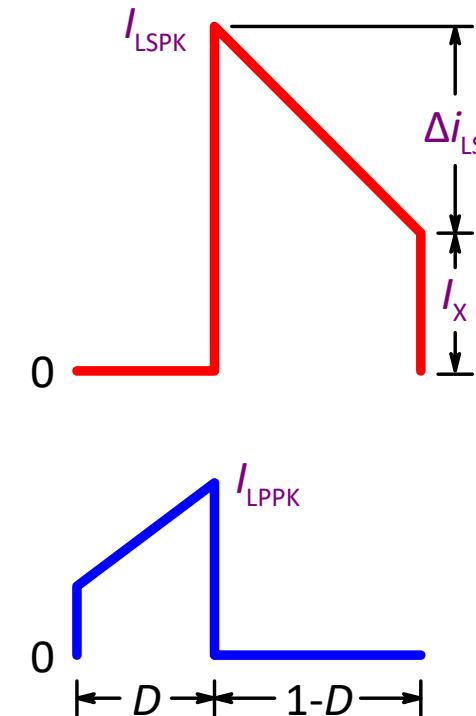
$$\Rightarrow I_{LSPK} = I_x + \Delta i_{LS} = 5.914(\text{A}) \quad I_{LPPK} = \frac{I_{LSPK}}{n} = 2.957(\text{A})$$



## Operating Point Calculation (II)

---

Sensing voltage :  $V_{SENSE} = I_{LPPK} \cdot R_s = 0.591(V)$

From PCMC theory,  $V_{SENSE} = [V_{FB} - (2 \cdot 0.7)] \cdot \frac{R}{4R} \Rightarrow V_{FB} = 3.766(V)$

Current in opto-transistor,  $I_{TR} = \frac{6 - V_{FB}}{5k} = 0.447m(A)$

Current in opto-diode,  $I_{LED} = \frac{I_{TR}}{CTR} = 0.894m(A)$

Assume voltage drop on opto-diode is 1V, then

$$V_C = 12 - I_{LED} \cdot 1k - 1 = 10.106(V)$$

Open-loop gain of TL431 is 560 (55dB), thus voltage on REF pin is

$$V_{REF} = 2.495 - \frac{10.106}{560} = 2.477(V)$$


Output voltage,  $V_o = 2.477 \cdot \frac{7.6k + 2k}{2k} = 11.889(V)$

# Off-line Flyback Converter

---

- Right-Half-Plane-Zero → Peak-Current-Mode Control
- Subharmonic Instability for  $D > 0.5$
- Slope Compensation is needed for  $D > 0.5$
- Primary-side Controller, Secondary-side Output
- Opto-coupler is often adopted
- Shunt Regulator (TL431) acts role of Error Amp +  $V_{REF}$
- Type II Compensator Implementation
- Parasitics of Opto-Coupler Issue


# PCMC Flyback Controller

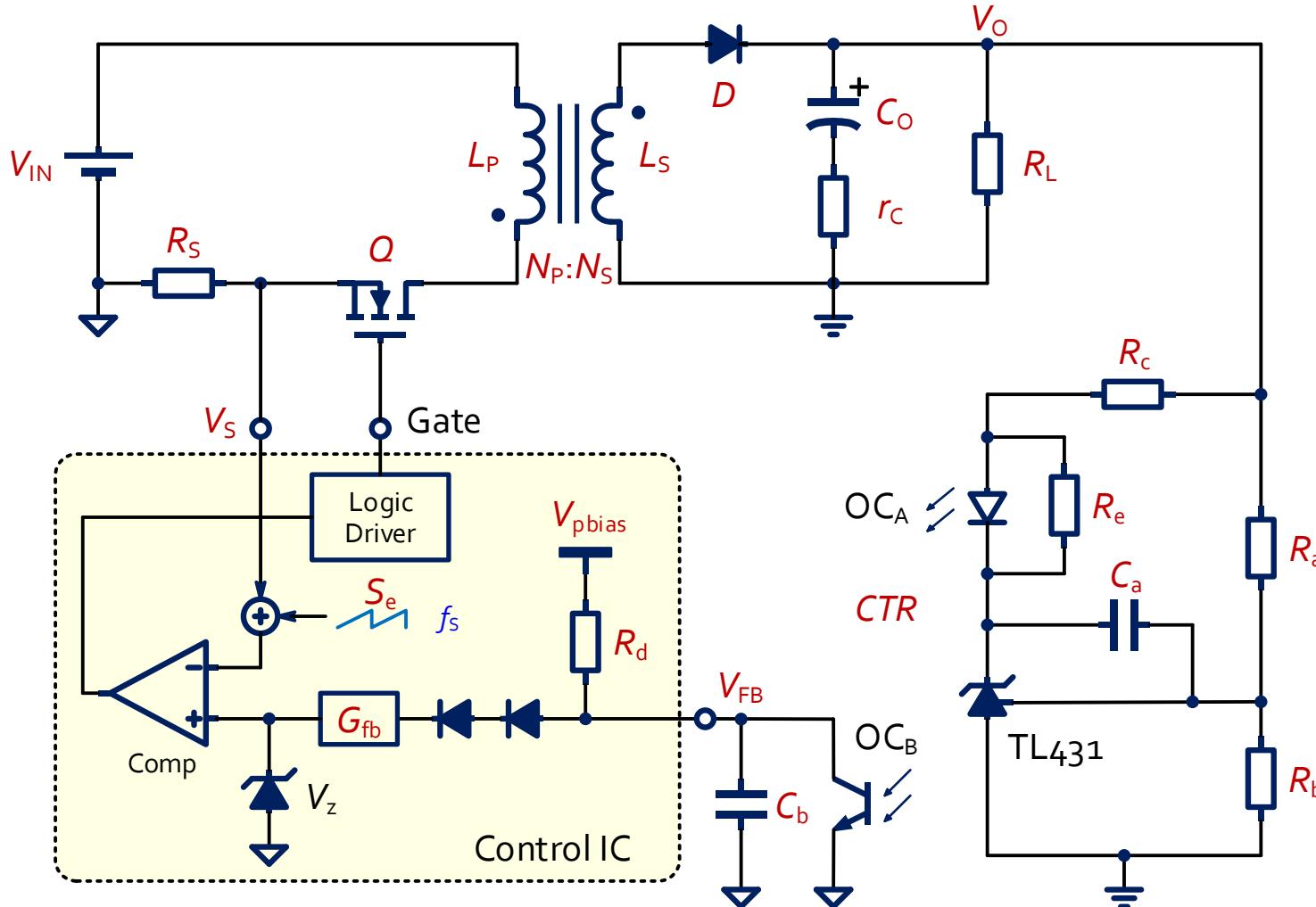

- PWM / PFM
- Slope Compensation
- No Error Amplifier and Reference

Shunt Regulator + Optocoupler

# Small-Signal Model for PCMC Converters

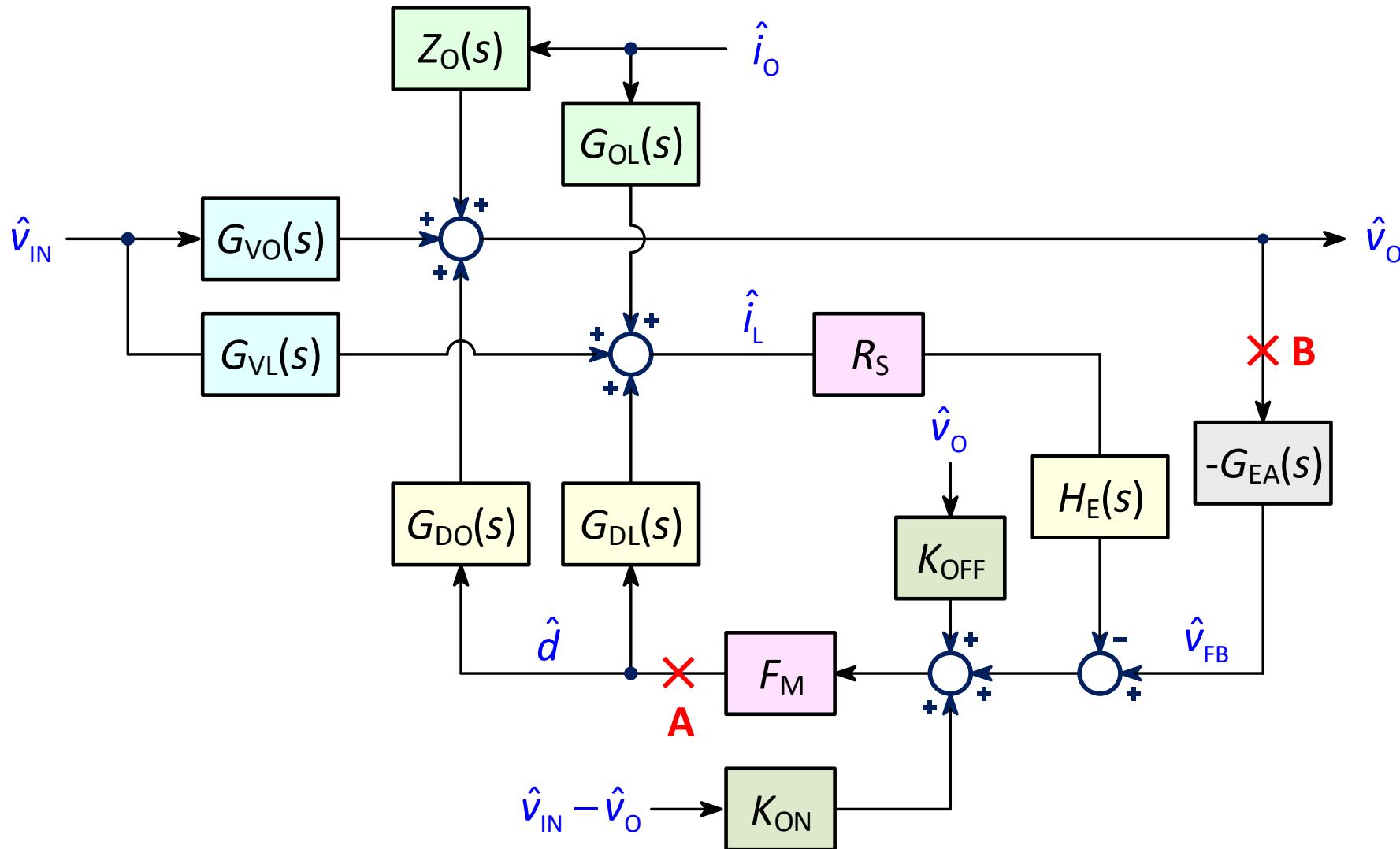

# Small-Signal Transfer Functions of C.C.M. Flyback Converter

$G_{DO}(s)$	$\frac{\hat{v}_o}{\hat{d}}$	$\frac{N_s}{N_p} \cdot \frac{V_{IN} \cdot (1+s \cdot C_o \cdot r_c) \cdot \left[ 1 - s \cdot \frac{D \cdot L_p}{R_L \cdot (1-D)^2} \cdot \left( \frac{N_s}{N_p} \right)^2 \right]}{s^2 \cdot \left( \frac{N_s}{N_p} \right)^2 \cdot L_p \cdot C_o + s \cdot \left[ \frac{L_p}{R_L} \cdot \left( \frac{N_s}{N_p} \right)^2 + C_o \cdot r_c \cdot (1-D)^2 \right] + (1-D)^2}$
$G_{DL}(s)$	$\frac{\hat{i}_L}{\hat{d}}$	$\left( \frac{N_s}{N_p} \right)^2 \cdot \frac{V_{IN} \cdot (1+D)}{R_L \cdot (1-D)} \cdot \frac{1 + s \cdot \frac{C_o \cdot R_L}{1+D}}{s^2 \cdot \left( \frac{N_s}{N_p} \right)^2 \cdot L_p \cdot C_o + s \cdot \left[ \frac{L_p}{R_L} \cdot \left( \frac{N_s}{N_p} \right)^2 + C_o \cdot r_c \cdot (1-D)^2 \right] + (1-D)^2}$
$G_{VO}(s)$	$\frac{\hat{v}_o}{\hat{v}_{IN}}$	$\frac{N_s \cdot D \cdot (1-D)}{N_p} \cdot \frac{1 + s \cdot C_o \cdot r_c}{s^2 \cdot \left( \frac{N_s}{N_p} \right)^2 \cdot L_p \cdot C_o + s \cdot \left[ \frac{L_p}{R_L} \cdot \left( \frac{N_s}{N_p} \right)^2 + C_o \cdot r_c \cdot (1-D)^2 \right] + (1-D)^2}$
$G_{VL}(s)$	$\frac{\hat{i}_L}{\hat{v}_{IN}}$	$\left( \frac{N_s}{N_p} \right)^2 \cdot \frac{D}{R_L} \cdot \frac{1 + s \cdot C_o \cdot R_L}{s^2 \cdot \left( \frac{N_s}{N_p} \right)^2 \cdot L_p \cdot C_o + s \cdot \left[ \frac{L_p}{R_L} \cdot \left( \frac{N_s}{N_p} \right)^2 + C_o \cdot r_c \cdot (1-D)^2 \right] + (1-D)^2}$
$Z_o(s)$	$\frac{\hat{v}_o}{\hat{i}_o}$	$\left( \frac{N_s}{N_p} \right)^2 \cdot \frac{s \cdot L_p \cdot (1+s \cdot C_o \cdot r_c)}{s^2 \cdot \left( \frac{N_s}{N_p} \right)^2 \cdot L_p \cdot C_o + s \cdot \left[ \frac{L_p}{R_L} \cdot \left( \frac{N_s}{N_p} \right)^2 + C_o \cdot r_c \cdot (1-D)^2 \right] + (1-D)^2}$
$G_{OL}(s)$	$\frac{\hat{i}_L}{\hat{i}_o}$	$\frac{N_s \cdot (1-D)}{N_p} \cdot \frac{1 + s \cdot C_o \cdot r_c}{s^2 \cdot \left( \frac{N_s}{N_p} \right)^2 \cdot L_p \cdot C_o + s \cdot \left[ \frac{L_p}{R_L} \cdot \left( \frac{N_s}{N_p} \right)^2 + C_o \cdot r_c \cdot (1-D)^2 \right] + (1-D)^2}$

$K_{ON}$		$-\frac{D \cdot T_s \cdot R_s}{L_p} \cdot \left( 1 - \frac{D}{2} \right)$
$K_{OFF}$		$\frac{(1-D)^2 \cdot T_s \cdot R_s}{2 \cdot L_p}$
$F_M$	$\frac{\hat{d}}{\hat{v}_{FB}}$	$\frac{1}{(S_N + S_E) \cdot T_s}$
$H_E(s)$		$\frac{s \cdot T_s}{e^{s \cdot T_s} - 1}$
$G_{FB}$		Constant Gain
$G_{COMP}(s)$	$\frac{\hat{v}_{FB}}{\hat{v}_o}$	To be Designed
$H_E(s)$	$\approx 1 - \frac{s}{\omega_n \cdot \frac{2}{\pi}} + \frac{s^2}{\omega_n^2}$	$\omega_n = \frac{\pi}{T_s}$

- Small-signal model is DC operating point dependent.

# Control to Output Transfer Function of PCMC Flyback

---

$V_{FB}$  to Output :  $\frac{\hat{v}_o(s)}{\hat{v}_{FB}(s)} = \frac{G_{FB} \cdot F_M \cdot G_{DO}(s)}{1 + F_M \cdot [R_S \cdot H_E(s) \cdot G_{DL}(s) - K_{OFF} \cdot G_{DO}(s)]}$

Approximated :  $\frac{\hat{v}_o(s)}{\hat{v}_{FB}(s)} \approx G_{DC} \cdot \frac{\left(1 + \frac{s}{\omega_z}\right) \cdot \left(1 - \frac{s}{\omega_{ZRHP}}\right)}{1 + \frac{s}{\omega_p}} \cdot \frac{1}{1 + \frac{s}{\omega_n \cdot Q_p} + \frac{s^2}{\omega_n^2}}$

Dr. Ray Ridley, "A Small-Signal Model for Current Mode Control"

$$G_{DC} = \frac{R_L}{R_S} \cdot \frac{G_{FB}}{\left(\frac{1+D}{1-D}\right) \cdot \frac{N_S}{N_P} + \frac{R_L \cdot T_S}{L_P} \cdot m_C \cdot (1-D)^2 \cdot \left(\frac{N_P}{N_S}\right)}$$

$$\omega_z = \frac{1}{C_O \cdot r_C}$$

$$m_C = 1 + \frac{S_E}{S_N}$$

$$\omega_p = \frac{1+D}{C_O \cdot R_L} + \frac{m_C \cdot T_S}{L_P \cdot C_O} \cdot \left(\frac{N_P}{N_S}\right)^2 \cdot (1-D)^3$$

$$\omega_{ZRHP} = \frac{R_L \cdot (1-D)^2}{L_P \cdot D} \cdot \left(\frac{N_P}{N_S}\right)^2$$

$$\omega_n = \frac{\pi}{T_S}$$

$$Q_p = \frac{1}{\pi \cdot [m_C \cdot (1-D) - 0.5]}$$

# Transfer Functions

---

## Definitions

$D$  = duty cycle

$f_s$  = switching frequency

$M = \frac{n \cdot V_o}{V_{IN}}$  = conversion ratio

$n = \frac{N_p}{N_s}$  = transformer turns ratio

$\tau_L = \frac{2 \cdot L_p \cdot f_s}{n^2 \cdot R_L}$

$S_N = \frac{V_{IN}}{L_p} \cdot R_S$  = on-time slope, V/sec

$S_E$  = external ramp slope, V/sec

$G_{FB} = \frac{\hat{V}_{RS}}{\hat{V}_{FB}}$  = small-signal gain (eg.  $\frac{1}{3}$ )

# Small-Signal Transfer Function of C.C.M. Flyback

---

- The flyback converter operated in CCM current-mode is a 3<sup>rd</sup>-order system. It features a low frequency pole  $\omega_{P_1}$ , followed by a double pole located at half the switching frequency.
- These two poles are affected by a quality coefficient,  $Q_P$ , that can create subharmonic oscillations in some cases. To prevent this problem, ramp or slope compensation has to be implemented :
- An artificial ramp of  $S_E$  slope is injected on the current-sense signal to oppose the duty cycle action and reduce the current-loop gain.

# D.C.M. Flyback Converter

$V_{FB}$  to Output :  $\frac{\hat{v}_o(s)}{\hat{v}_{FB}(s)} \approx G_{DC} \cdot \frac{\left(1 + \frac{s}{\omega_{Z_1}}\right) \cdot \left(1 - \frac{s}{\omega_{ZRHP}}\right)}{\left(1 + \frac{s}{\omega_{P_1}}\right) \cdot \left(1 + \frac{s}{\omega_{P_2}}\right)}$

$$G_{DC} = V_{IN} \cdot G_{FB} \cdot \sqrt{\frac{f_s \cdot R_L}{2 \cdot L_p} \cdot \frac{1}{(S_E + S_N)}}$$

$$\omega_{P_1} = \frac{2}{C_O \cdot R_L}$$

$$\omega_{P_2} = \left(\frac{N_p}{N_s}\right)^2 \cdot \frac{R_L}{L_p \cdot (M+1)^2}$$


$$\omega_{ZRHP} = \left(\frac{N_p}{N_s}\right)^2 \cdot \frac{R_L}{L_p \cdot M \cdot (M+1)}$$

$$\omega_{Z_1} = \frac{1}{C_O \cdot r_C}$$

$$M = \frac{N_p}{N_s} \cdot \frac{V_o}{V_{IN}}$$

- The flyback converter operated in D.C.M. PCMC features a low frequency pole  $\omega_{P_1}$ , followed by a high-frequency pole  $\omega_{P_2}$ . A RHPZ is also present but its effects are pushed to high frequency portion of the spectrum. Its effects are therefore less sensitive than in C.C.M.. The zero, as in C.C.M., is provided by  $C_O$ , and its equivalent series resistor.

# 12V/2A Off-Line Flyback Converter

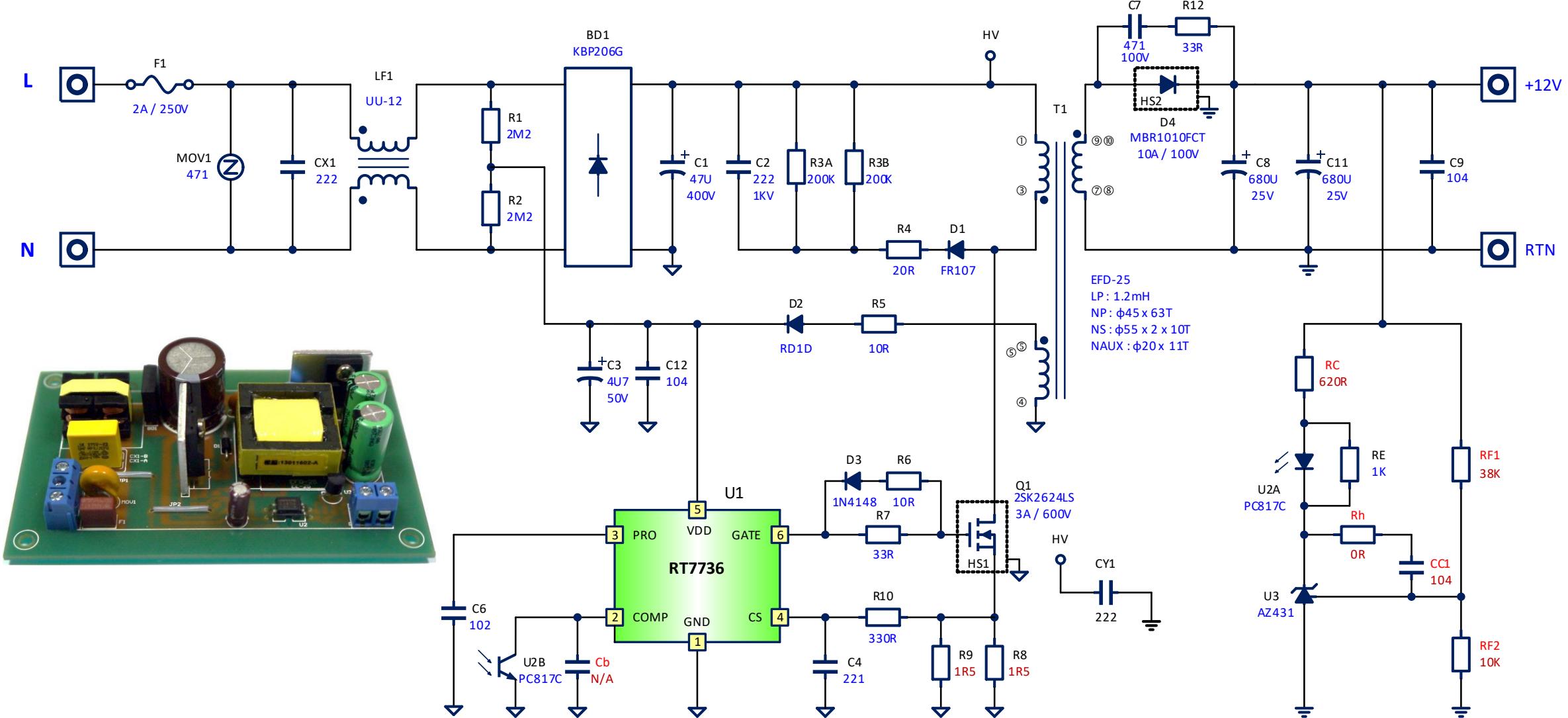

# Power Circuit

## Engineer's Spec.


1. Max Duty Cycle @ 90Vdc :  $D_{\max} = 0.47$
2.  $I_{OB}$  @ 90Vdc = 0.9A
3. Peak Flux Density of Flyback Transformer @90Vdc :  $B_{\max} = 0.28$  Tesla

Transformer Core : EFD-25 (PC40)

$N_P$  : 63T,  $N_S$  : 10T

$L_P$  : 1.2mH,  $L_S \approx 30\mu H$

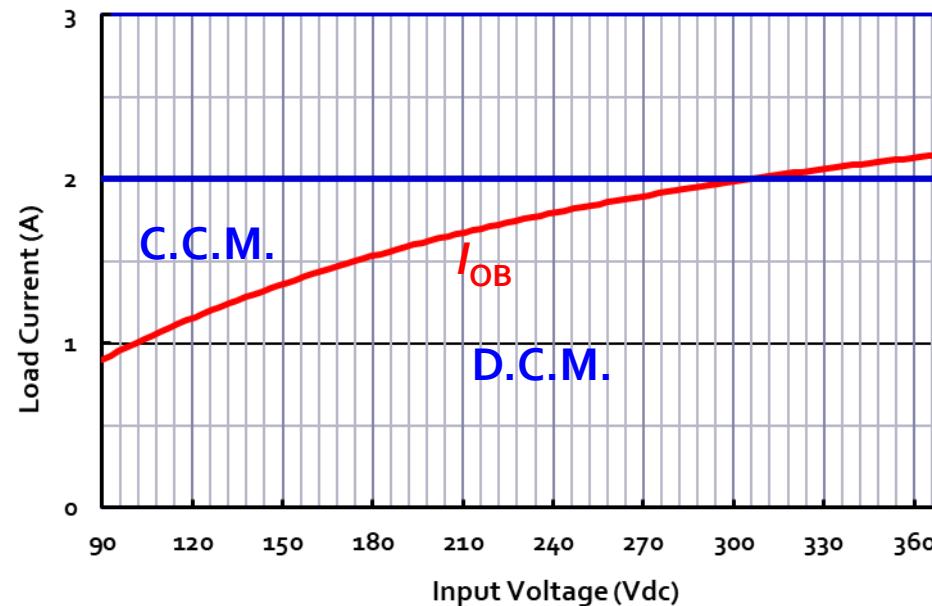$C_O$  : 680 $\mu F$  x 2 (ESR = 20 m $\Omega$ )



# Control Circuit

---

Operating Point  $V_{IN} = 90Vdc / I_O = 2A$

Control IC      Switching Frequency : 65kHz (Frequency Dithering +/- 3k Hz)

External Ramp :  $3.33 \times 10^4 V/sec$

Sense Resistor :  $0.75\Omega$  (OCP concerned)

Power Circuit Transfer Function with Current-Loop Closed

$$G_{DC} = \frac{R_L}{R_S} \cdot \frac{G_{FB}}{\left( \frac{1+D}{1-D} \right) \cdot \frac{N_s}{N_p} + \frac{R_L \cdot T_s}{L_p} \cdot m_c \cdot (1-D)^2 \cdot \left( \frac{N_p}{N_s} \right)} = 4.08 = 12.2dB$$

$$\omega_p = \frac{1+D}{C_o \cdot R_L} + \frac{m_c \cdot T_s}{L_p \cdot C_o} \cdot \left( \frac{N_p}{N_s} \right)^2 \cdot (1-D)^3 = 244.1 \text{ (rad)} \quad f_p = \frac{\omega_p}{2\pi} = 39 \text{ (Hz)}$$

$$\omega_z = \frac{1}{C_o \cdot r_c} = 3.68k \text{ (rad)}$$

$$f_z = \frac{\omega_z}{2\pi} = 5.85k \text{ (Hz)}$$

# Control Circuit



$$\omega_{ZRHP} = \frac{R_L \cdot (1-D)^2}{L_P \cdot D} \cdot \left( \frac{N_P}{N_S} \right)^2 = 128.5k \text{ (rad)}$$

$$\omega_n = \frac{\pi}{T_s} = 204.2k \text{ (rad)}$$


$$f_{RHPZ} = \frac{\omega_{RHPZ}}{2\pi} = 20.4k \text{ (Hz)}$$

$$f_n = \frac{1}{2T_s} = 32.5k \text{ (Hz)}$$



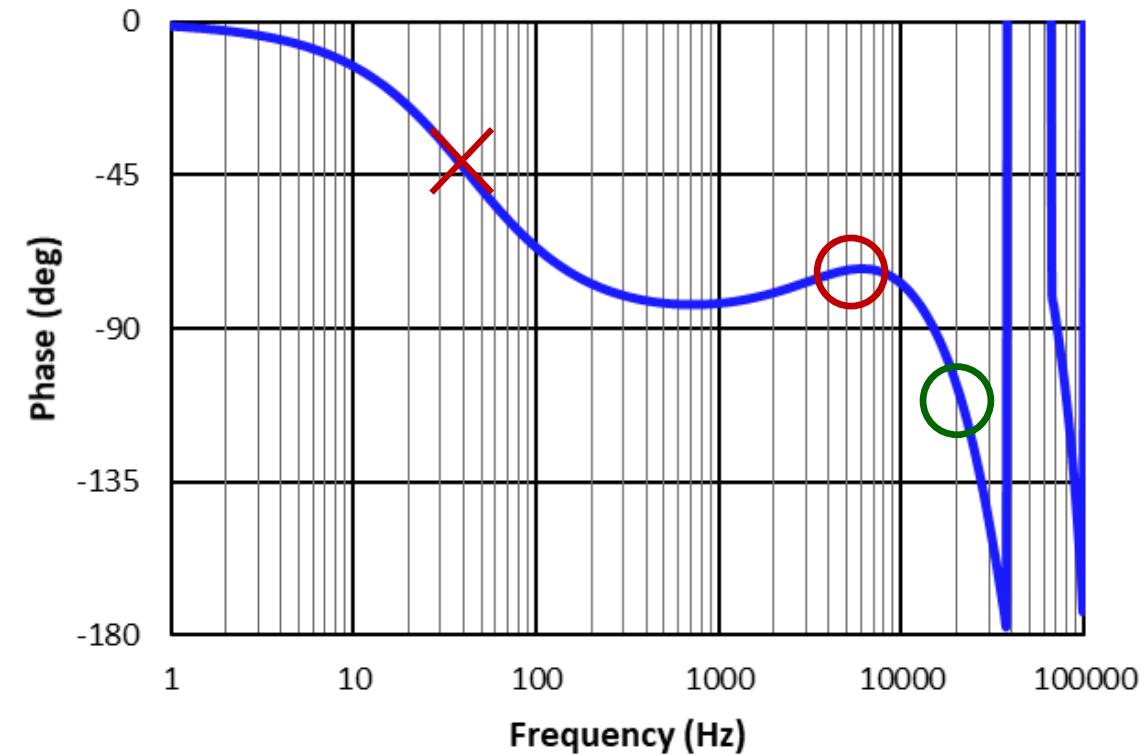
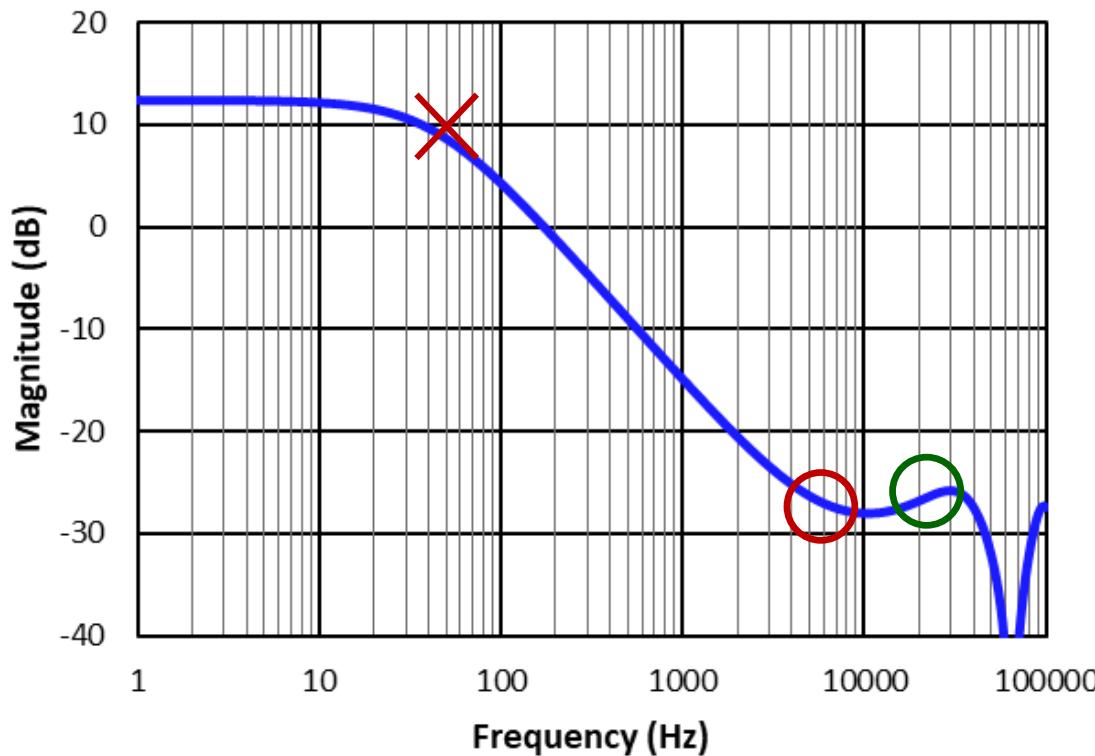
$$Q_p = \frac{1}{\pi \cdot [m_c \cdot (1-D) - 0.5]} = 0.872$$



# SIMPLIS Simulation Example (12V/2A)

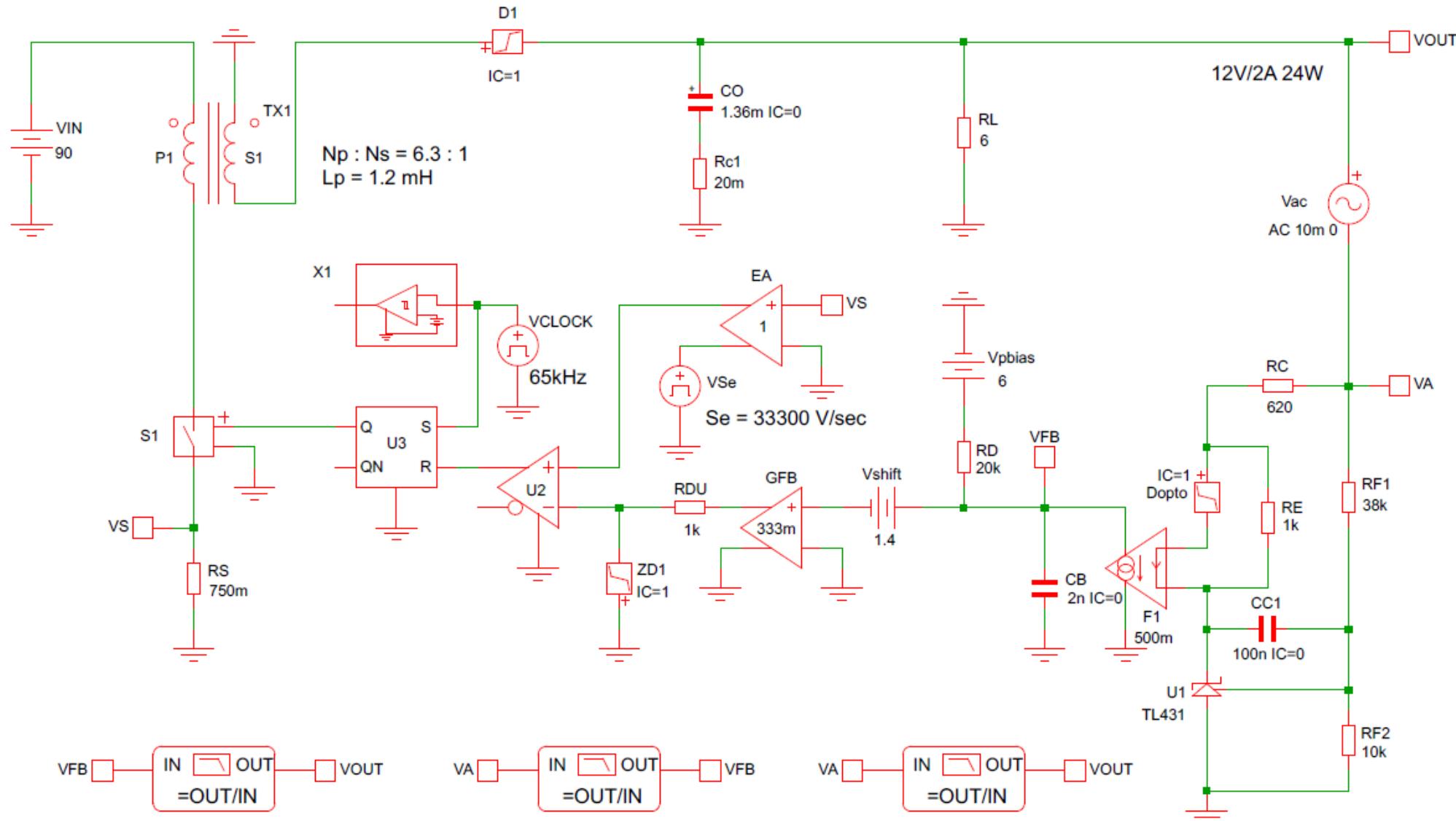
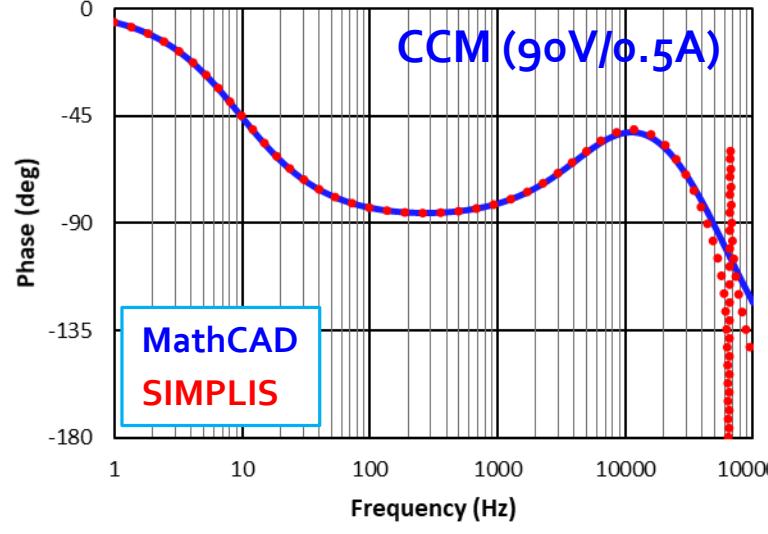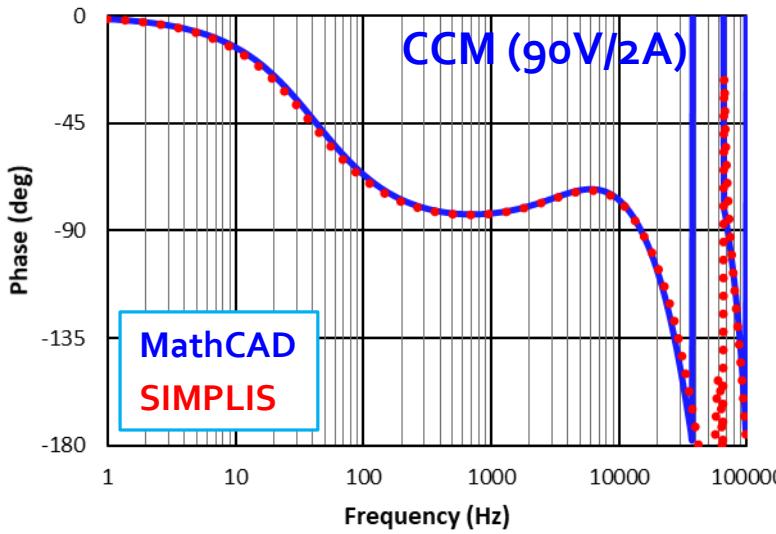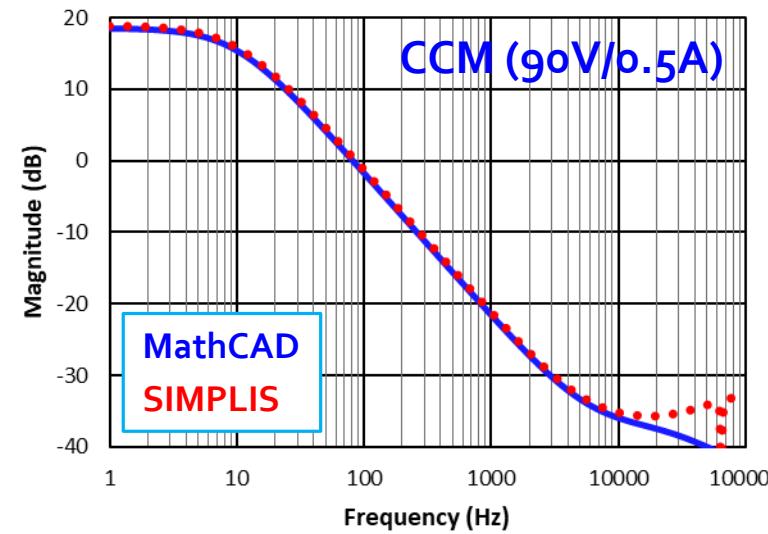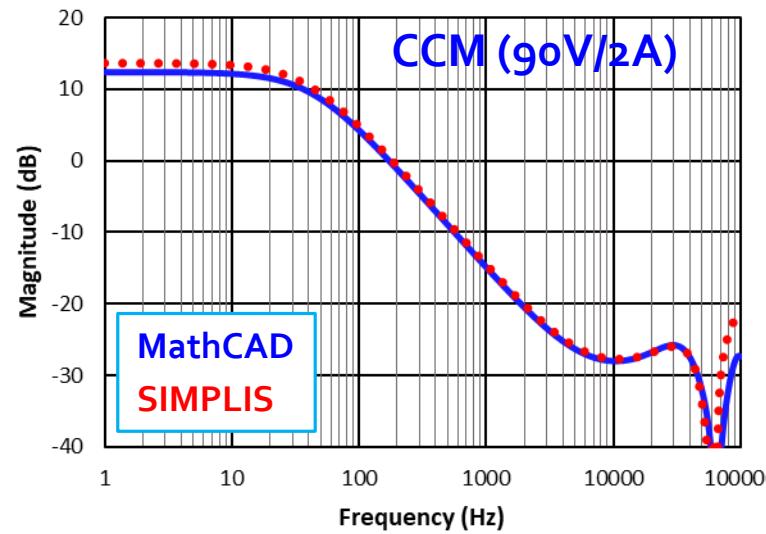
# $V_{FB}$ to $V_O$ Transfer Function (with Current-Loop Closed)



- Operating Point dependent.
- $\frac{1}{2}P_1Z$  (up to  $\frac{1}{2}f_S$ ) for both CCM and DCM.


Will Be Back  
At 16:10

Time	Topic
16:00-16:10	Break Time
16:10-16:50	返結合光耦和分路穩壓器的返馳電源回授設計－2 Off-line Flyback Feedback Design with Optocoupler and Shunt Regulator
16:50-17:00	QA
17:00	Lucky Draw



王信雄博士


# Compensation

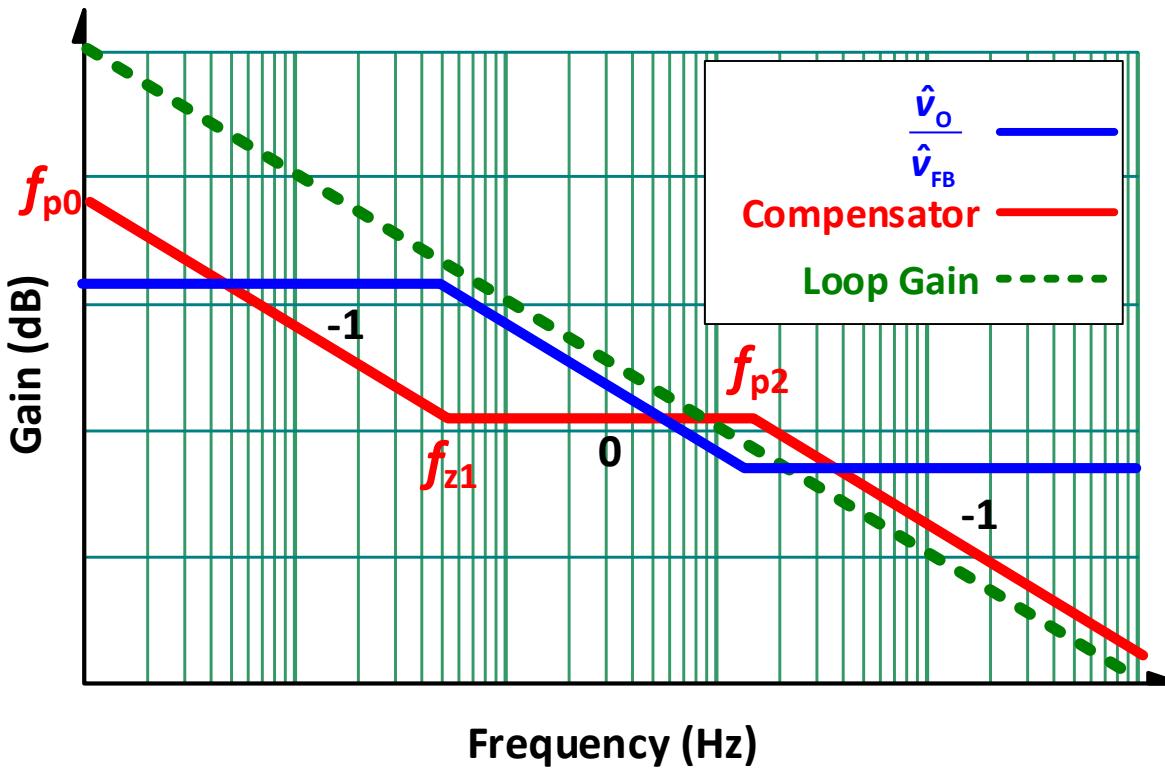


- Generally, a Type II ( $2P_1Z$ ) compensator is adequate for both C.C.M. and D.C.M. flyback.
- Based on an operating point to design the compensator. Pole-Zero placement of K-factor approaches are commonly used.

# Isolated Compensating Network

Opamp Type II

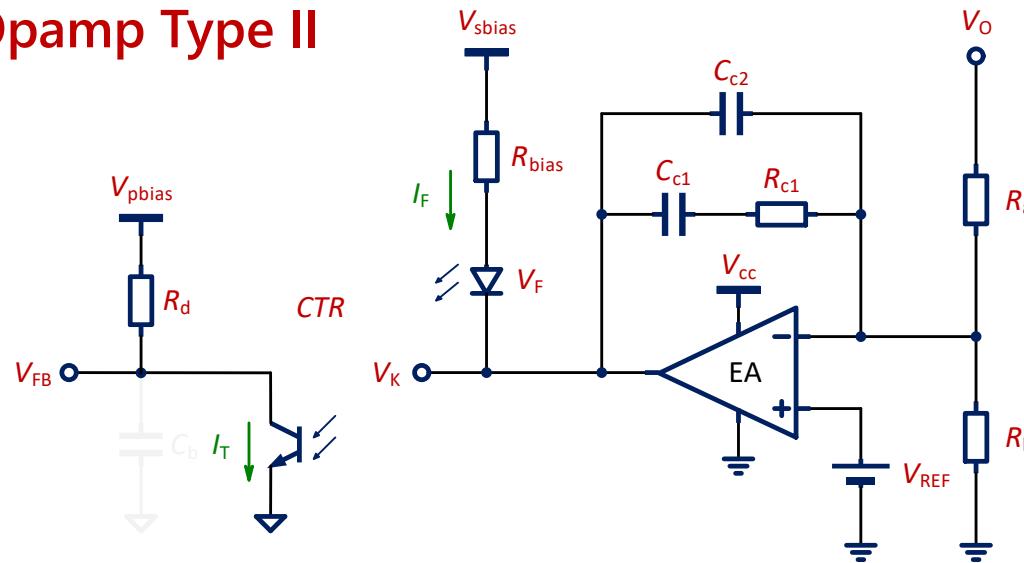


TL431 Type II

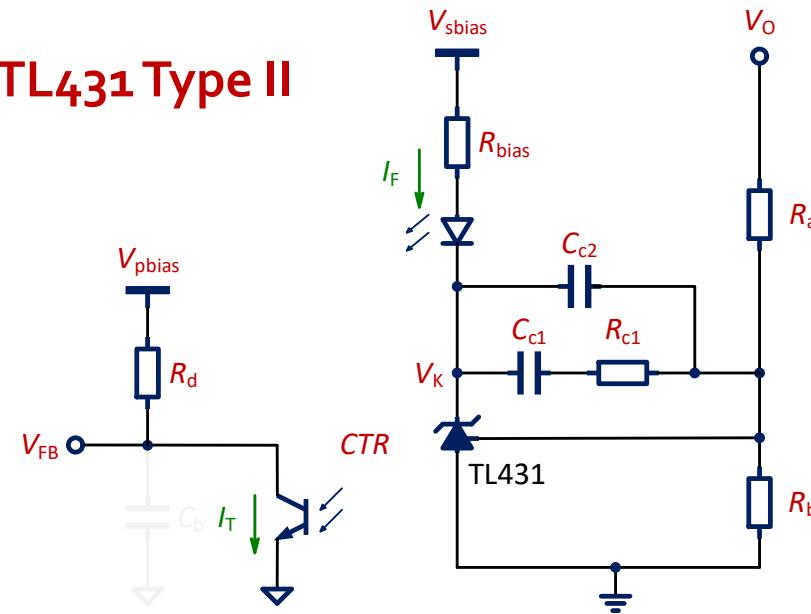


$$G_{\text{comp}}(s) = \text{CTR} \cdot \frac{R_d}{R_{\text{bias}} \cdot R_a (C_{c1} + C_{c2})} \cdot \frac{1 + s R_{c1} C_{c1}}{s \cdot (1 + s R_{c1} \cdot \frac{C_{c1} C_{c2}}{C_{c1} + C_{c2}})}$$

- Opamp network with  $V_{\text{REF}}$  and optocoupler can conceptually fit the requirement.
- A shunt regulator (TL431) with optocoupler is the most commonly adopted for its simplicity and low cost.

# Practical Compensator Structure

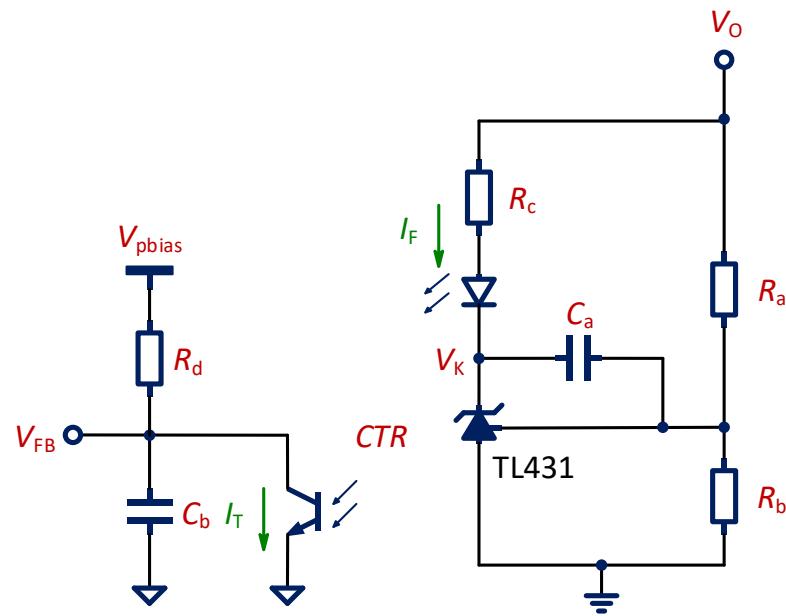

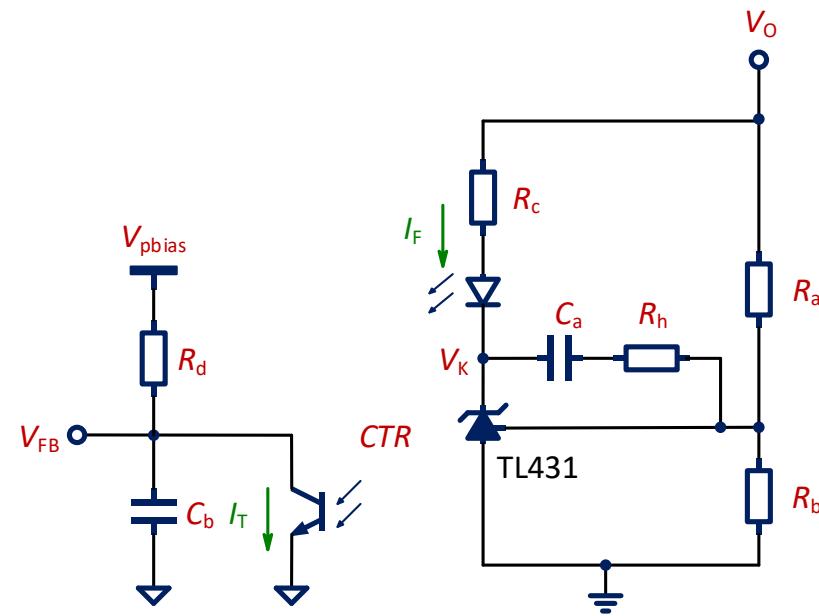
$$G_{\text{COMP}}(s) = \text{CTR} \cdot \frac{R_d}{R_c} \cdot \frac{1 + sR_a C_a}{sR_a C_a (1 + sR_d C_b)}$$




$$G_{\text{COMP}}(s) = \text{CTR} \cdot \frac{R_d}{R_c} \cdot \frac{1 + s(R_a + R_h)C_a}{sR_a C_a (1 + sR_d C_b)}$$

- TL431 is powered by output voltage.
- Both two compensating networks have Type II structure.
- The right one has more design degree of freedom.


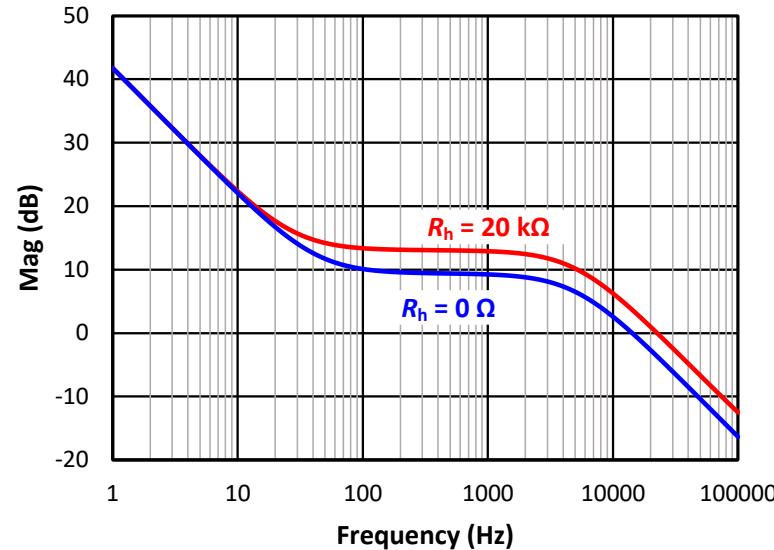
# Compensation Network of Flyback Converter



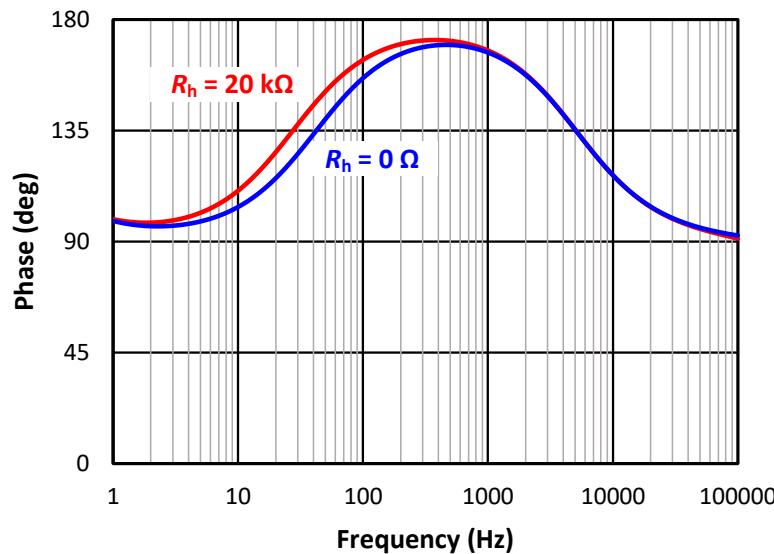- The existence of  $R_h$  can increase the gain in the middle frequency range.
- At the same time, more split the location of pole-zero pair, which changes the phase arising of compensator.





# Flyback Feedback

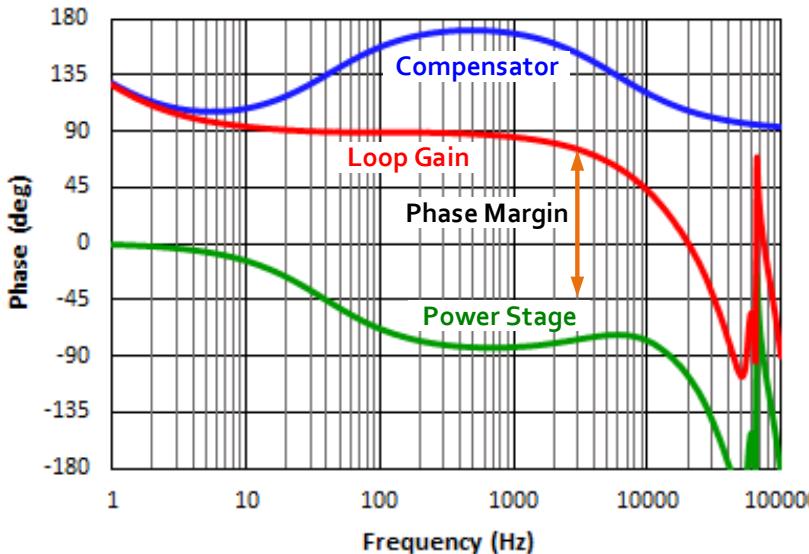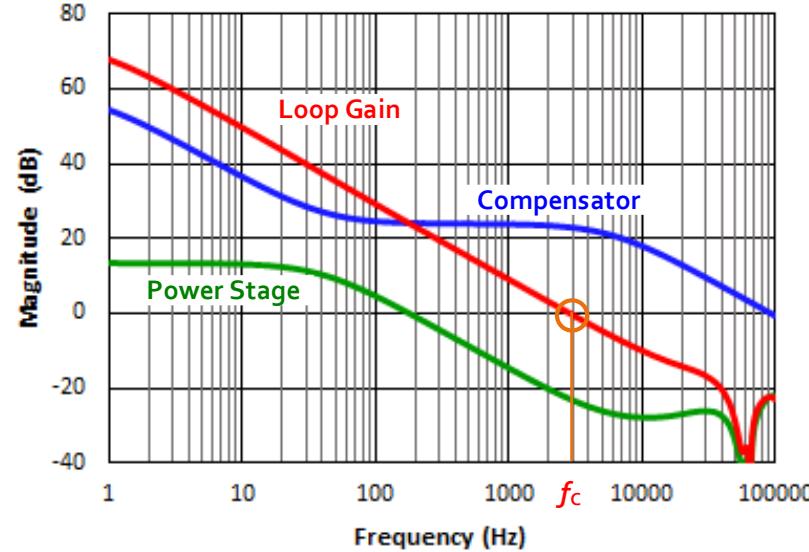


- With proper design of compensator, one can easily achieve very good loop gain with quite high cross-over frequency and phase margin.
- Pole-zero placement (pole-zero cancellation) approach is recommended to obtain **-1** slope of loop gain.
- For PCMC, there is no LC peaking in loop gain.
- RHPZ and two-pole at half of switching frequency results in phase drop in high frequency range.
- Due to feedforward characteristics, the input variation only affect little in loop gain.

# D.C.M. of Flyback Converter

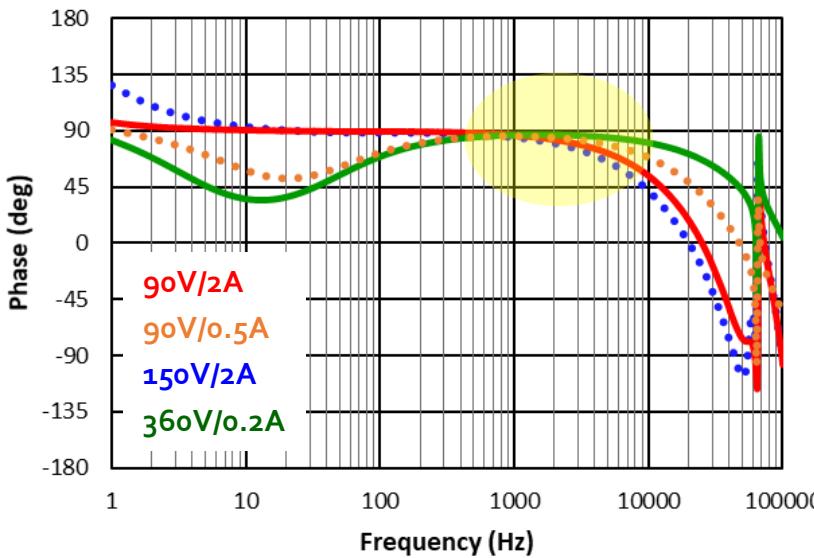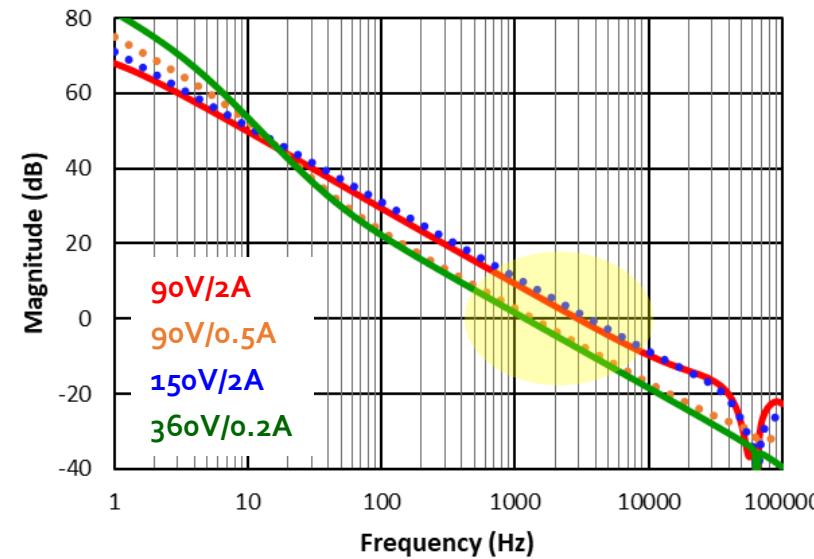


- Once the converter operates in D.C.M., the crossover frequency will be decreased if same compensator applied.
- Pay more attention to the compensator design based on which operating point. Check every corner to ensure stability.
- In the modern flyback controller, the switching frequency will be decreased in light load condition, which will result in worse frequency response. Adaptive gain design in control IC can mitigate the symptom.

# Dynamic Load Change Transient Response

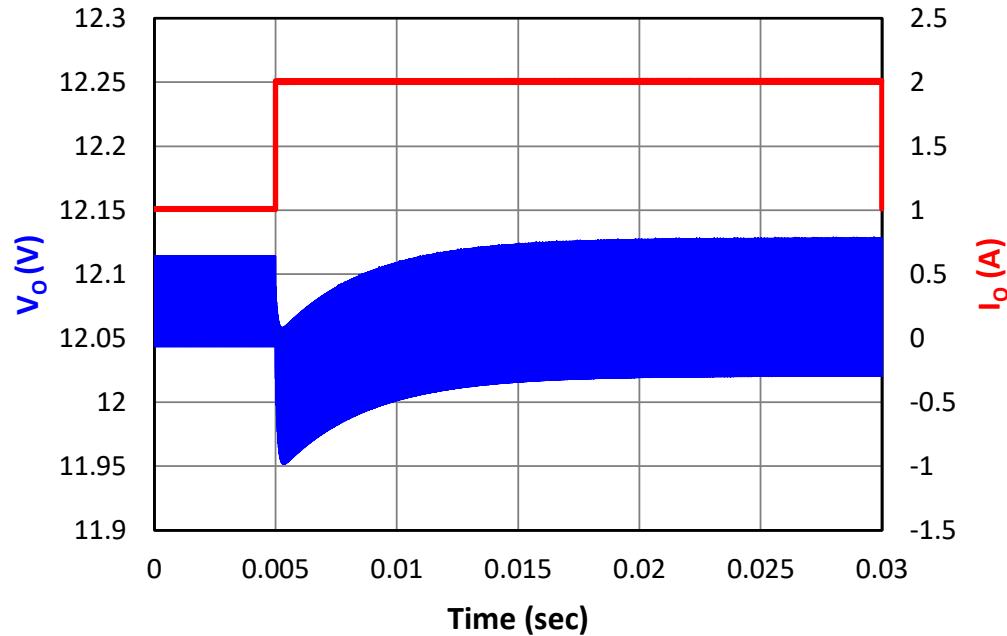

$I_o : 1A \rightarrow 2A$

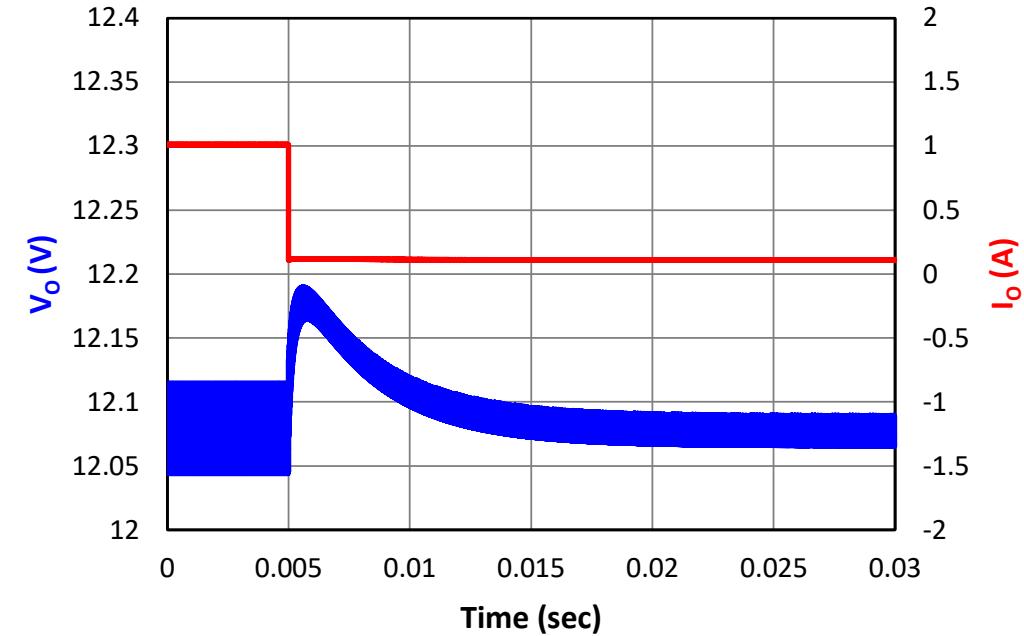


$I_o : 1A \rightarrow 0.1A$


- Dynamic load change response indicates the discrepancy of target operating points.
- Higher over-shoot and slow settling time in D.C.M.

# Shunt Regulator TL431

## Symbol

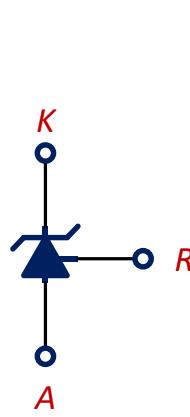

## Functional Block Diagram

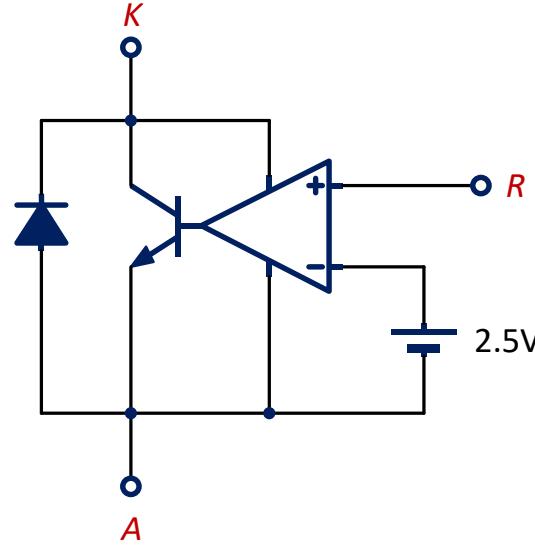


## Reference Voltage

### ELECTRICAL CHARACTERISTICS

$T_{amb} = 25^\circ\text{C}$  (unless otherwise specified)



## Equivalent Schematics

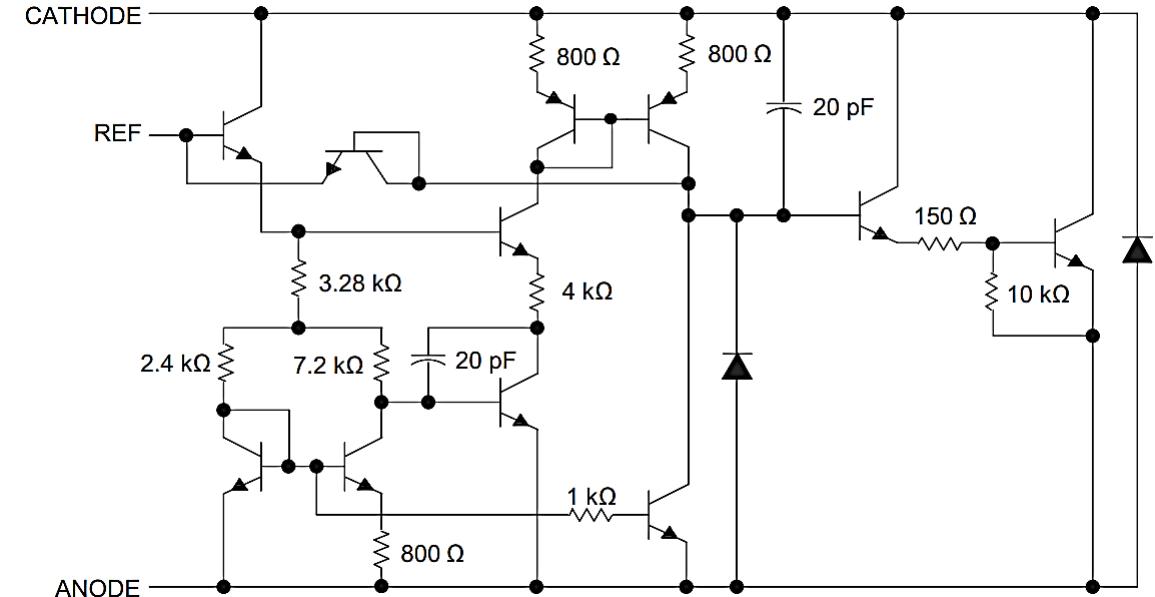

Symbol	Parameter	TL431C			TL431AC			Unit
		Min.	Typ.	Max.	Min.	Typ.	Max.	
$V_{ref}$	Reference Input Voltage $V_{KA} = V_{ref}, I_k = 10 \text{ mA}$ $T_{amb} = 25^\circ\text{C}$ $T_{min} \leq T_{amb} \leq T_{max}$	2.44 2.423	2.495	2.55 2.567	2.47	2.495	2.52 2.537	V
$\Delta V_{ref}$	Reference Input Voltage Deviation Over-Temperature Range - note 1 $V_{KA} = V_{ref}, I_k = 10 \text{ mA}, T_{min} \leq T_{amb} \leq T_{max}$		3	17		3	15	mV

# Shunt Regulator TL431



## Regulation vs. Cathode Current

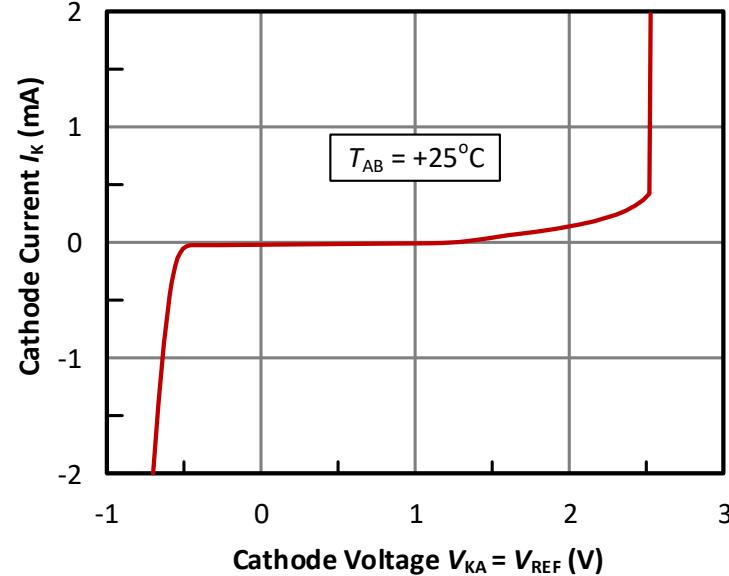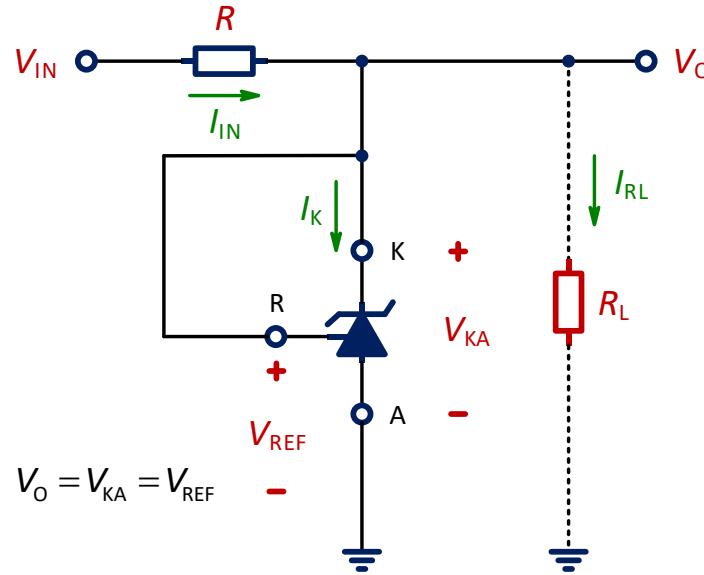

- The cathode current should be higher than  $500\mu\text{A}$  (depending on spec.) to guarantee the regulation.
- The current flowing into reference pin of TL431 is around  $2\mu\text{A}$ , such that the current on lower voltage divider is chosen as more than 100 times to ensure the accuracy.
- In other words, the lower resistance should be lower than  $12.5\text{k}\Omega$ .


# Frequency-Domain Characteristics of TL431

## Gain and Phase

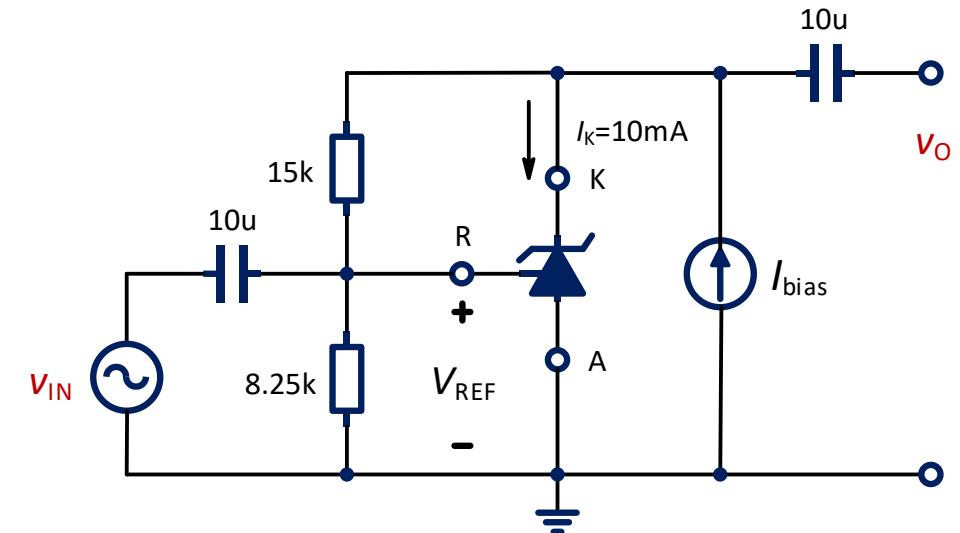
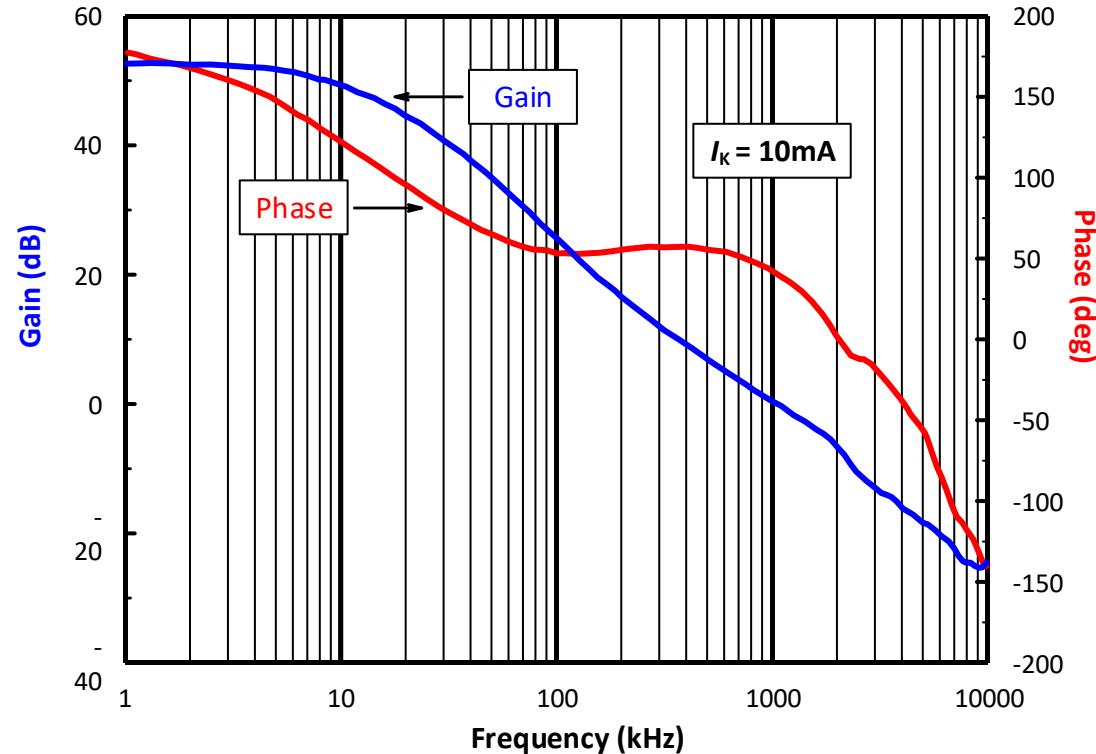


- DC Gain = 53 dB, Pole = 10kHz

# Opto-Coupler PC817C

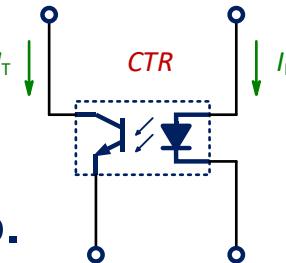

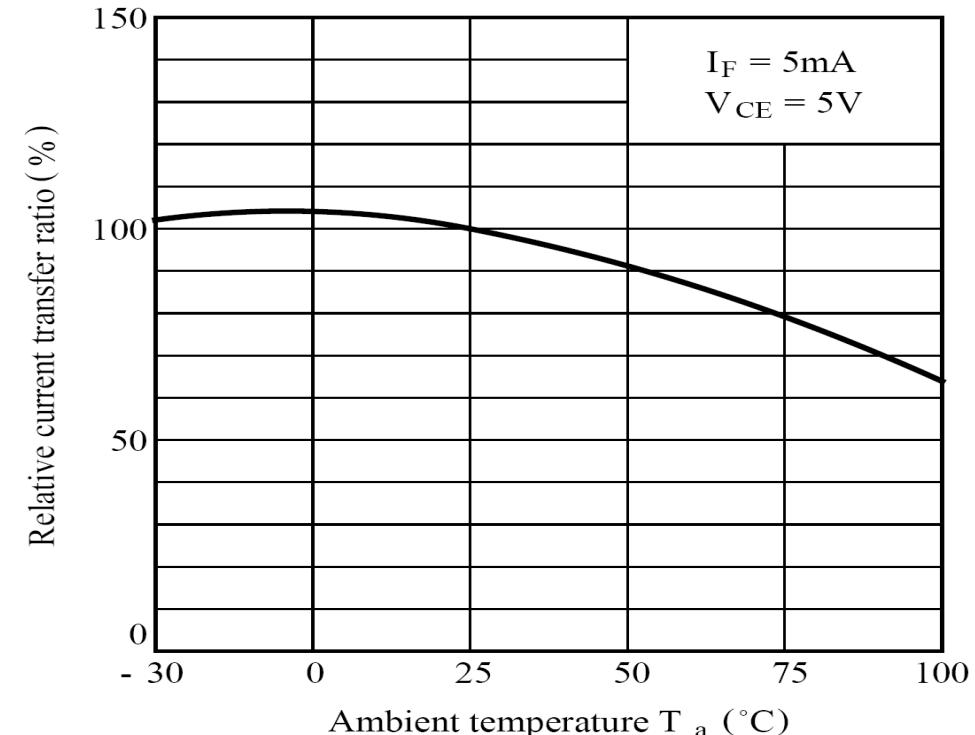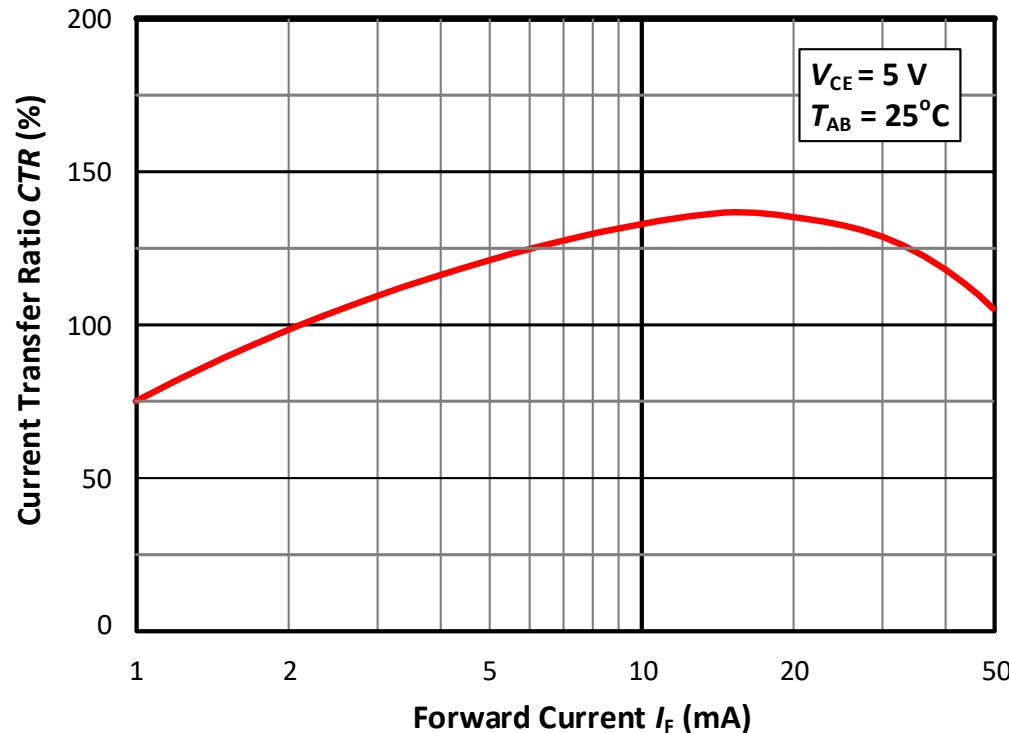Forward Current vs. CTR vs. Ambient Temp.




- CTR is quite nonlinear with forward current and temperature.

# Opto-Coupler PC817C

---



## Forward Current vs. Forward Voltage

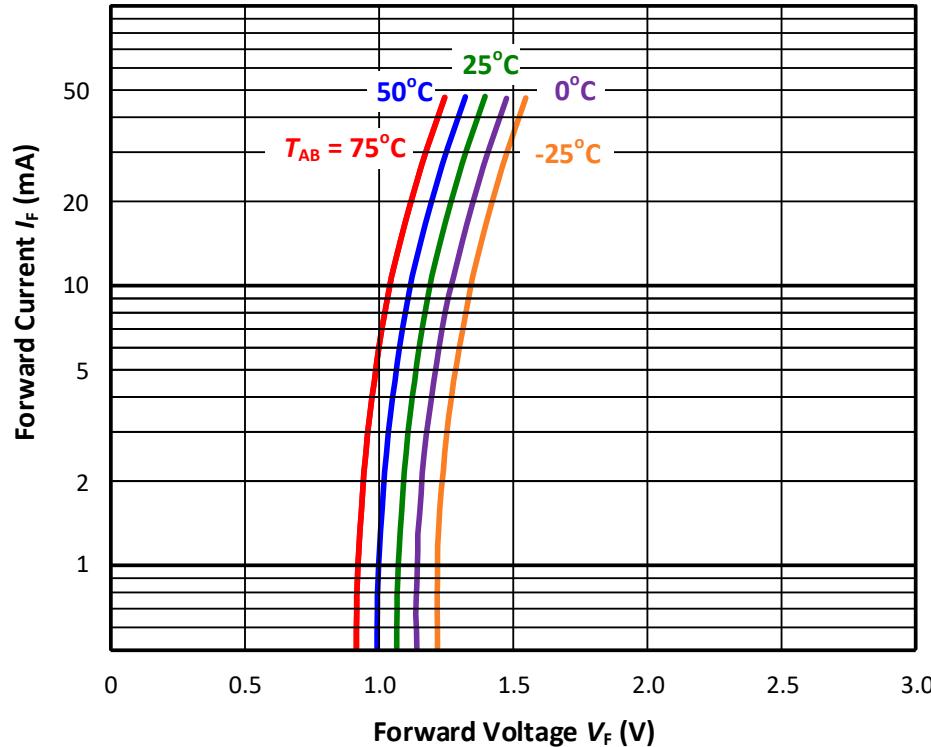

- Forward voltage on opto-diode has only small variation in low forward current range. Assumed to be constant for simplicity.
- Forward voltage is getting lower when higher ambient temperature.

# Opto-Coupler PC817C


Frequency Response of PC817C

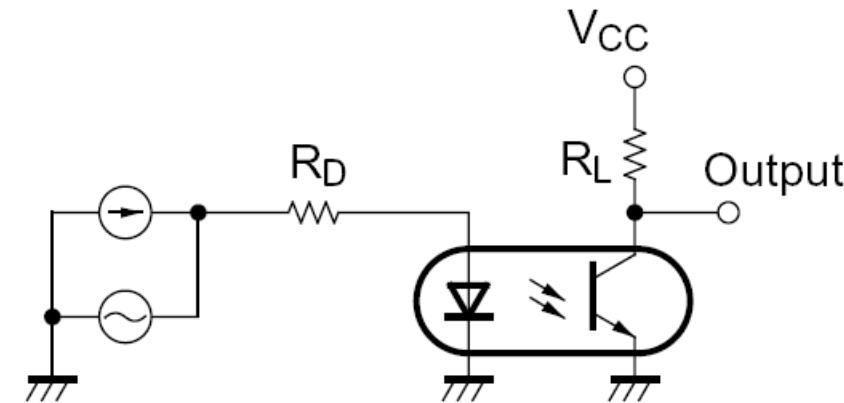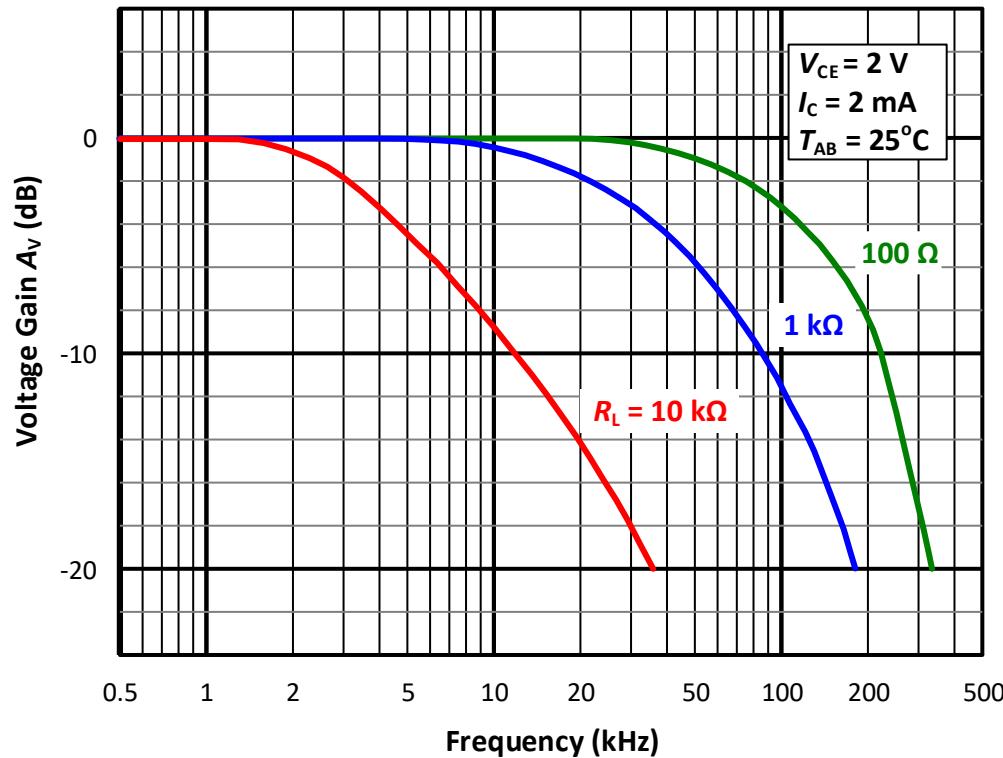

$$G_{\text{opto}}(s) = \frac{\Delta V_c(s)}{\Delta V_i(s)} = CTR \cdot \frac{R_L}{R_D \cdot (1 + \frac{s}{2\pi f_{po}})}$$

$f_{po}$  : pole on optocoupler  $1 \sim 50 \text{ kHz}$

# Characterization of PC817C

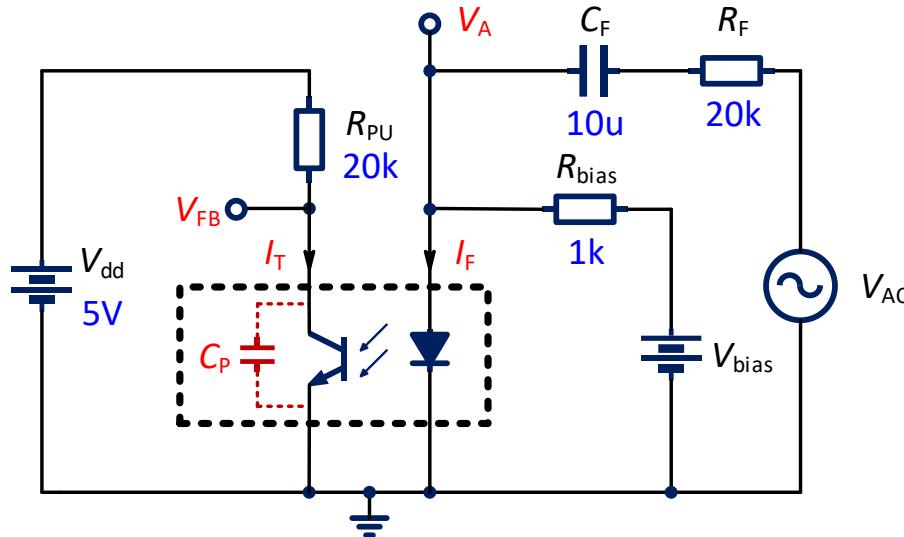


Frequency of -3dB point



$$f_{po} \approx 1.188 \text{ kHz}$$

Parasitic Capacitance :
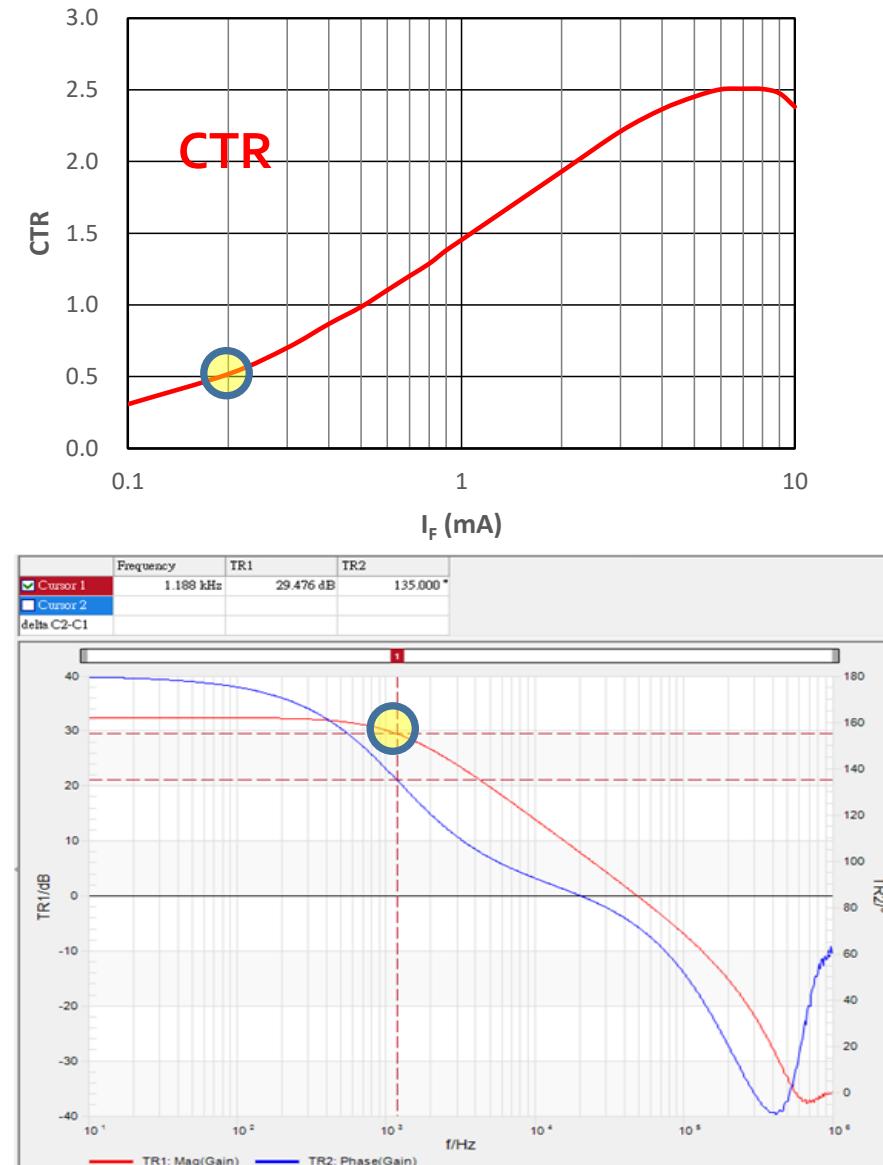
$$C_b = \frac{1}{2\pi \cdot R_{pu} \cdot f_{po}} = 6.7 \text{ nF}$$




# Parasitic Cap. of Opto-Transistor

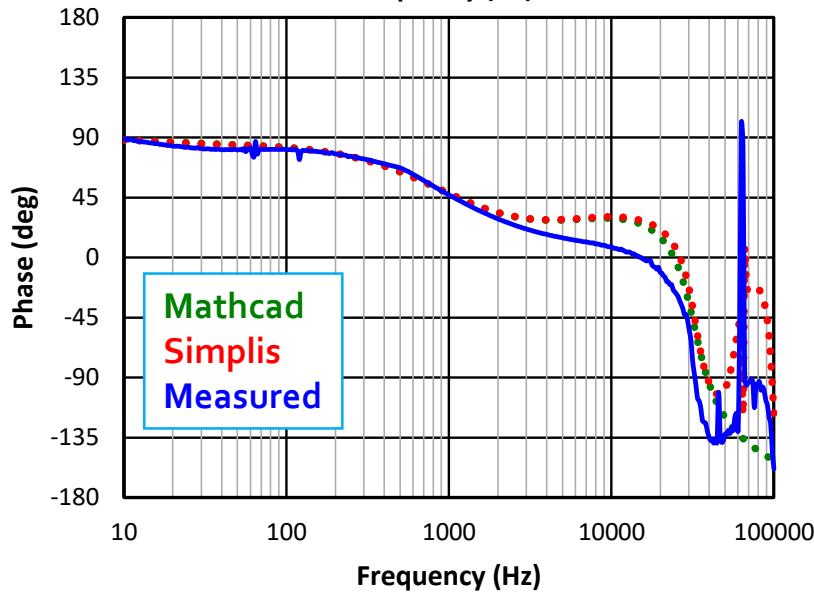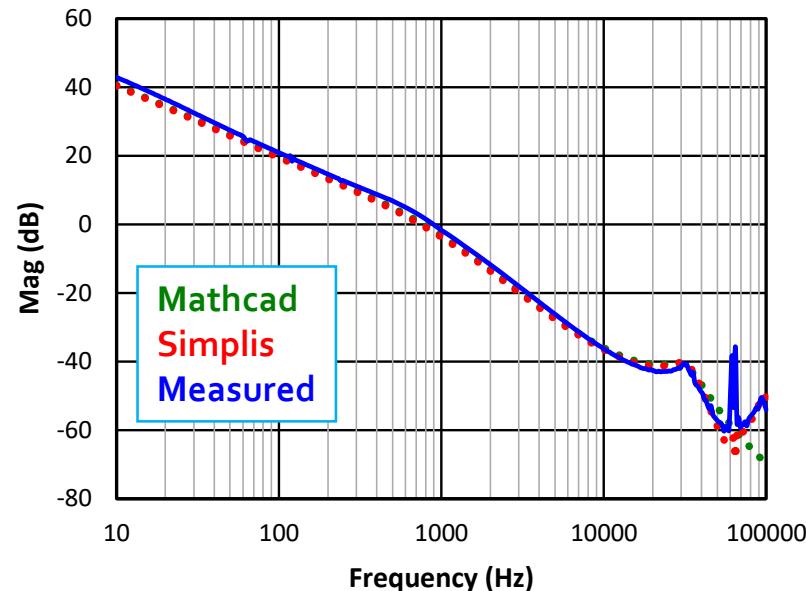

- Operating point :  $V_{IN} = 150V$ ,  $I_O = 2A$ ; C.C.M. operation, Duty cycle  $\approx 0.335$ .
- Crossover frequency,  $f_c = 2\text{kHz}$ ;
- Voltage divider :  $R_a = 38\text{ k}\Omega$ ,  $R_b = 10\text{ k}\Omega$ ;
- Feedback capacitance,  $C_a = 100\text{ nF}$ ;
- Gain Resistance,  $R_c = 620\text{ }\Omega$ ;
- ESR zero of output capacitor is around  $5.85\text{ kHz}$ ;
- Pull-up resistance inside controller is  $20\text{ k}\Omega$ . Together with parasitic capacitance ( $8\text{nF}$ ) of opto-transistor, the pole is located around  $1\text{ kHz}$ . The pole is inherently much lower than ESR zero, such that lower crossover frequency and lower phase margin are expected.
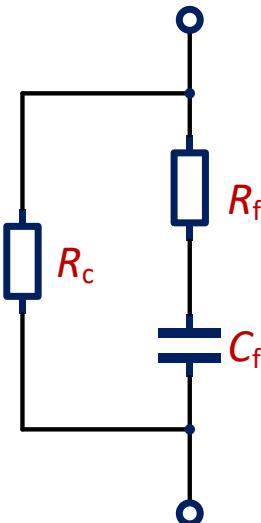
# Countermeasure Proposed (Phase Booster)

- The countermeasure could be adding a “phase booster”.
- A series  $R_f$  and  $C_f$  is paralleled to cathode resistor  $R_c$ . It can equivalently form a phase booster.
- The pole ( $R_d$ ,  $C_b$ ) is aimed to cancel ESR zero of output capacitor. However, if the location of pole is much lower than ESR zero, the gain will be decreased before ESR zero. The crossover frequency will be lower, and the phase margin will be lower accordingly.




$$\begin{aligned} Z(s) &= R_c \parallel \left( R_f + \frac{1}{sC_f} \right) = R_c \parallel \left( \frac{1+sR_fC_f}{sC_f} \right) \\ &= \frac{R_c(1+sR_fC_f)}{1+s(R_c+R_f)C_f} \quad \boxed{\frac{R_c \left( 1 + \frac{s}{\omega_z} \right)}{\left( 1 + \frac{s}{\omega_p} \right)}} \end{aligned}$$
$$\omega_p = \frac{1}{R_f C_f}, \quad \omega_z = \frac{1}{(R_c + R_f)C_f}$$

$$\begin{cases} R_f C_f = r_c C_o \\ (R_c + R_f) C_f = R_d C_b \end{cases}$$

$$R_f = \frac{R_c}{\frac{R_d C_b}{r_c C_o} - 1}, \quad C_f = \frac{r_c C_o}{R_f}$$


▪ ESR Zero is getting higher for new output capacitors.

# Phase Booster of Compensator


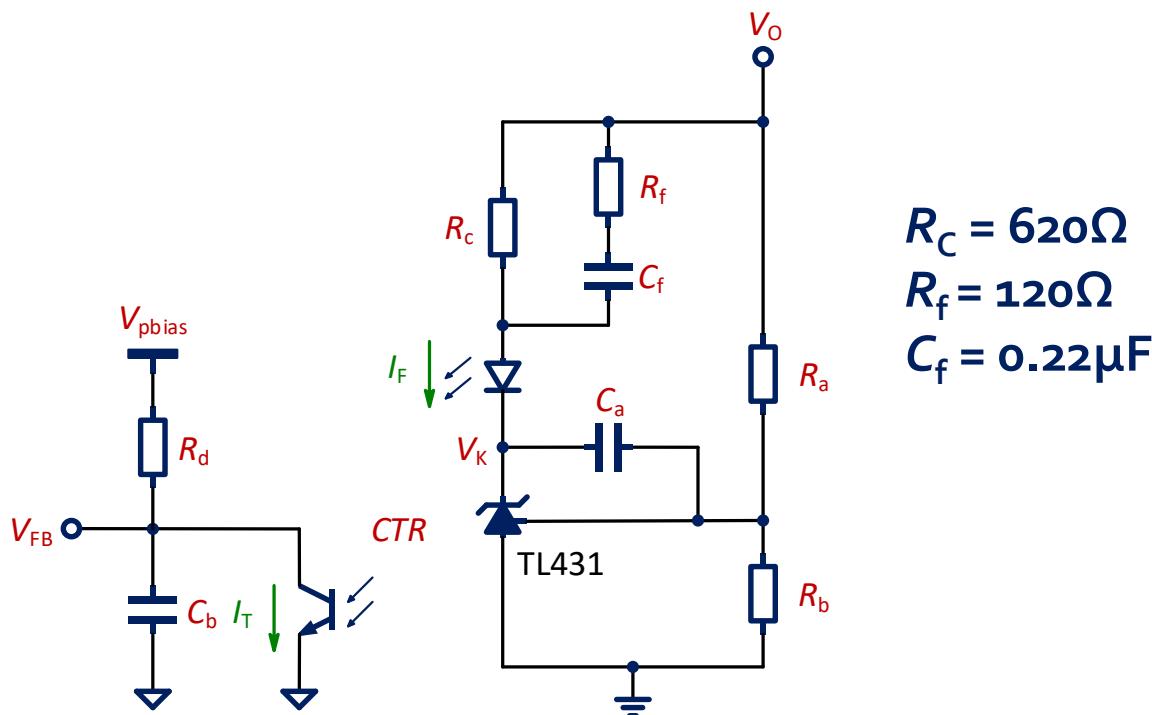


$$G_{COMP}(s) = CTR \cdot \frac{R_d}{R_c} \cdot \frac{(1 + s \cdot R_a C_a) \cdot [1 + s(R_c + R_f)C_f]}{s R_a C_a \cdot (1 + s R_d C_b) \cdot (1 + s R_f C_f)}$$

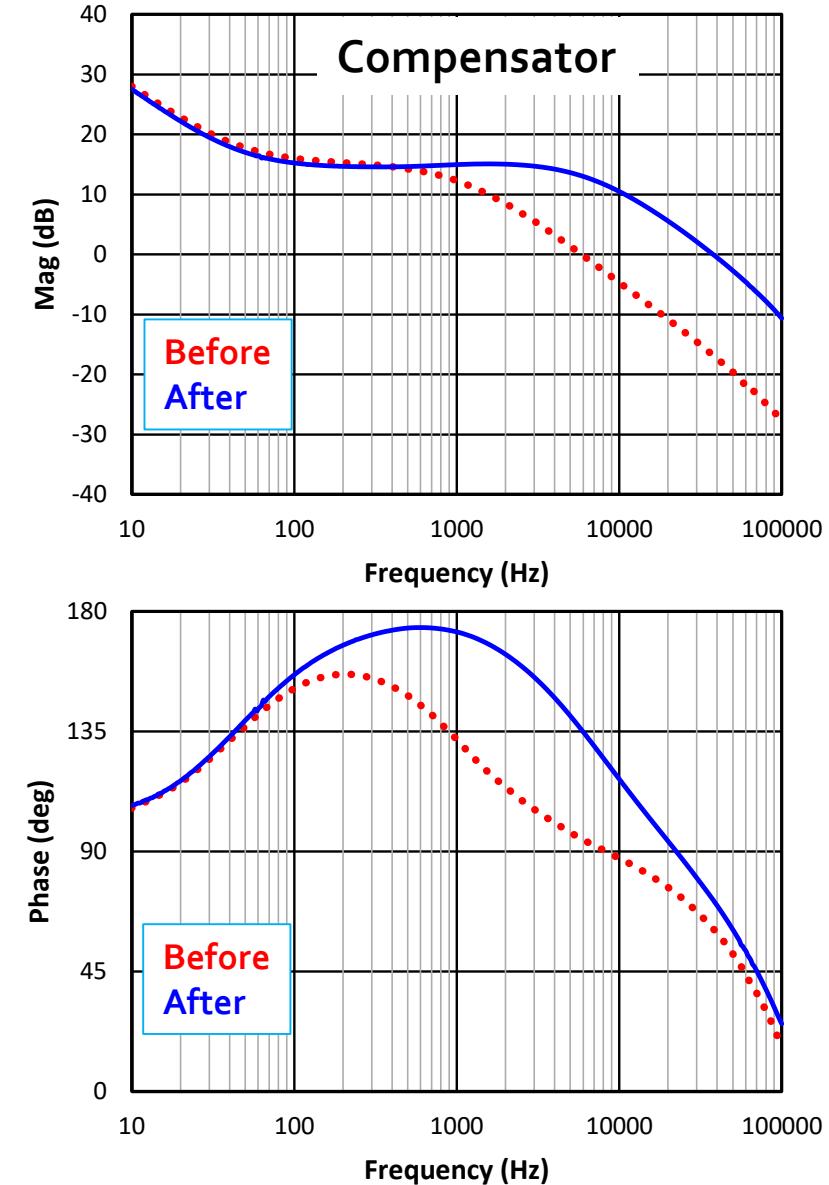- Additional  $R_f/C_f$  acts as phase booster. One lower zero compensates  $R_d/C_b$  pole. Another new high-frequency pole to cancel the ESR zero.



# Loop Gain and Dynamic Load Measurement

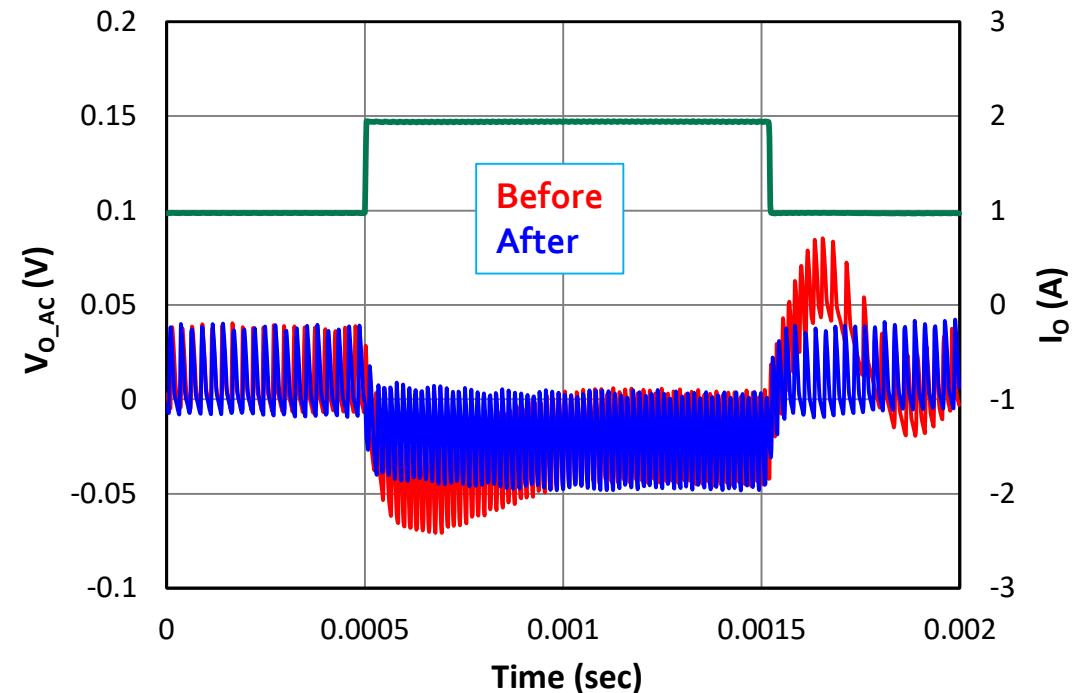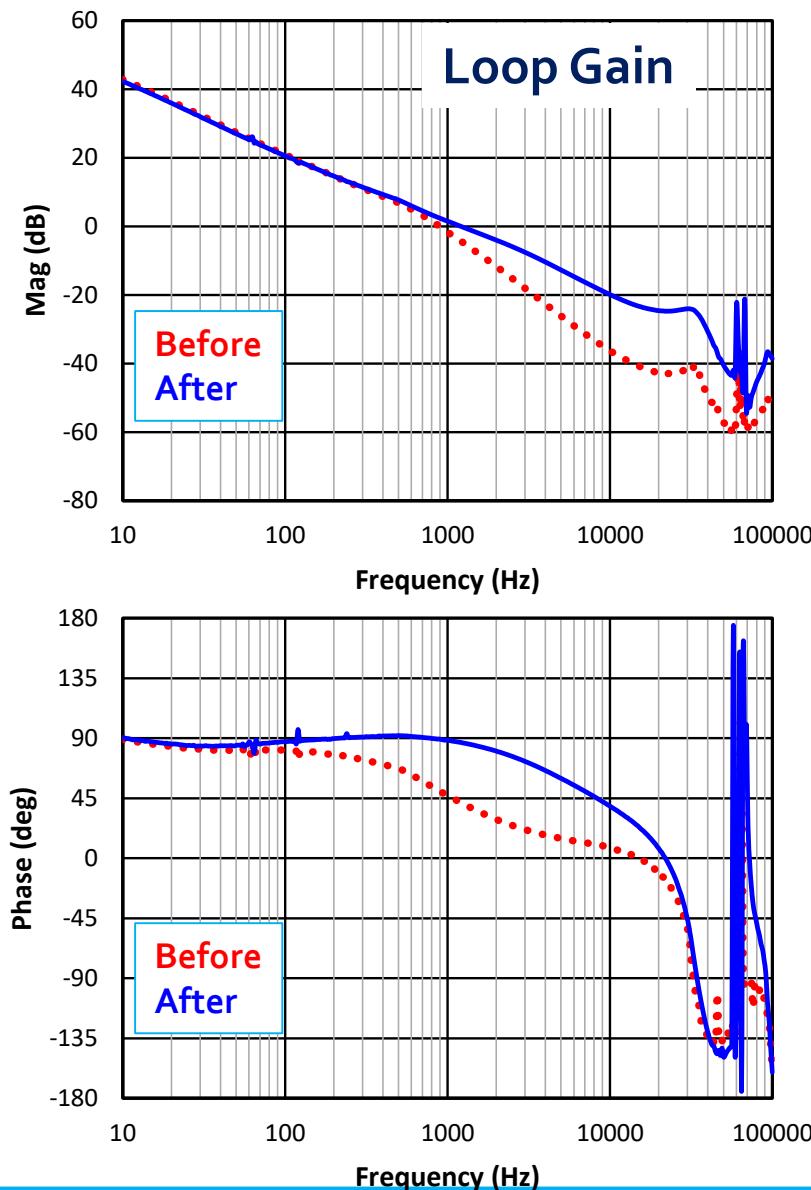


- Loop gain as well as phase margin is improved significantly.
- Dynamic load change response is improved. (Steady-state error results from output terminal measured)

# Conclusions

---


1. 1P1Z plant for both C.C.M. and D.C.M. PCMC Flyback.
2. A Type II (2P1Z) compensator is the most adequate for PCMC Flyback.
3. Opto-coupler + Shunt regulator is the most cost effective way to implement Type II compensator for isolated power converters.
4. Parasitic capacitance of Opto-coupler could degrade the loop performance (bandwidth , phase margin) and dynamic load change response, especially for higher ESR zero capacitors.
5. A simple phase booster is proposed to eliminate the effect from opto-coupler's parasitic capacitance.

# Transfer Function Measurement

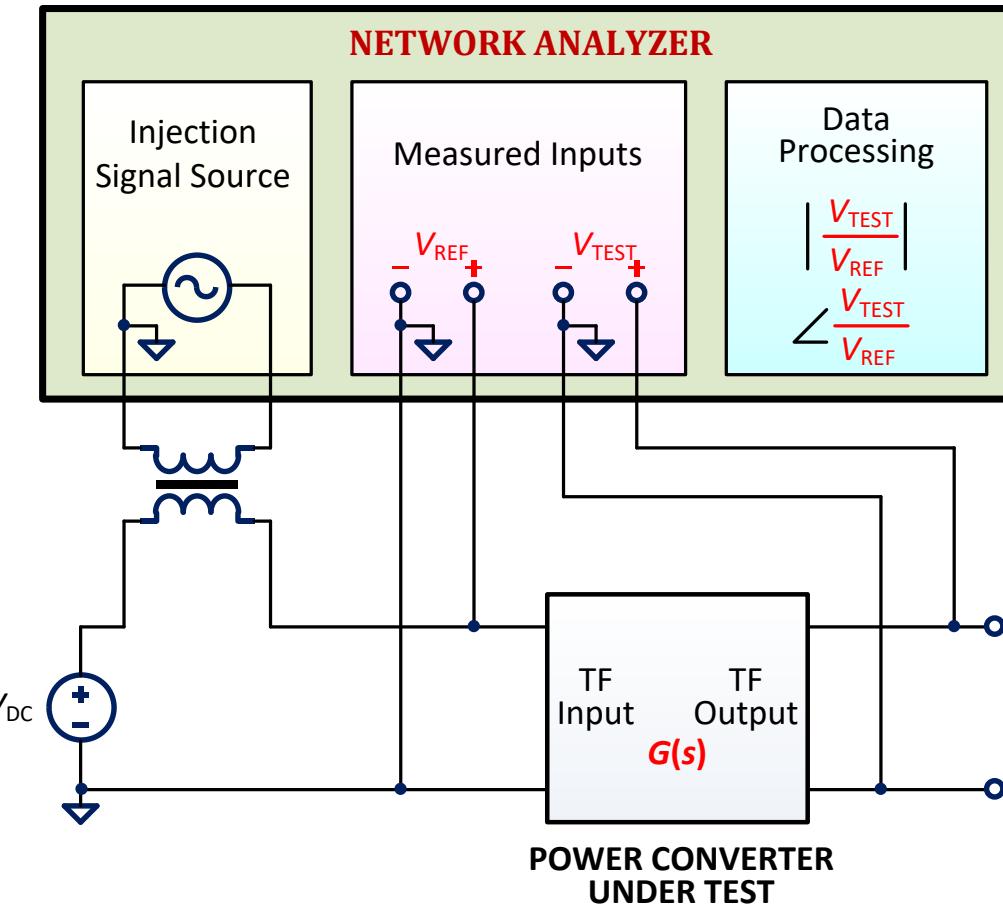


- Network Analyzer automatically generates Bode Plots of  $V_{TEST}/V_{REF}$ , including magnitude and phase.

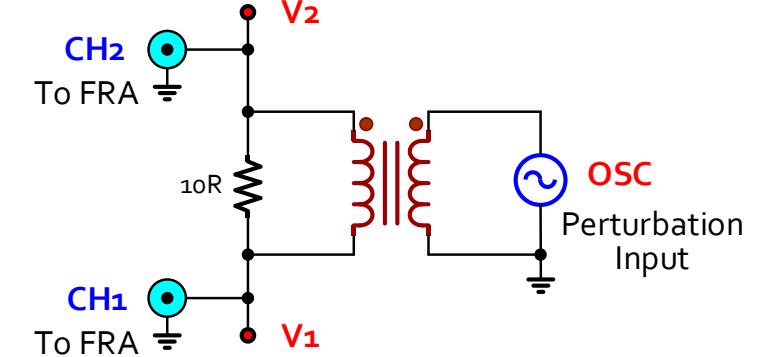- Impedance of Passive Components
- Gain-Phase of a Transformer
- Loop Gain / Compensator / Power Stage Transfer Functions / Output Impedance of Switching Converters



# Loop Gain Measurement with OSC Options

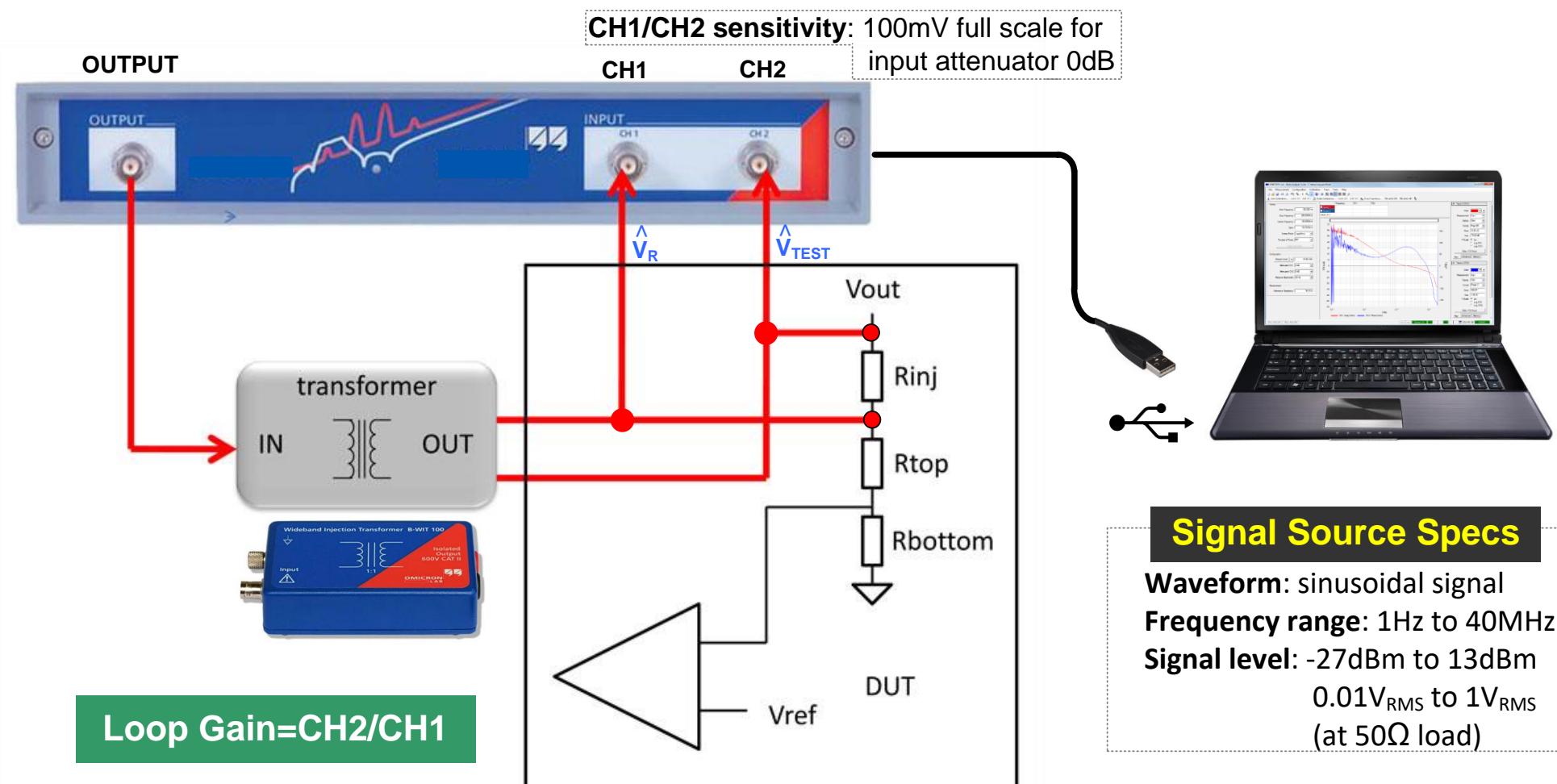

Demo : Loop Gain Measurement (RTA4004-K36, R&S)



---

期待再相會

Thanks

# Transfer Functions Derivation for Various Type II Compensator Based on Opto-Coupler and Shunt Regulator

# Configuration I

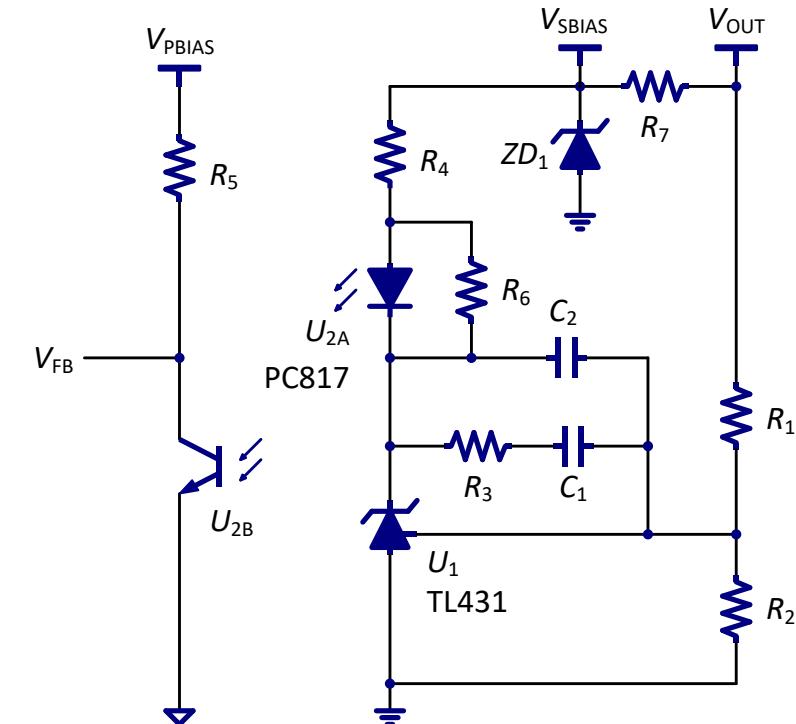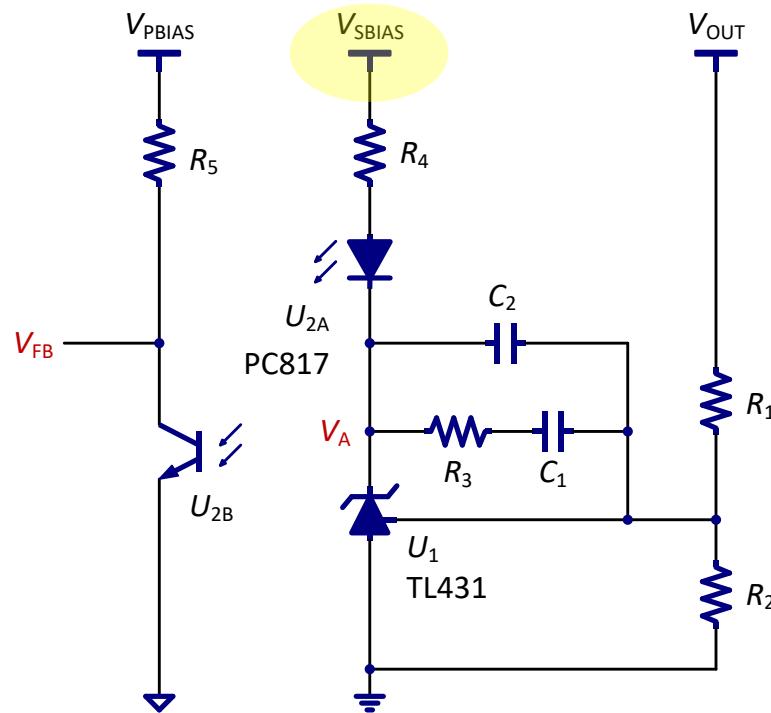

## Assumptions

1. Open-Loop Gain of TL431 is  $K$ .
2. Only constant gain (CTR) is in Opto-coupler.
3.  $V_{LED}$  is constant.
4. Loading of  $V_{FB}$  is zero.

## Implementation of $V_{SBIAS}$

# DC Analysis

---

$$V_A = K \cdot \left[ (V_{OUT} \times \frac{R_2}{R_1 + R_2}) - V_{REF} \right] \quad (1)$$

$$V_A = V_{SBIAS} - I_{LED} \times R_4 - V_{LED} \quad (2)$$

$$I_{TR} = CTR \times I_{LED} \quad (3)$$

$$V_{PBIAS} = I_{R5} \times R_5 + V_{FB} = I_{TR} \times R_5 + V_{FB} \quad (4)$$



$$\begin{aligned} V_{FB} &= V_{PBIAS} - I_{TR} \times R_5 \\ &= V_{PBIAS} - CTR \times I_{LED} \times R_5 \\ &= V_{PBIAS} - CTR \times \frac{(V_{SBIAS} - V_A - V_{LED})}{R_4} \times R_5 \\ &= V_{PBIAS} - CTR \times \frac{R_5}{R_4} \times \left\{ K \cdot \left[ V_{REF} - \left( V_{OUT} \times \frac{R_2}{R_1 + R_2} \right) \right] + V_{SBIAS} - V_{LED} \right\} \end{aligned} \quad (5)$$

# AC Analysis

The feedback network, including  $C_1$ ,  $C_2$  and  $R_3$  is represented as  $Z_{FB}$ .

$$Z_{FB}(s) = \frac{1 + sC_1 R_3}{s(C_1 + C_2)(1 + s \frac{C_1 C_2}{C_1 + C_2} R_3)} \quad (6)$$

$$\frac{\hat{v}_A(s)}{\hat{v}_{OUT}(s)} = \frac{Z_{FB}(s)}{R_1} \quad (7)$$


$$\hat{v}_A(s) = -\hat{i}_{LED}(s) \times R_4 \quad (8)$$

$$\hat{v}_{FB}(s) = -CTR \times R_5 \times \hat{i}_{LED}(s) \quad (9)$$

$$\frac{\hat{v}_{FB}(s)}{\hat{v}_{OUT}(s)} = CTR \times \frac{R_5}{R_4} \times \frac{Z_{FB}(s)}{R_1} = CTR \times \frac{R_5}{R_4} \times \frac{1 + sC_1 R_3}{sR_1(C_1 + C_2)(1 + s \frac{C_1 C_2}{C_1 + C_2} R_3)} \quad (10)$$

2-pole 1-zero (Type II)
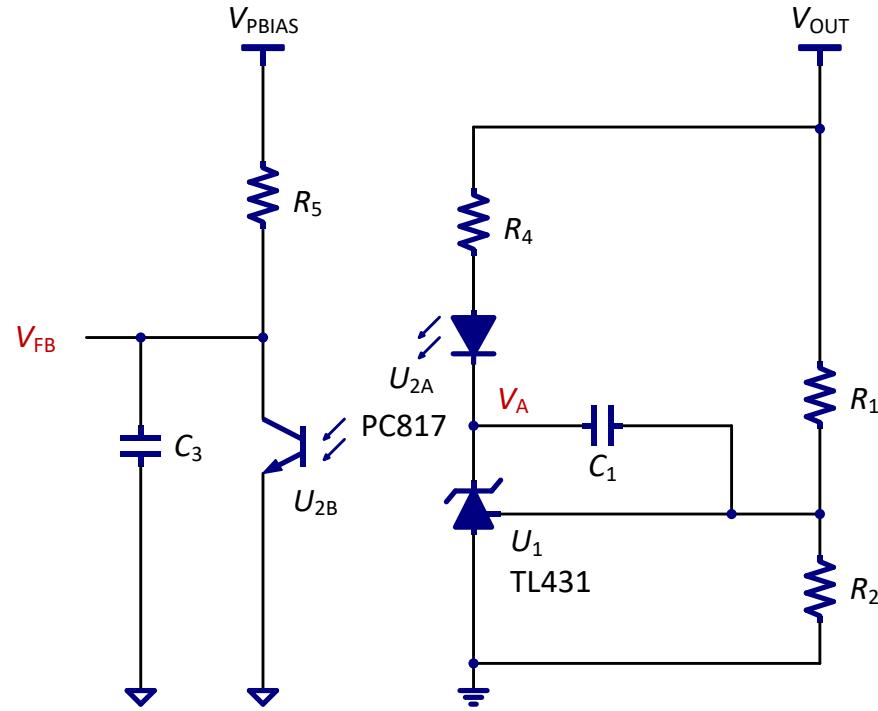
## Configuration II (the most commonly adopted)



- TL431 is powered by output voltage.
- Perturbation on  $V_{OUT}$  can go through both voltage divider (error amplifier) and opto-diode directly.

## DC Analysis

$$V_A = K \cdot \left[ \left( V_{\text{OUT}} \times \frac{R_1}{R_1 + R_2} \right) - V_{\text{REF}} \right] \quad (11)$$

$$V_A = V_{\text{OUT}} - I_{\text{LED}} \times R_4 - V_{\text{LED}} \quad (12)$$

$$I_{\text{TR}} = CTR \times I_{\text{LED}} \quad (13)$$

$$V_{\text{PBIAS}} = I_{R5} \times R_5 + V_{\text{FB}} = I_{\text{TR}} \times R_5 + V_{\text{FB}} \quad (14)$$

Similar with (1) ~ (4), except  $V_{\text{SBIAS}}$  in (2) is changed to  $V_{\text{OUT}}$ .

2-pole 1-zero (Type II)

## AC Analysis

$$\frac{\hat{v}_A(s)}{\hat{v}_{\text{OUT}}(s)} = \frac{Z_{\text{FB}}(s)}{R_1} \quad (15)$$

$$\hat{v}_A(s) = \hat{v}_{\text{OUT}}(s) - \hat{i}_{\text{LED}}(s) \times R_4 \quad (16)$$


$$\hat{v}_{\text{FB}}(s) = -CTR \times \frac{R_5}{1 + sR_5C_3} \times \hat{i}_{\text{LED}}(s) \quad (17)$$

$$\frac{\hat{v}_{\text{FB}}(s)}{\hat{v}_{\text{OUT}}(s)} = CTR \times \frac{R_5}{R_4} \times \frac{1 + \frac{Z_{\text{FB}}(s)}{R_1}}{1 + sR_5C_3} \quad (18)$$

$$Z_{\text{FB}}(s) = \frac{1}{sC_1} \quad (19)$$


$$\frac{\hat{v}_{\text{FB}}(s)}{\hat{v}_{\text{OUT}}(s)} = CTR \times \frac{R_5}{R_4} \times \frac{1 + sR_1C_1}{sR_1C_1(1 + sR_5C_3)} \quad (20)$$

# Superposition

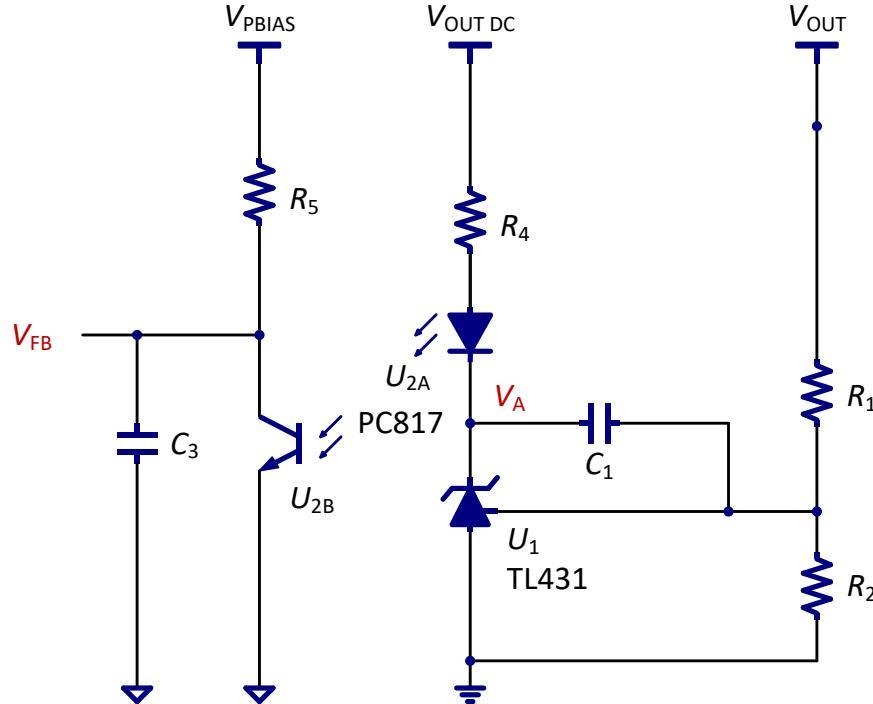

$$\frac{\hat{v}_{FB}(s)}{\hat{v}_{OUT}(s)} = CTR \times \frac{R_5}{R_4} \times \frac{1}{sR_1C_1(1 + sR_5C_3)}$$

(Slow Lane)

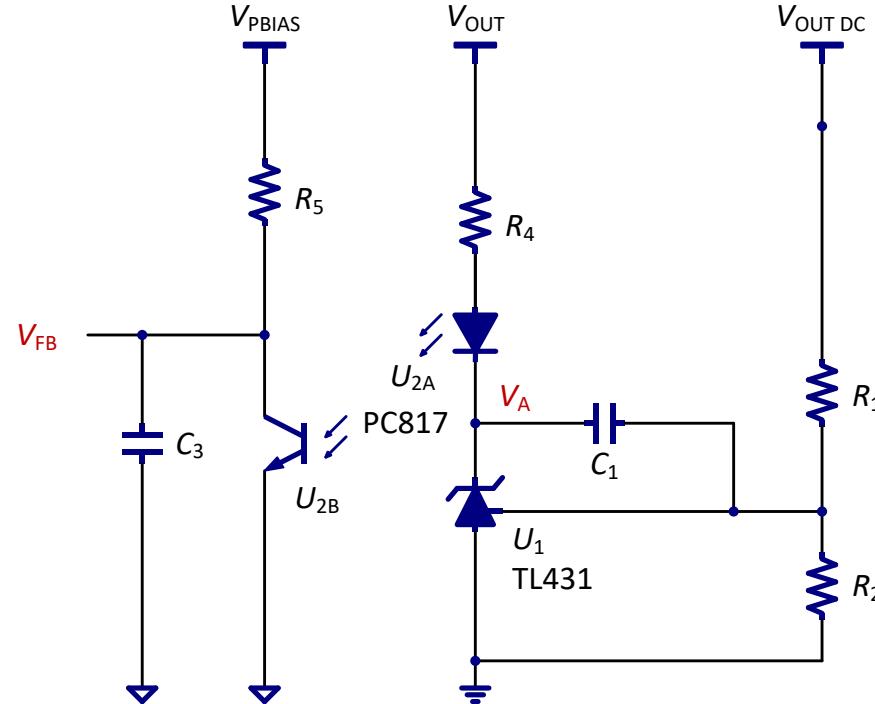

$$\frac{\hat{v}_{FB}(s)}{\hat{v}_{OUT}(s)} = CTR \times \frac{R_5}{R_4} \times \frac{1}{1 + sR_5C_3}$$

(Fast Lane)

- Superposition can be applied to get slow-lane and fast-lane transfer function with respectively.

# Bode plot of a Type II (2P1Z) Compensator

