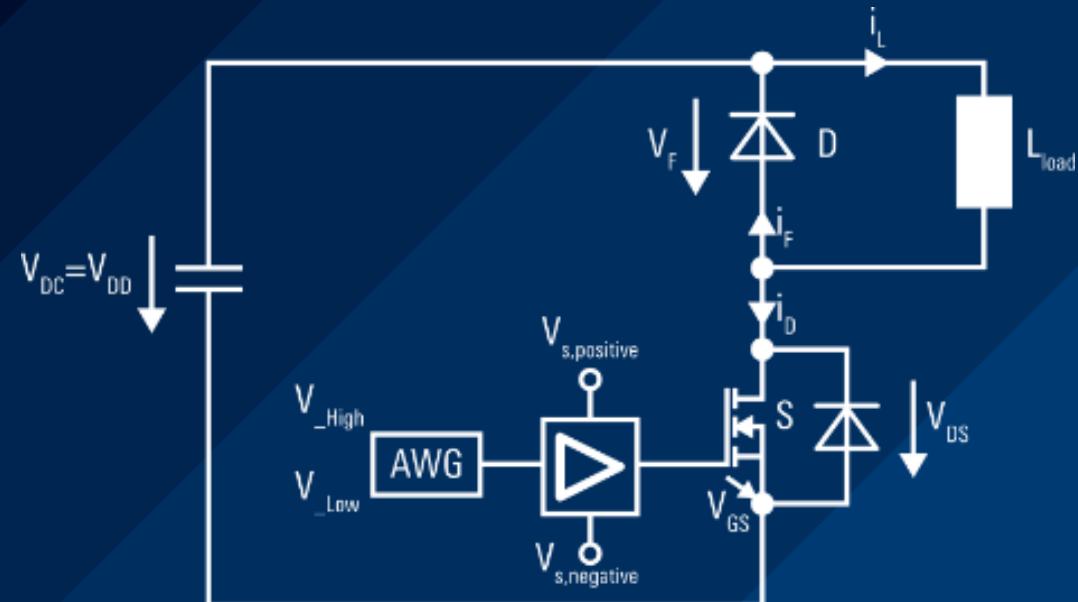


新一代示波器與雙脈衝測試



CS Wong 黃俊雄
Product Manager (Oscilloscope)
示波器產品經理


ROHDE & SCHWARZ
Make ideas real



OUTLINE

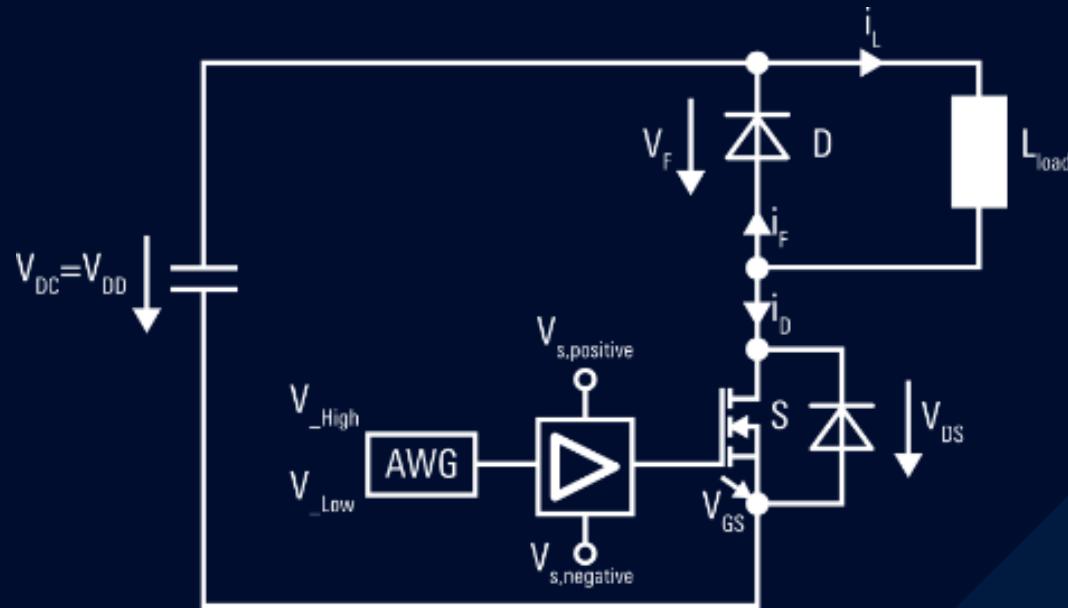- ▶ Overview of Double Pulse Test 雙脈衝測試概述
- ▶ Double Pulse Test Setup 雙脈衝測試設置
- ▶ Today's oscilloscope 示波器新功能
- ▶ Example of measurements 測量範例





2023 寬能隙半導體之設計及雙脈衝測試研討會

OVERVIEW OF DOUBLE PULSE TEST 雙脈衝測試概述

DOUBLE-PULSE TESTING 雙脈衝測試

MANY USE-CASES 應用

Datasheet generation

Maximum ratings

1 Maximum ratings

For optimum lifetime and reliability, Infineon recommends operating conditions that do not exceed 80% of the maximum ratings stated in this datasheet.

Table 2 Maximum ratings

Parameter	Symbol	Value	Unit
Drain source voltage, $T_{\text{J}} \geq 25^{\circ}\text{C}$	V_{DS}	1200	V
DC drain current for $R_{\text{DS(on),max}}$, limited by $T_{\text{J,max}}$, $V_{\text{DS}} = 18\text{V}$, $T_{\text{C}} = 25^{\circ}\text{C}$	I_{D}	56	A
$T_{\text{C}} = 100^{\circ}\text{C}$		47	
Pulsed drain current, t_{r} , limited by $T_{\text{J,max}}$, $V_{\text{DS}} = 18\text{V}$	$I_{\text{D,pulse}}^1$	169	A
DC body diode forward current for $R_{\text{SD(max)}}$, limited by $T_{\text{J,max}}$, $V_{\text{DS}} = 0\text{V}$, $T_{\text{C}} = 25^{\circ}\text{C}$	I_{SD}	56	A
$T_{\text{C}} = 100^{\circ}\text{C}$		36	
Pulsed body diode current, t_{r} , limited by $T_{\text{J,max}}$	$I_{\text{SD,pulse}}^1$	169	A
Gate-source voltage ²			
Max transient voltage, < 1% duty cycle	V_{GS}	-7 ... 23	V
Recommended turn-on gate voltage ³	V_{GSS}	15 ... 18	

Module production test



Module selection



Converter Design




WHY DOUBLE PULSE TESTING 雙脈衝測試主要原因


EXAMPLE: TWO-LEVEL CONVERTER 雙準位轉換器

Active


Buck 降壓式

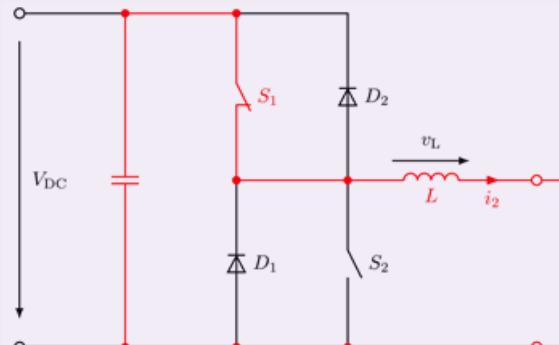

Boost 升壓斬波

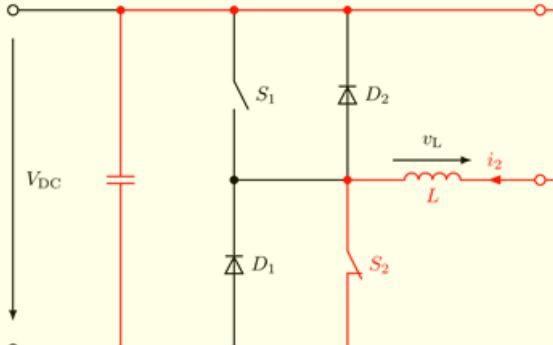

Freewheeling

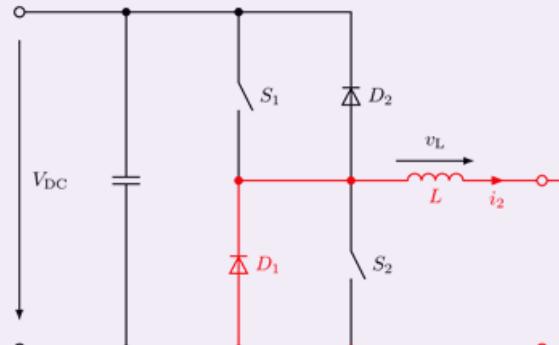


Rohde & Schwarz

- ▶ A double-pulse test allows to cover all four basic operation modes
- ▶ All main parameters can be measured
 - Switching losses 開關損耗
 - Reverse recovery losses 反向恢复损耗
 - Switching times
 - Turn-on/off delay time (TDelay-On/Off)
 - Rise and fall times (TRise, TFall)
 - Speed (di/dt , dv/dt)
 - Switching Energy (E_{ON} , E_{OFF} , E_{RR})






THEORY AND TEST PROCEDURE

原理及測試步驟

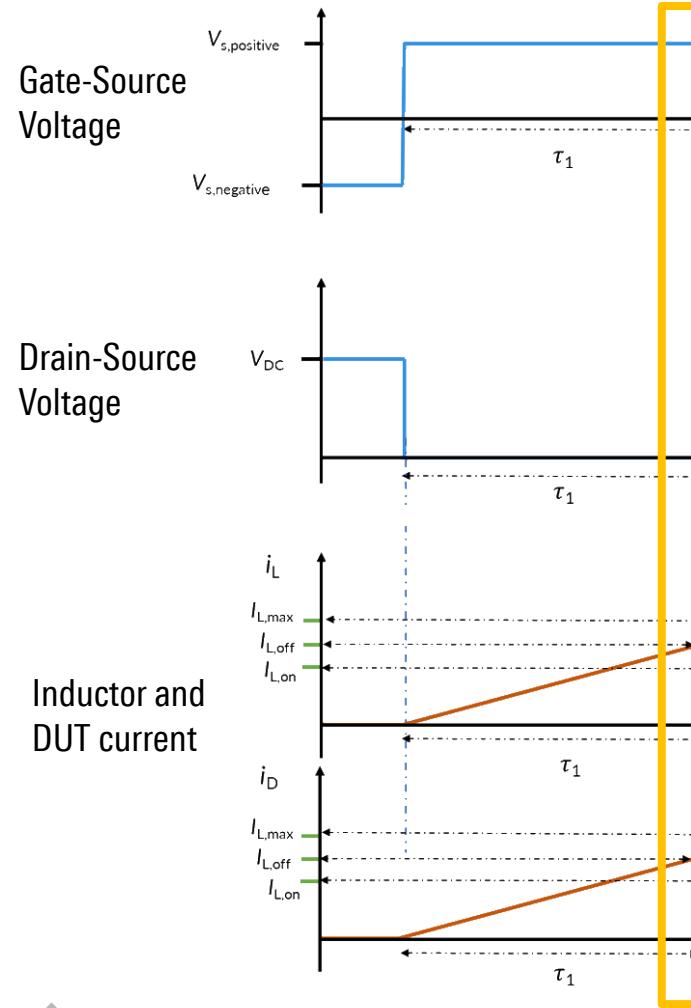

Turn-off Event

Turn-on Event

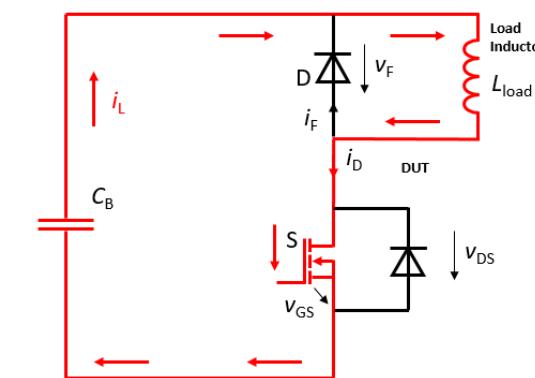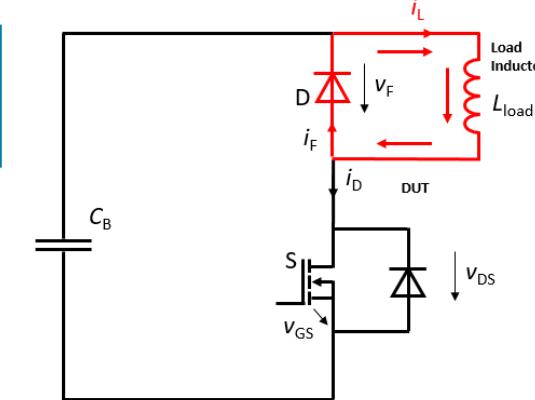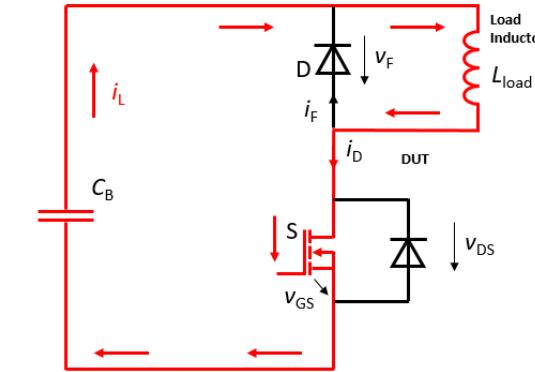


Interval τ_1
Inductor is
“charged”

Interval τ_{break}
Turn-off
measurement at
target current

Interval τ_2
Turn-on
measurement at
target current

BASIC OBSERVATION WAVEFORM

基本實驗波形

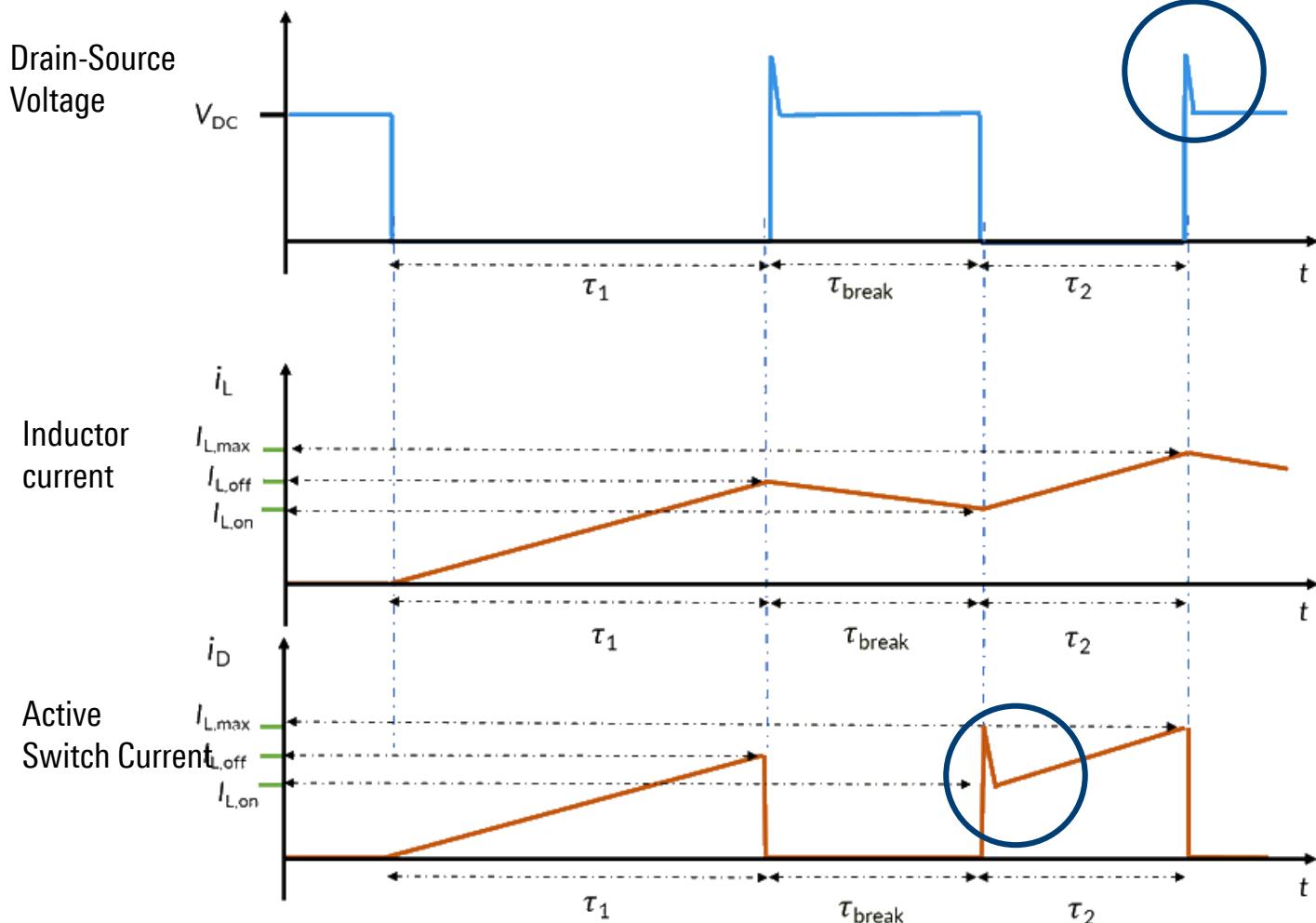


Loop inductances voltage spikes
雜散電感導致的電壓尖峰




Reverse Recovery Current
反向恢復電流

SWITCHING LOSS MEASUREMENT


開關損耗測量

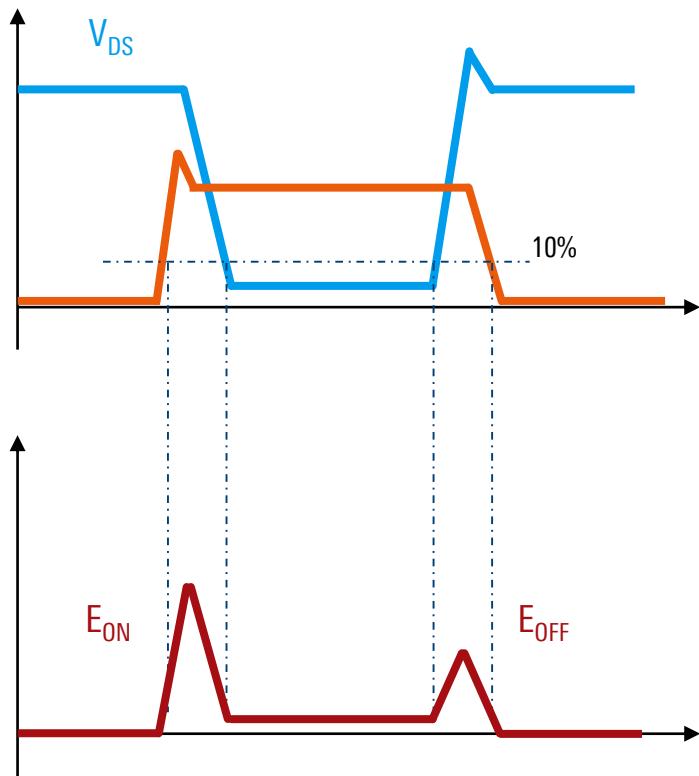

MOSFET Turn-on (E_{ON})

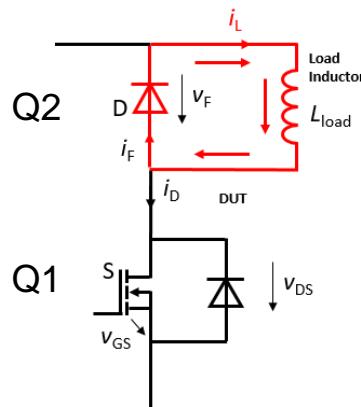


MOSFET Turn-off (E_{OFF})

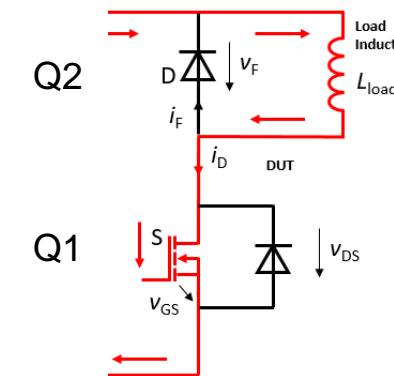

- I_D start to flow through Q2
- V_{DS} remain across Q2 until diode finished conducting
- $P_{ON} = V_{DS} \times I_D$

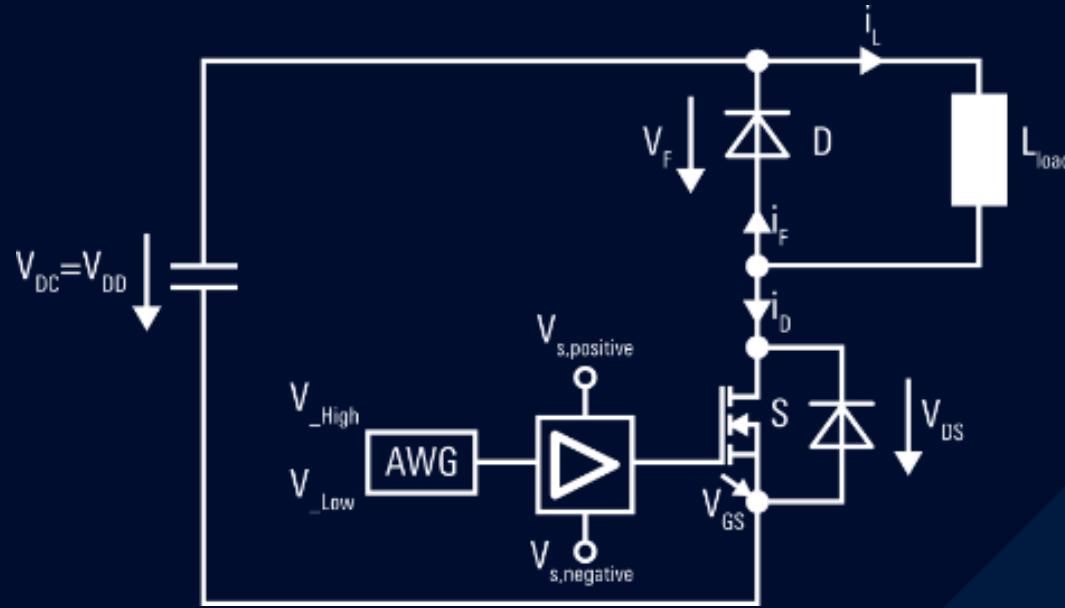
- V_{DS} rise across Q2
- I_D remain flowing through Q2 until diode is forward biased
- $P_{OFF} = V_{DS} \times I_D$



2023 寬能隙半導體之設計及雙脈衝測試研討會
DOUBLE PULSE TEST SETUP
雙脈衝測試設置

TYPICAL SETUP


建立雙脈衝測試平臺

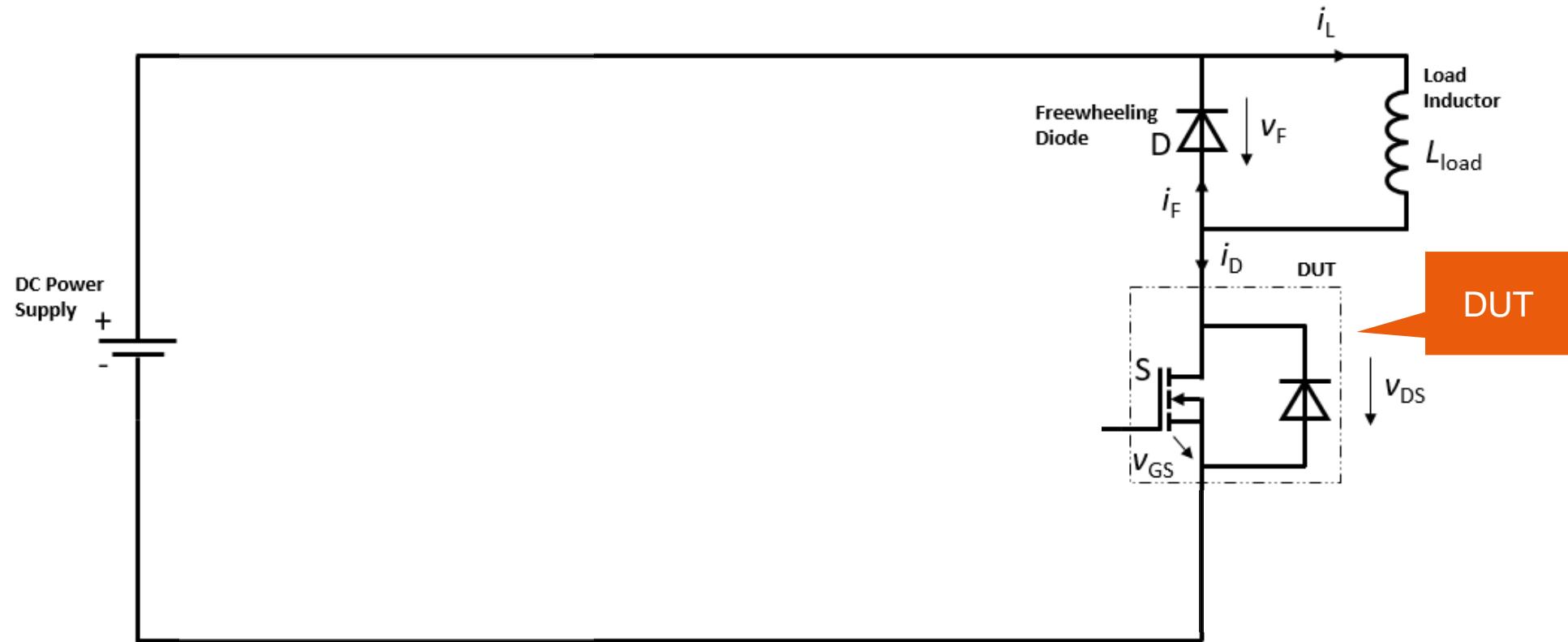

TYPICAL SETUP

建立雙脈衝測試平臺

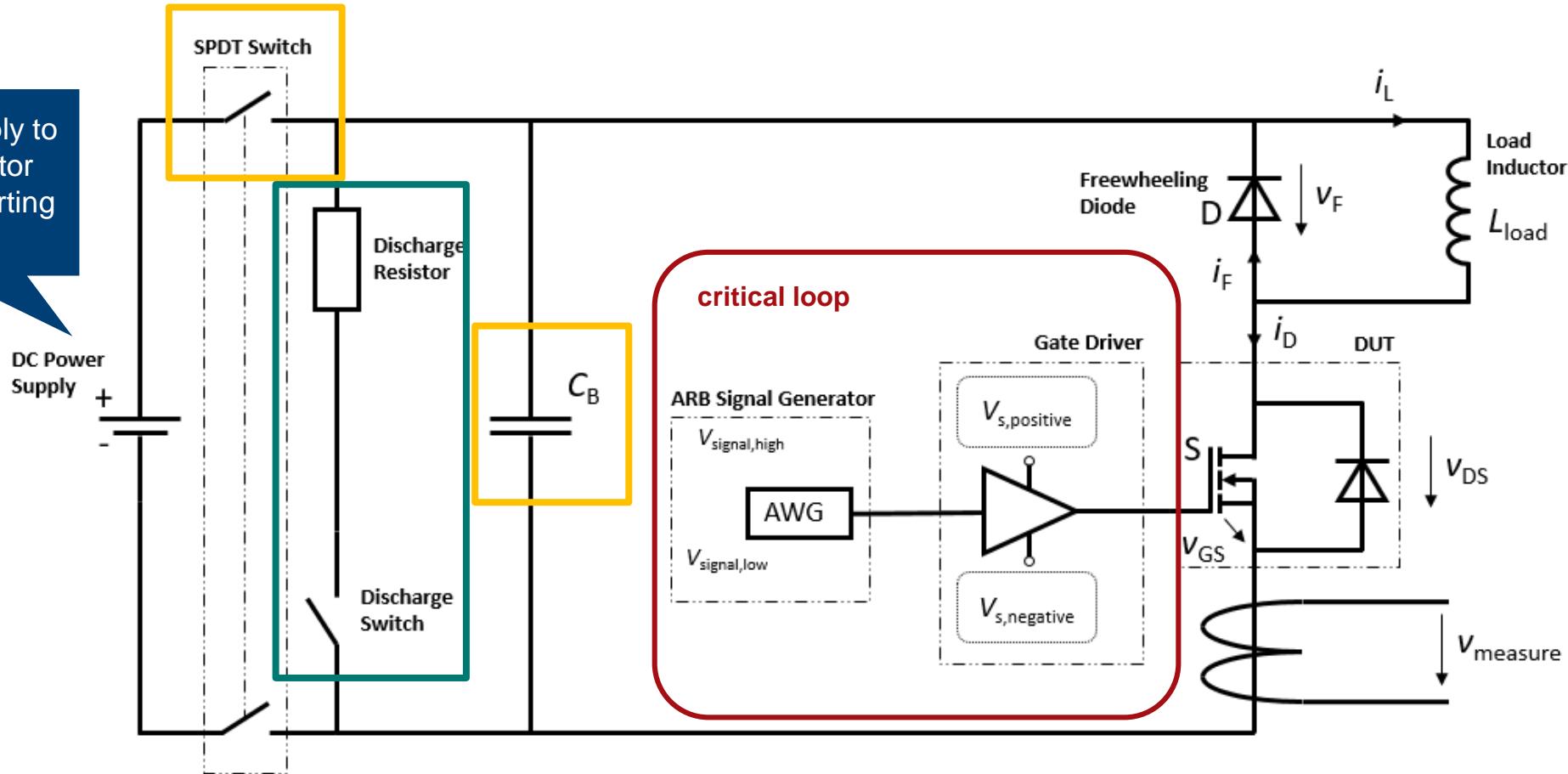DC Power Supply to charge capacitor bank before starting the test




INSTRUMENT INVOLVED

相關儀器

DC Power Supply to charge capacitor bank before starting the test



Floating output important!

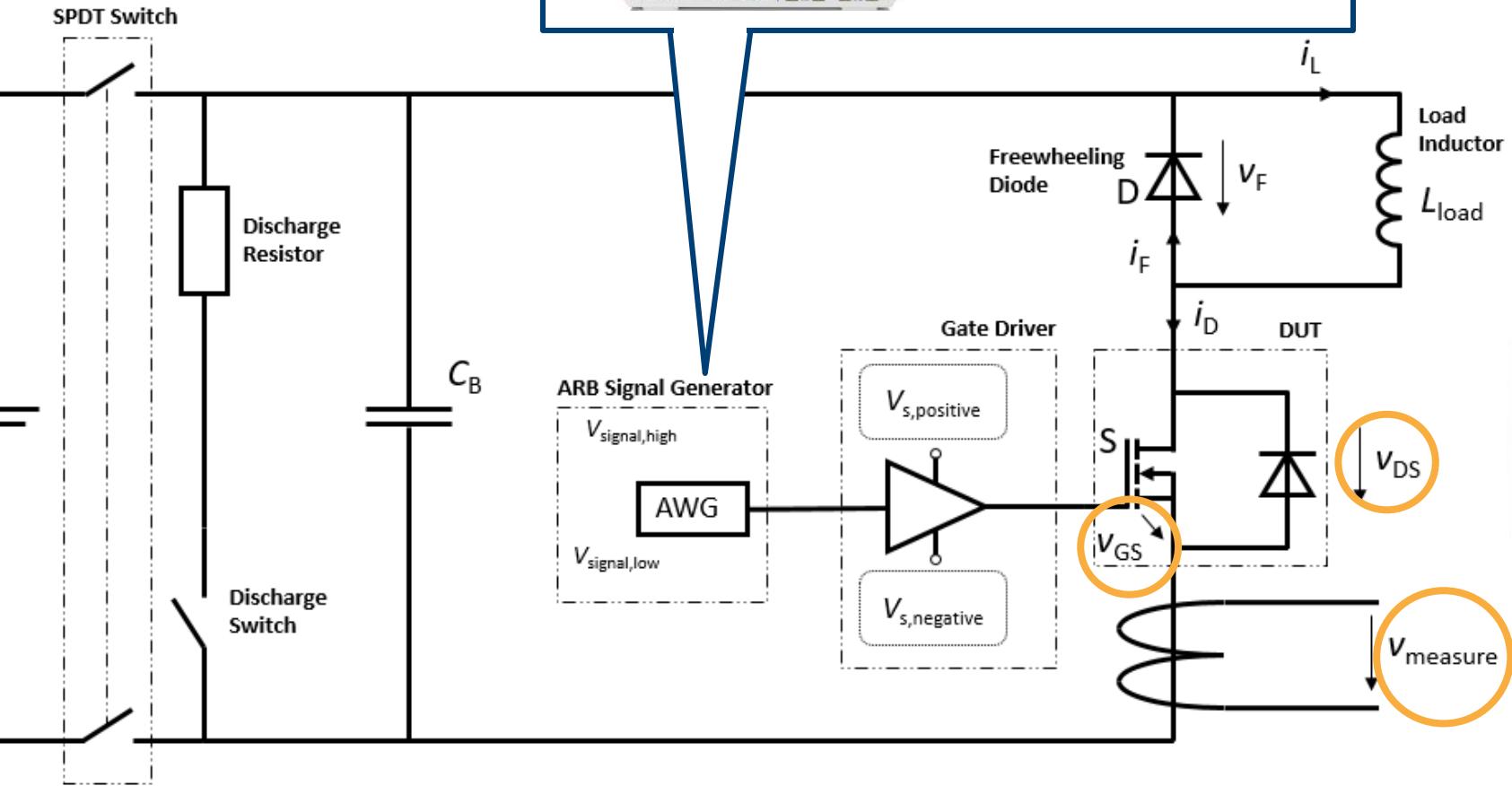


HMF2550 ARB Generator



RTM3000 Oscilloscope



DBT SW

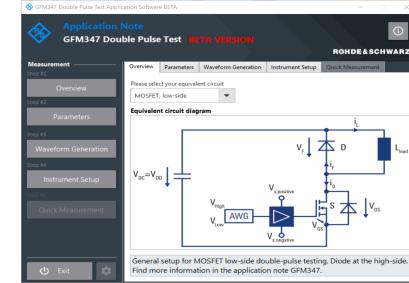

Load inductor,
“stores” current for
the actual test

MXO 4 Oscilloscope





RTM3000 Oscilloscope



SETTING UP THE PULSE

建立雙脈衝波形的特性

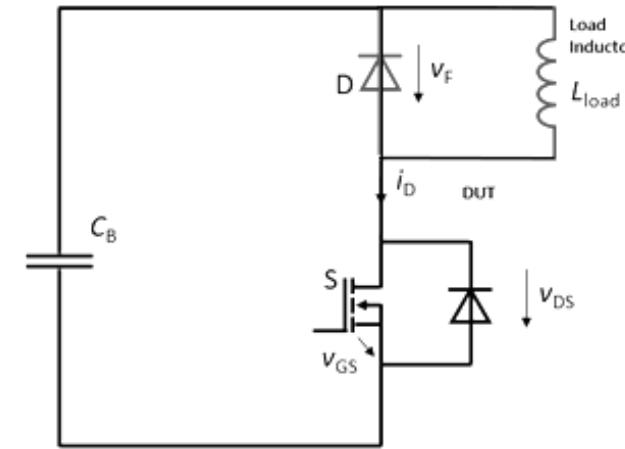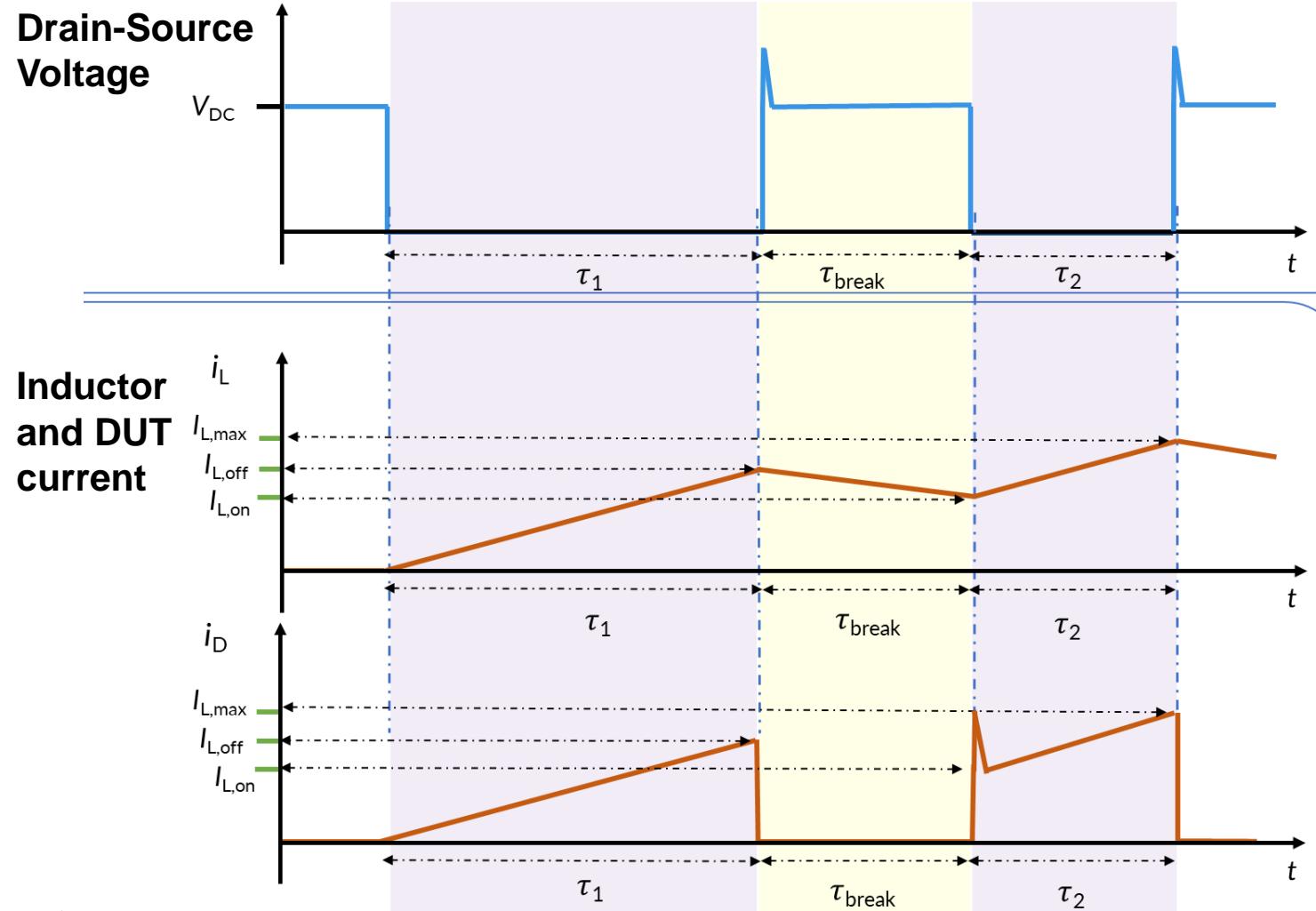

$$\tau_1 = L_{LOAD} * \frac{i_L}{V_{DC}}$$

τ_{break} is set long enough for the voltage and currents to settle out

τ_2 usually short enough not to exceed the reverse bias SOA

$\tau_1 + \tau_2$ should not be too large to create self heating of the DUT

SETTING UP THE MEASUREMENT

測量搭配 – 電壓探棒篇

► Passive probes are sufficient for floating setups

- Typically possible for device characterization setups
- Care has to be taken on any (unintentional) grounding


► Broadband differential probes are an attractive alternative for floating setups

- Very high bandwidth of up to 1 or 2 GHz
- Very low loading ($\sim 1\text{pF}$)
- Input voltage range of $\pm 50\text{V DC}$ with 10:1 attenuator


► High-voltage differential probes are necessary if system-under-test is grounded

- Typically the case for prototypes
- Provide CMRR to suppress switch-node signal

Floating High-side DUT

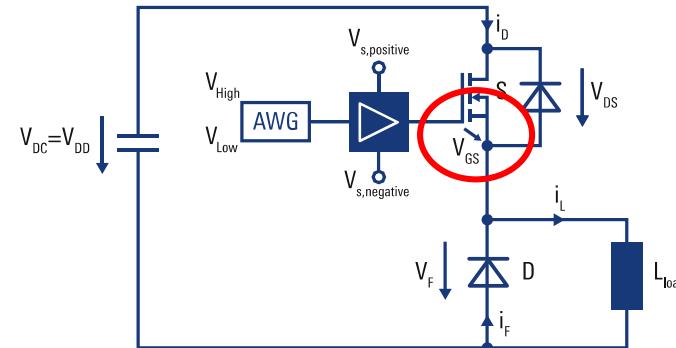

Grounded High-side DUT

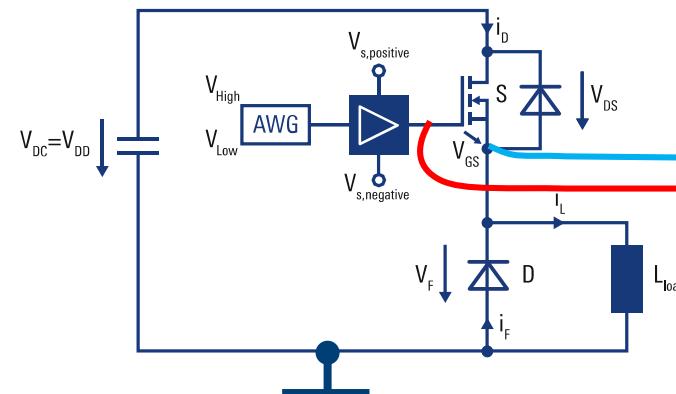


SETTING UP THE MEASUREMENT


測量搭配 – 電流探棒篇

► Basic requirements

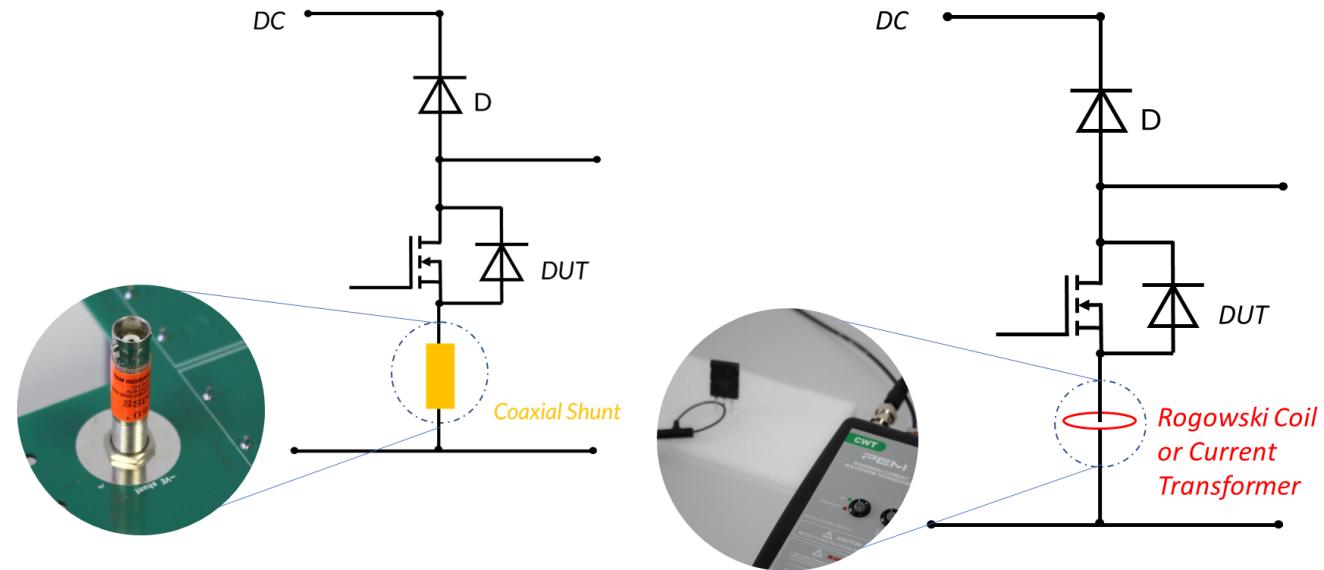- High measurement bandwidth
- Sensor as small as possible
- Low insertion inductance



	Coaxial shunt	Rogowski probe	Current transformer
Pro's	<ul style="list-style-type: none">• Very high bandwidth (2 GHz)• DC-measurement capability• Very low insertion inductance	<ul style="list-style-type: none">• Physically small, no “design-in” of sensor necessary	<ul style="list-style-type: none">• High bandwidth (~200 MHz)• High current possible
Con's	<ul style="list-style-type: none">• Limited maximum current• Design-in of sensor necessary	<ul style="list-style-type: none">• Limited bandwidth (typically 30-50 MHz but recently also higher bandwidth up to 100 MHz available)• Limited accuracy	<ul style="list-style-type: none">• Design-in of sensor necessary• Large sensor with core, limits the possibility to have low-insertion inductance designs

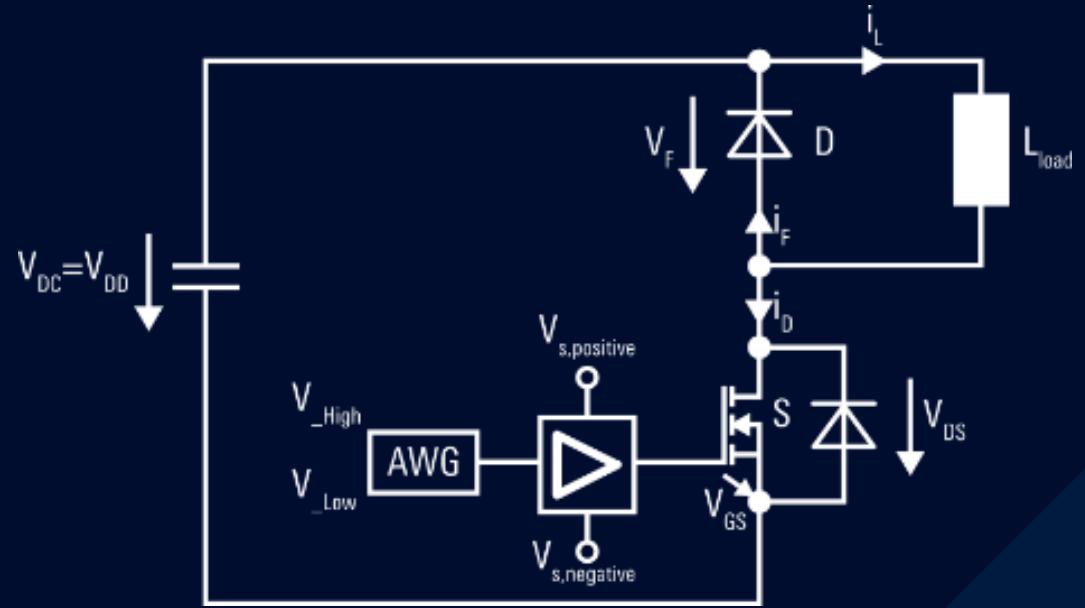

2023 寬能隙半導體之設計及雙脈衝測試研討會 TODAY'S OSCILLOSCOPE 示波器新功能

SIGNAL AND ARB GENERATOR

信號和任意波形產生器



- Signal generator has becoming a norm in basic scope model



- Most scopes are equipped with:
 - Function generator: Predefined waveform shapes with configurable frequency & amplitude
 - Arbitrary generator: Generate any waveform shapes based on generator sampling rate


SIMPLE EDITING VIA EXCEL

簡單編輯

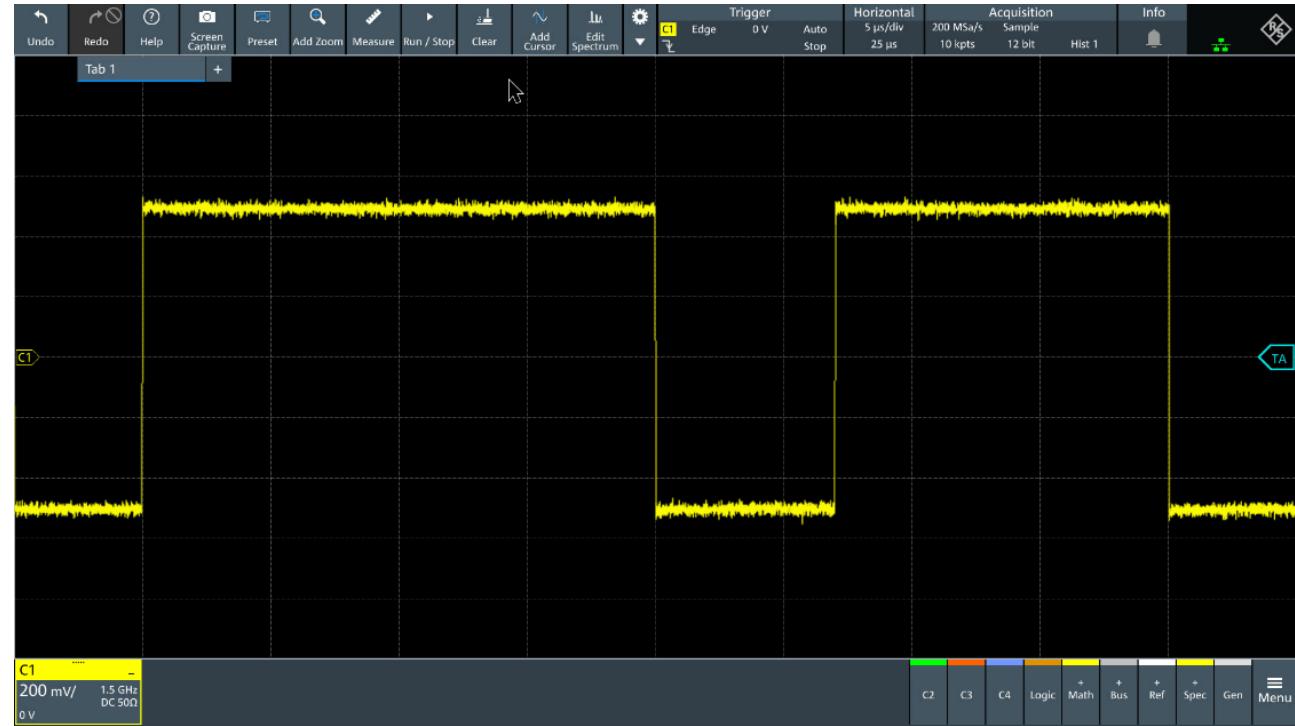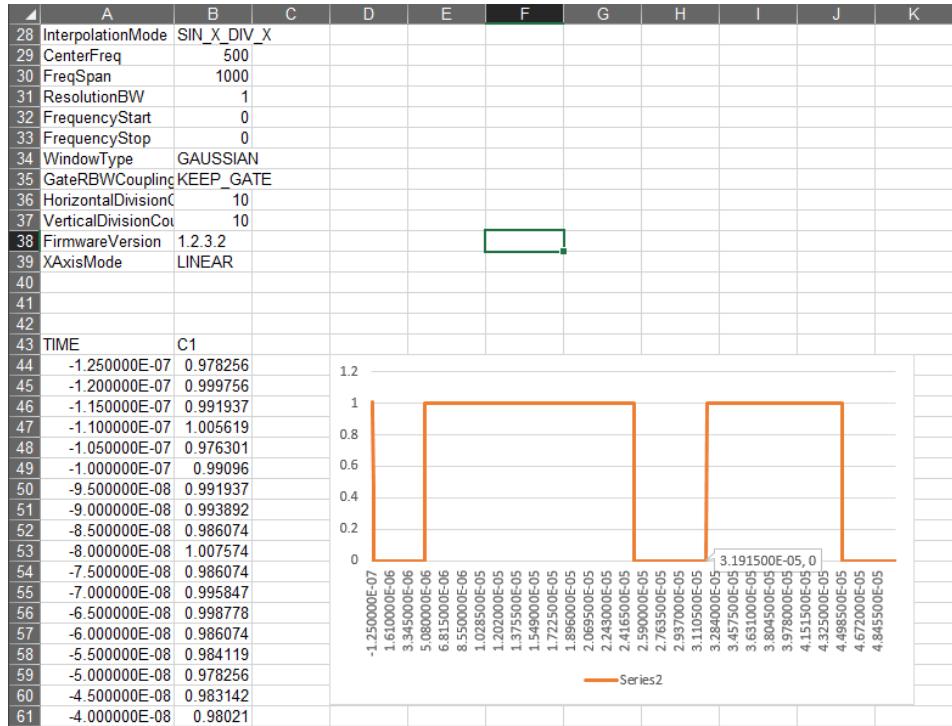

SETTING UP THE ARB WITH APP

建立任意波形軟體

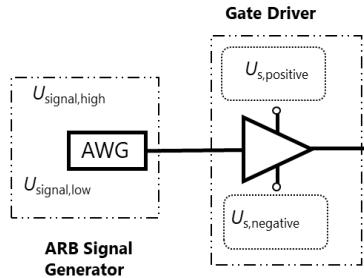


► Important considerations

- Clean turn-on procedure without any spikes
- Right signal levels

► Double pulse test App

- Create ARB waveform based on test parameters
- Recall ARB waveforms using descriptive names
- Directly upload to external ARB or oscilloscope

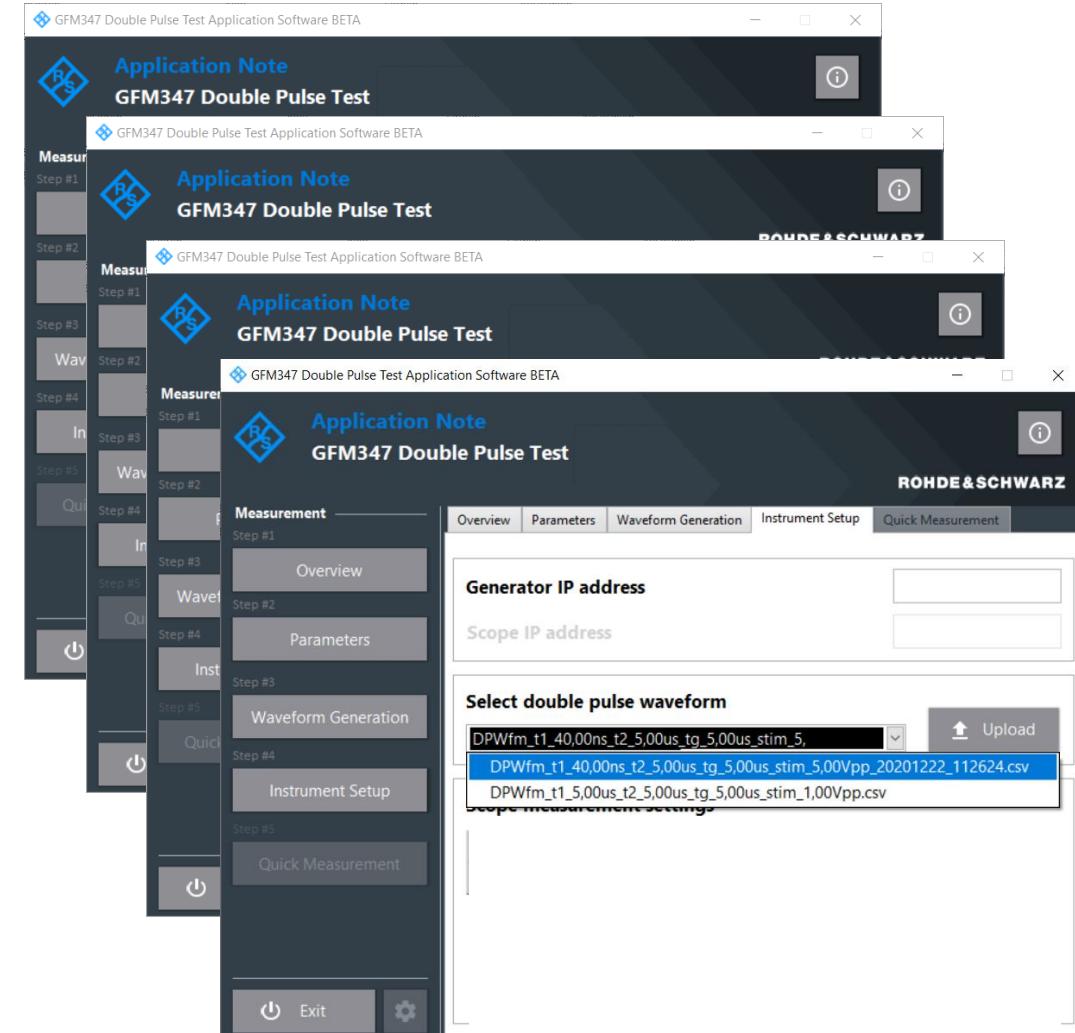► Tips: Always check ARB signal when creating new setup



INDUSTRY'S FIRST...

業界領先...

>4.5 Million wfms / sec

12 -bit ADC 18-bit HD

400 Mpts memory /ch

Digital trigger

2x ARB Gen 100 MHz

Standardized MSO 16ch 5GSa/s




ISOLATE EVENTS WITH MORE PRECISION

更精確地隔離觸發

New in 4000 class
Digital Trigger

Precision triggering and control

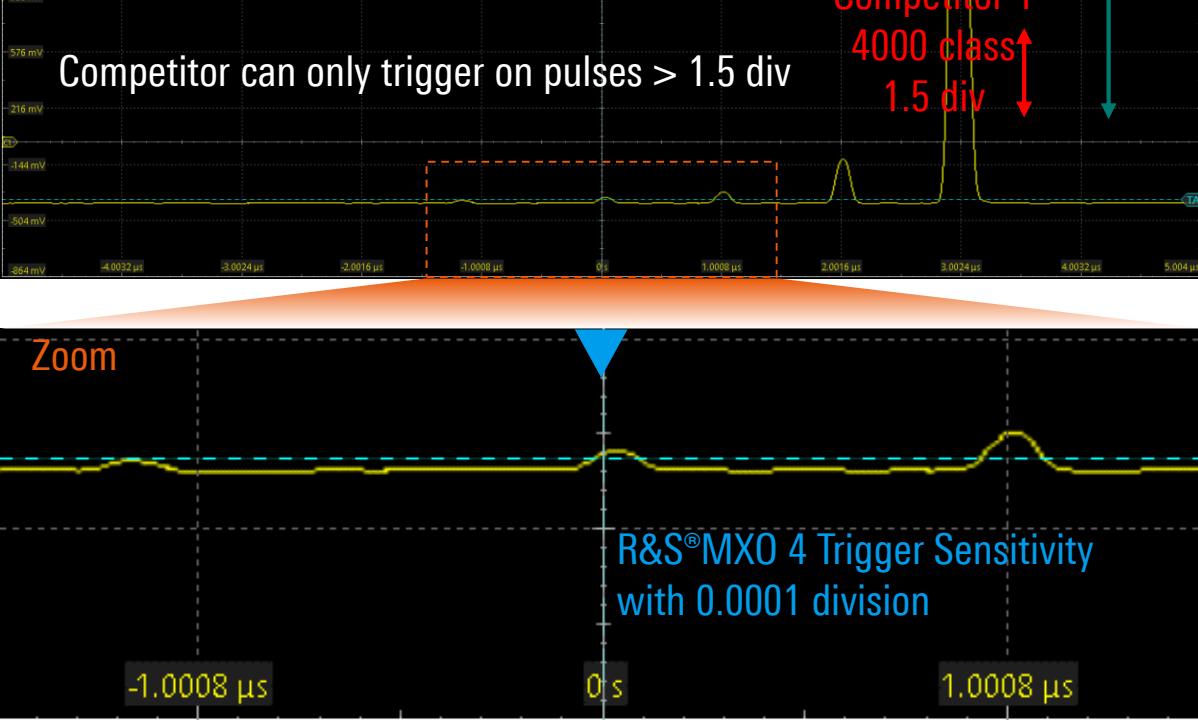Competitor can only trigger on pulses > 1.5 div




Rohde & Schwarz

R&S®MXO 4 features

- Detect trigger event on sampled waveforms
- Adjustable trigger sensitivity
- Minimal trigger jitter < 1ps
- 18 bit architecture


MXO 4 Digital Trigger

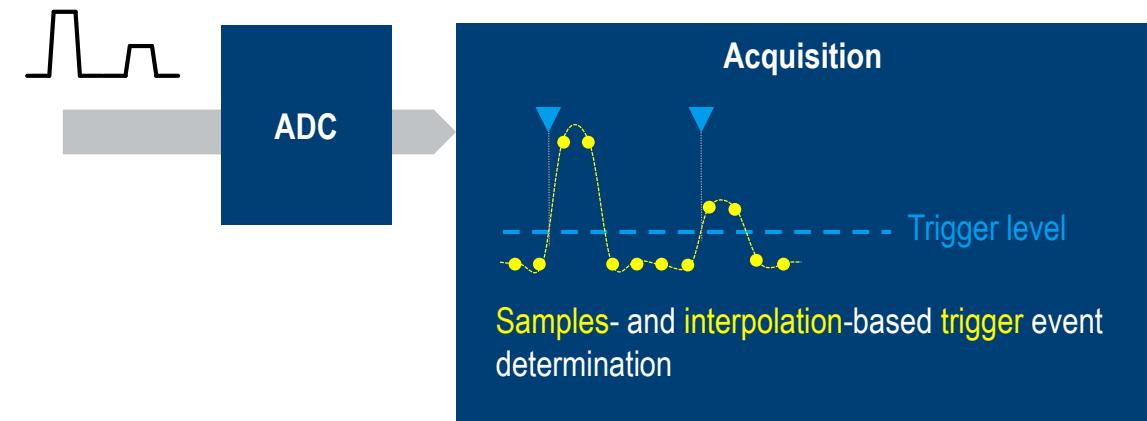

HIGH PRECISION DIGITAL TRIGGER


高精度數位觸發

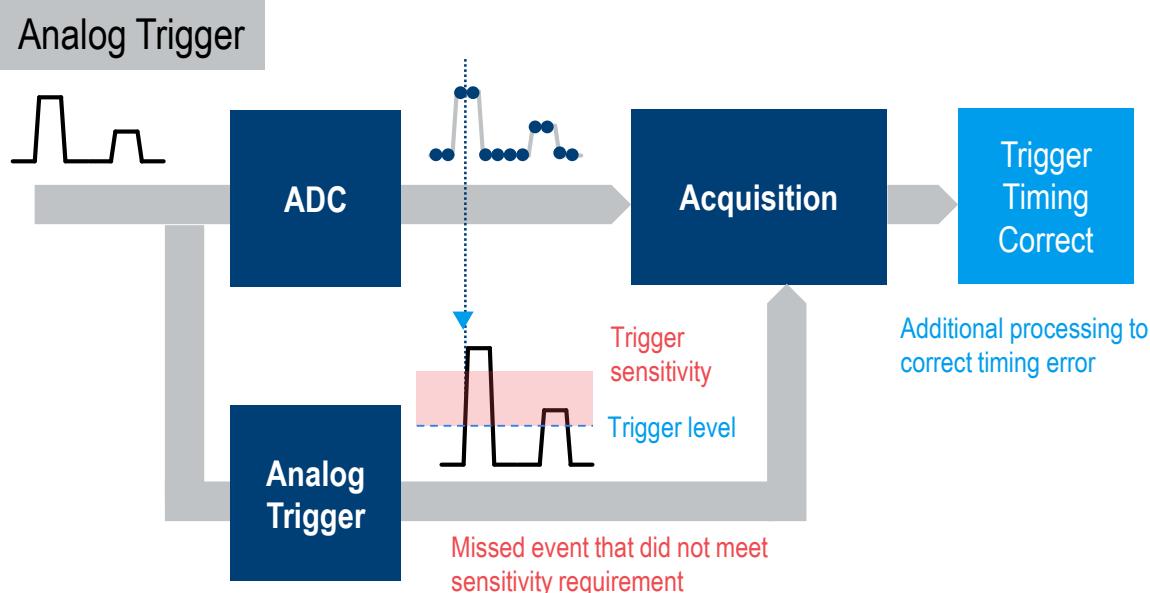- In most 4000 class oscilloscope, limited processing power often use analog trigger



Limitation:

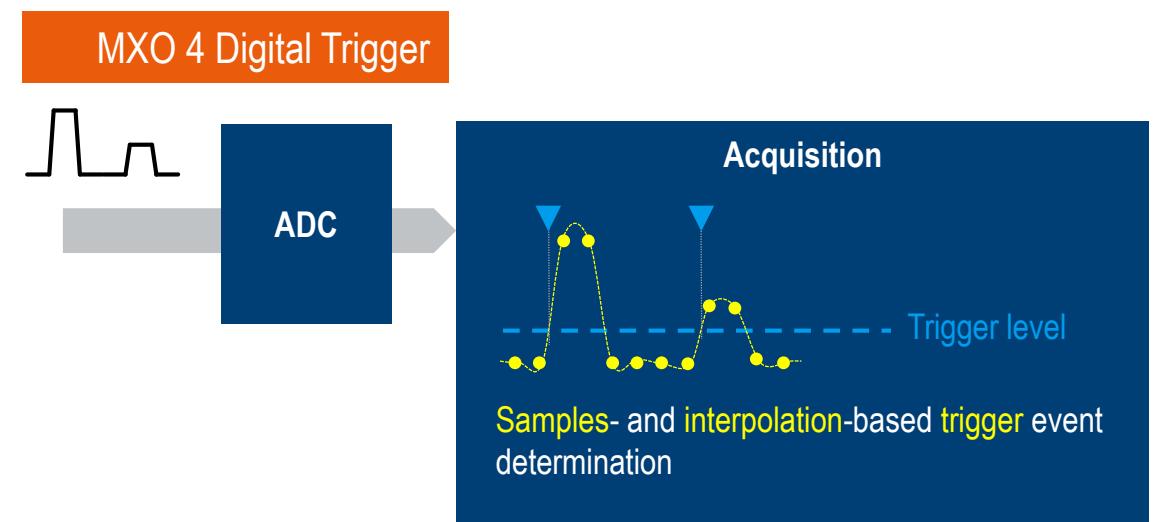- Lower trigger sensitivity, more than 0.5 div
- Timing alignment between trigger and acquisition block




Advantages:

- Trigger sensitivity > ADC resolution
- Essentially no trigger jitter



THE EFFECTS OF PARASITICS

散雜電容電感的影響

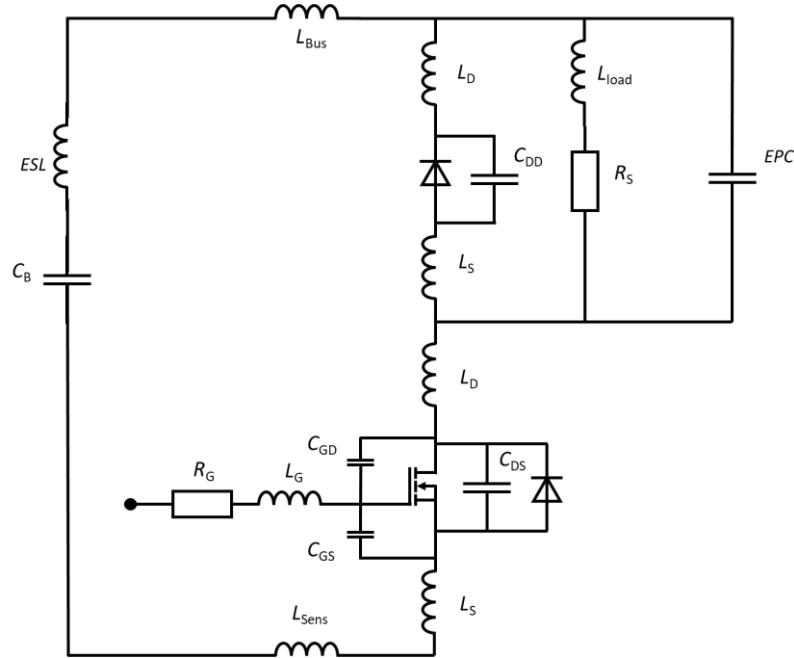


- Parasitic components cause voltage spikes and ringing, EMI interference and reliability problems
- Parasitics in application do not match with datasheet setup
→ device losses differ additional testing required
- Stray inductance of utmost importance

Impact of stray inductance L_σ

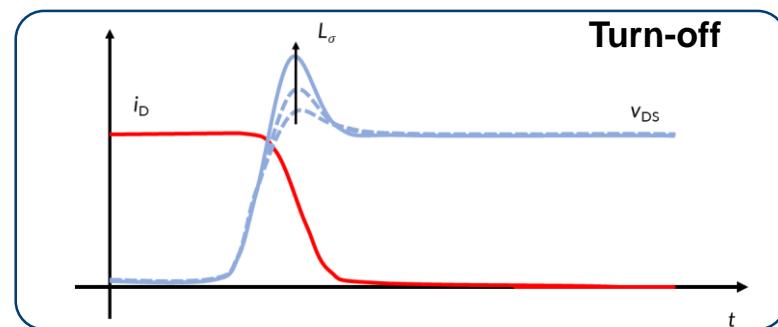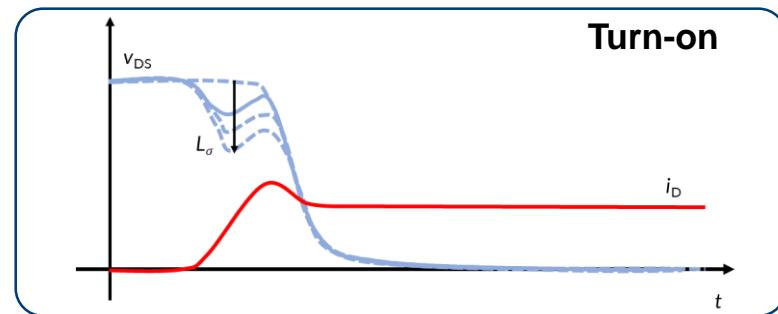


Impact of stored charge $C_{DD} + EPC$

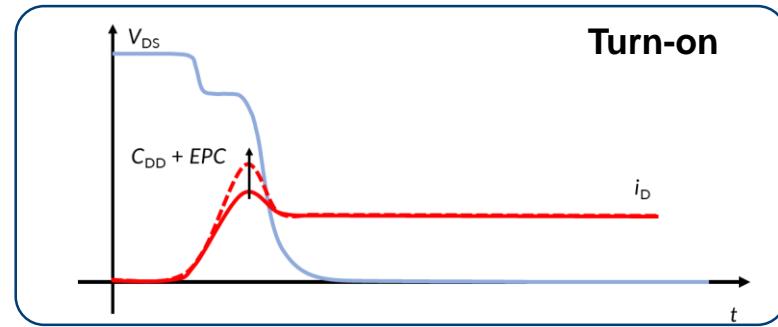

TRIGGERING SWITCHING EDGES




觸發開關邊緣

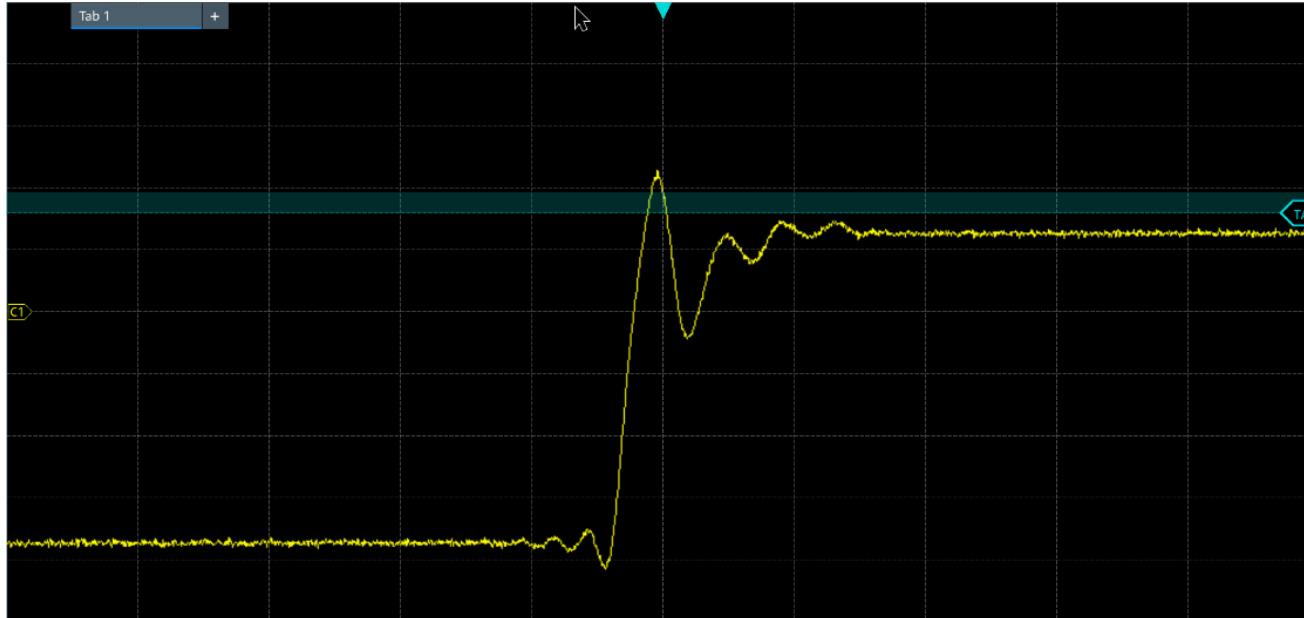


- ▶ Parasitic and Miller effects will cause irregular waveforms noises especially around Turn-On and Turn-Off.
- ▶ Digital trigger allows settings of a signal levels require that help to filter off ringing noises

ADVANCE TOOLS IN MODERN OSCILLOSCOPE

現代示波器中的先進工具

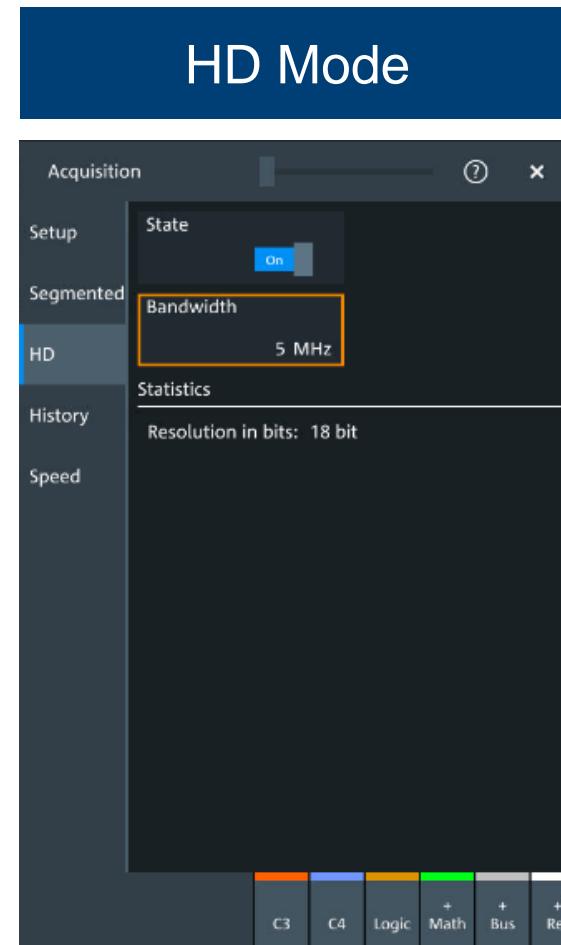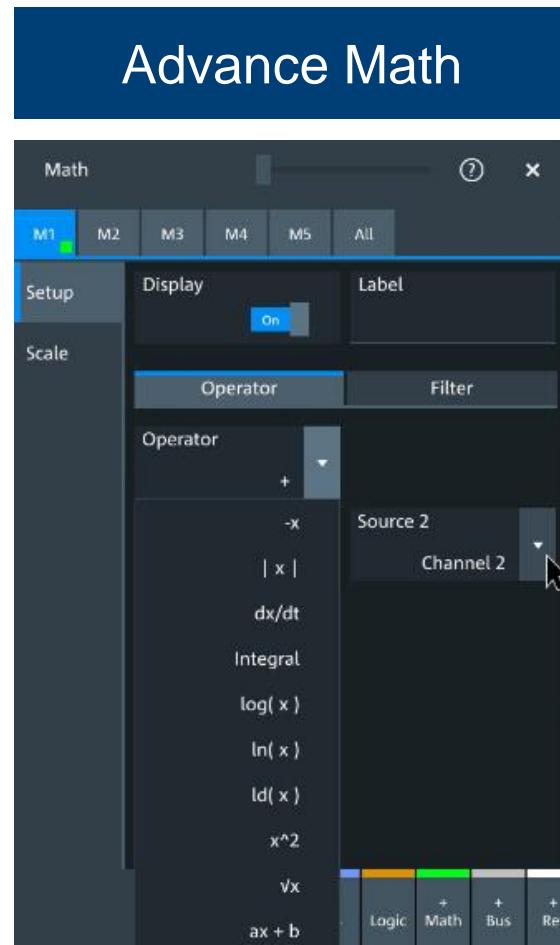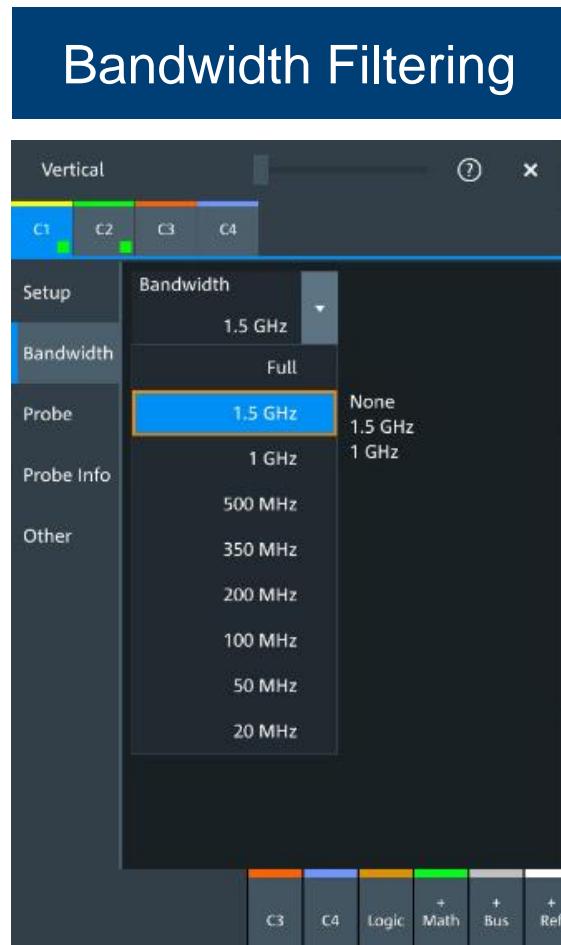

... and a lot more

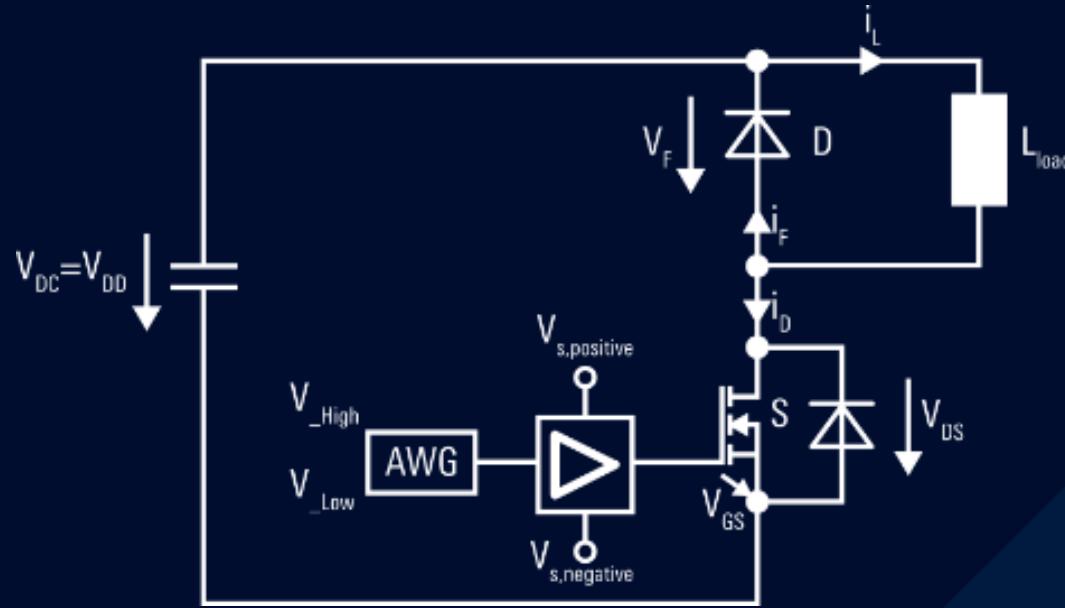


2023 寬能隙半導體之設計及雙脈衝測試研討會

EXAMPLE OF MEASUREMENTS 測量範例


A PRACTICAL EXAMPLE 實測案列

650V 4-PIN TO-247 SIC MOSFET (ROHM), 400V DC LINK



Gate-Source Voltage

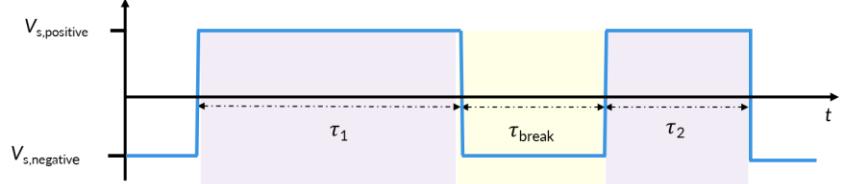

Drain-Source Voltage

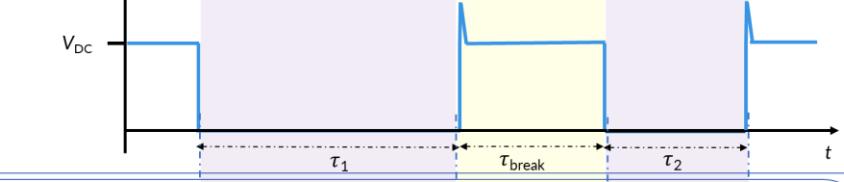

Inductor and DUT current

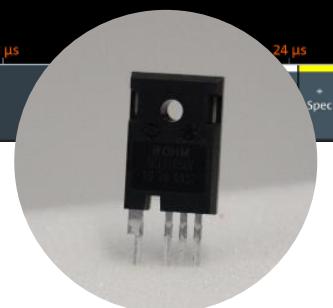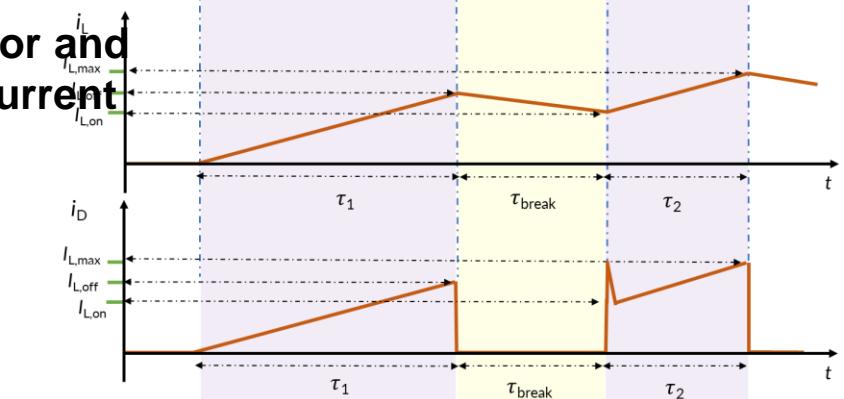


A PRACTICAL EXAMPLE 實測案例

TURN-ON ENERGY 打開功率



$$P_{\text{turn-on}} = v_{\text{DS}}(t) \cdot i_{\text{D}}(t)$$
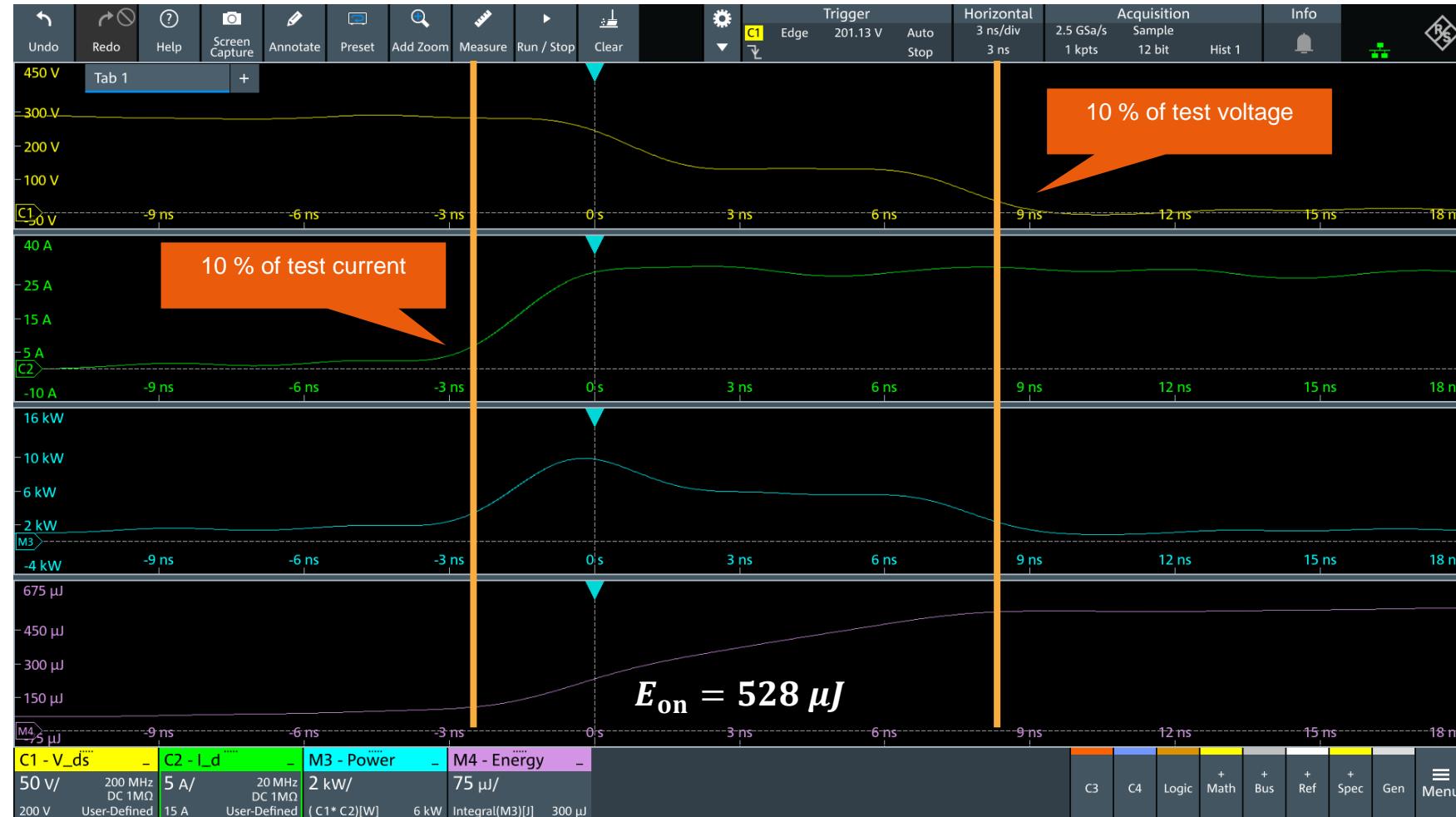
$$E_{\text{on}} = \int_{t_{I_{\text{test}10}}}^{t_{V_{\text{DC}10}}} P_{\text{turn-on}} dt$$



PRACTICAL EXAMPLE 實測案例

DE-SKEW 相位校正

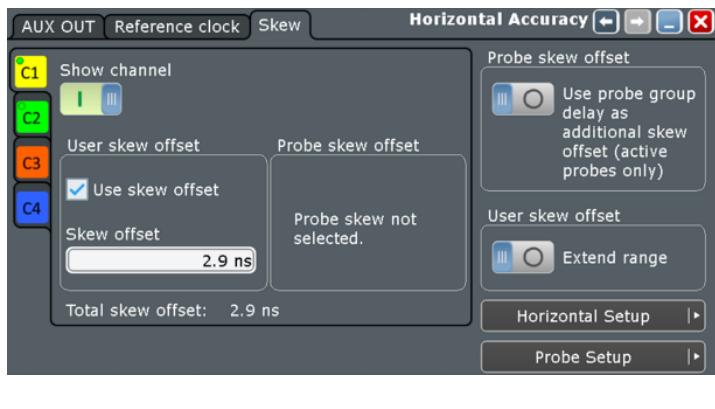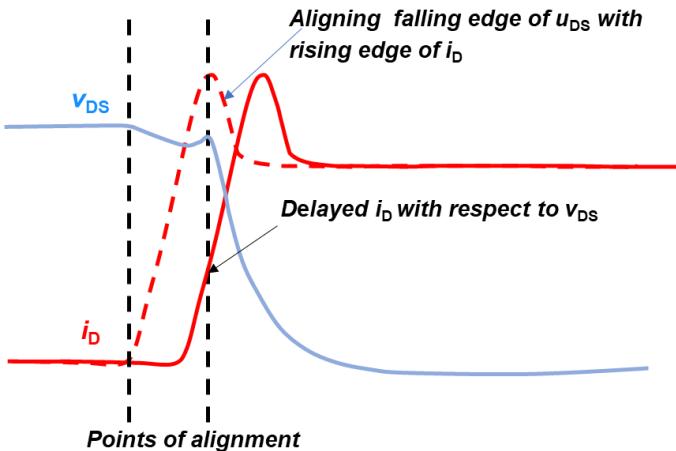

CONCLUSIONS 總結

- ▶ Double pulse test is simple in concept but there are many underlying factors that can impact measurement accuracy
 - DUT setup parasitic
 - Instruments artefacts
 - Basic compensation and deskewing
- ▶ Newer scopes are built with advance tools that help in tackling the above
 - Built in ARB with simple editing
 - Digital trigger with precision
 - Advance Math and Measurement capabilities



2023 寬能隙半導體之設計及雙脈衝測試研討會

THANK YOU
謝謝

For more information:
www.rohde-schwarz.com

ROHDE & SCHWARZ

Make ideas real

