


# Impact of inductors saturation on EMI

***N.Femia***

***Professor of Power  
Electronics***

***University of Salerno***

***President of IPERA S.r.l.***

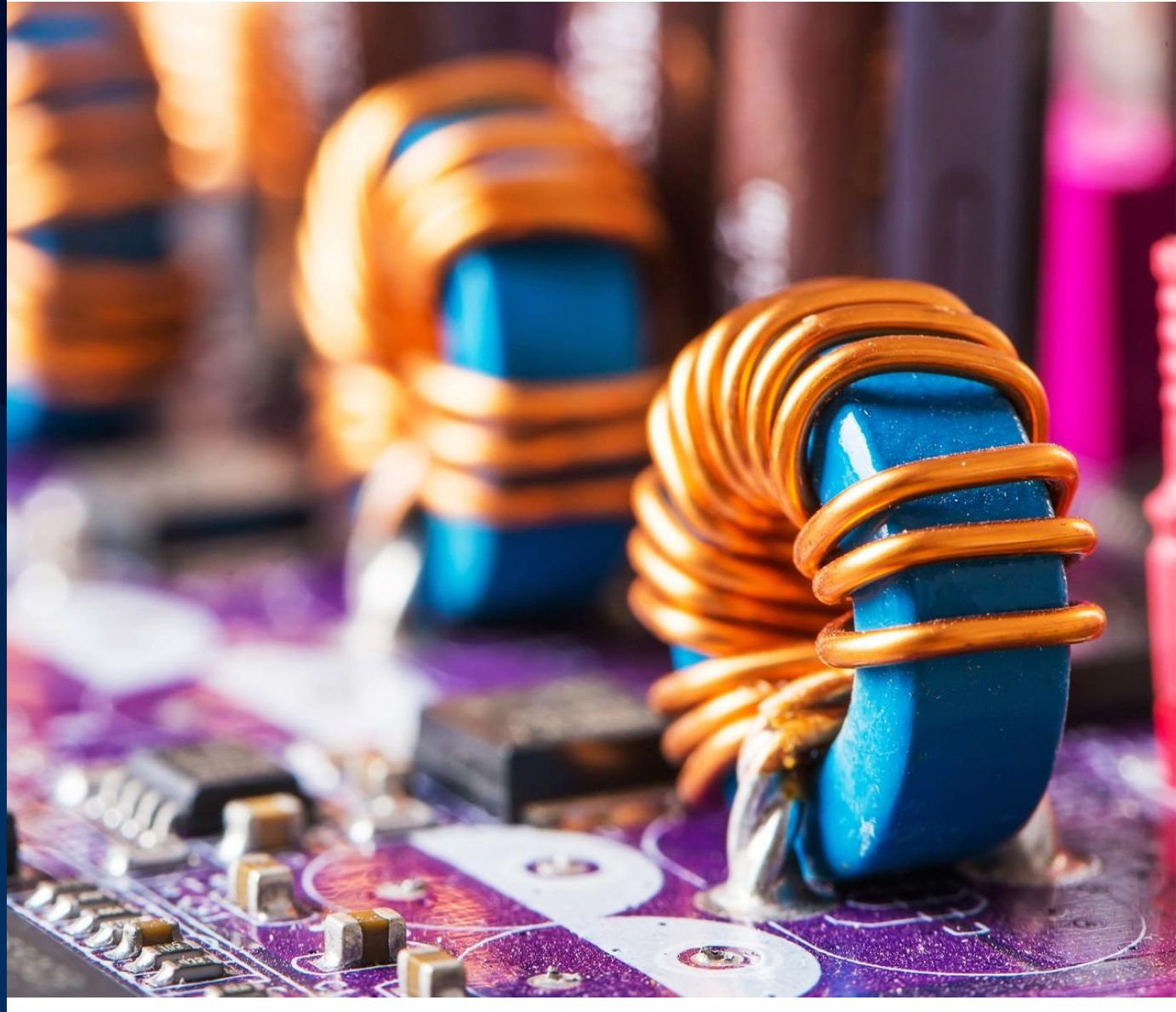




- power inductors inductance and DC and AC power losses can be easily measured by means of an oscilloscope
- power inductors saturation does not cause ripple increase, losses increase and thermal instability, provided that the inductor is intelligently chosen
- saturating inductors may outperform non-saturating inductors




- the effects of power inductors saturation on the operation and performance of SMPS control can be mathematically predicted
- SMPS control techniques sensitive to inductors saturation, like hysteretic and peak-current mode, do not undergo performance degradation or instability issues if the saturating inductor is selected and validated under the worst-case OCP, OVP, and UVP conditions
- (de)saturating inductors allow size/weight and switching loss reduction compared to non-(de)saturating inductors



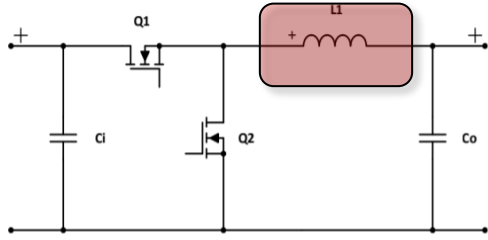
- Can saturable inductors cause EMI issues?
- Can saturable inductors be used in EMI filters design?
- Can saturable inductors provide benefits in EMI reduction?




buck

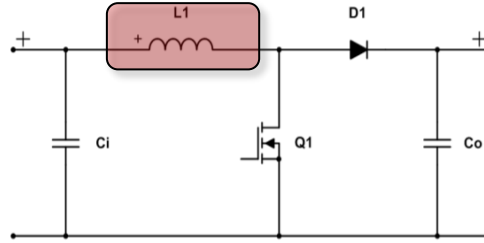


boost

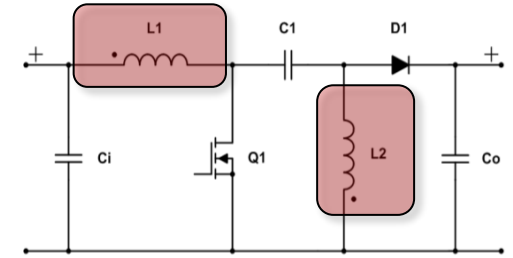


SEPIC

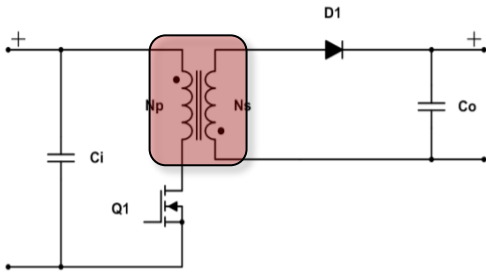

flyback

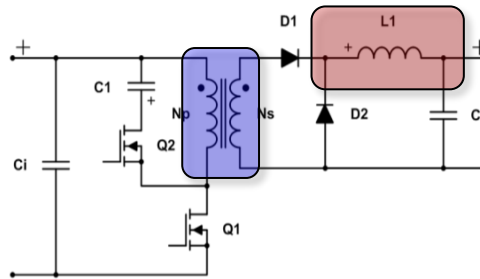


forward

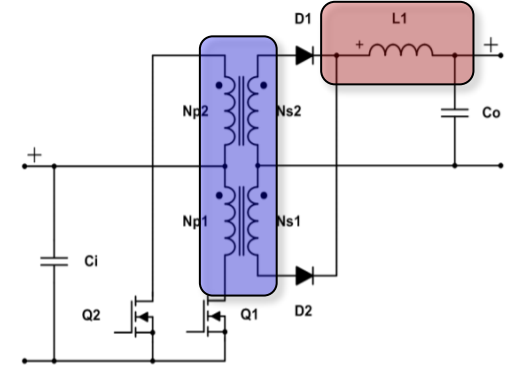


push-pull



NO

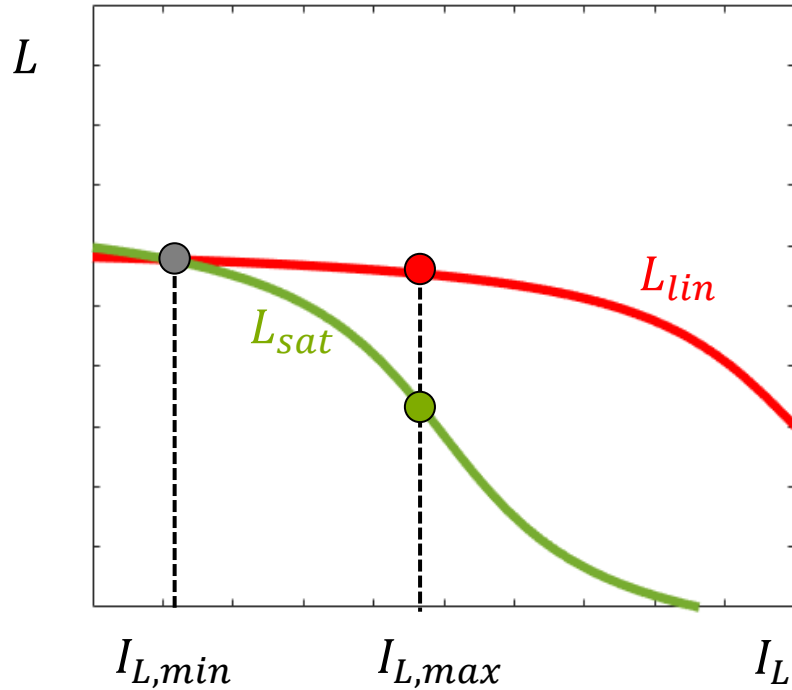

YES

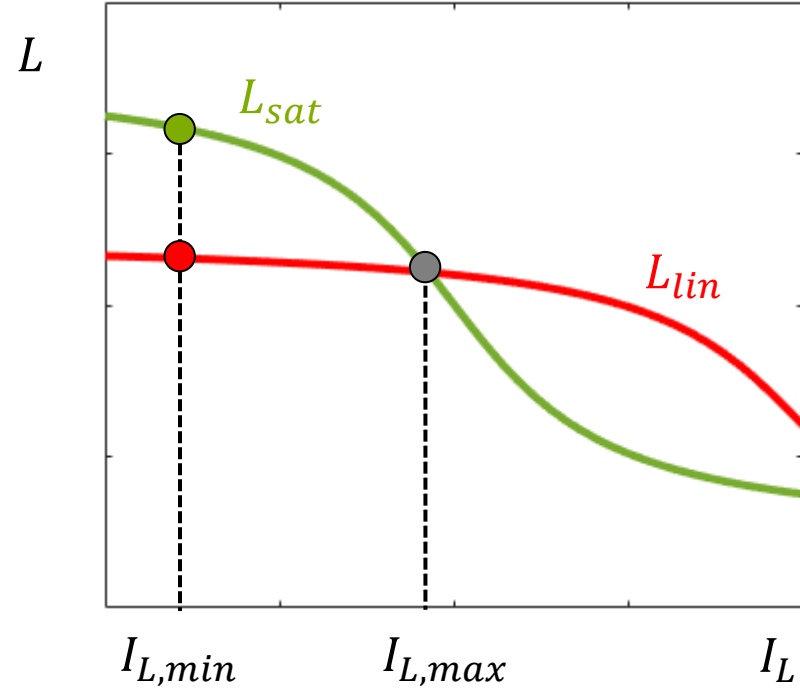

$I_{L,max}$  = DC inductor current under worst-case operating conditions (OCP, UVP, OVP,  $T_{amax}$ )


$$P_{L@I_{L,max}} < P_{max}, T_{core@I_{L,max}} < T_{max}$$



# EMI


## the good job

EMC certificate  
 EMI measurements  
 hardware prototype  
 design validation  
 PCB layout design  
 system design  
 design decisions  
 problems analysis  
 design specifications


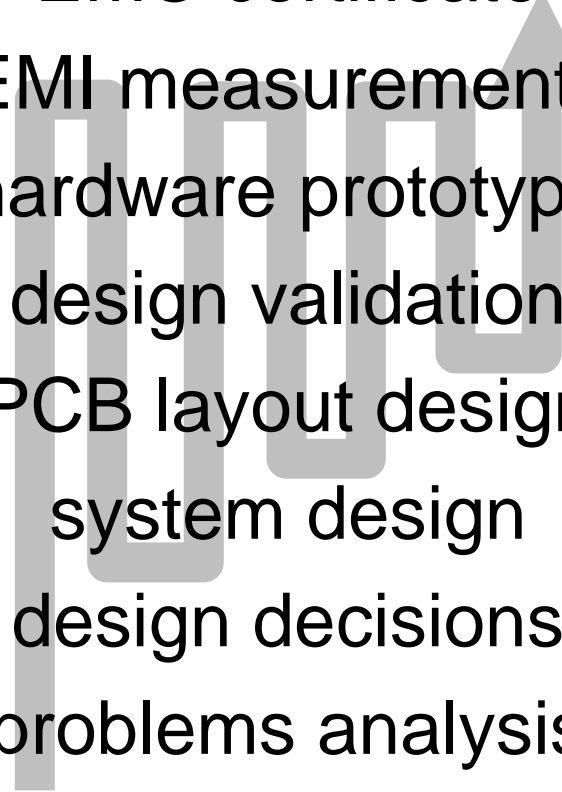
## the bad job


EMC certificate  
 EMI measurements  
 hardware prototype  
 design validation  
 PCB layout design  
 system design  
 design decisions  
 problems analysis  
 design specifications









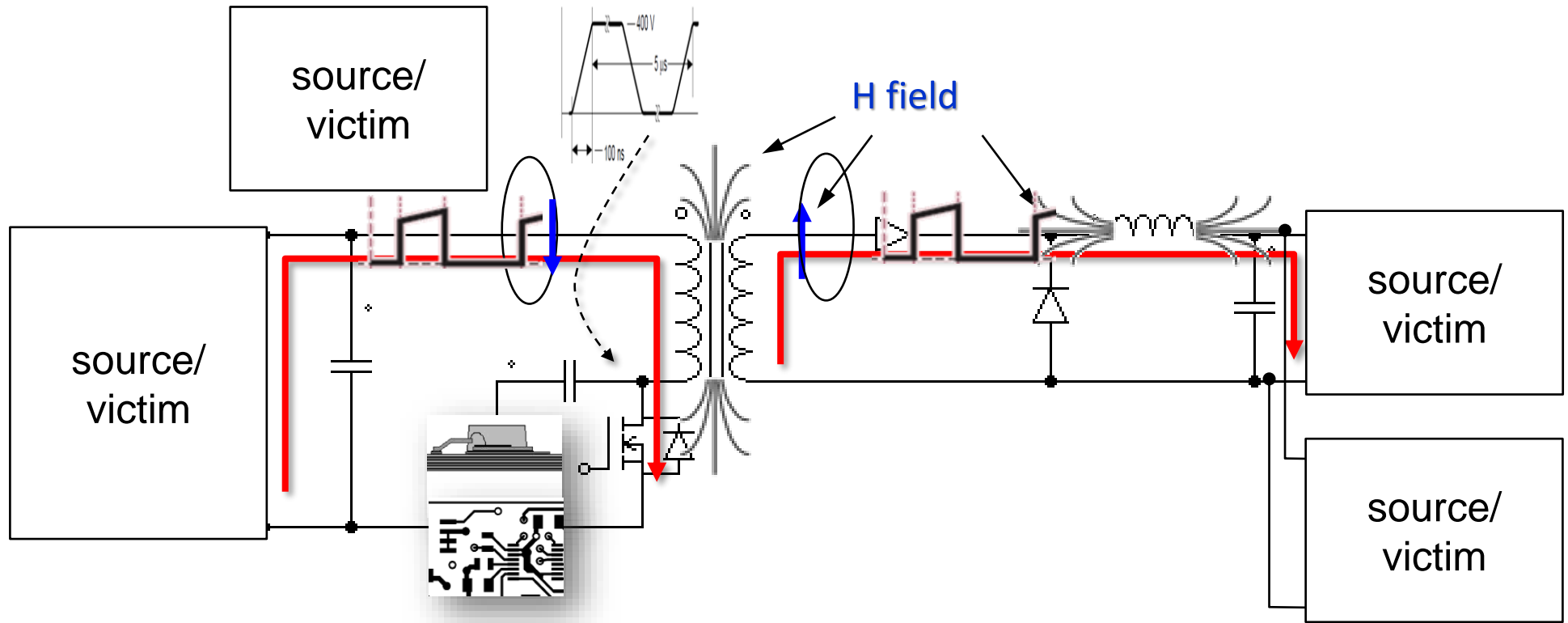- EMC regulations
- conducted and radiated EMI
- measurement setup
- noise analysis and understanding
  - sources
  - mechanisms
  - paths
  - boosters
  - mixing




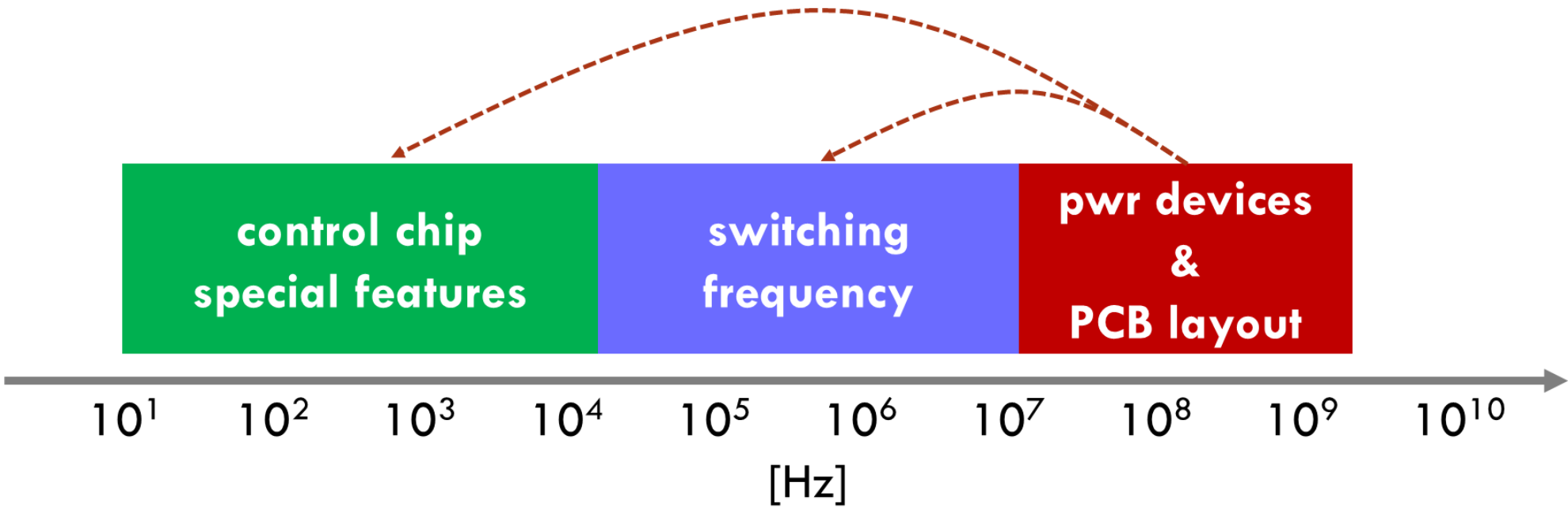

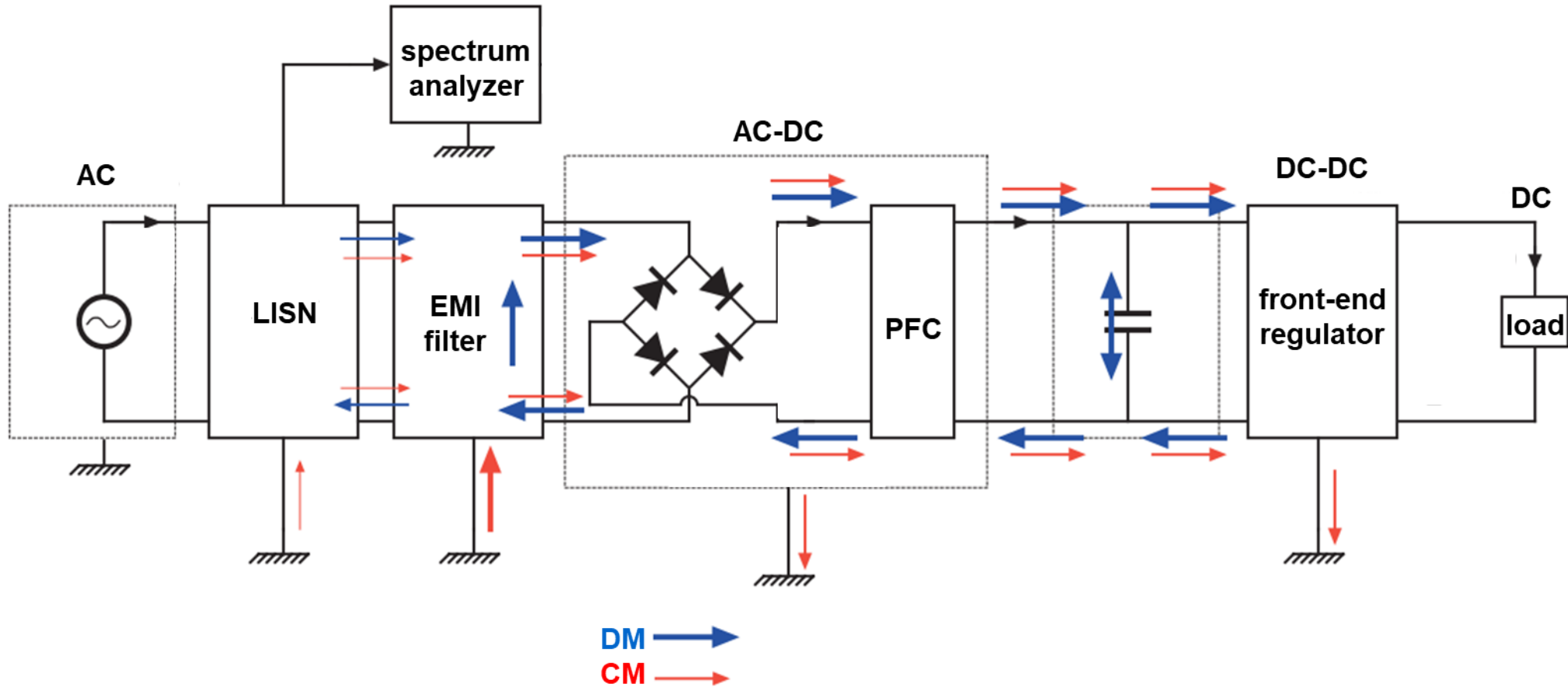



# Input Noise

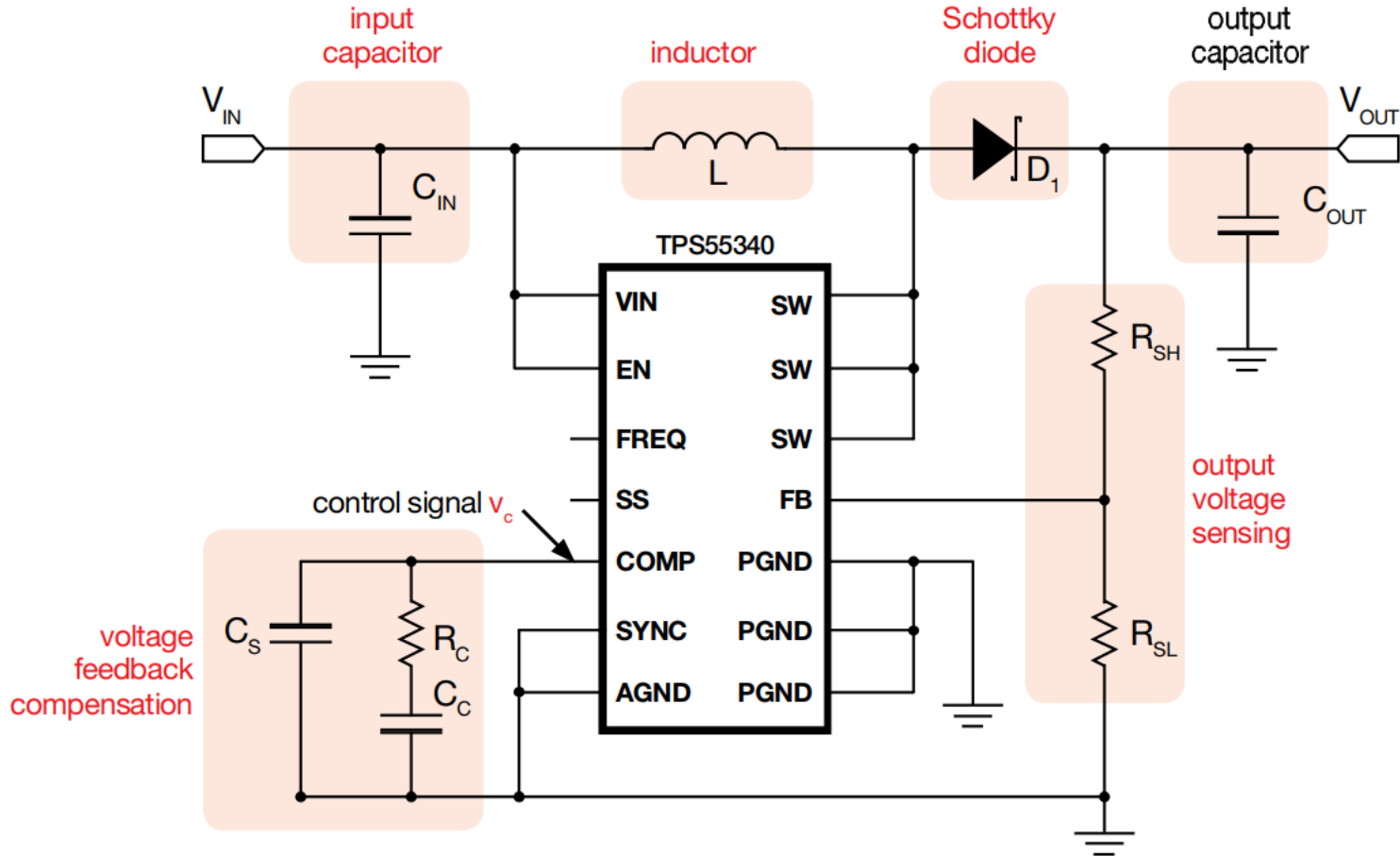

TI-PMLK Buck

**TI-PMLK Buck**  
Step down your voltage



TI-PMLK Boost

**TI-PMLK Boost**  
Step up your voltage



TI-PMLK Buck-Boost

**TI-PMLK BuckBoost**  
Manage your voltage magnitude



TI-PMLK LDO

**TI-PMLK LDO**  
Regulate your output voltage



TI-PMLK Buck Würth Elektronik Edition

**TI-PMLK Buck  
Würth Elektronik Edition**  
Impact of magnetics for  
power supply design




TI Power Electronics Board for NI ELVIS III


**TI Power Electronics  
Board for NI ELVIS III**  
Using functional blocks, build buck converters,  
regulators and both DC-AC converters to  
AC-DC converters


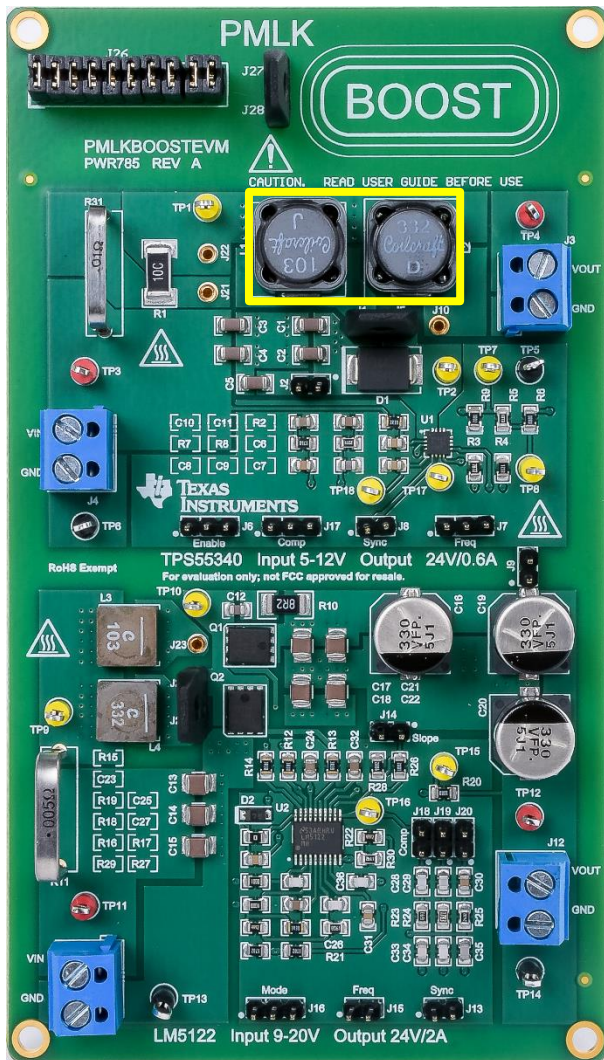
<https://university.ti.com/en/faculty/teaching-materials-and-classroom-resources/ti-based-teaching-kits-for-analog-and-power-design/power-management-lab-kit-series>



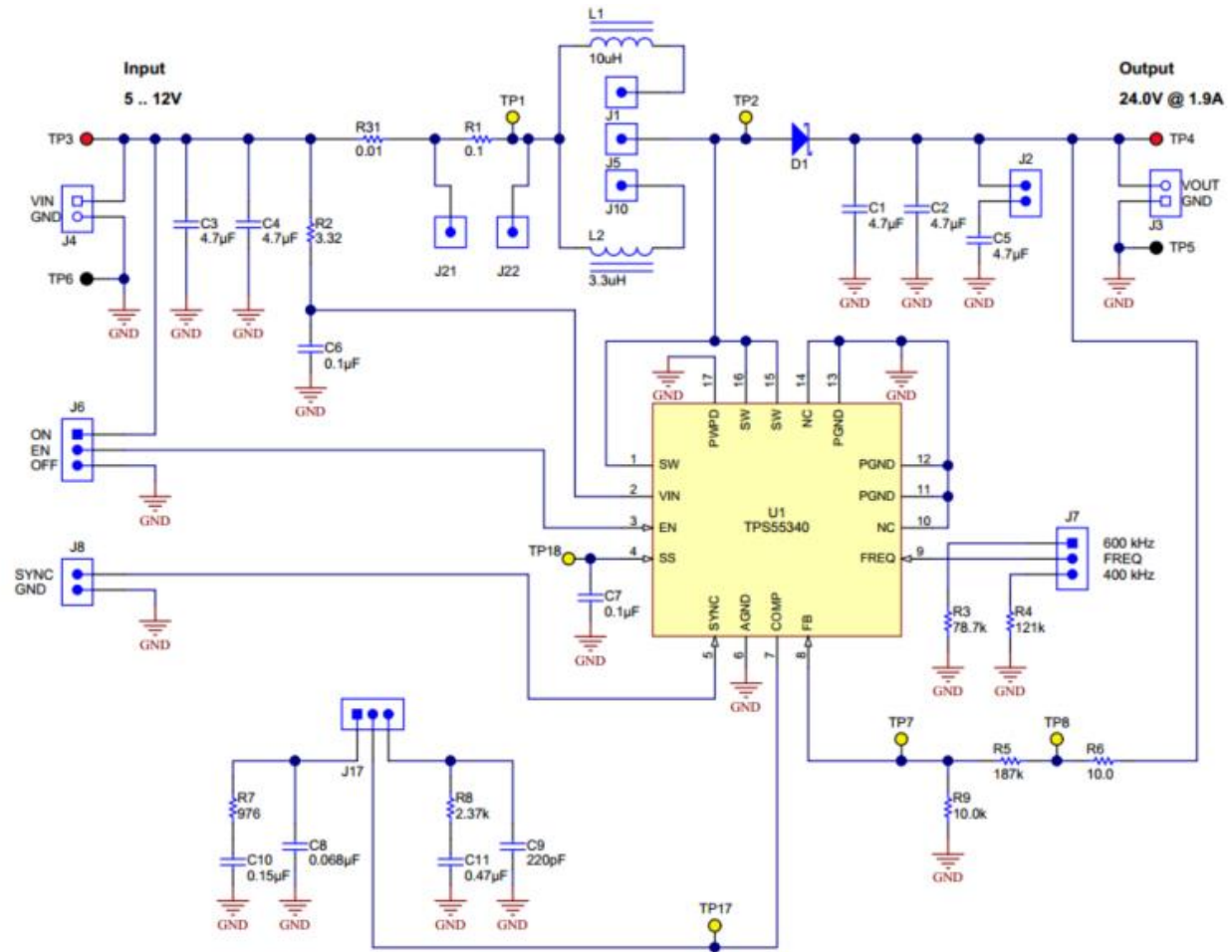
$$V_{in}=[5,12] \text{ V}, V_{out}= 24 \text{ V}, I_{out}=0.6 \text{ A}, f_s= 300/600 \text{ kHz}$$






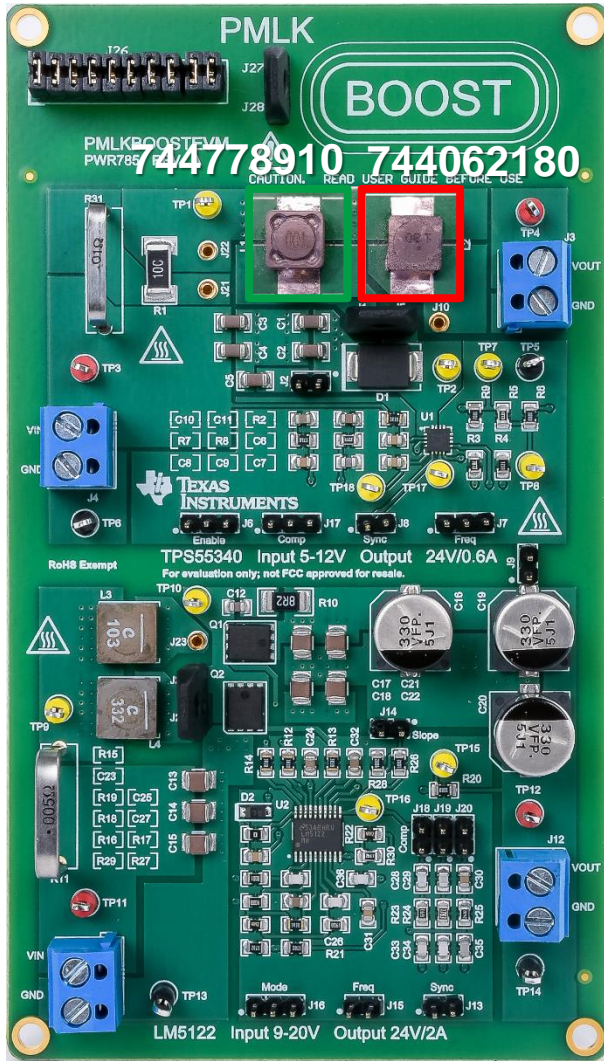
# TI-PMLK BOOST: de-saturating vs linear inductor test



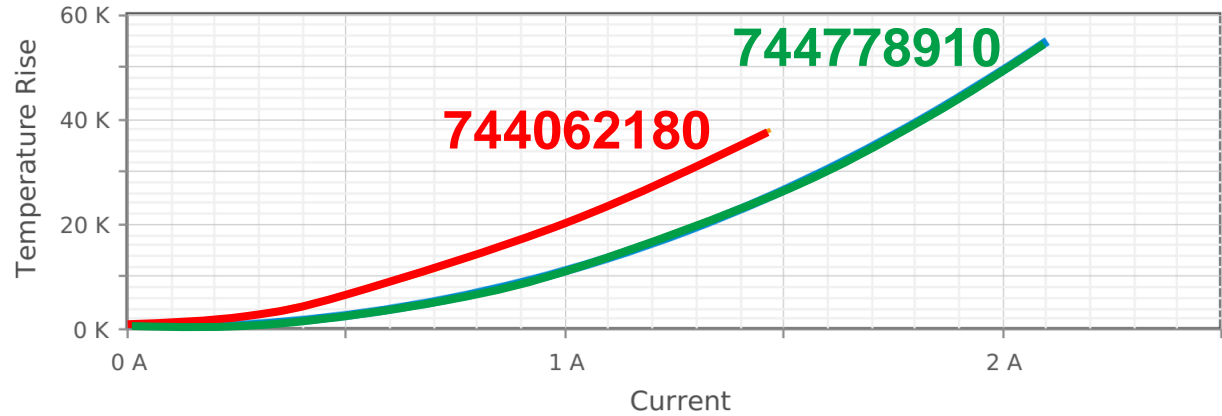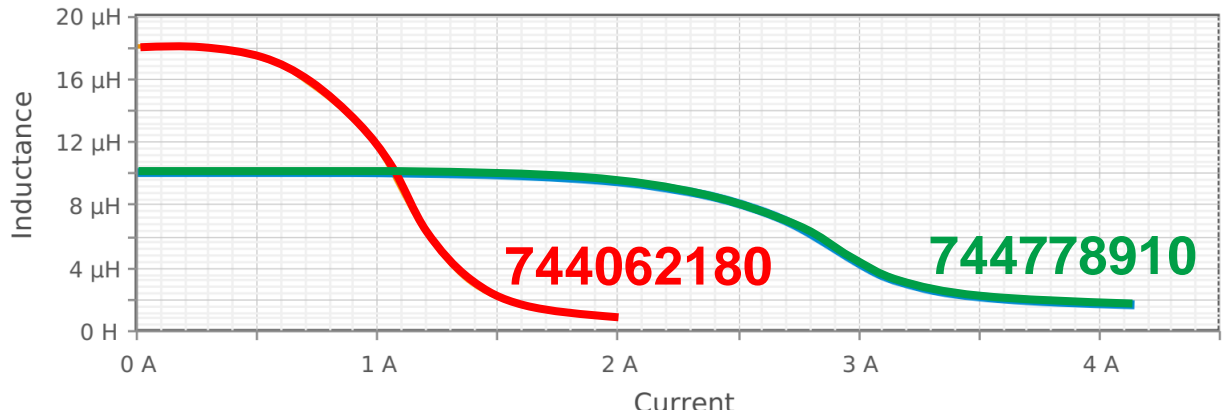$V_{in} = 10\text{ V}$ ,  $V_{out} = 24\text{ V}$ ,  $I_{out} = 0.4/0.2\text{ A}$ ,  $f_s = 300\text{ kHz}$



part code	L [μH]	R [mΩ]	Isat [A]	H [mm]	L [mm]	W [mm]	FP [mm <sup>2</sup> ]	Vol. [mm <sup>3</sup> ]
744062180	18	90	1	2.3	7	7	49	113
744778910	10	64	2.2	3.2	7.6	7.6	58	185






R&S NGL/NGM power supply



R&S RTM3004 oscilloscope



R&S RT-ZC20B current probe




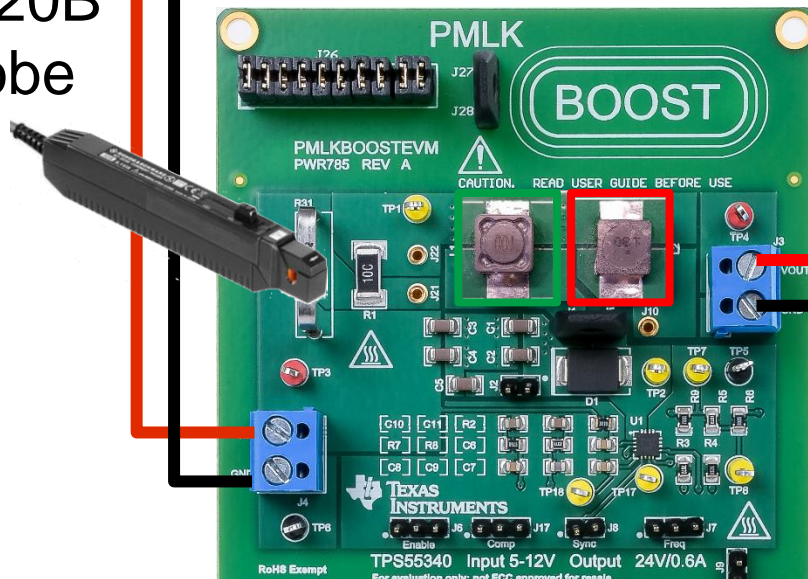


EA EL 3080-60 B electronic load



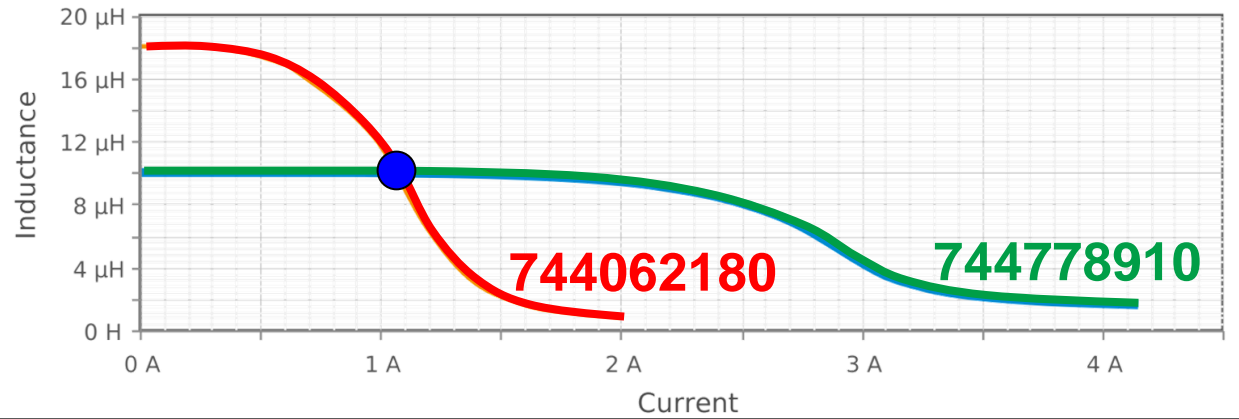
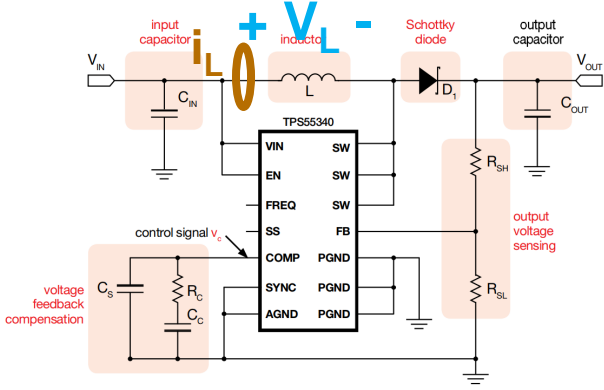
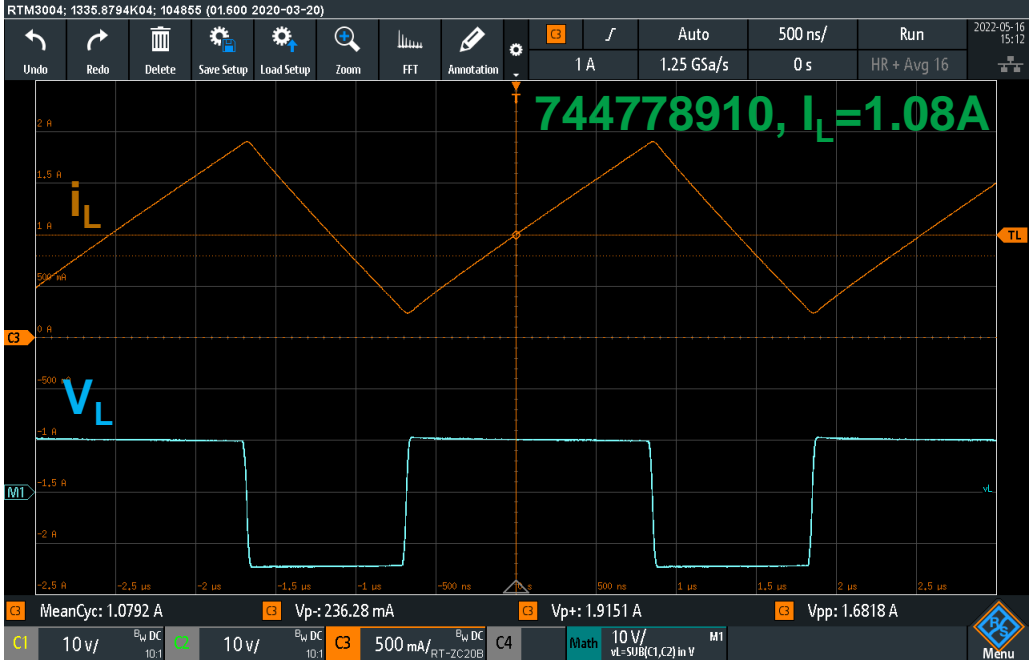
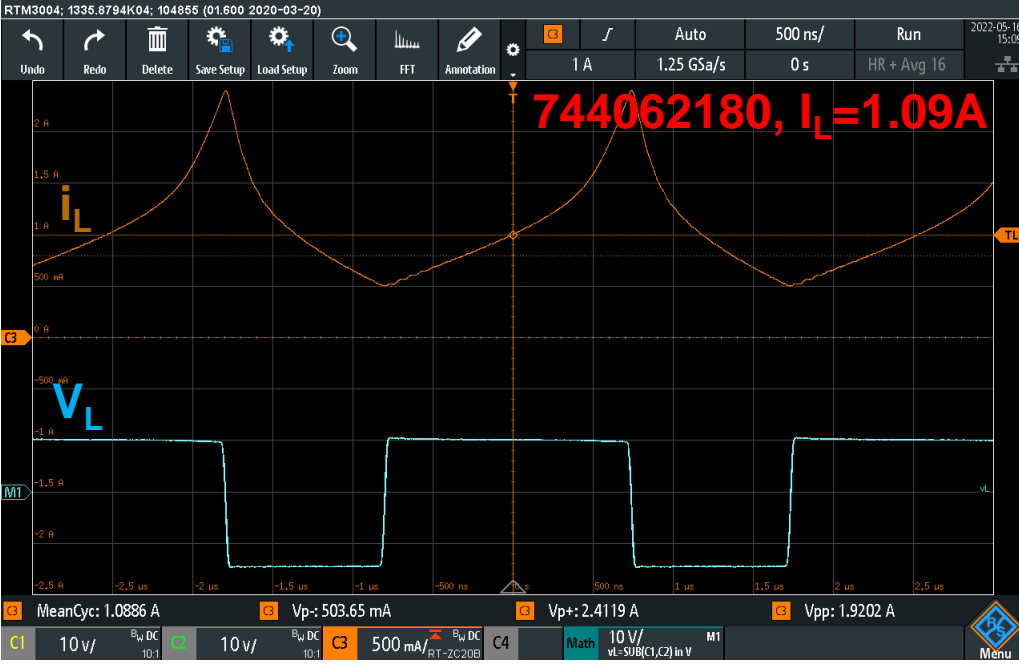
# TI-PMLK BOOST: high-current waveforms

$V_{in} 10V, V_{out} = 24 V, I_{out} = 0.4 A, f_s = 300 kHz$



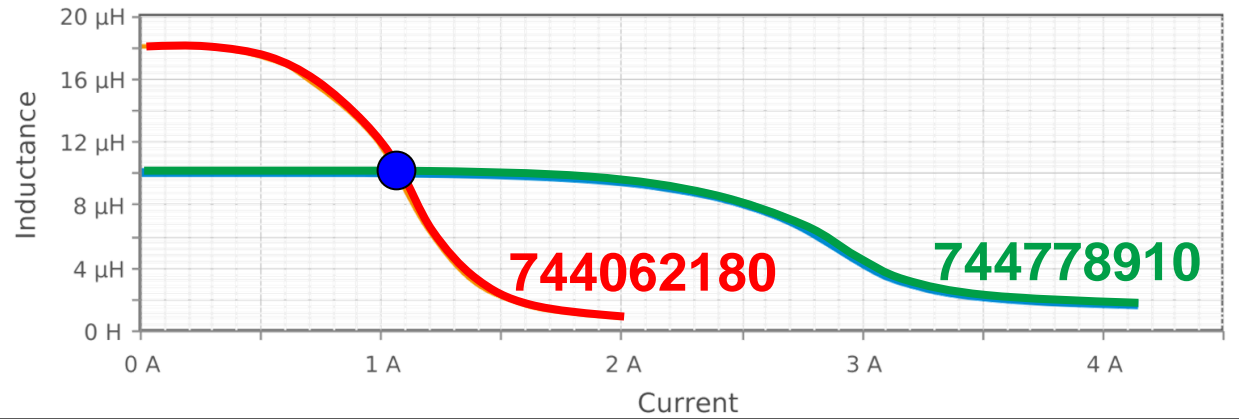
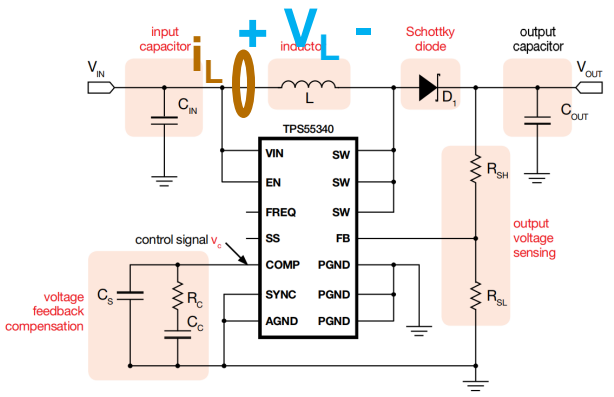
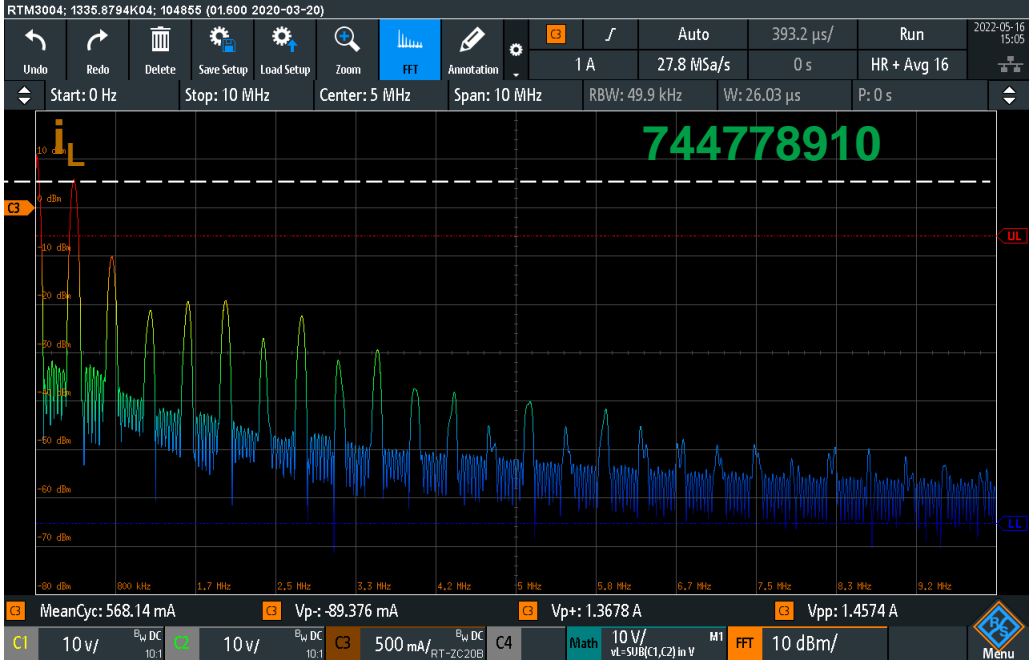
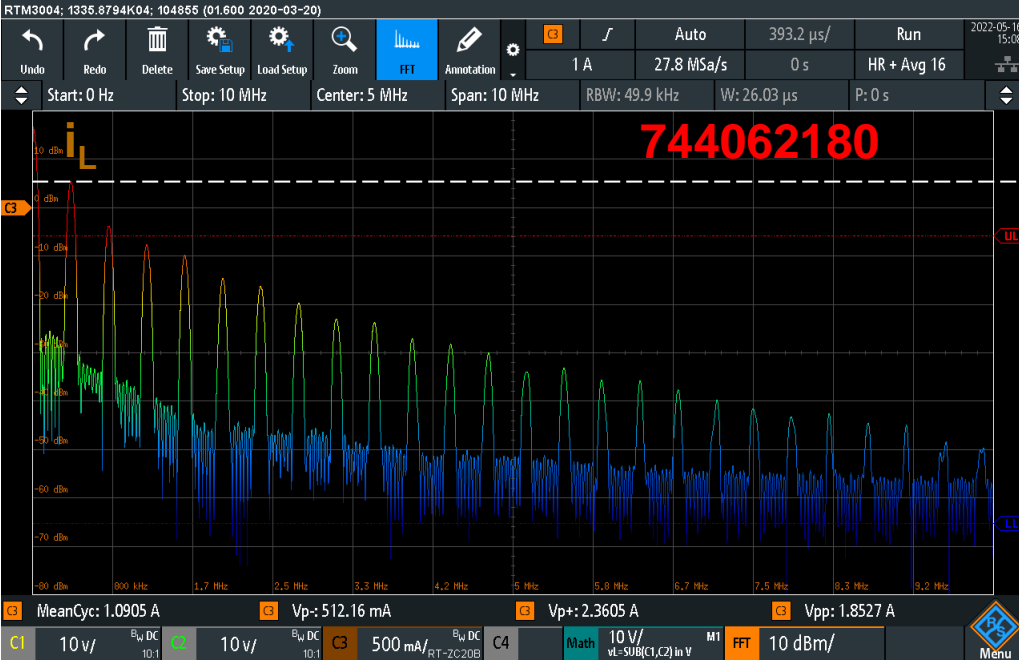
# TI-PMLK BOOST: high-current current spectrum

$V_{in} 10V, V_{out} = 24 V, I_{out} = 0.4 A, f_s = 300 kHz$



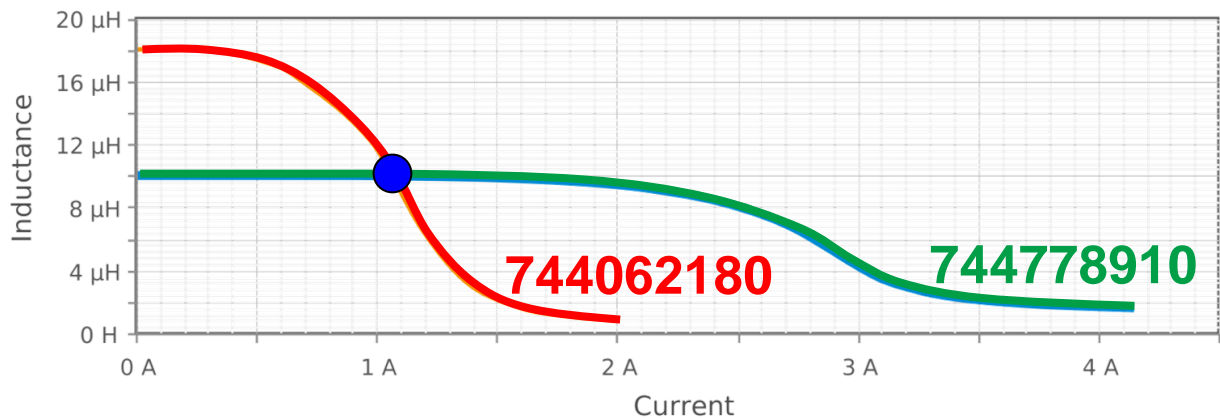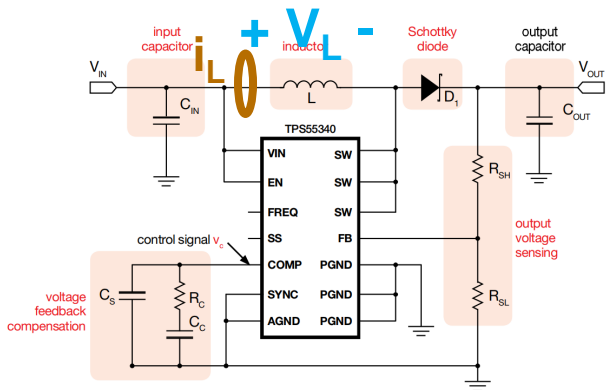
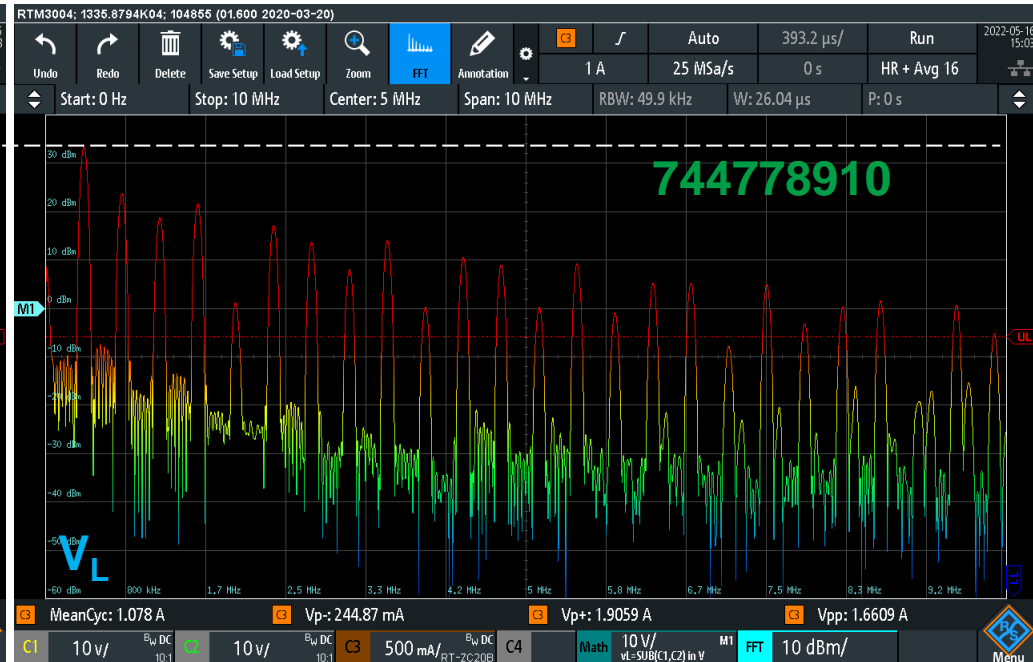
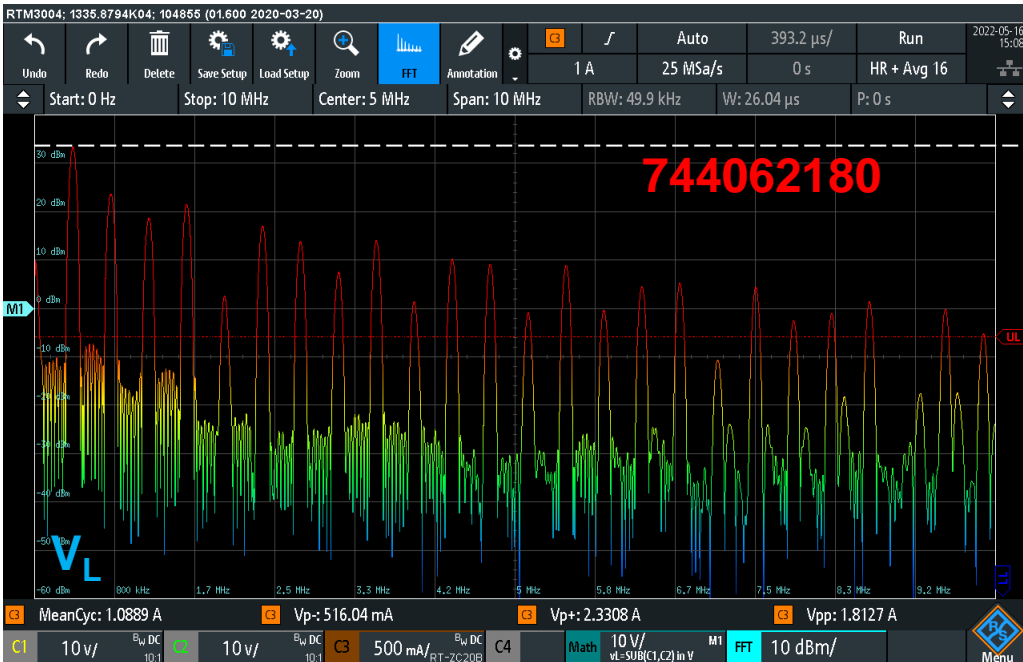
# TI-PMLK BOOST: high-current voltage spectrum

$V_{in} 10V, V_{out} = 24 V, I_{out} = 0.4 A, f_s = 300 kHz$



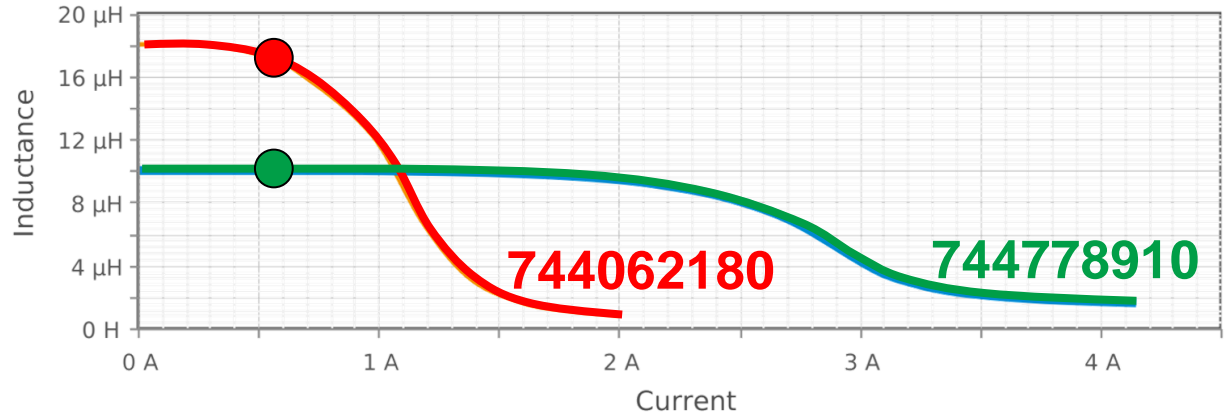
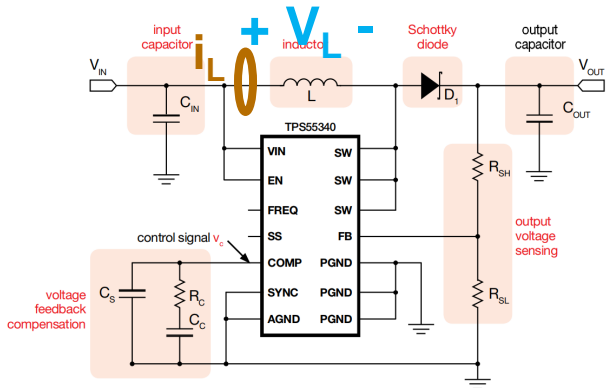
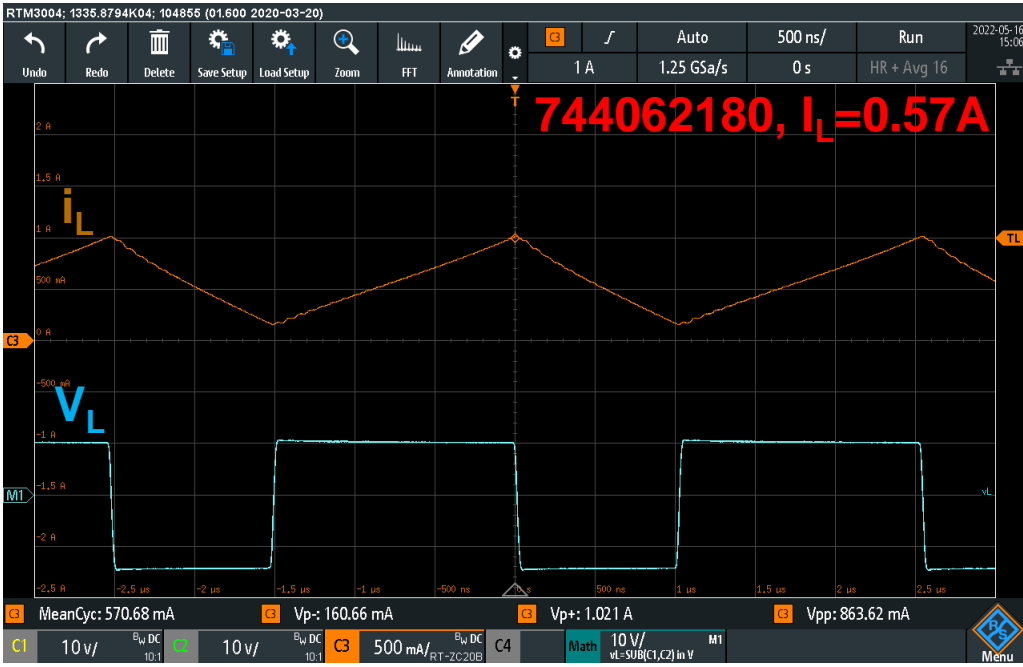
# TI-PMLK BOOST: low-current waveforms

$V_{in} 10V, V_{out} = 24 V, I_{out} = 0.2 A, f_s = 300 kHz$




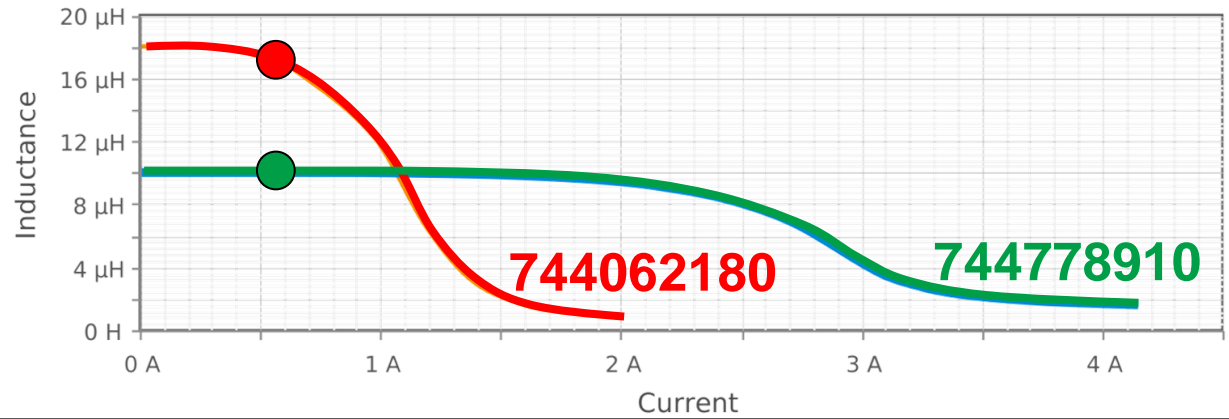
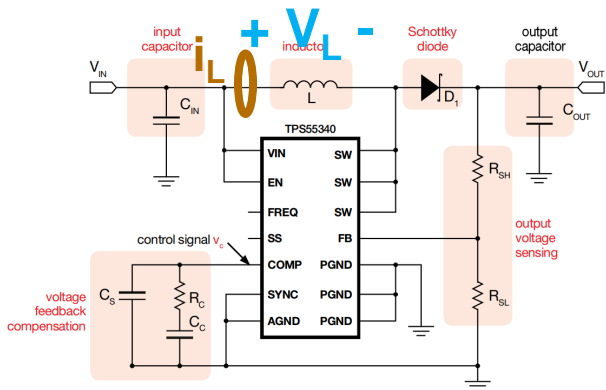
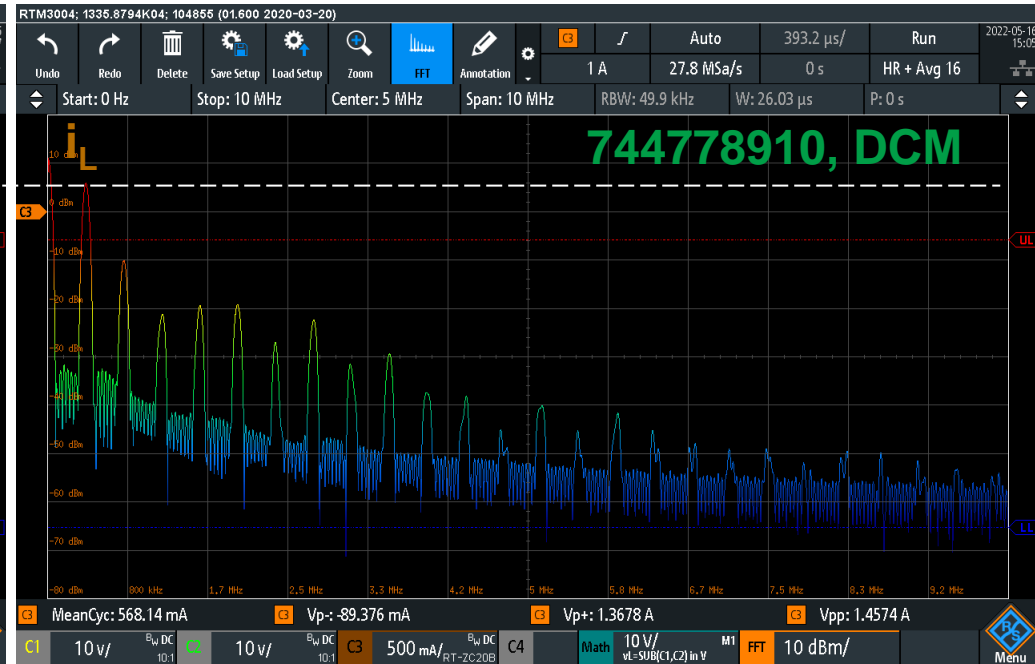
# TI-PMLK BOOST: low-current current spectrum

$V_{in} 10V, V_{out} = 24 V, I_{out} = 0.2 A, f_s = 300 kHz$


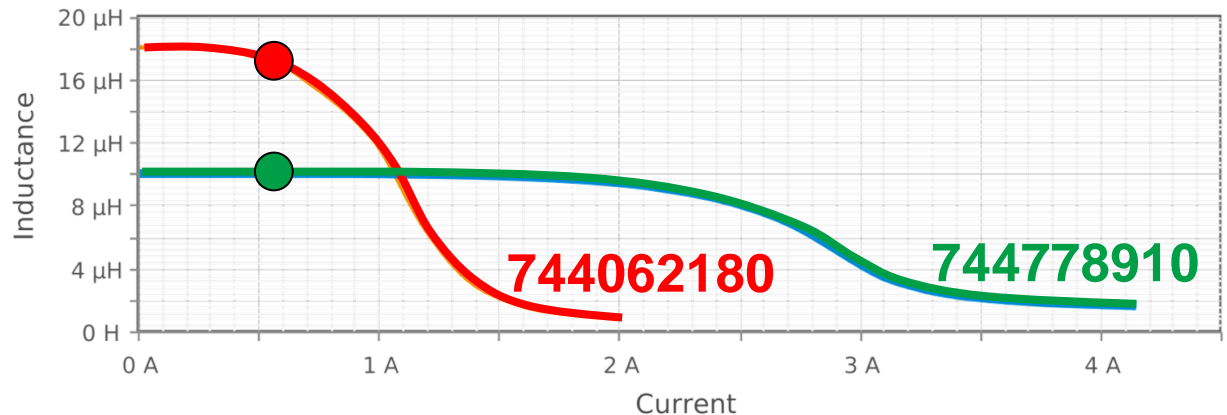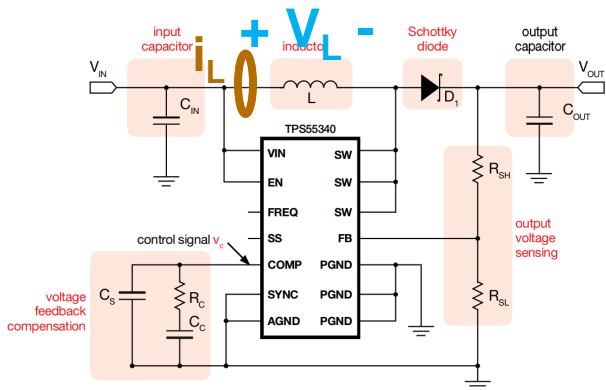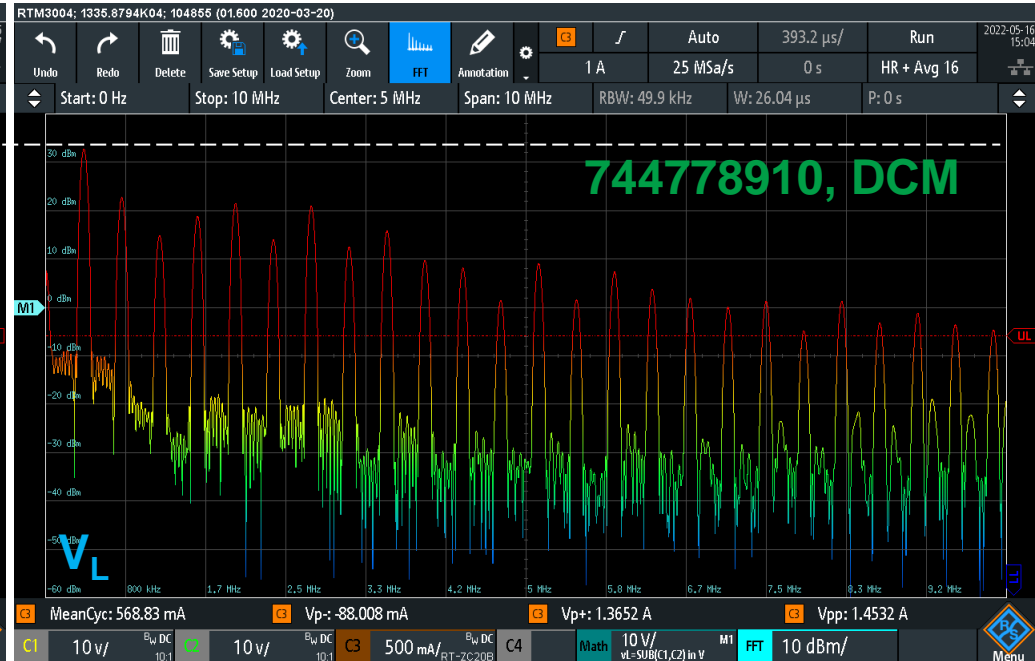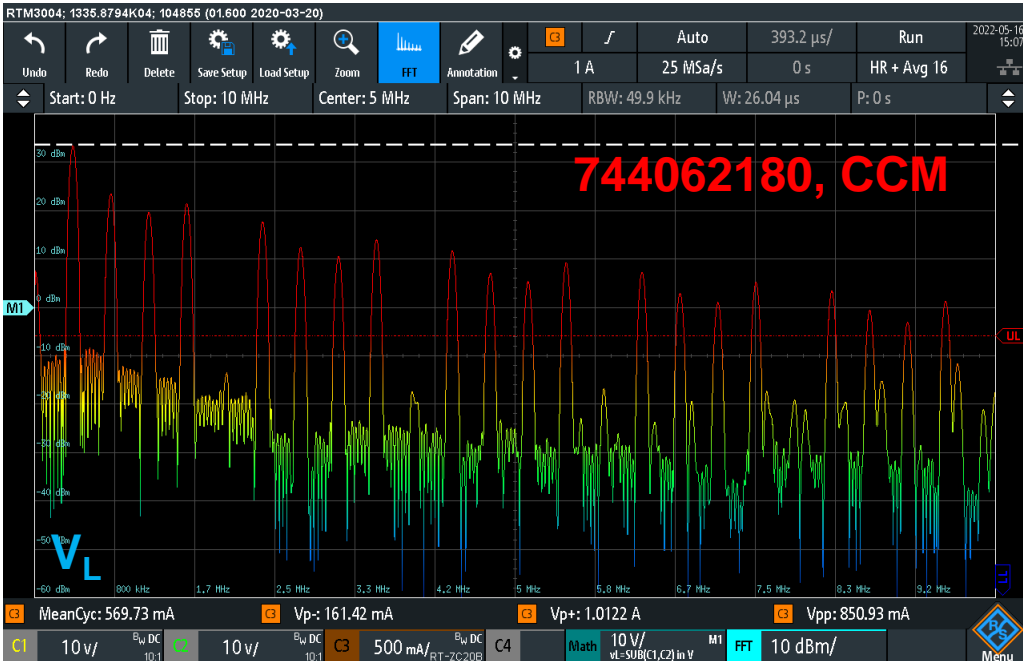
# TI-PMLK BOOST: low-current voltage spectrum



$V_{in} 10V, V_{out} = 24 V, I_{out} = 0.2 A, f_s = 300 kHz$









# Input Filter

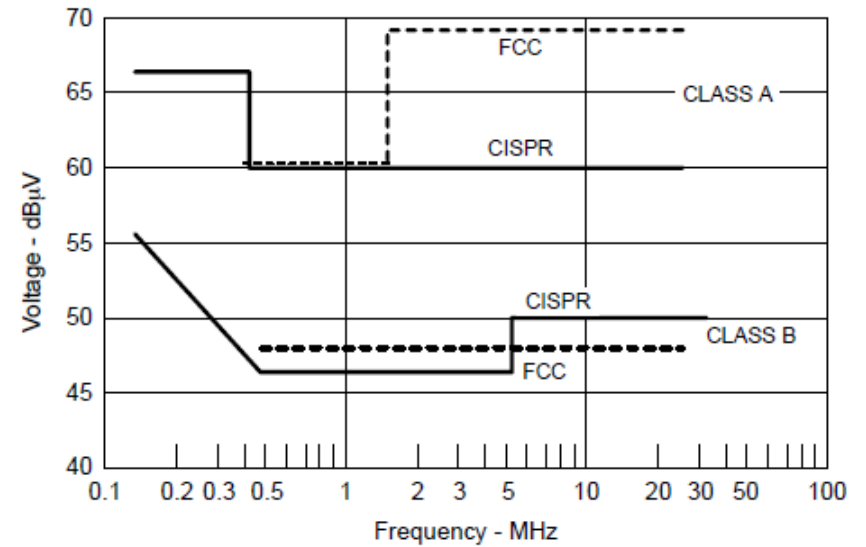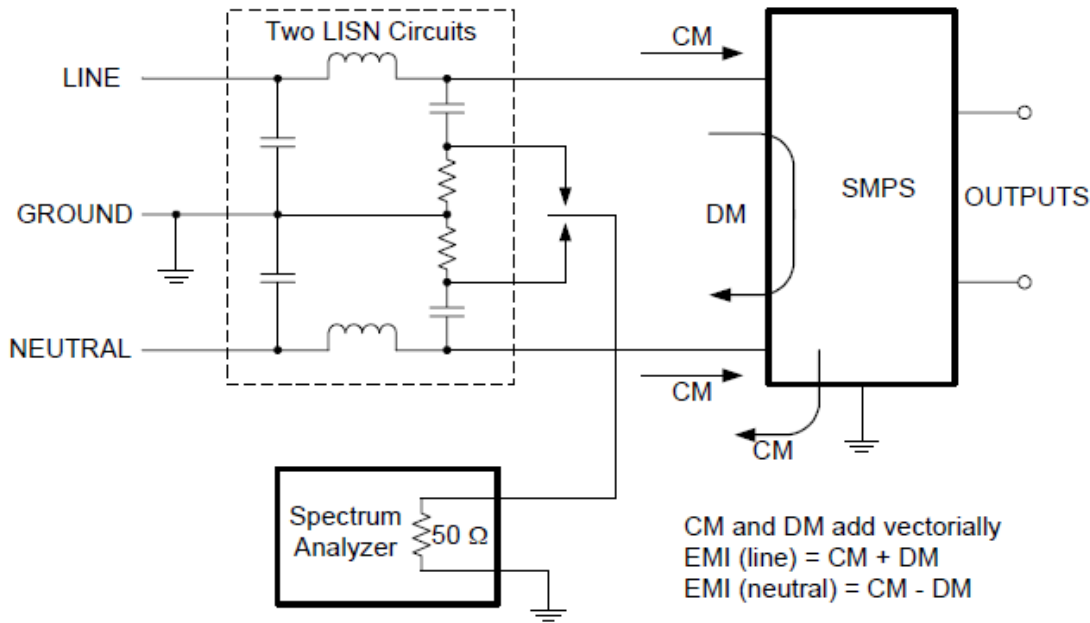

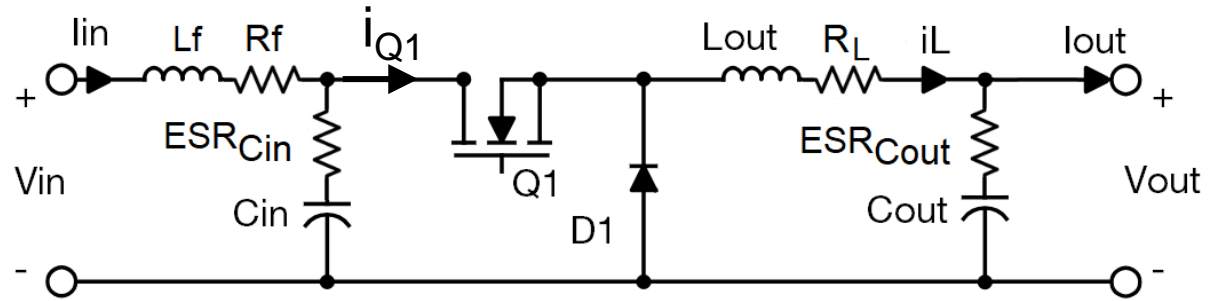


lin IQ1


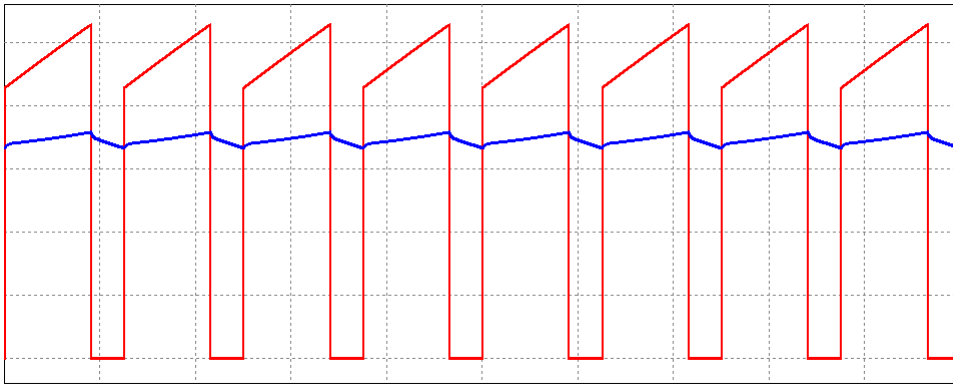


time


lin IQ1

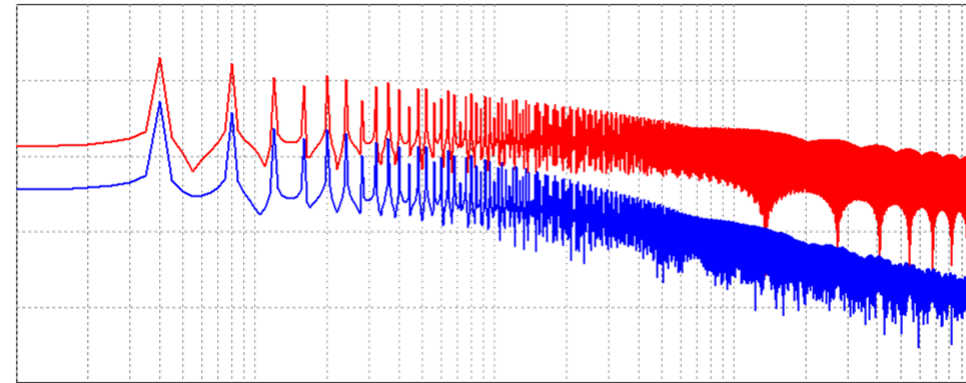


frequency

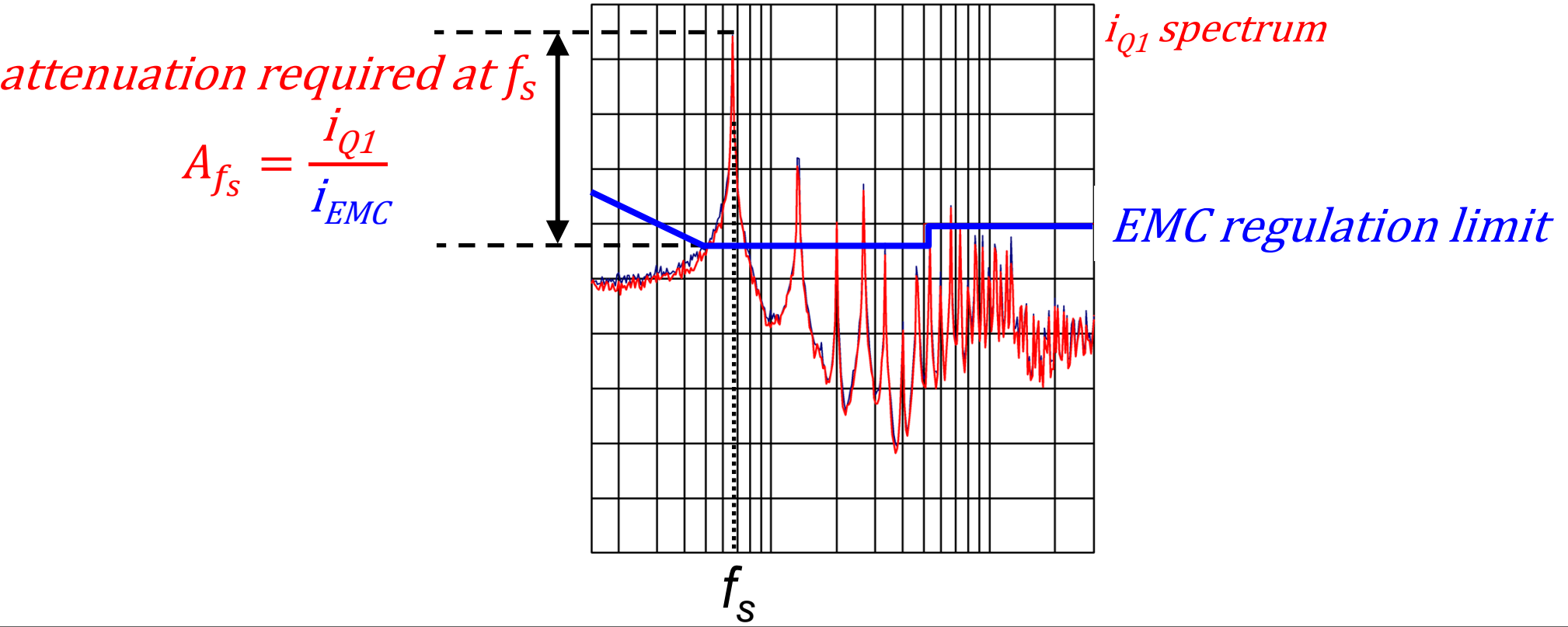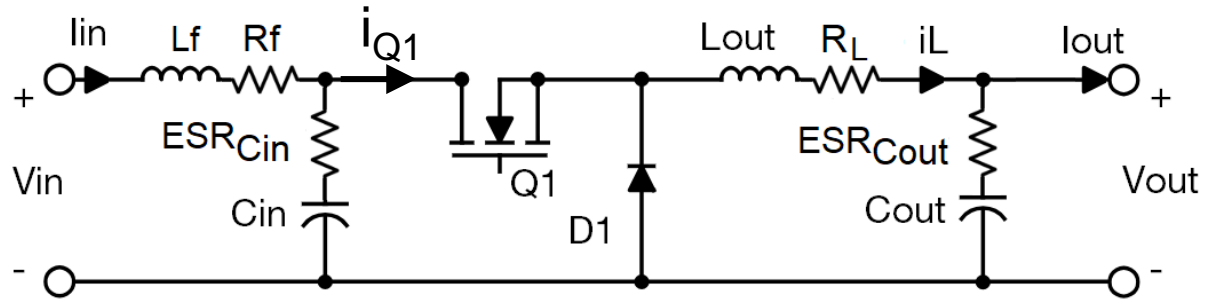


# Input filter: resonance frequency

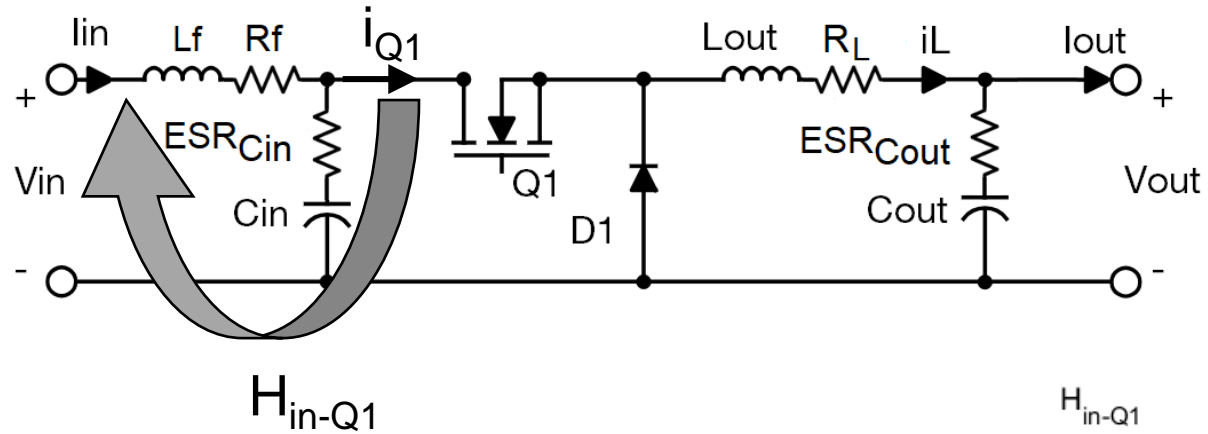
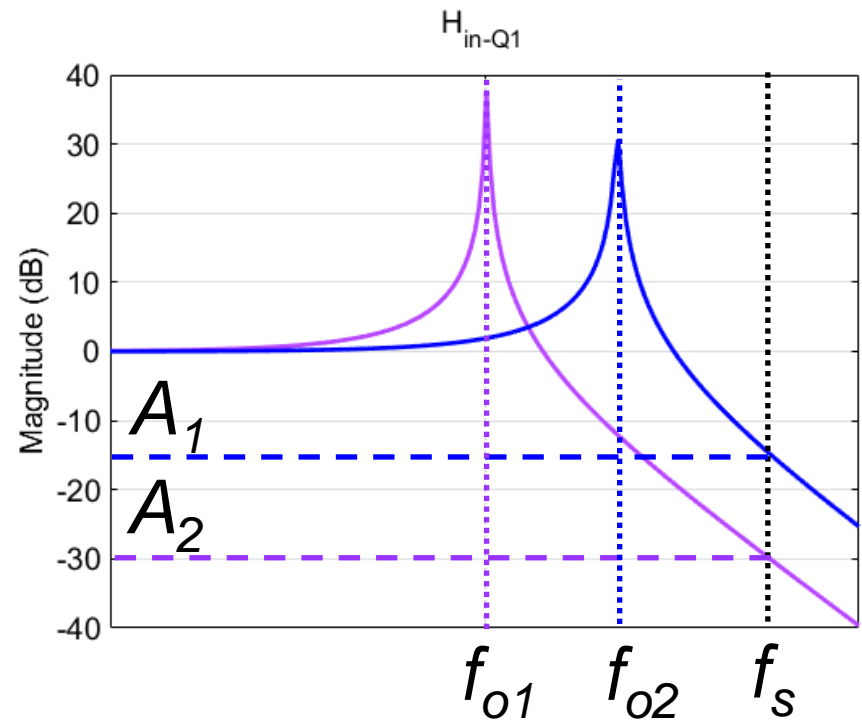
$$A_x \cong \frac{f_s^2}{f_{ox}^2} \quad x = 1,2$$



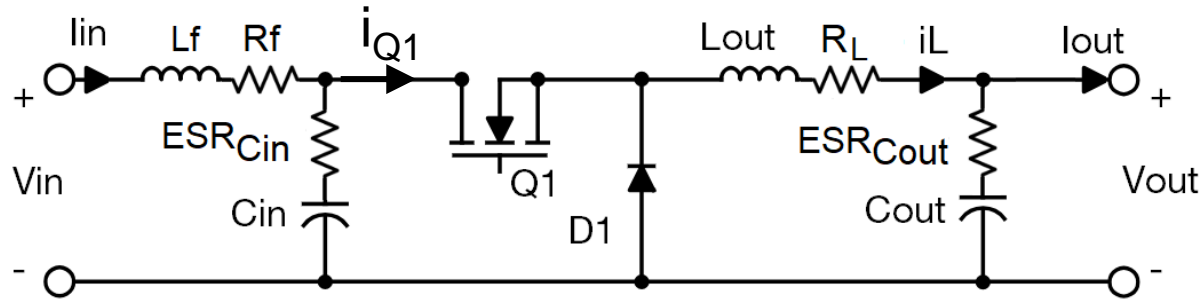


$$f_o = \frac{f_s}{\sqrt{A_{f_s}}}$$

$$L_{f,nom} > \frac{1}{(2\pi f_o)^2 C_{in}}$$

$$R_f < \frac{P_{f,max}}{I_{inDC,max}^2}$$

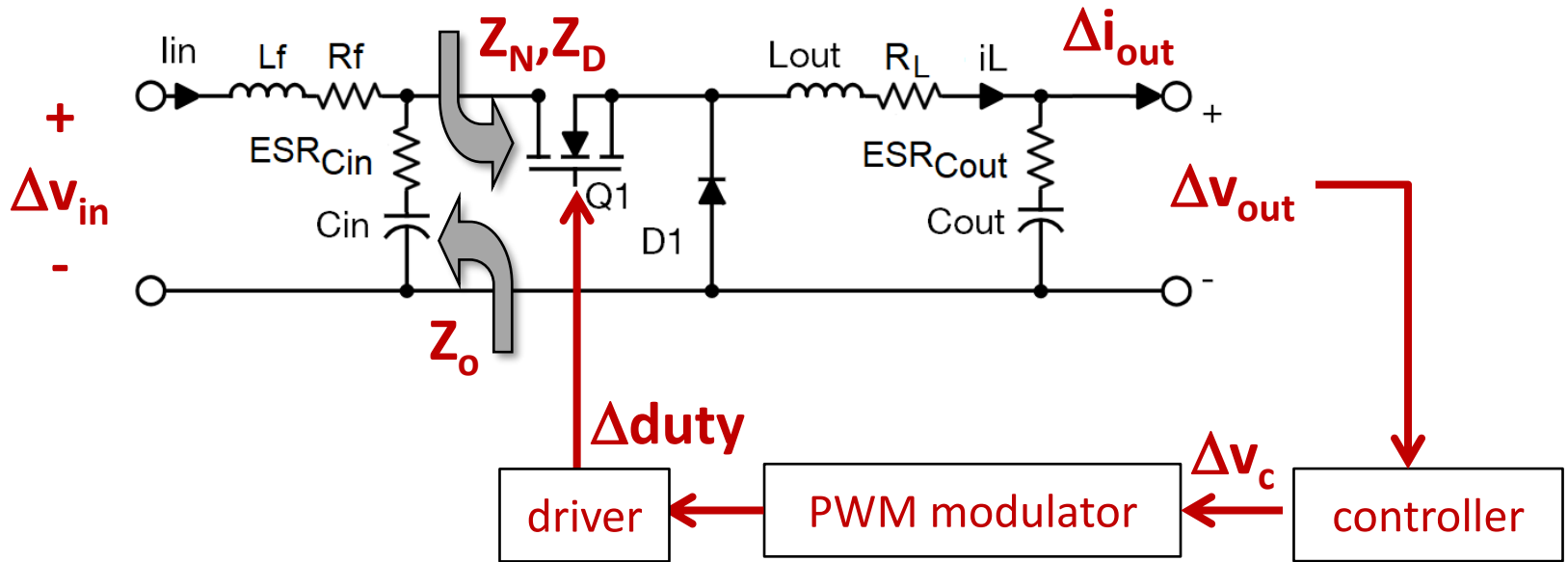
$[v_{noise} = 80dB_{\mu V} \rightarrow I_{in,ac} = 200\mu A]$



$$G_{vc} = G_{vc,nf} H_b$$


$$G_{vc,nf} = G_o \frac{1 + \frac{s}{\omega_r}}{1 + \frac{s}{Q\omega_n} + \frac{s^2}{\omega_n^2}}$$
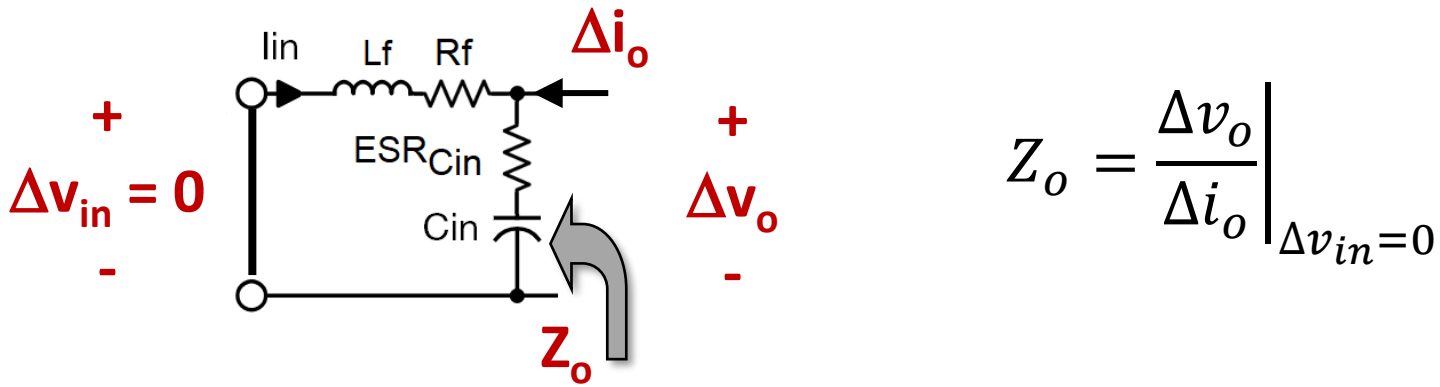
$$H_b = \frac{1 + \frac{Z_o}{Z_N}}{1 + \frac{Z_o}{Z_D}}$$



$$Z_N = \left. \frac{\Delta v_o}{\Delta i_o} \right|_{\Delta v_{out}=0}$$

$$Z_D = \left. \frac{\Delta v_o}{\Delta i_o} \right|_{\Delta v_c=0}$$

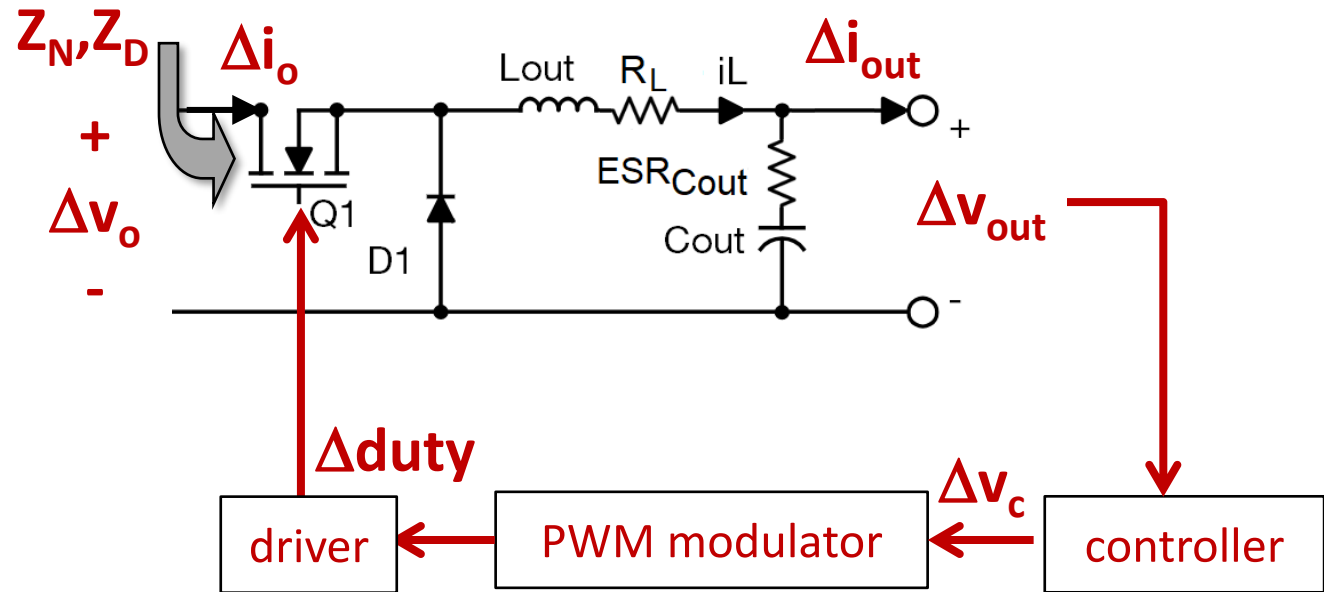




# Input filter: filter with low output impedance




$$Z_o \ll Z_N, Z_D$$

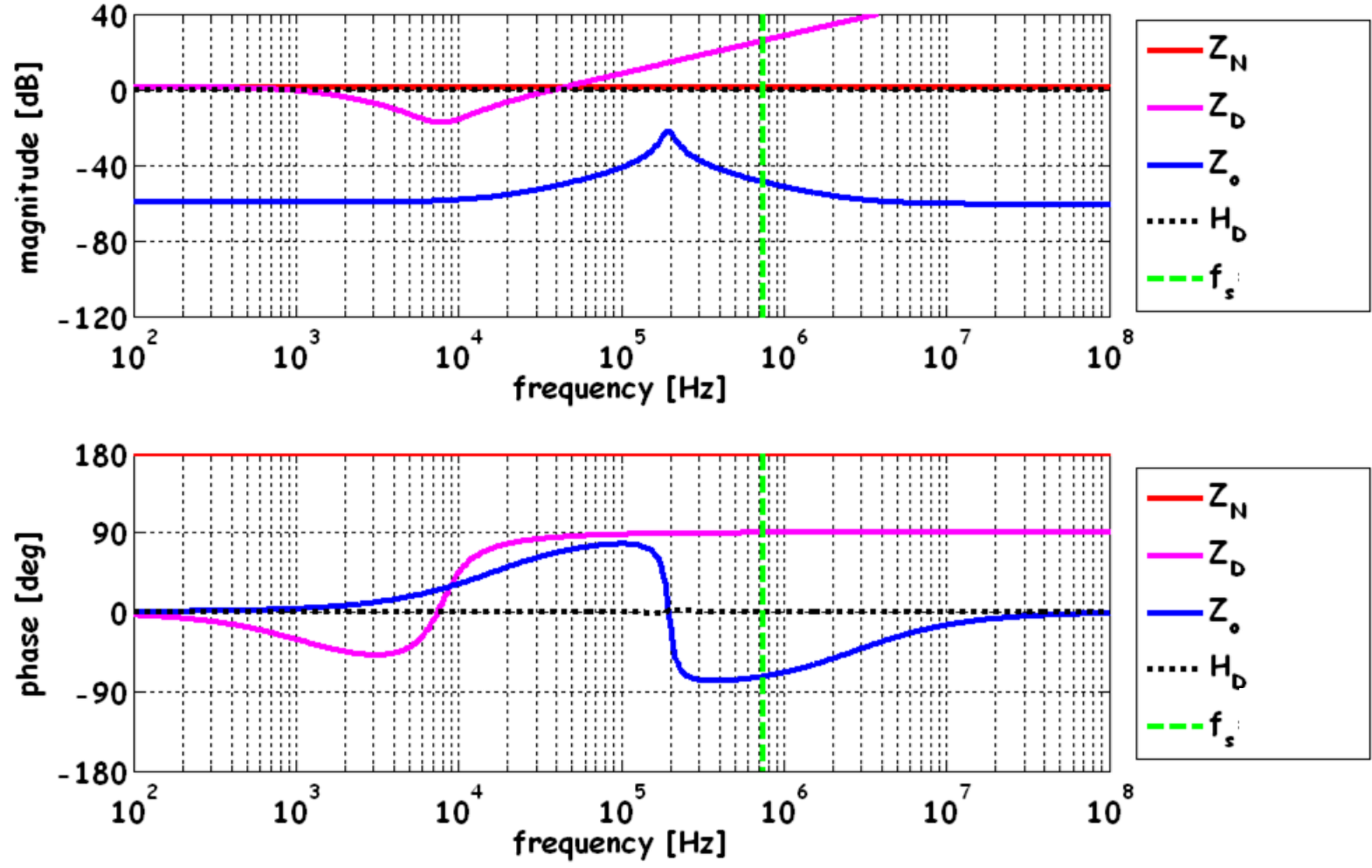
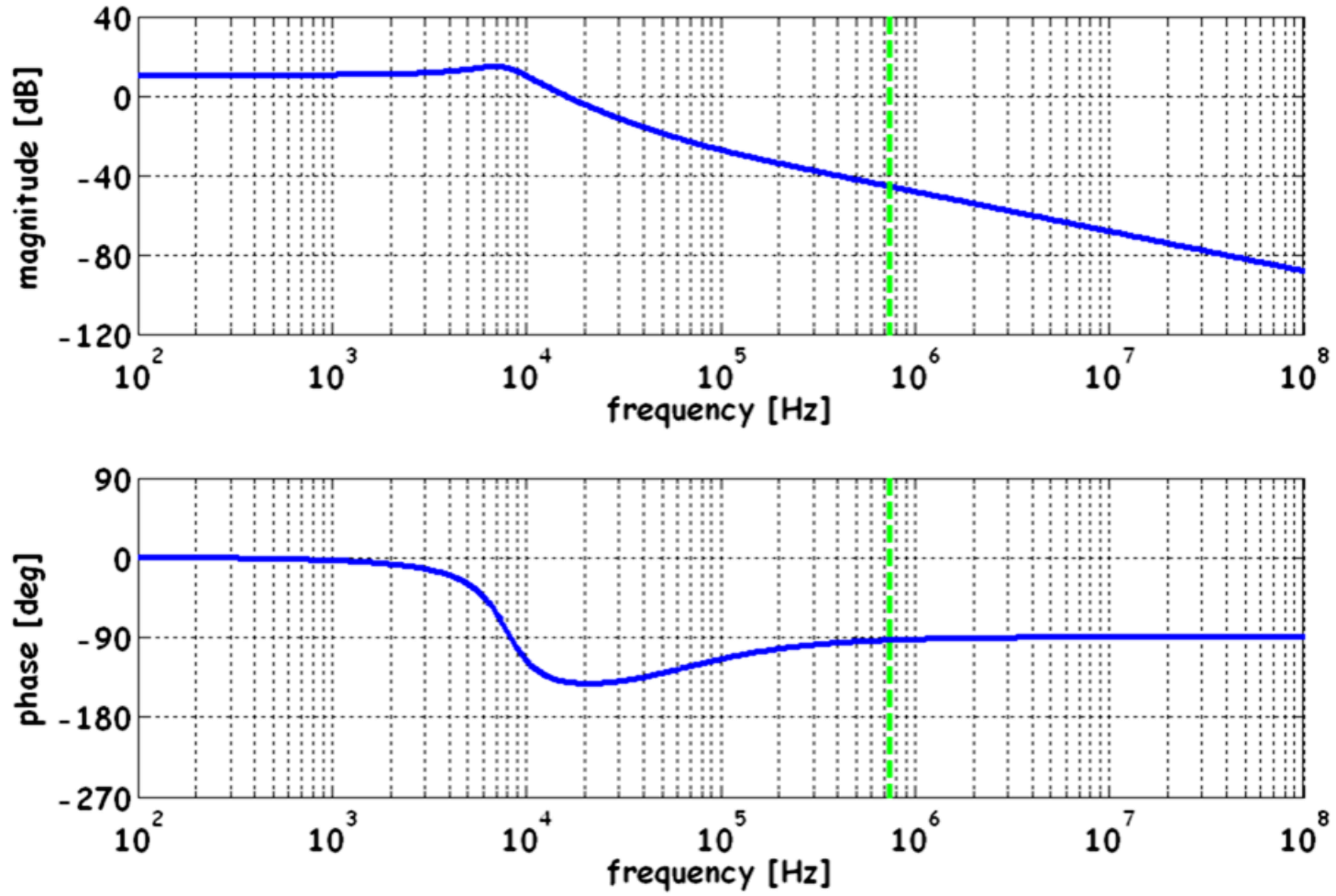
# Input filter: resonance-free loop gain



$$Z_O \ll Z_N, Z_D \rightarrow G_{vc} = G_{vc,nf}$$



# Input filter: filter with large impedance








$$Z_O \approx Z_N, Z_D$$

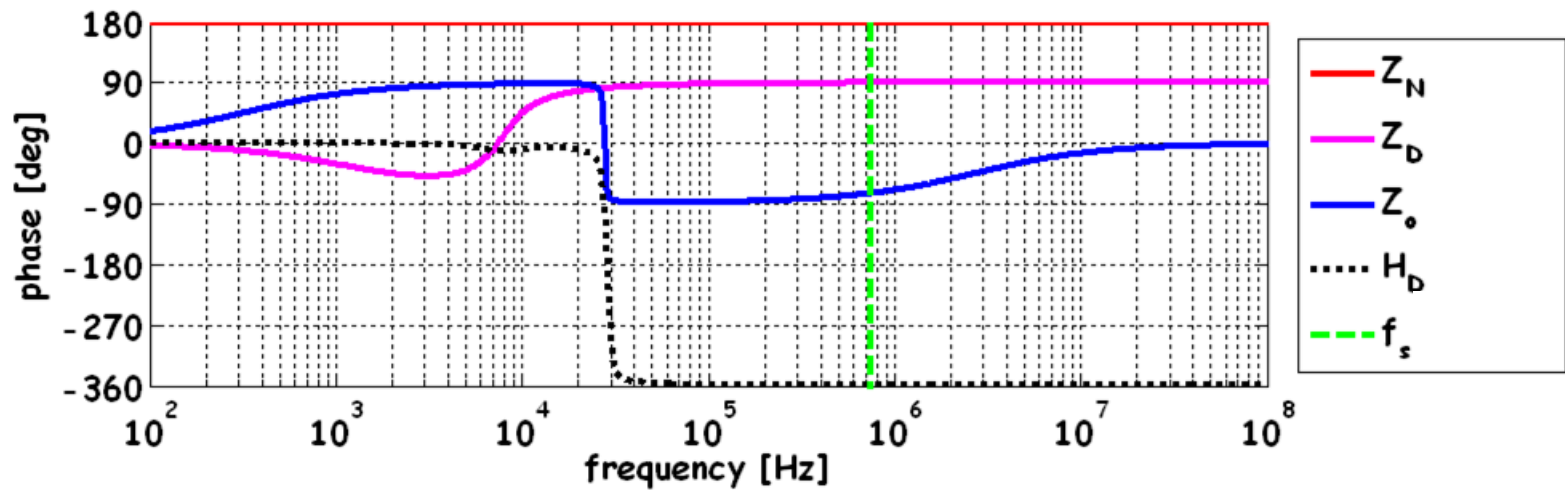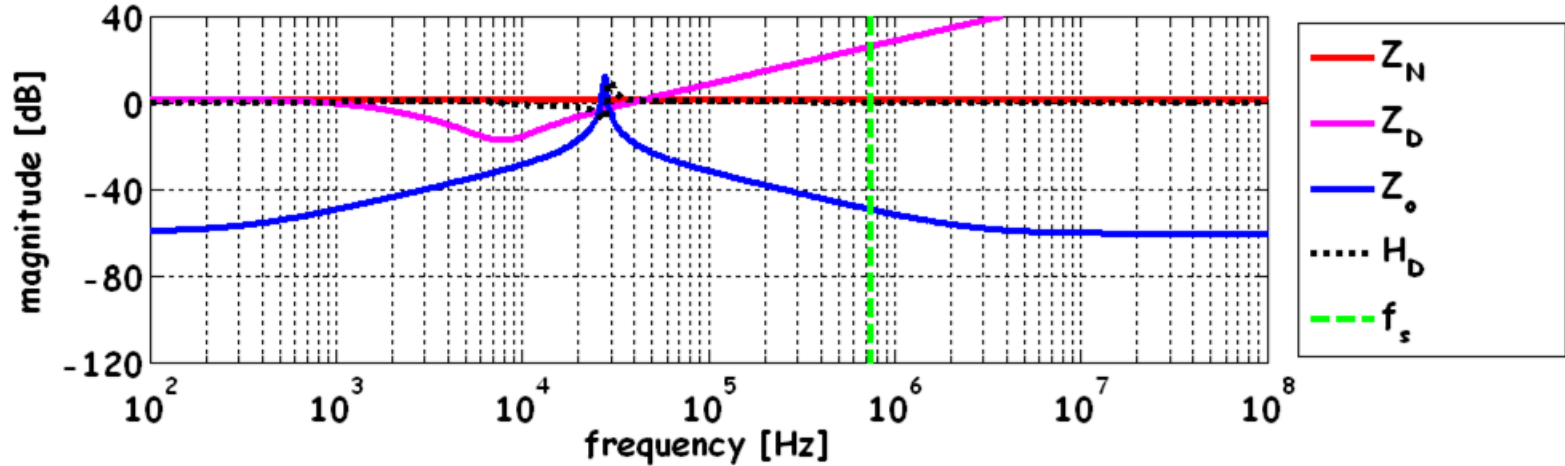



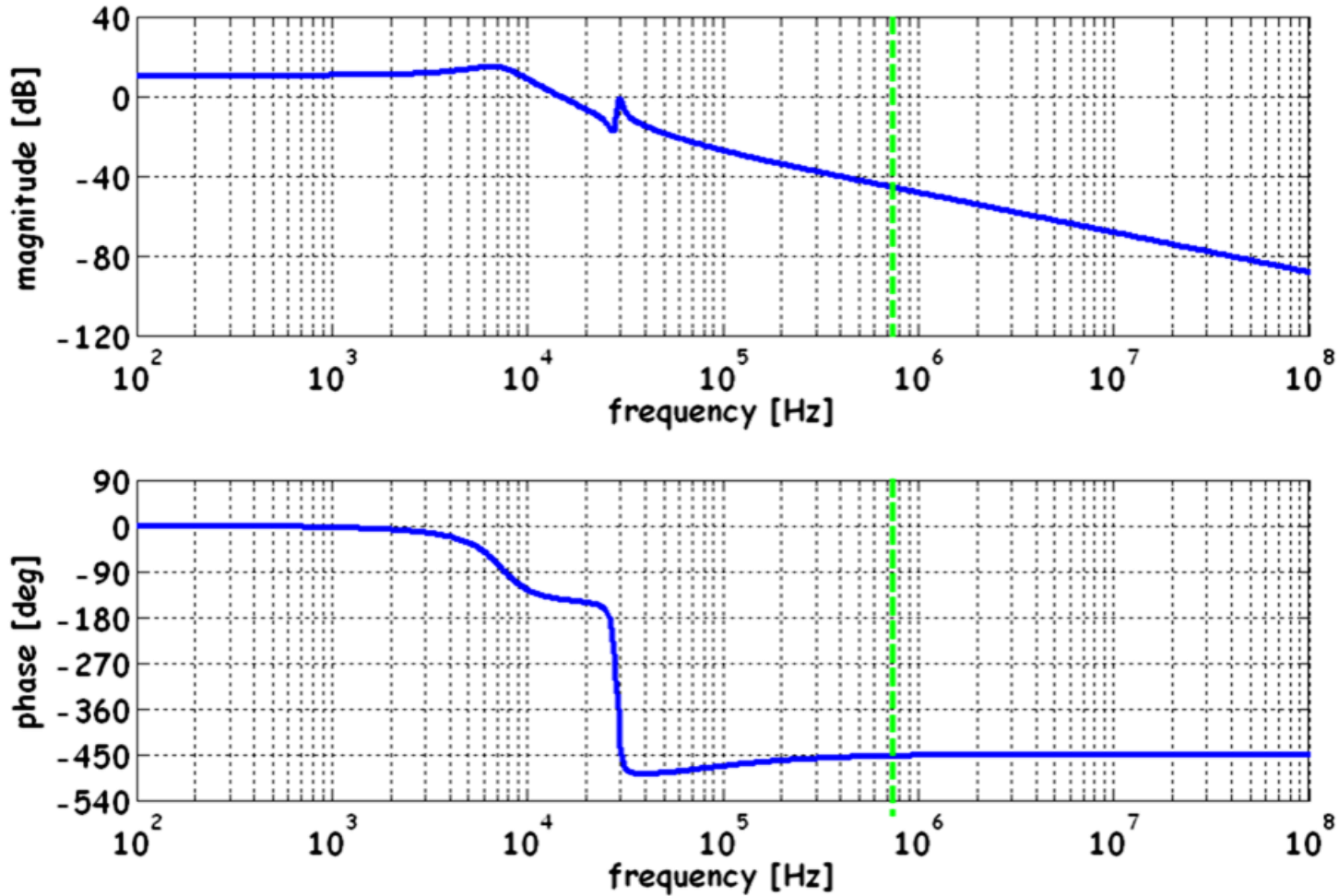
$$Z_O \approx Z_N, Z_D \rightarrow G_{vc} \neq G_{vc,nf}$$



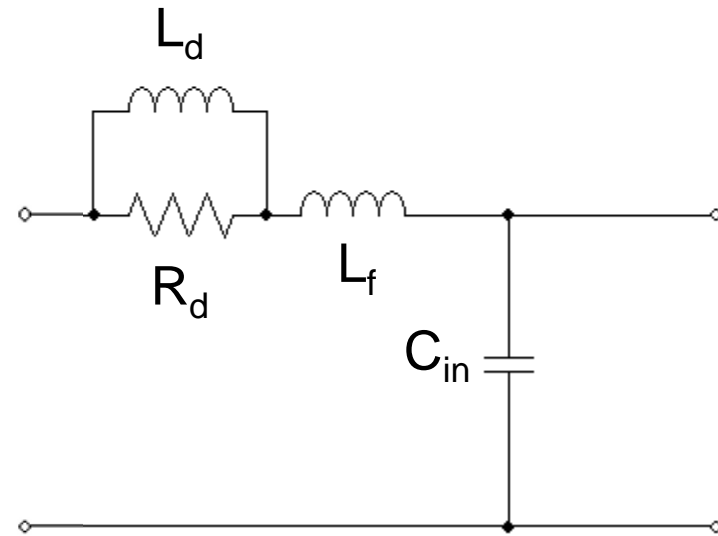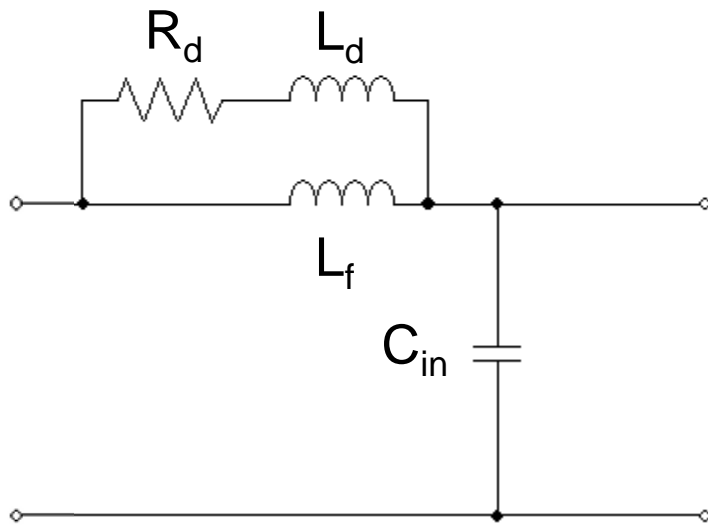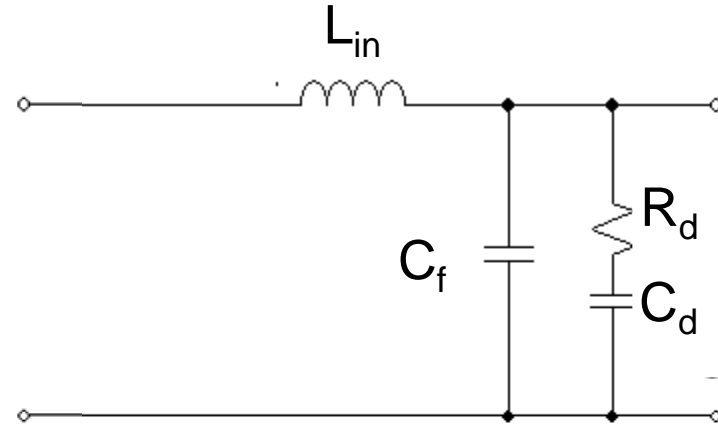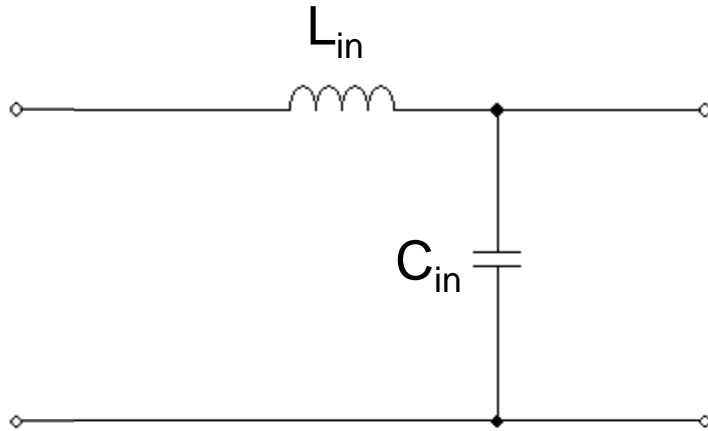

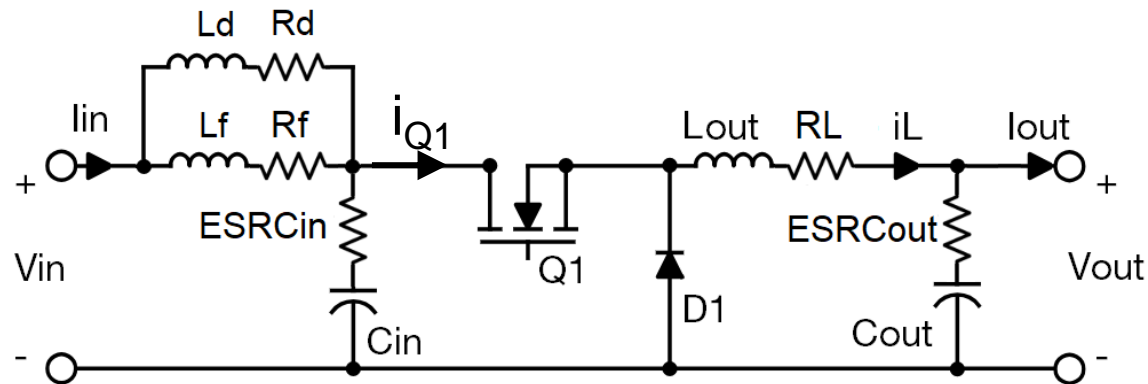R. W. Erickson, "Optimal single resistors damping of input filters", *14th Annual Applied Power Electronics Conf. and Expo. (APEC)*, Dallas, March 1999



$$f_o = \frac{f_s}{\sqrt{A_{f_s}}}$$

$$L_d = \alpha L_f \quad (\alpha > 1)$$

$$\frac{I_{d,DC}}{I_{f,DC}} = \frac{R_f}{R_d} \ll 1$$

$$L_{eq} > \frac{1}{(2\pi f_o)^2 C_{in}}$$


$$L_f > L_{eq} \left( 1 + \frac{1}{\alpha} \right)$$

$$R_f < \frac{P_{f,max}}{I_{inDC,max}^2}$$

$$\frac{1}{L_f} + \frac{1}{L_d} < (2\pi f_o)^2 C_{in}$$

$$L_d > L_{eq} (1 + \alpha)$$

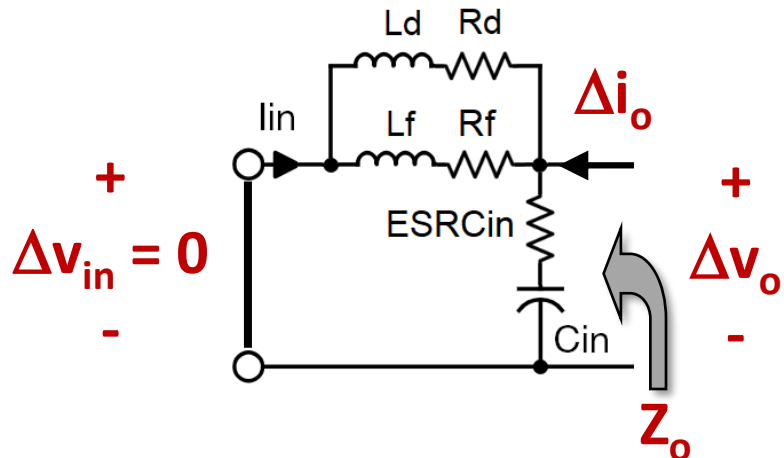
$$R_{d,opt} \cong \frac{1 + \alpha}{2\pi f_o C_{in}}$$



$$Z_o = \left. \frac{\Delta v_o}{\Delta i_o} \right|_{\Delta v_{in}=0}$$

$$Z_{opt} = \frac{\sqrt{2(1+\alpha)(1+2\alpha)}}{2\pi f_o C_{in}}$$
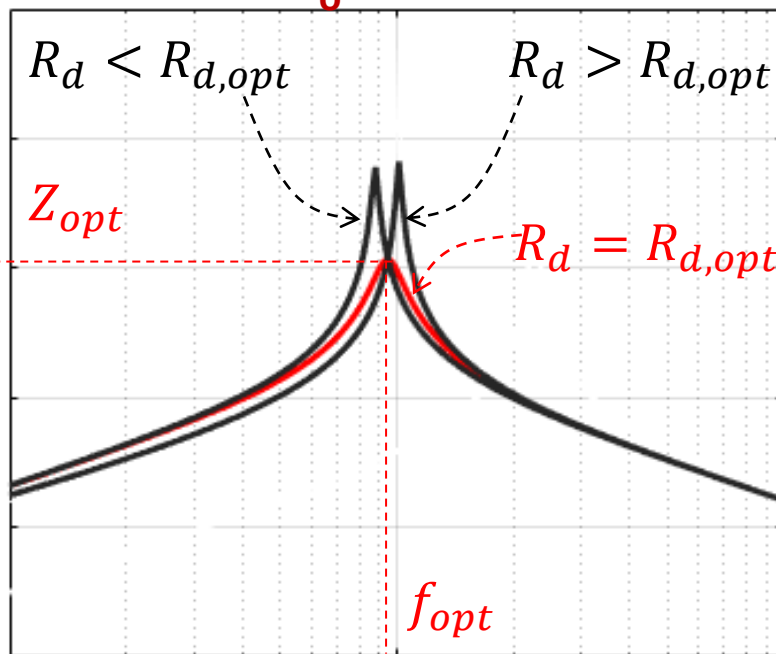
$$f_{opt} = f_o \sqrt{\frac{1+2\alpha}{2(1+\alpha)}}$$



$$L_f > L_{eq} \left( 1 + \frac{1}{\alpha} \right)$$

$$L_d > L_{eq} (1 + \alpha)$$

$$R_f < \frac{P_{f,max}}{I_{inDC,max}^2}$$

$$R_{d,opt} = \frac{1 + \alpha}{2\pi f_o C_{in}}$$

# Input filter: design example

$V_{in} = 5 \text{ V}$

$I_{out} = 1.2 \text{ A}$

$V_{out} = 3.3 \text{ V}$

$f_{sw} = 400 \text{ kHz}$

$C_{in} = 50 \text{ }\mu\text{F}$



$ESRC_{in} = 5 \text{ m}\Omega$

$Att_{fsw} = 73.4 \text{ dB}\mu\text{V}$

$\eta = 90\%$

$P_{loss} = 440 \text{ mW}$

$L_{eq} = 15 \text{ }\mu\text{H}$

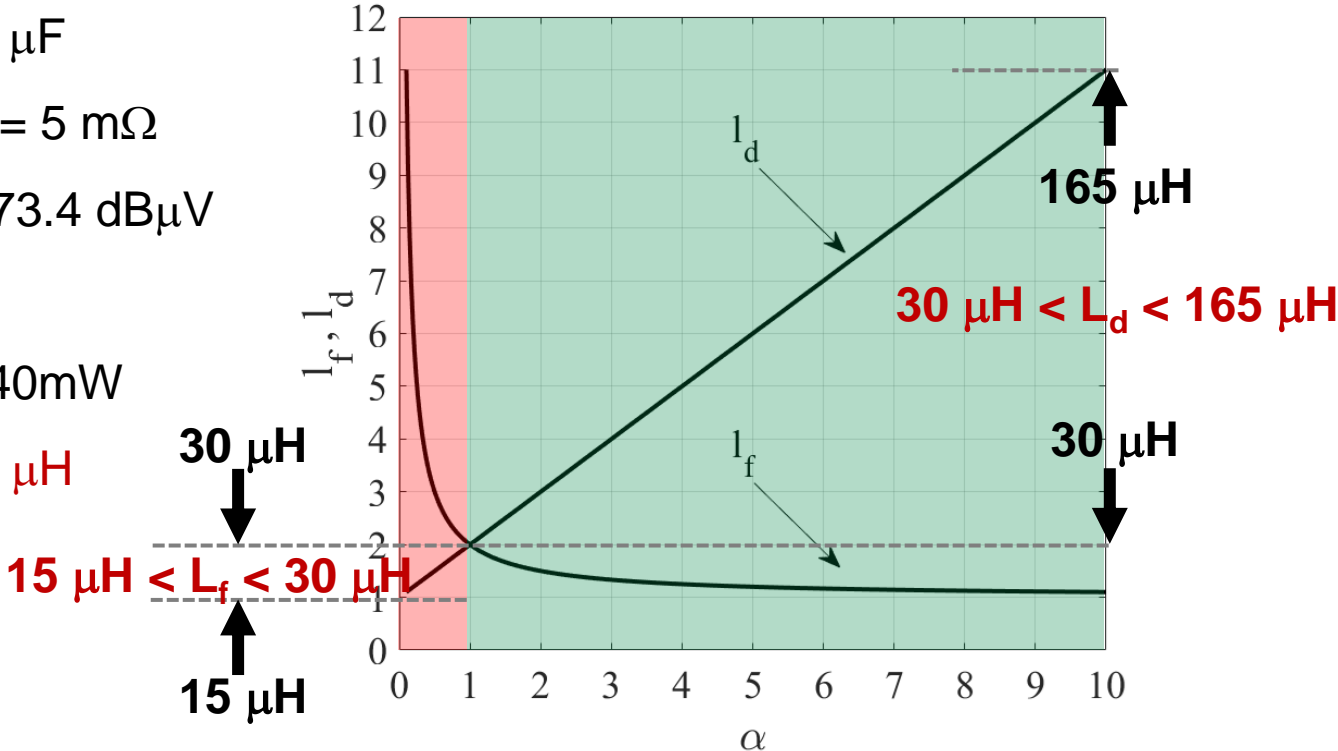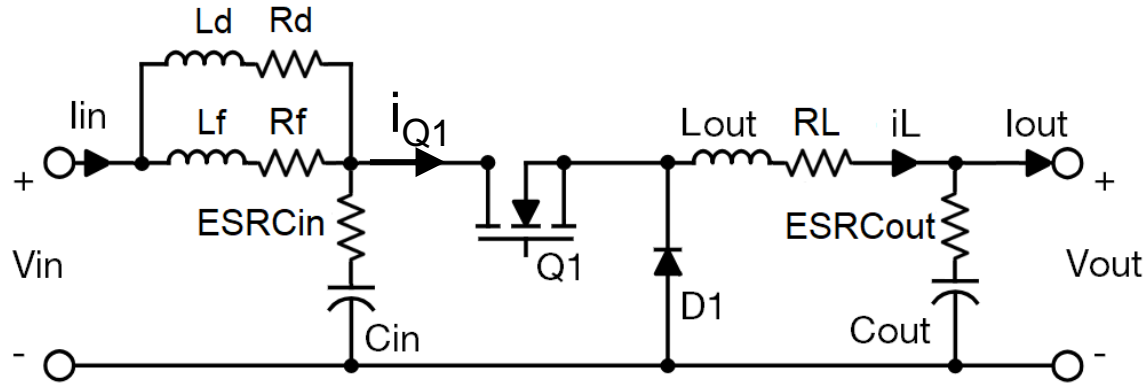

$$l_f = \frac{L_f}{L_{eq}} = 1 + \frac{1}{\alpha}$$

$$l_d = \frac{L_d}{L_{eq}} = 1 + \alpha$$


$$R_f < \frac{P_{f,max}}{I_{inDC,max}^2}$$

$$R_{d,opt} = \frac{1 + \alpha}{2\pi f_o C_{in}}$$


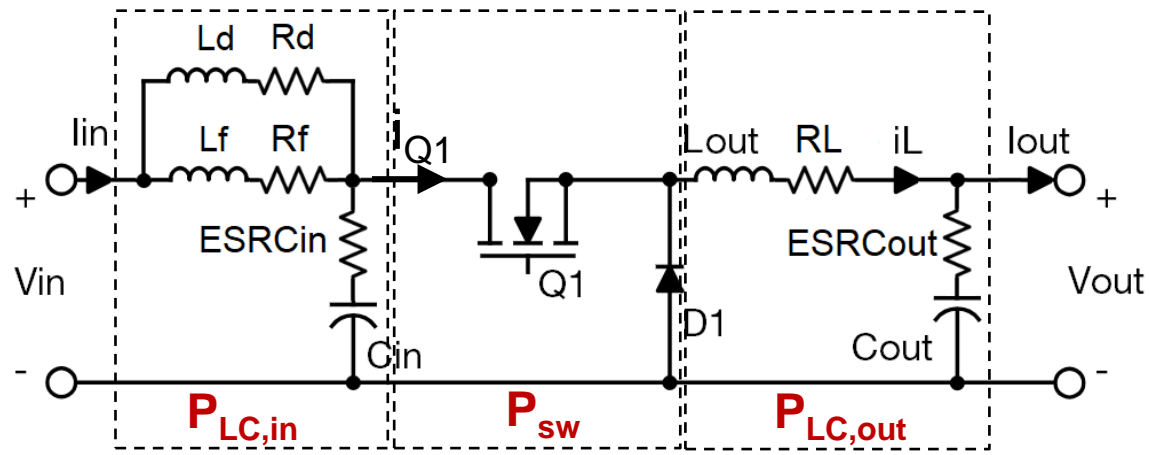
# Input filter: loss budget allocation

$V_{in} = 5 \text{ V}$   
 $I_{out} = 1.2 \text{ A}$   
 $V_{out} = 3.3 \text{ V}$   
 $f_{sw} = 400 \text{ kHz}$   
 $C_{in} = 50 \text{ }\mu\text{F}$   
 $ESRC_{in} = 5 \text{ m}\Omega$   
 $Att_{fsw} = 73.4 \text{ dB}\mu\text{V}$   
 $\eta = 90\%$   
 $P_{loss} = 440 \text{ mW}$   
 $I_{inDC,max} = 0.88 \text{ A}$   
 $L_{eq} = 15 \text{ }\mu\text{H}$



$P_f / P_{loss} \text{ [%]}$	$P_{f,max} \text{ [mW]}$	$R_{f,max} \text{ [m}\Omega\text{]}$
2	8.8	11.4
5	22	38.5
10	44	57.0
20	88	114.0



$$l_f = \frac{L_f}{L_{eq}} = 1 + \frac{1}{\alpha}$$

$$l_d = \frac{L_d}{L_{eq}} = 1 + \alpha$$

$$R_f < \frac{P_{f,max}}{I_{inDC,max}^2}$$

$$R_{d,opt} = \frac{1 + \alpha}{2\pi f_o C_{in}}$$

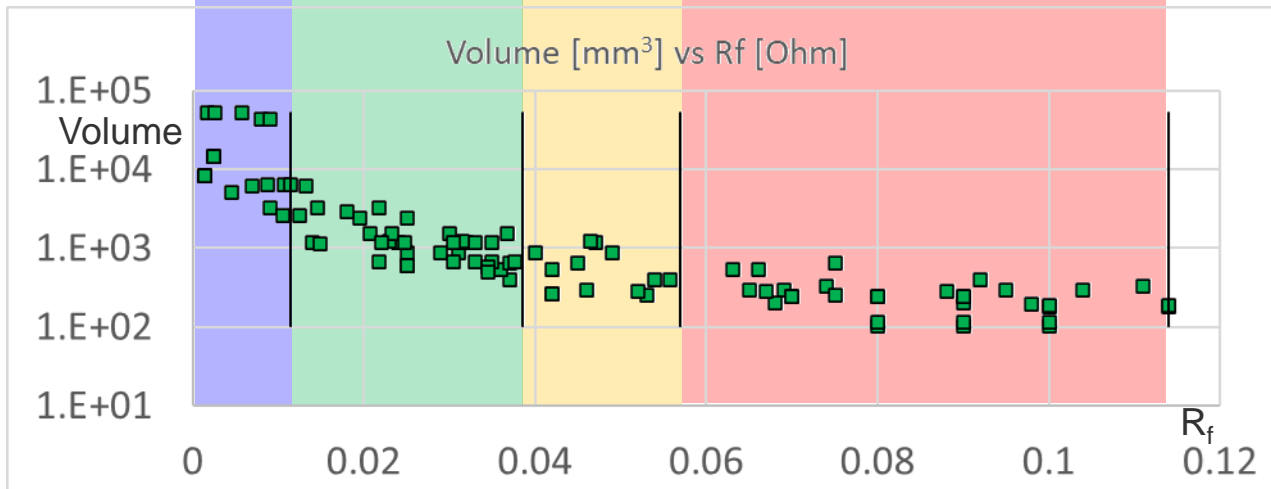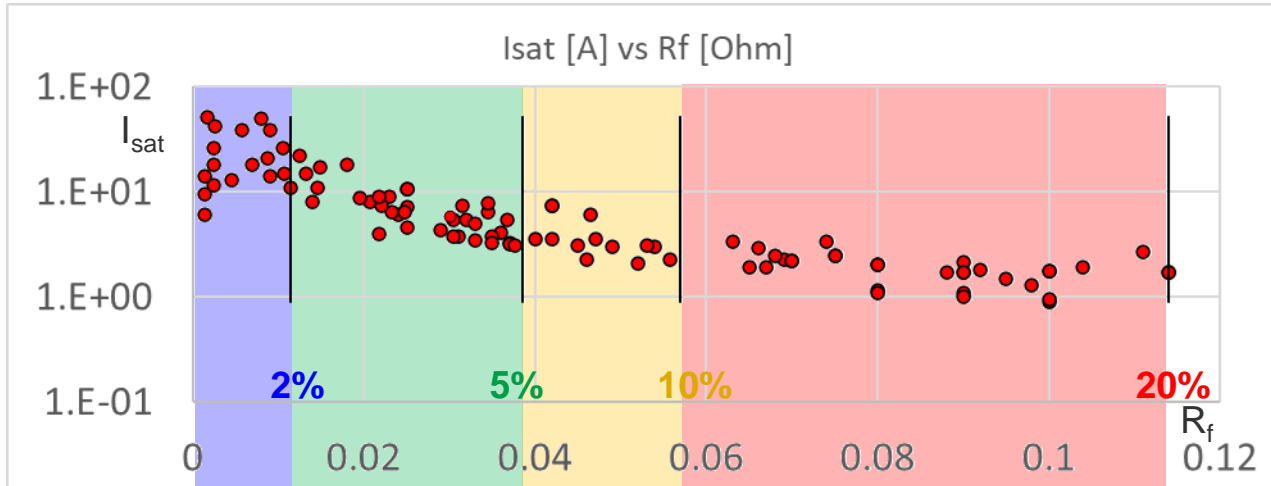power inductors with  $15 \mu\text{H} \leq L \leq 33 \mu\text{H}$  and  $R_f \leq 114 \text{ m}\Omega$



smallest parts with  $57.0 \text{ m}\Omega \leq R_f < 114 \text{ m}\Omega$

Part Code	L [ $\mu\text{H}$ ]	R [ $\text{m}\Omega$ ]	Isat [A]	Vol. [ $\text{mm}^3$ ]
744062220	22	100.0	0.95	113
744071220	22	65.0	1.9	296
744071330	33	95.0	1.5	296

smallest parts with  $38.5 \text{ m}\Omega \leq R_f < 57.0 \text{ m}\Omega$

Part Code	L [ $\mu\text{H}$ ]	R [ $\text{m}\Omega$ ]	Isat [A]	Vol. [ $\text{mm}^3$ ]
7447773150	15	53.0	3.1	252
78439346150	15	42.0	7.4	264
74439346150	15	42.0	7.4	264

smallest parts with  $11.4 \text{ m}\Omega \leq R_f < 38.5 \text{ m}\Omega$

Part Code	L [ $\mu\text{H}$ ]	R [ $\text{m}\Omega$ ]	Isat [A]	Vol. [ $\text{mm}^3$ ]
744066150	15	37.0	3.25	403
784325160	16.7	34.5	7.8	503
7447714150	15	36.0	4.1	541

smallest parts with  $R_f < 11.4 \text{ m}\Omega$

Part Code	L [ $\mu\text{H}$ ]	R [ $\text{m}\Omega$ ]	Isat [A]	Vol. [ $\text{mm}^3$ ]
78439370150	15	10.5	26.1	2622
74435571500	15	9.0	14	3212
7443782012150	15	4.6	12.9	5049


[<https://www.we-online.com/catalog/en>]

# Input filter: design with saturating filter inductor


power inductors with  $15 \mu\text{H} \leq L \leq 33 \mu\text{H}$  and  $R_f \leq 114 \text{ m}\Omega$

$L_A = 18 \mu\text{H} @ I_{\text{inDC,max}} = 0.9\text{A}$

$P_f \leq 20\% P_{\text{loss}}$

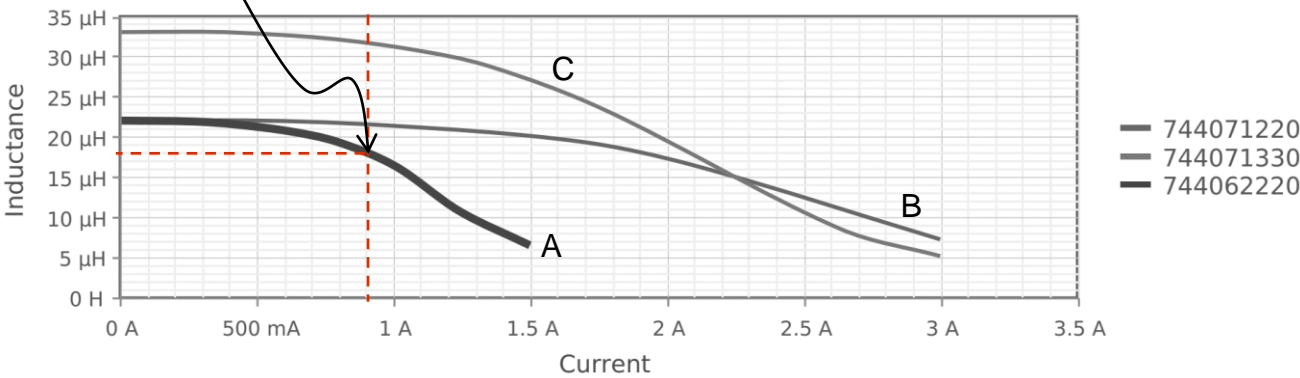
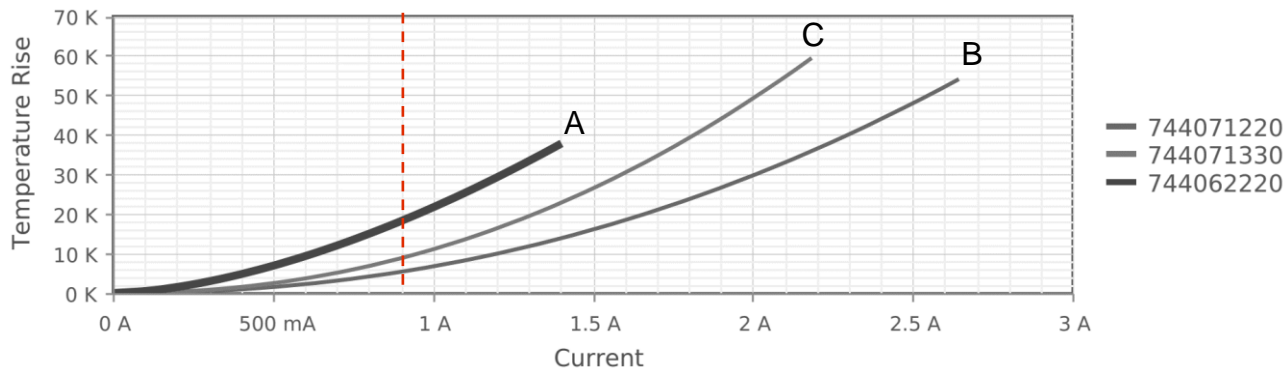
$$L_f = LA \rightarrow l_f = 1.2 \rightarrow \alpha = 5 \rightarrow L_d = 90\mu\text{H}, R_{d,opt} = 3.26\Omega$$



smallest parts with  $57.0 \text{ m}\Omega \leq R_f < 114 \text{ m}\Omega$

Part Code	L [ $\mu\text{H}$ ]	R [ $\text{m}\Omega$ ]	Isat [A]	Vol. [ $\text{mm}^3$ ]
<b>A - 744062220</b>	<b>22</b>	<b>100.0</b>	<b>0.95</b>	<b>113</b>
B - 744071220	22	65.0	1.9	296
C - 744071330	33	95.0	1.5	296

smallest parts with  $38.5 \text{ m}\Omega \leq R_f < 57.0 \text{ m}\Omega$

Part Code	L [ $\mu\text{H}$ ]	R [ $\text{m}\Omega$ ]	Isat [A]	Vol. [ $\text{mm}^3$ ]
7447773150	15	53.0	3.1	252
78439346150	15	42.0	7.4	264
74439346150	15	42.0	7.4	264

smallest parts with  $11.4 \text{ m}\Omega \leq R_f < 38.5 \text{ m}\Omega$

Part Code	L [ $\mu\text{H}$ ]	R [ $\text{m}\Omega$ ]	Isat [A]	Vol. [ $\text{mm}^3$ ]
744066150	15	37.0	3.25	403
784325160	16.7	34.5	7.8	503
7447714150	15	36.0	4.1	541

smallest parts with  $R_f < 11.4 \text{ m}\Omega$

Part Code	L [ $\mu\text{H}$ ]	R [ $\text{m}\Omega$ ]	Isat [A]	Vol. [ $\text{mm}^3$ ]
78439370150	15	10.5	26.1	2622
74435571500	15	9.0	14	3212
7443782012150	15	4.6	12.9	5049

[<https://www.we-online.com/catalog/en>]

# Input filter: optimal damping inductor

power inductors with  $100 \mu\text{H} \leq L \leq 150 \mu\text{H}$  and  $2\Omega \leq R_d \leq 5\Omega$


$$P_f \leq 20\% P_{\text{loss}}$$

$$P_f + P_d = (0.1\Omega / 4.25\Omega) 0.9^2 = 79\text{mW} = 18\% P_{\text{loss}}$$


- 74404042151
- 7447732210
- 744032101

smallest parts with  $2\Omega \leq R_d < 5\Omega$


Part Code	L [ $\mu\text{H}$ ]	R [ $\text{m}\Omega$ ]	Isat [A]	Vol. [ $\text{mm}^3$ ]
<b>D - 744032101</b>	<b>100</b>	<b>4.25</b>	<b>0.25</b>	<b>16</b>
E - 7447732210	100	2.42	0.41	22
F - 74404042151	150	2.85	0.45	26

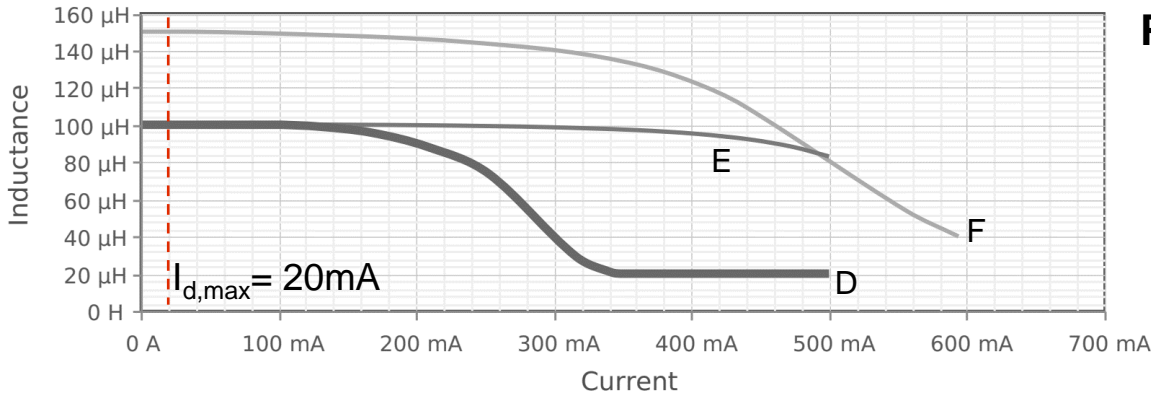
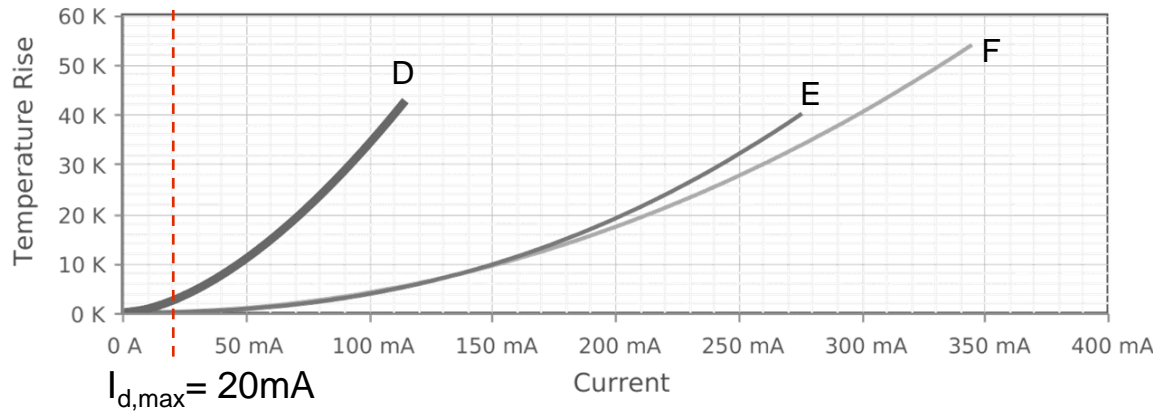
$$L_d = LD \rightarrow R_d = 4.25\Omega \rightarrow I_{d,max} = 20\text{mA}$$



- 74404042151
- 7447732210
- 744032101

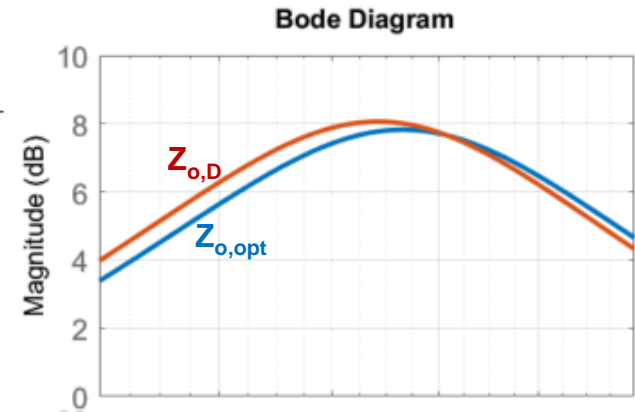


[<https://www.we-online.com/catalog/en>]


# Input filter: design with non-saturating filter inductor (1)

power inductors with  $15 \mu\text{H} \leq L \leq 33 \mu\text{H}$  and  $R_f \leq 114 \text{ m}\Omega$

$$P_f \leq 10\% P_{\text{loss}}$$

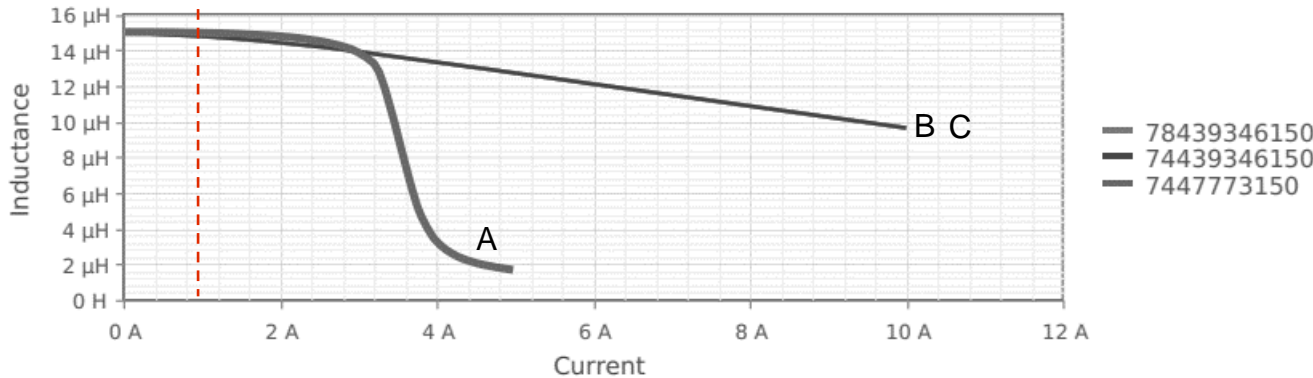
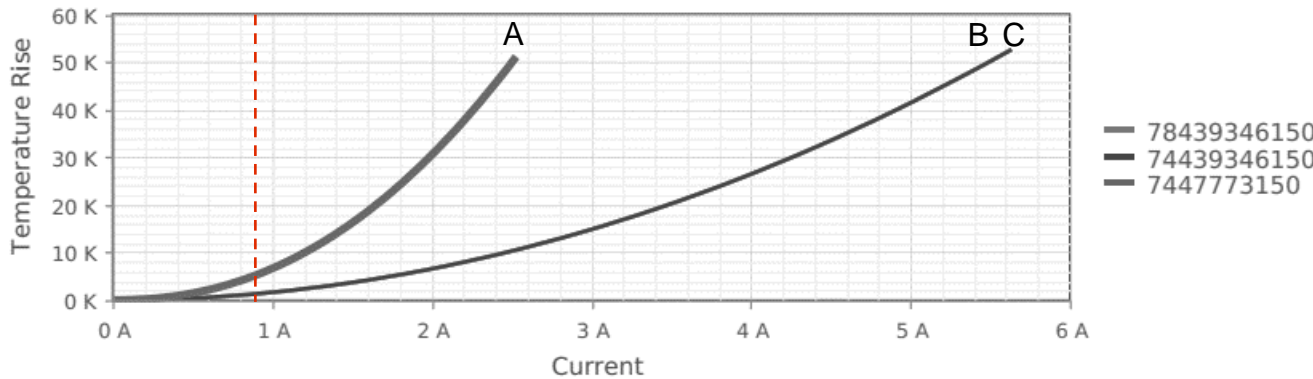
$$l_f \cong 1 \rightarrow \alpha = 11 \rightarrow L_d = 165 \mu\text{H}, R_{d,opt} = 6.53 \Omega$$



smallest parts with  $57.0 \text{ m}\Omega \leq R_f < 114 \text{ m}\Omega$

Part Code	L [ $\mu\text{H}$ ]	R [ $\text{m}\Omega$ ]	Isat [A]	Vol. [ $\text{mm}^3$ ]
<b>744062220</b>	<b>22</b>	<b>100.0</b>	<b>0.95</b>	<b>113</b>
744071220	22	65.0	1.9	296
744071330	33	95.0	1.5	296

smallest parts with  $38.5 \text{ m}\Omega \leq R_f < 57.0 \text{ m}\Omega$

Part Code	L [ $\mu\text{H}$ ]	R [ $\text{m}\Omega$ ]	Isat [A]	Vol. [ $\text{mm}^3$ ]
<b>A - 7447773150</b>	<b>15</b>	<b>53.0</b>	<b>3.1</b>	<b>252 (2.23x)</b>
B - 78439346150	15	42.0	7.4	264
C - 74439346150	15	42.0	7.4	264

smallest parts with  $11.4 \text{ m}\Omega \leq R_f < 38.5 \text{ m}\Omega$

Part Code	L [ $\mu\text{H}$ ]	R [ $\text{m}\Omega$ ]	Isat [A]	Vol. [ $\text{mm}^3$ ]
744066150	15	37.0	3.25	403
784325160	16.7	34.5	7.8	503
7447714150	15	36.0	4.1	541

smallest parts with  $R_f < 11.4 \text{ m}\Omega$


Part Code	L [ $\mu\text{H}$ ]	R [ $\text{m}\Omega$ ]	Isat [A]	Vol. [ $\text{mm}^3$ ]
78439370150	15	10.5	26.1	2622
74435571500	15	9.0	14	3212
7443782012150	15	4.6	12.9	5049

[<https://www.we-online.com/catalog/en>]


# Input filter: design with non-saturating filter inductor (2)

power inductors with  $15 \mu\text{H} \leq L \leq 33 \mu\text{H}$  and  $R_f \leq 114 \text{ m}\Omega$

$$P_f \leq 5\% P_{\text{loss}}$$

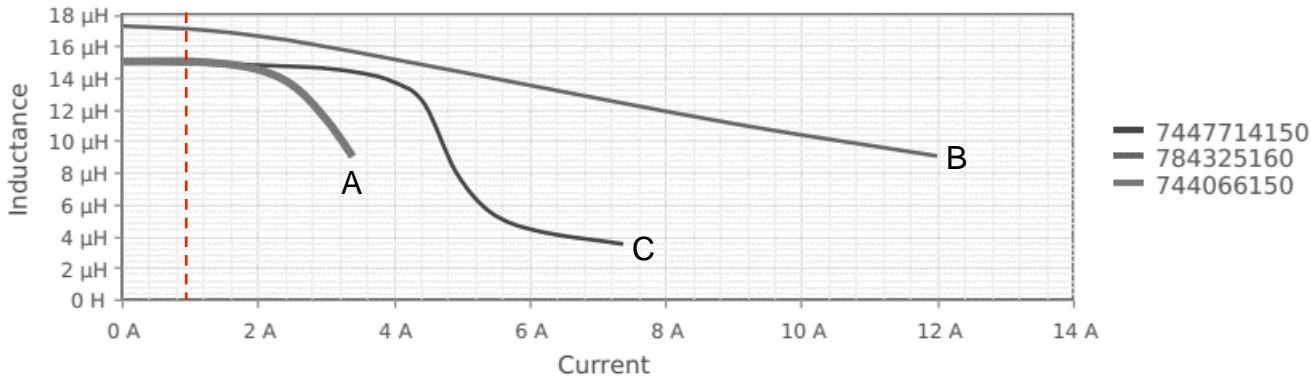
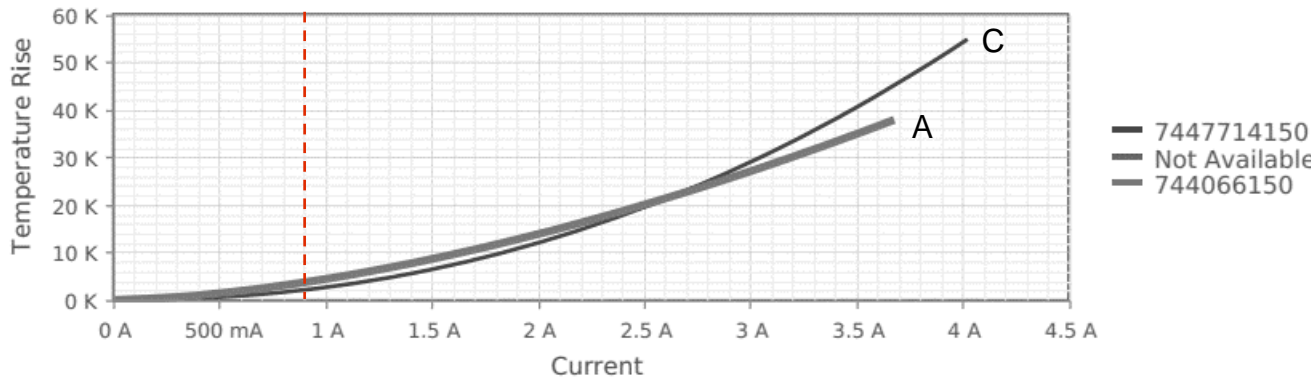
$$l_f \cong 1 \rightarrow \alpha = 11 \rightarrow L_d = 165 \mu\text{H}, R_{d,opt} = 6.53 \Omega$$



smallest parts with  $57.0 \text{ m}\Omega \leq R_f < 114 \text{ m}\Omega$

Part Code	L [ $\mu\text{H}$ ]	R [ $\text{m}\Omega$ ]	Isat [A]	Vol. [ $\text{mm}^3$ ]
<b>744062220</b>	<b>22</b>	<b>100.0</b>	<b>0.95</b>	<b>113</b>
744071220	22	65.0	1.9	296
744071330	33	95.0	1.5	296

smallest parts with  $38.5 \text{ m}\Omega \leq R_f < 57.0 \text{ m}\Omega$

Part Code	L [ $\mu\text{H}$ ]	R [ $\text{m}\Omega$ ]	Isat [A]	Vol. [ $\text{mm}^3$ ]
7447773150	15	53.0	3.1	252
78439346150	15	42.0	7.4	264
74439346150	15	42.0	7.4	264

smallest parts with  $11.4 \text{ m}\Omega \leq R_f < 38.5 \text{ m}\Omega$

Part Code	L [ $\mu\text{H}$ ]	R [ $\text{m}\Omega$ ]	Isat [A]	Vol. [ $\text{mm}^3$ ]
<b>A - 744066150</b>	<b>15</b>	<b>37.0</b>	<b>3.25</b>	<b>403 (3.57x)</b>
B - 784325160	16.7	34.5	7.8	503
C - 7447714150	15	36.0	4.1	541

smallest parts with  $R_f < 11.4 \text{ m}\Omega$


Part Code	L [ $\mu\text{H}$ ]	R [ $\text{m}\Omega$ ]	Isat [A]	Vol. [ $\text{mm}^3$ ]
78439370150	15	10.5	26.1	2622
74435571500	15	9.0	14	3212
7443782012150	15	4.6	12.9	5049

[<https://www.we-online.com/catalog/en>]

# Input filter: design with non-saturating filter inductor (3)

power inductors with  $15 \mu\text{H} \leq L \leq 33 \mu\text{H}$  and  $R_f \leq 114 \text{ m}\Omega$

$$P_f \leq 2\% P_{\text{loss}}$$

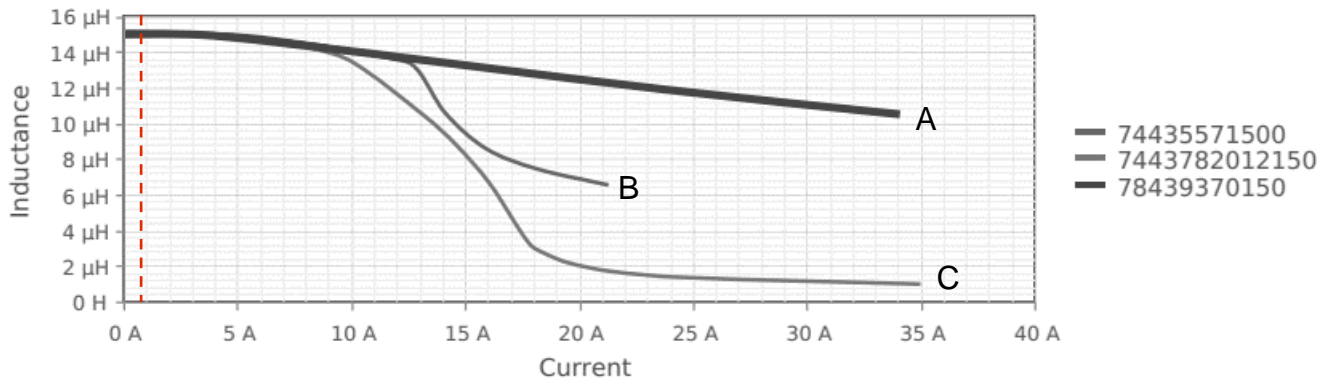


smallest parts with  $57.0 \text{ m}\Omega \leq R_f < 114 \text{ m}\Omega$

Part Code	L [μH]	R [mΩ]	Isat [A]	Vol. [mm <sup>3</sup> ]
<b>744062220</b>	<b>22</b>	<b>100.0</b>	<b>0.95</b>	<b>113</b>
744071220	22	65.0	1.9	296
744071330	33	95.0	1.5	296

smallest parts with  $38.5 \text{ m}\Omega \leq R_f < 57.0 \text{ m}\Omega$

Part Code	L [μH]	R [mΩ]	Isat [A]	Vol. [mm <sup>3</sup> ]
7447773150	15	53.0	3.1	252
78439346150	15	42.0	7.4	264
74439346150	15	42.0	7.4	264
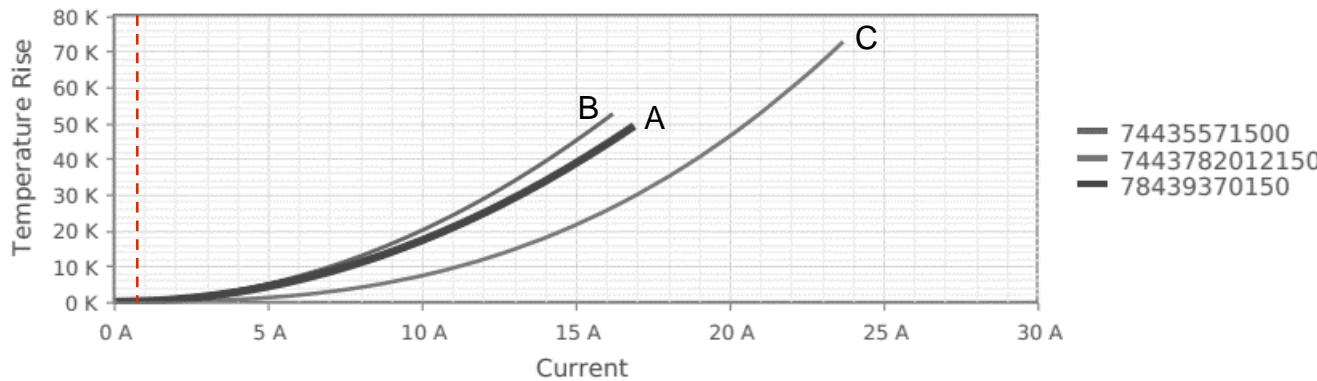
$$l_f \cong 1 \rightarrow \alpha = 11 \rightarrow L_d = 165 \mu\text{H}, R_{d,opt} = 6.53 \Omega$$



smallest parts with  $11.4 \text{ m}\Omega \leq R_f < 38.5 \text{ m}\Omega$



Part Code	L [μH]	R [mΩ]	Isat [A]	Vol. [mm <sup>3</sup> ]
744066150	15	37.0	3.25	403
784325160	16.7	34.5	7.8	503
7447714150	15	36.0	4.1	541

smallest parts with  $R_f < 11.4 \text{ m}\Omega$

Part Code	L [μH]	R [mΩ]	Isat [A]	Vol. [mm <sup>3</sup> ]
<b>A - 78439370150</b>	<b>15</b>	<b>10.5</b>	<b>26.1</b>	<b>2622 (23.2x)</b>
B - 74435571500	15	9.0	14	3212
C - 7443782012150	15	4.6	12.9	5049


[<https://www.we-online.com/catalog/en>]
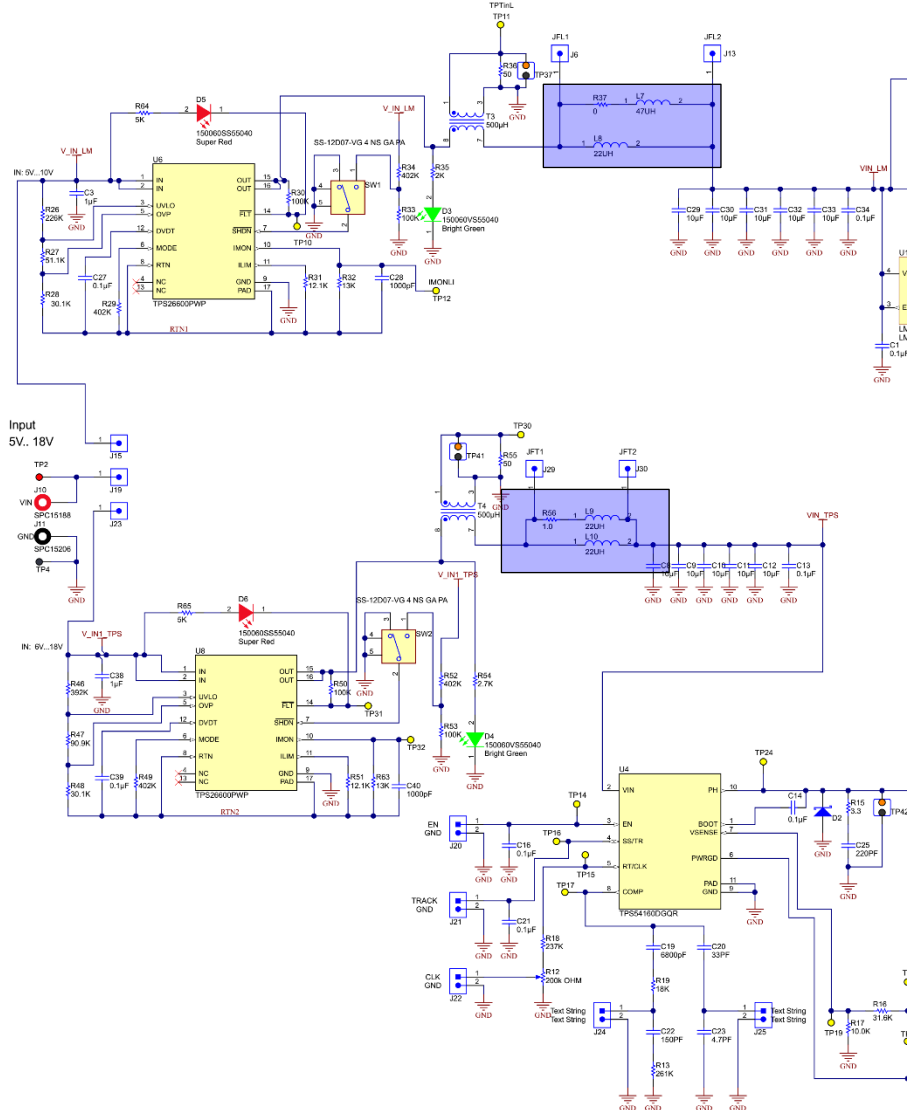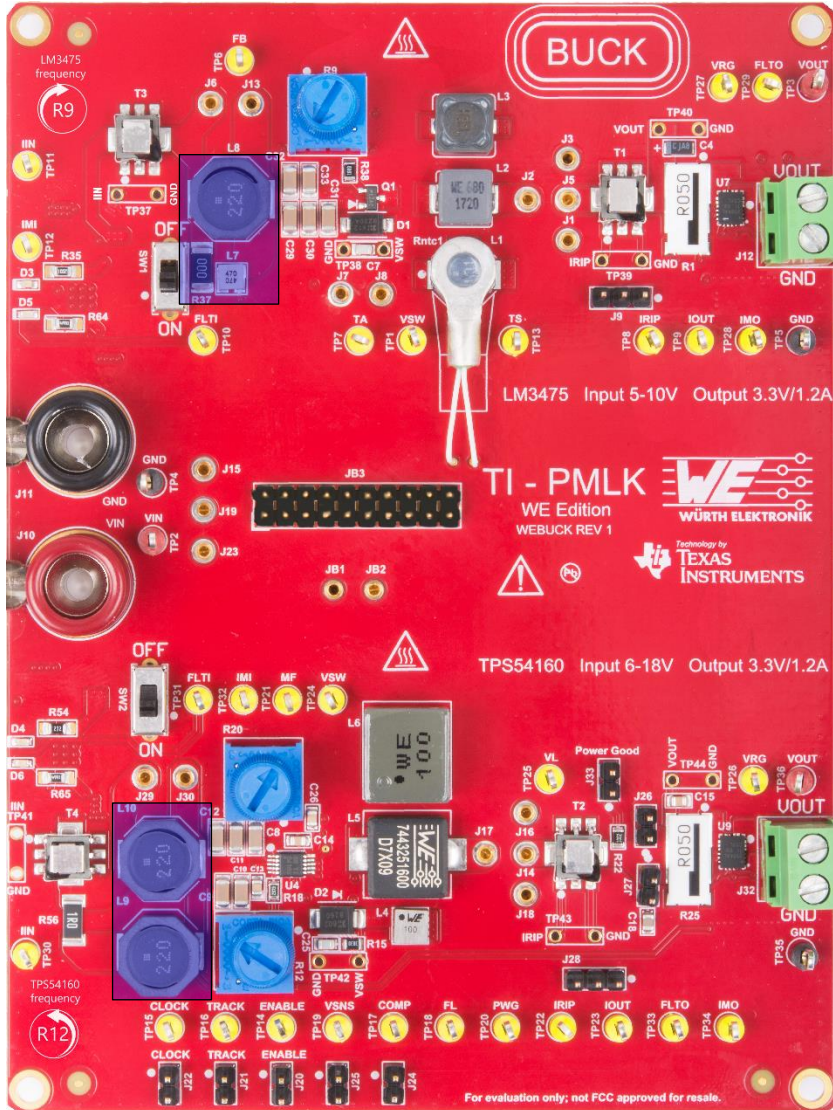
# Input filter: TI-PMLK BUCK WE test board






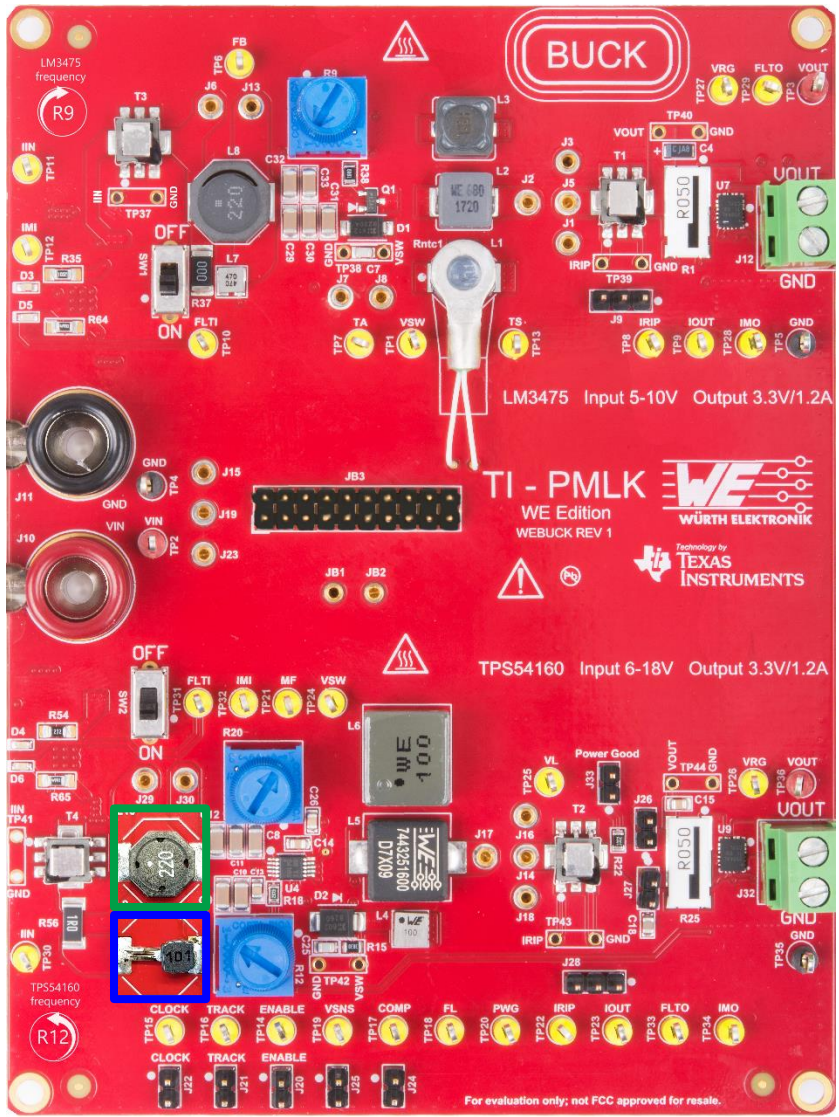
# Input filter: experimental test with saturating inductor



Part Code	L [ $\mu\text{H}$ ]	R [ $\text{m}\Omega$ ]	Isat [A]	Vol. [ $\text{mm}^3$ ]
<b>744062220</b>	<b>22</b>	<b>100.0</b>	<b>0.95</b>	<b>113</b>

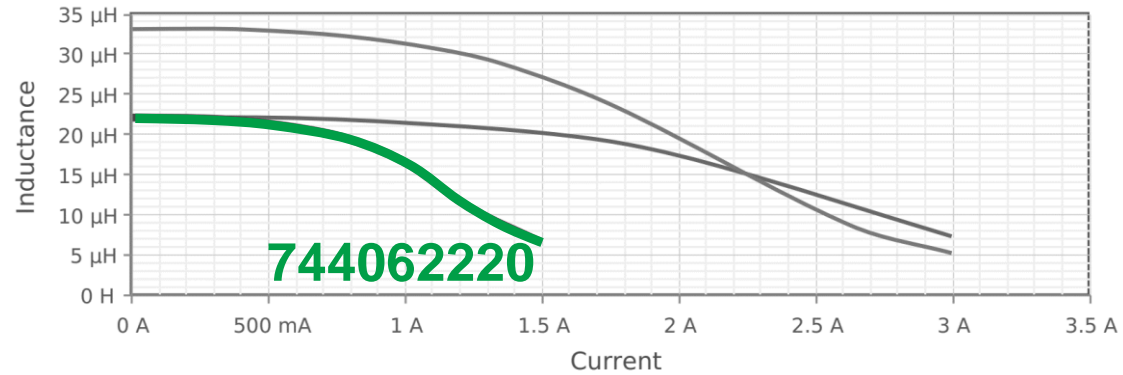

Part Code	L [ $\mu\text{H}$ ]	R [ $\text{m}\Omega$ ]	Isat [A]	Vol. [ $\text{mm}^3$ ]
<b>744032101</b>	<b>100</b>	<b>4.25</b>	<b>0.25</b>	<b>16</b>

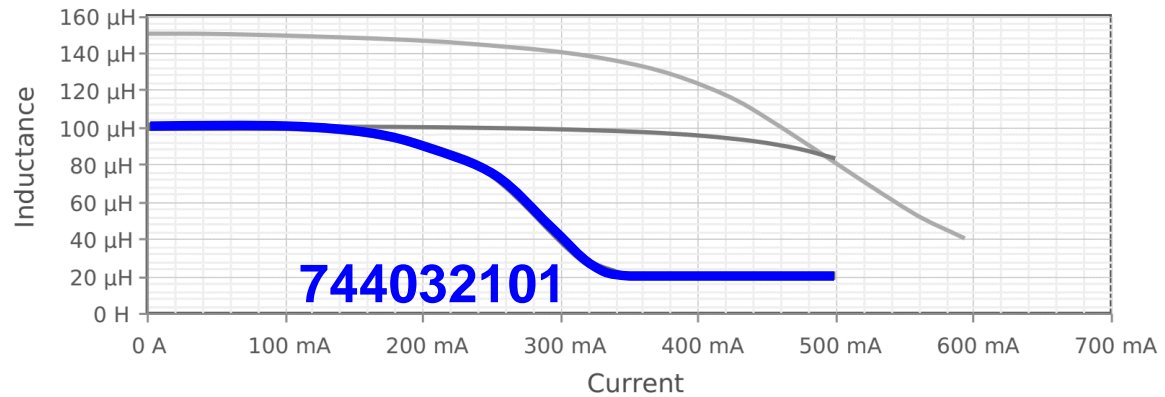

# Input filter: test setup

R&S RT-ZC20B current probe




R&S NGL/NGM power supply

R&S RTM3004 oscilloscope



CH1 CH2 CH3 CH4

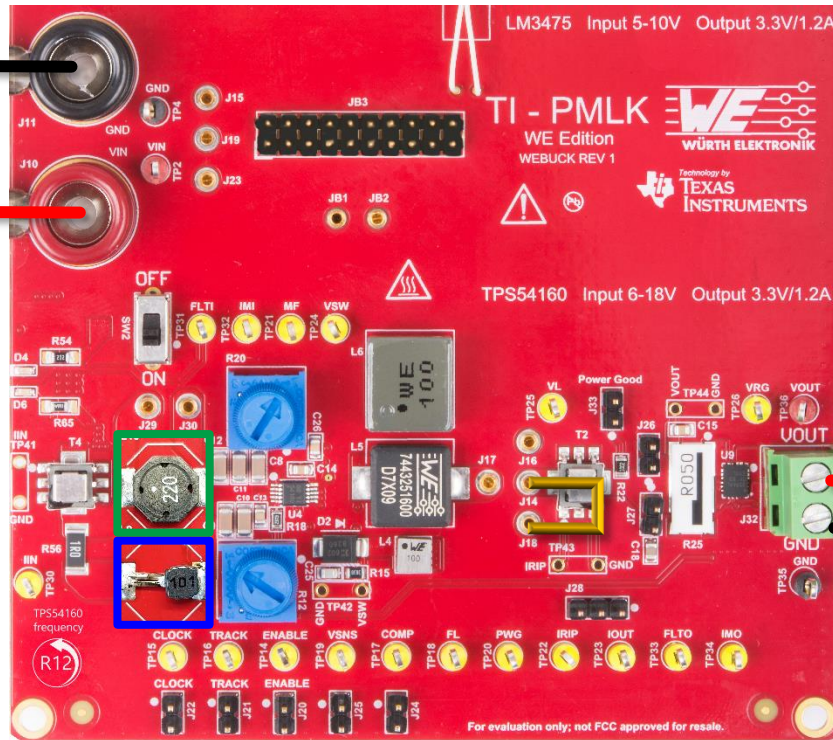


EA EL 3080-60 B electronic load



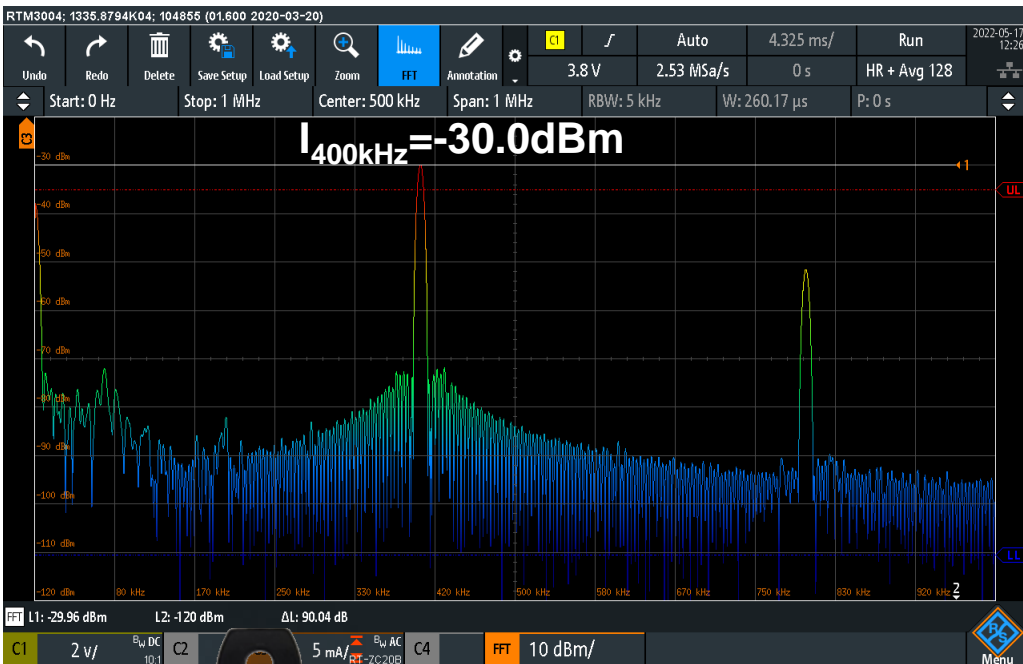
# Input filter: experimental input current spectrum



$$V_{in}=5V, V_{out}= 3.3 V , I_{out}=1.2 A, f_s= 400 kHz$$



**inductors shorted**

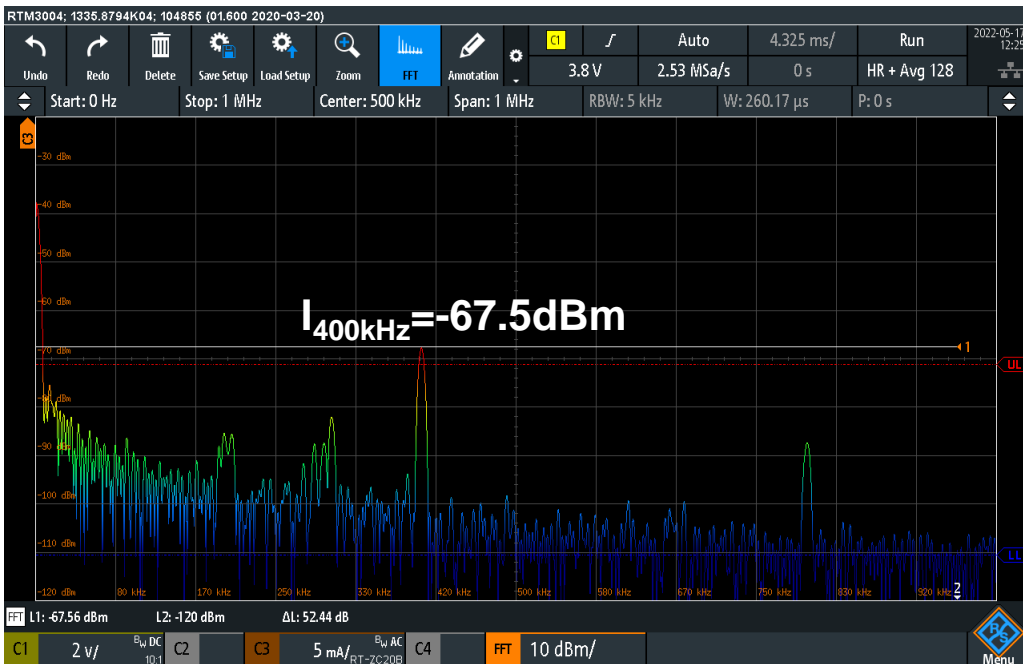


**inductors unshorted**


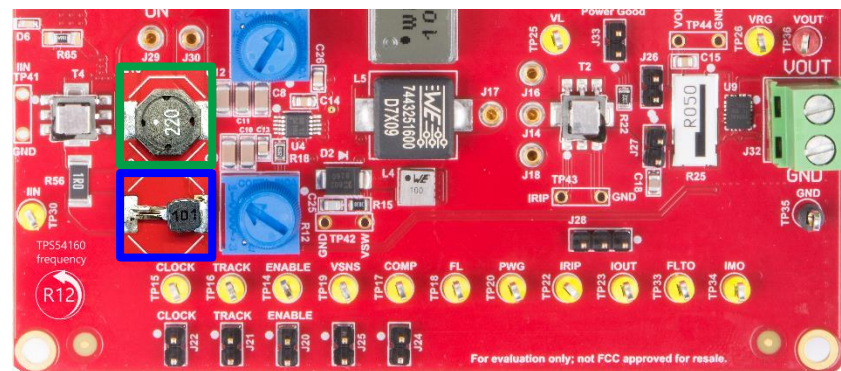
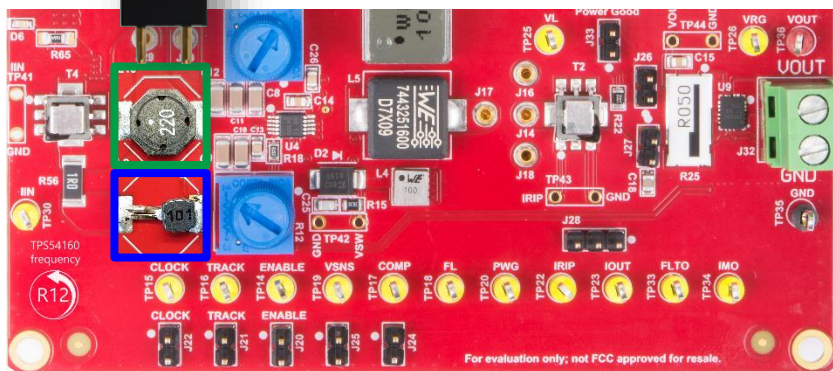








# Power-to-Control PCB cross-talk

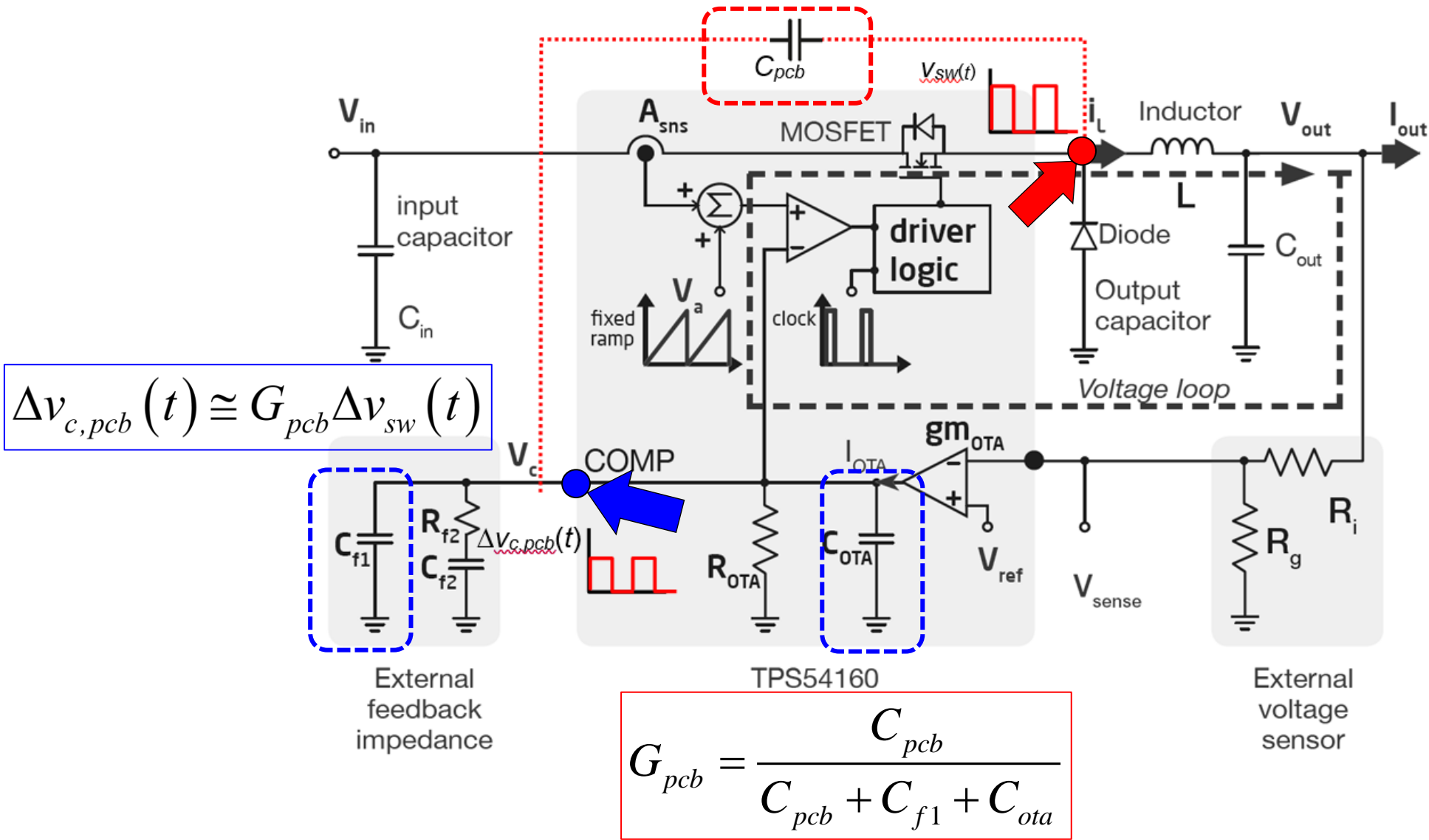
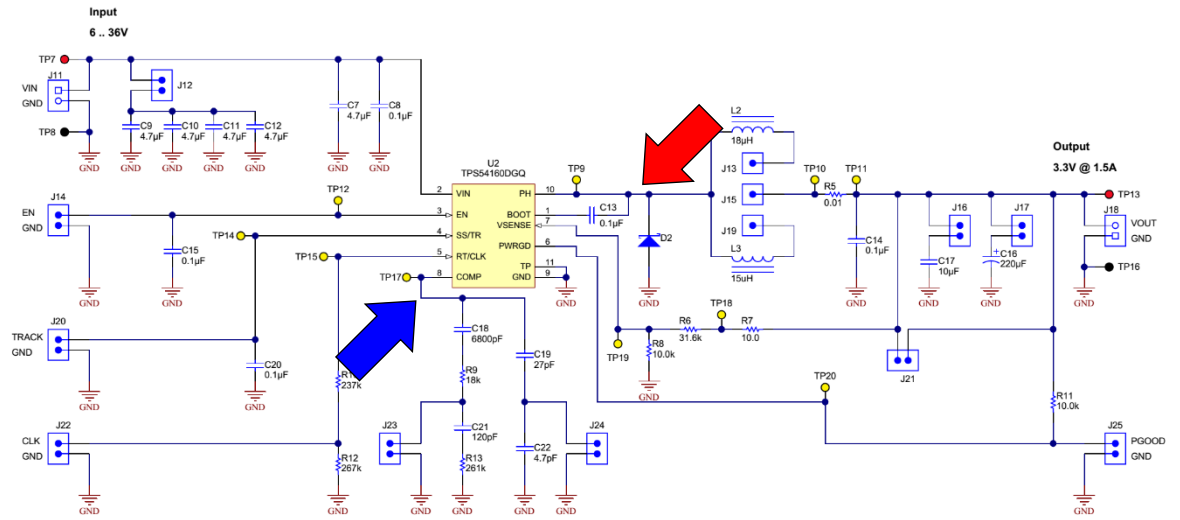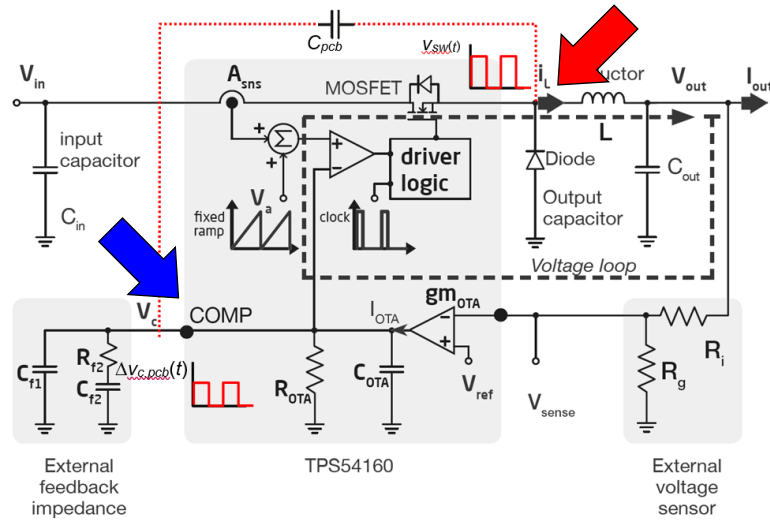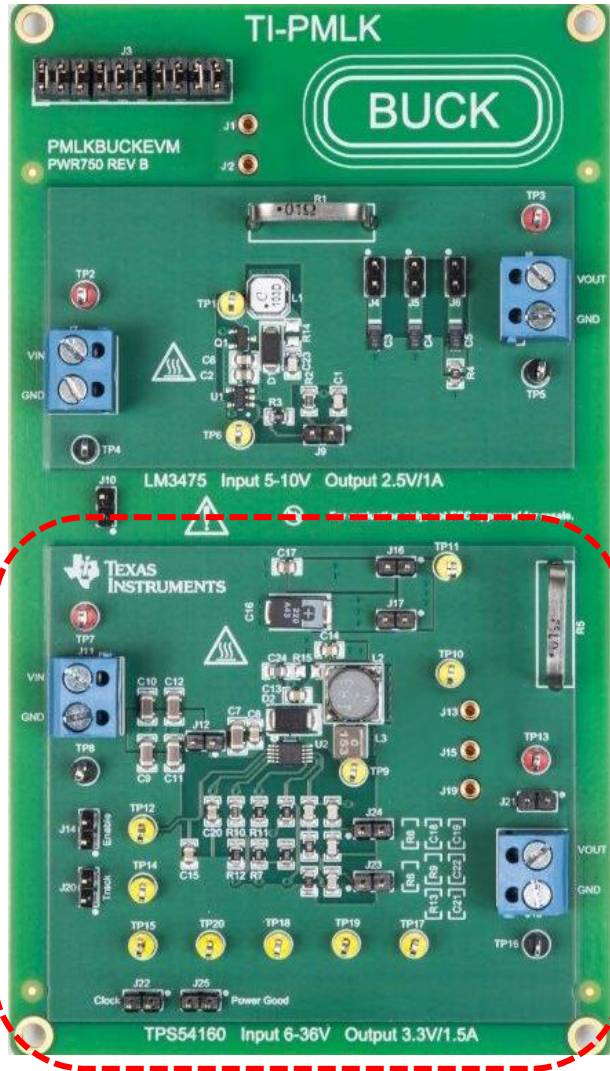
# Crosstalk: TI-PMLK BUCK experimental example


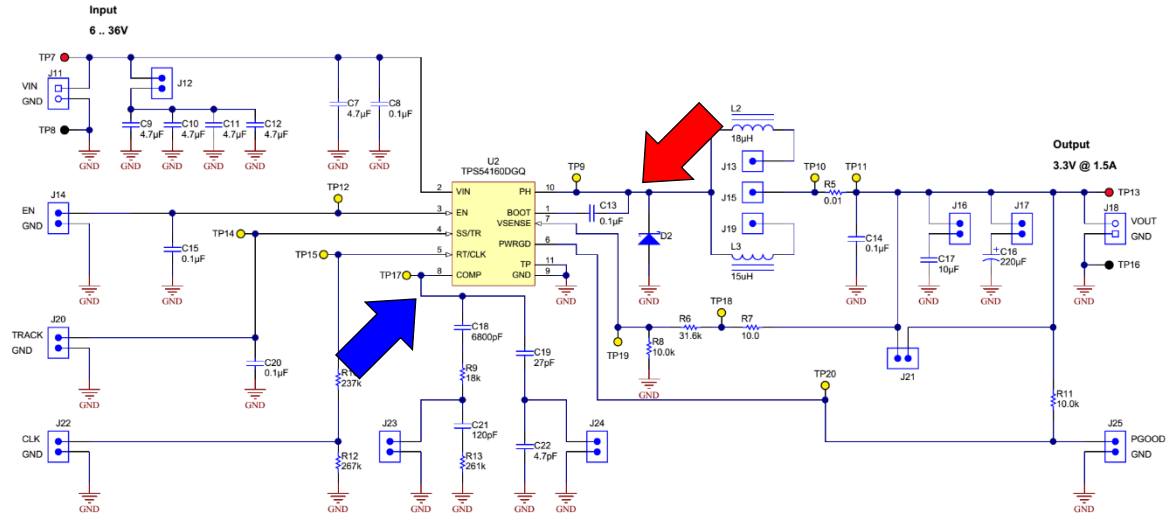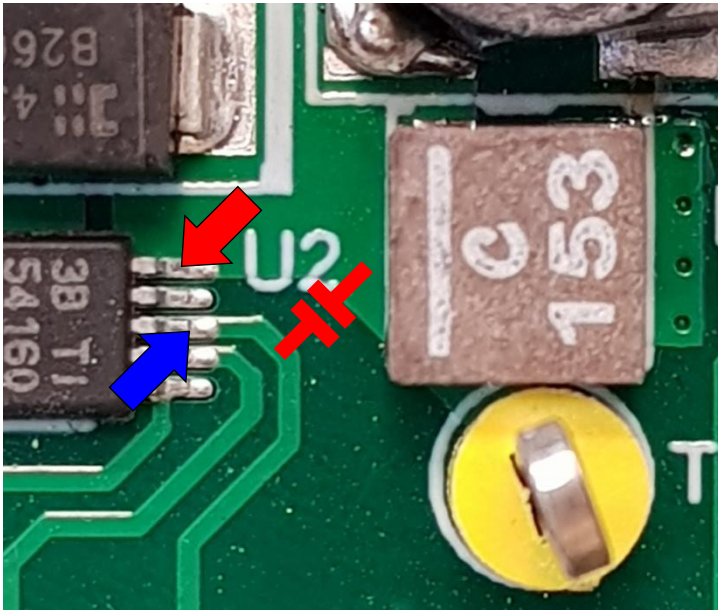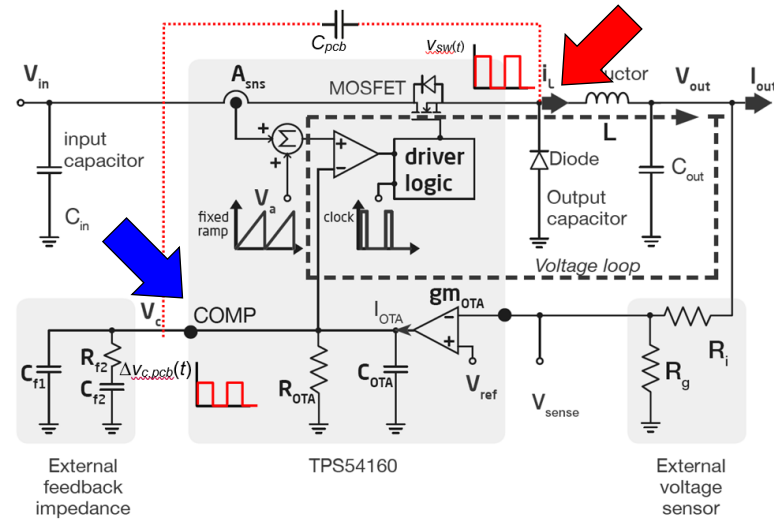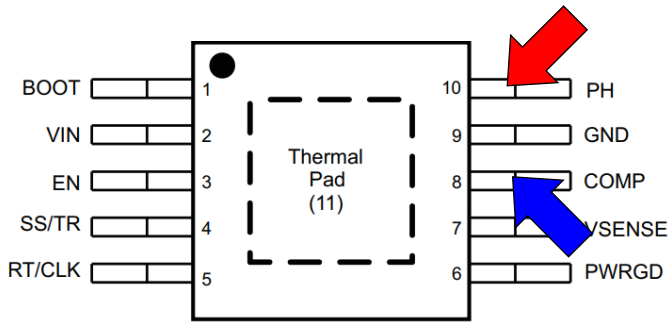
# Crosstalk: TI-PMLK BUCK : SW-to-COMP PCB coupling



## R&S NGL/NGM power supply




2 x R&S RT-ZP05S voltage probe



## R&S RTM3004 oscilloscope



R&S RT-ZC20B current probe

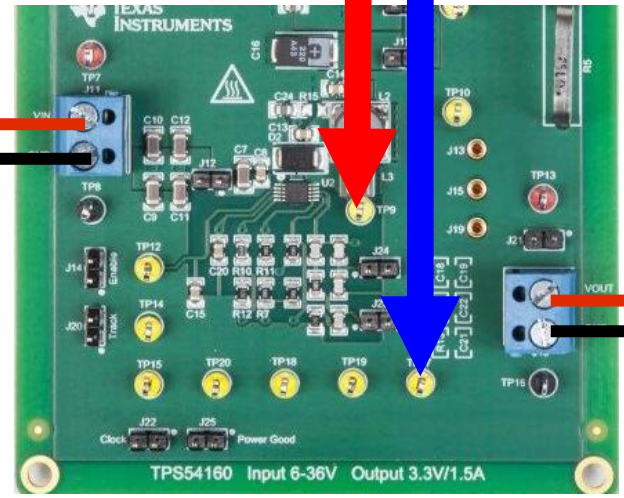


**SW** **COMP**



EA EL 3080-60 B electronic load







# Crosstalk: voltage probe capacitance

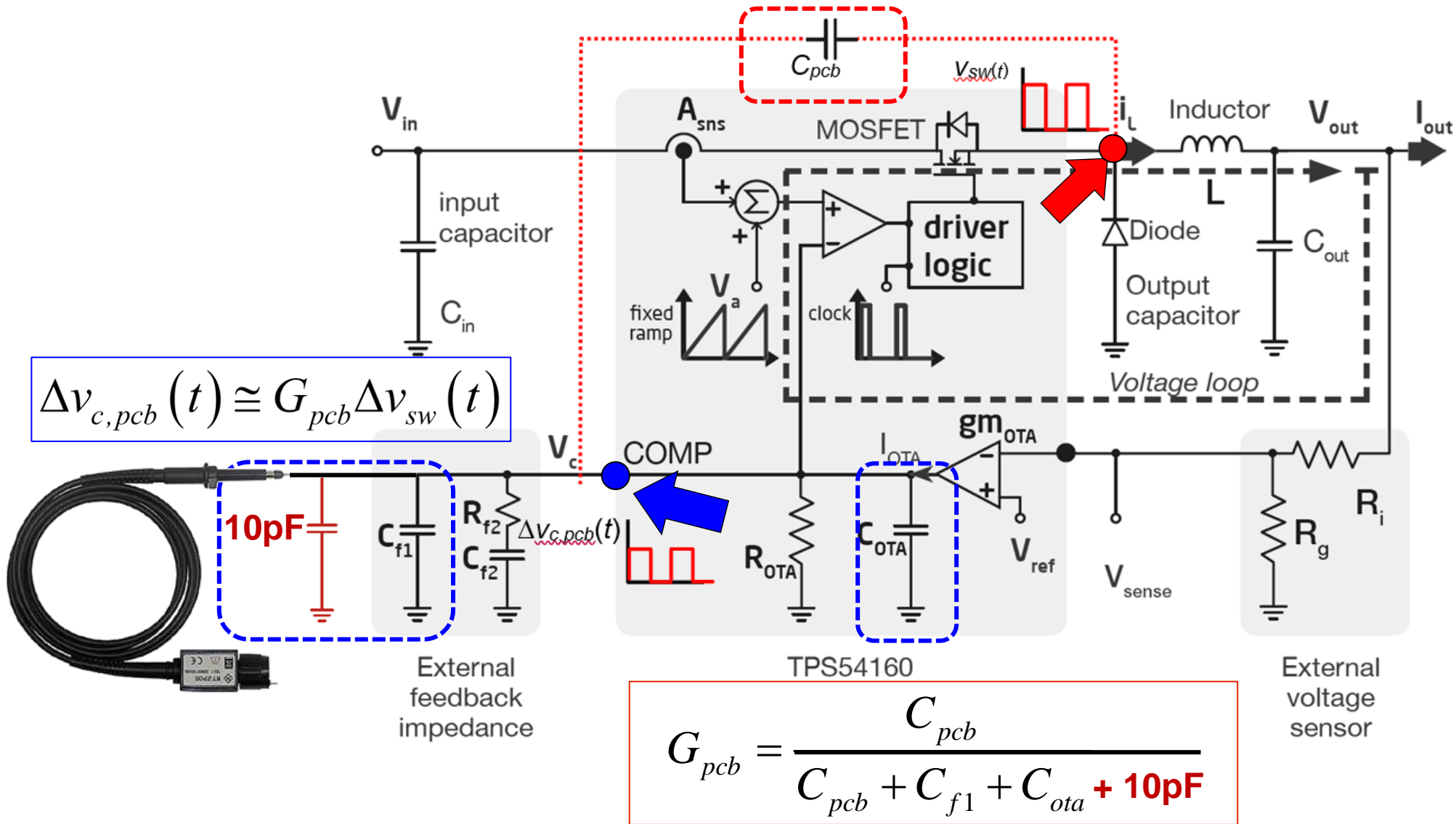

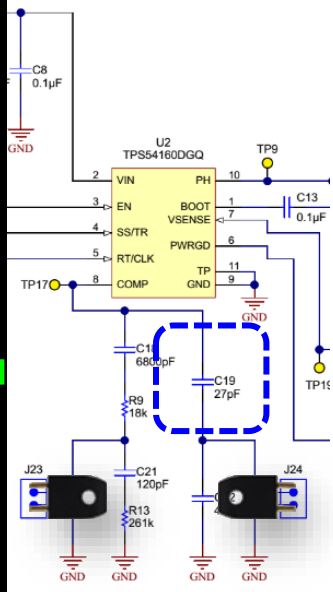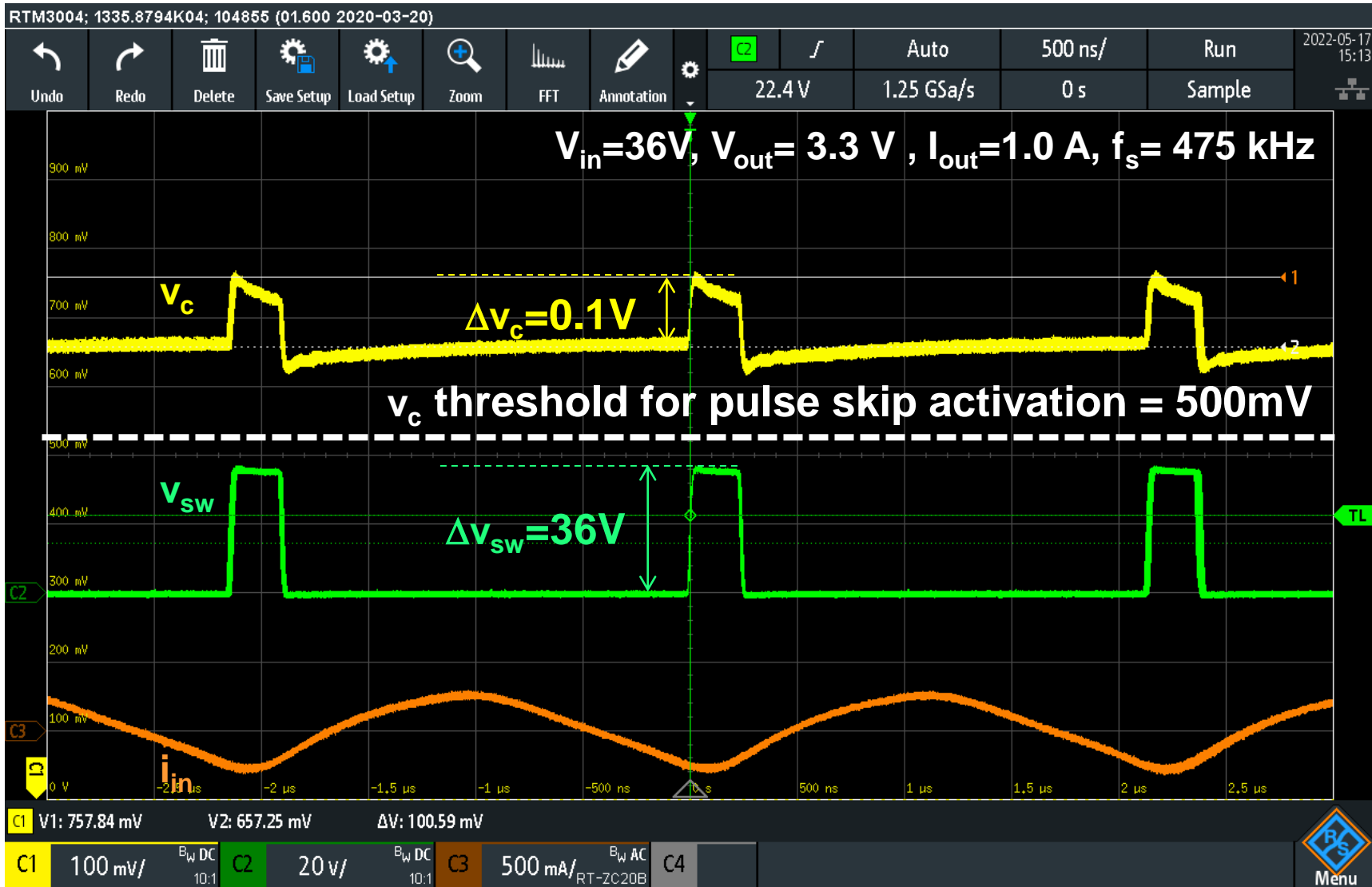


$C_{f1} = 27pF$
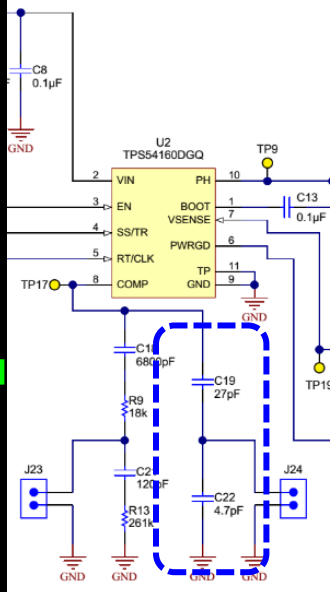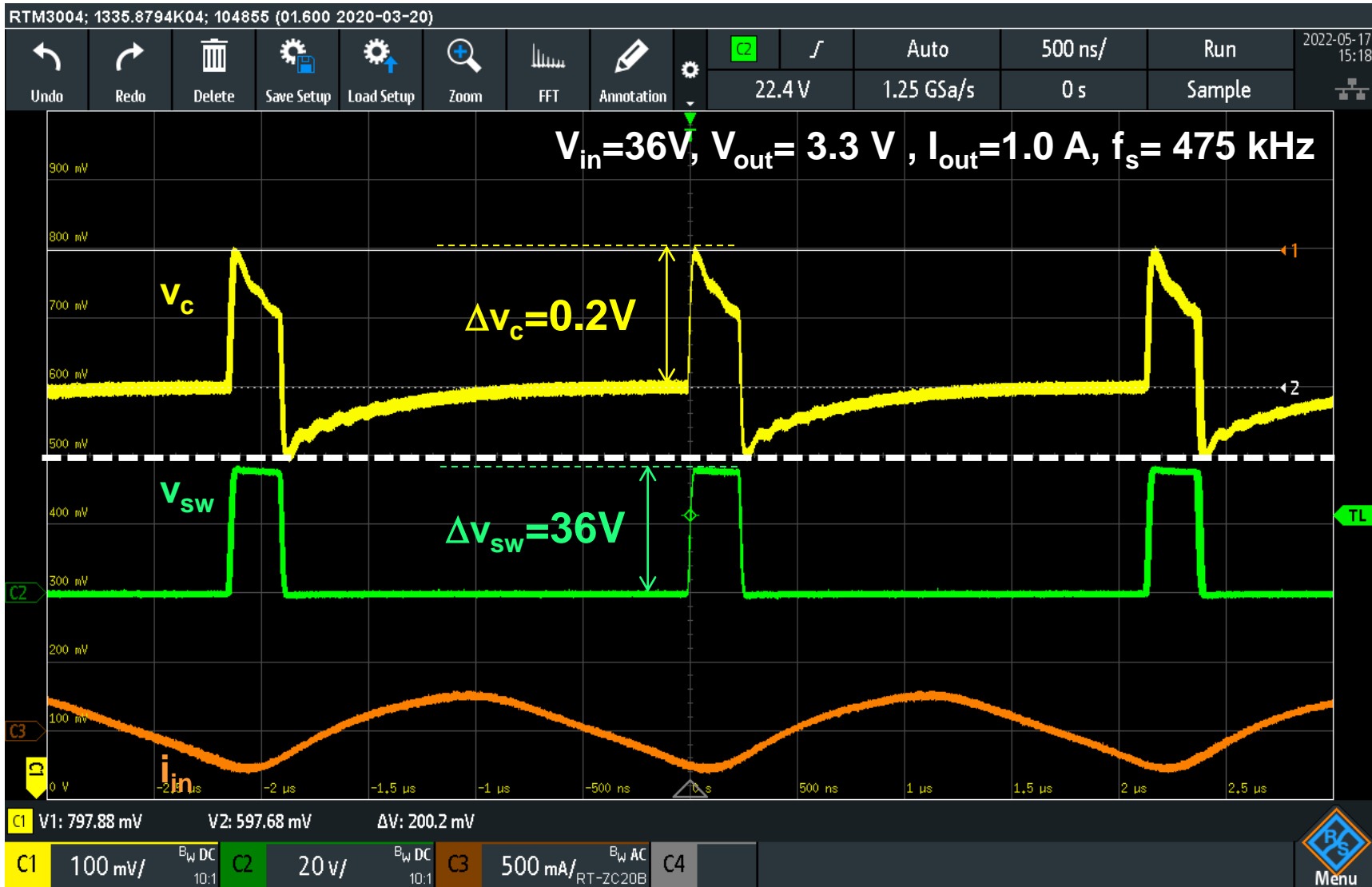
# Crosstalk: SW-to-COMP gain with large BW control




$C_{f1} = 4pF$

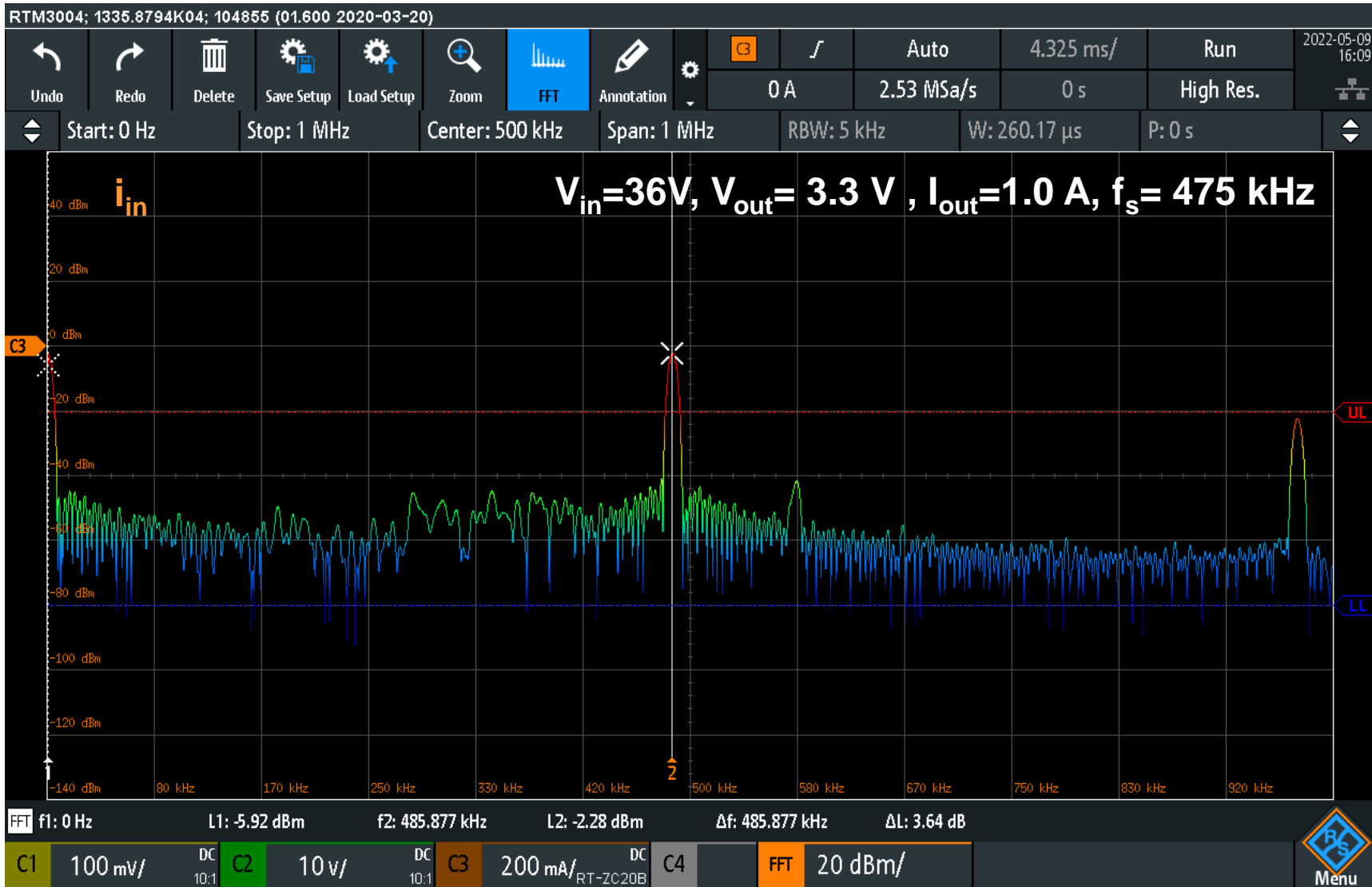
# Crosstalk: input current spectrum with voltage probe



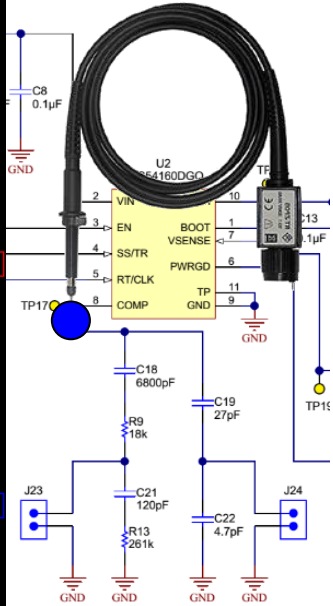
probe on COMP pin  
( $v_c$ )  $\Rightarrow$  +10pF


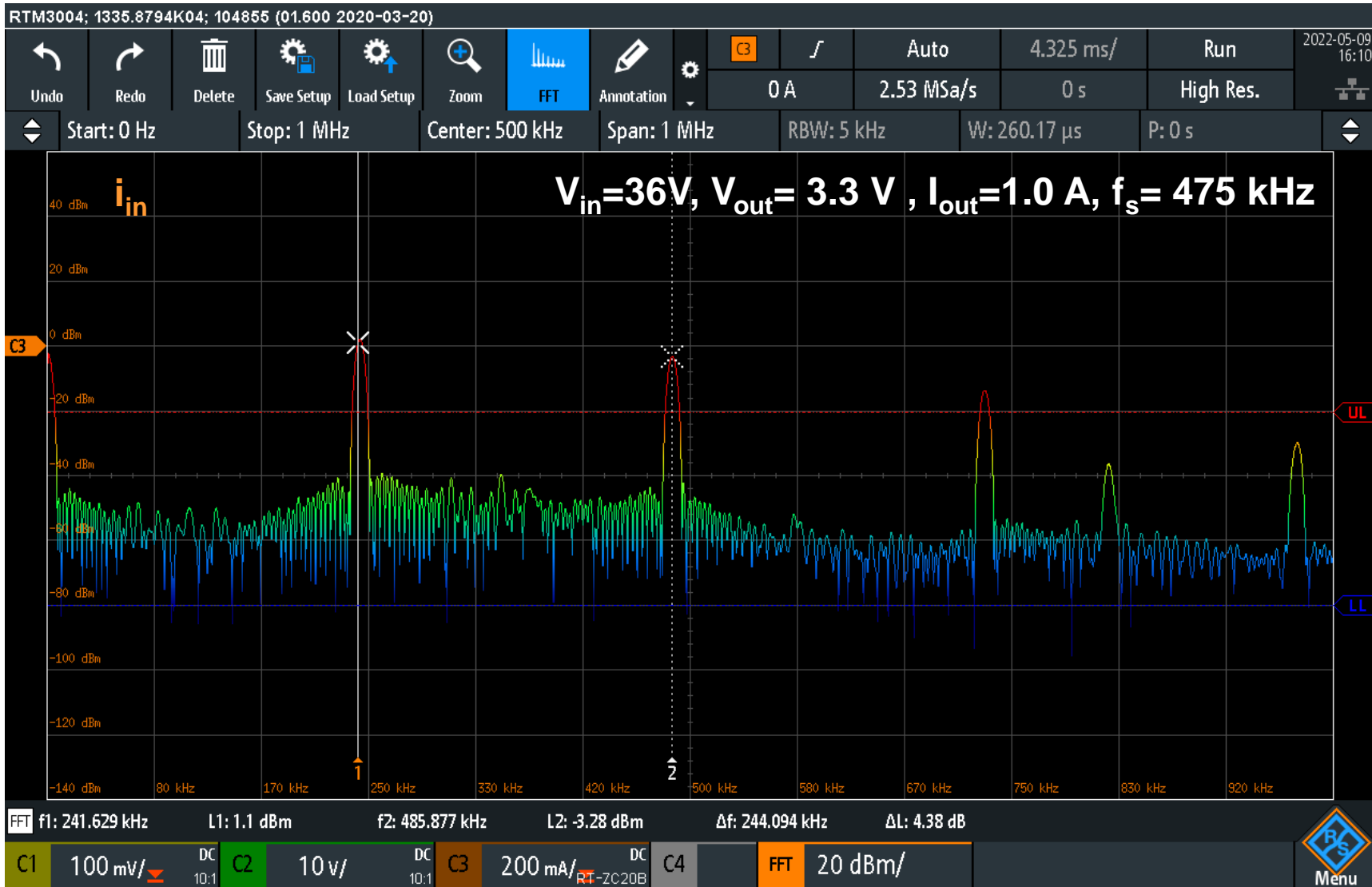
# Crosstalk: input current spectrum without voltage probe



no probe on COMP pin ( $v_c$ )

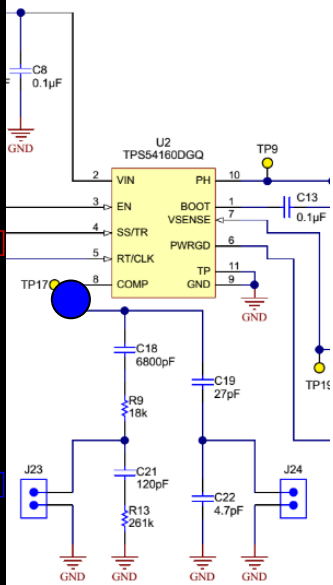

# Crosstalk: pulse-skip effects




**$I_{out}=0.33\text{ A}$**





**$I_{out}=0.28\text{ A}$**




**$I_{out}=0.20\text{ A}$**



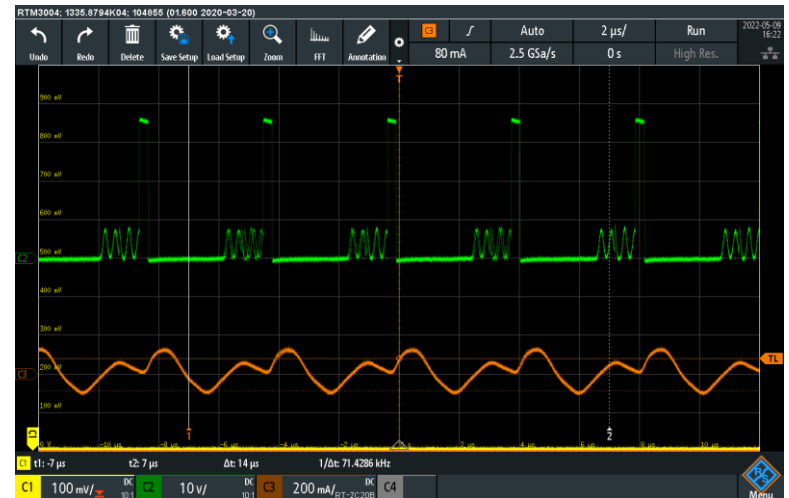


**$I_{out}=0.18\text{ A}$**

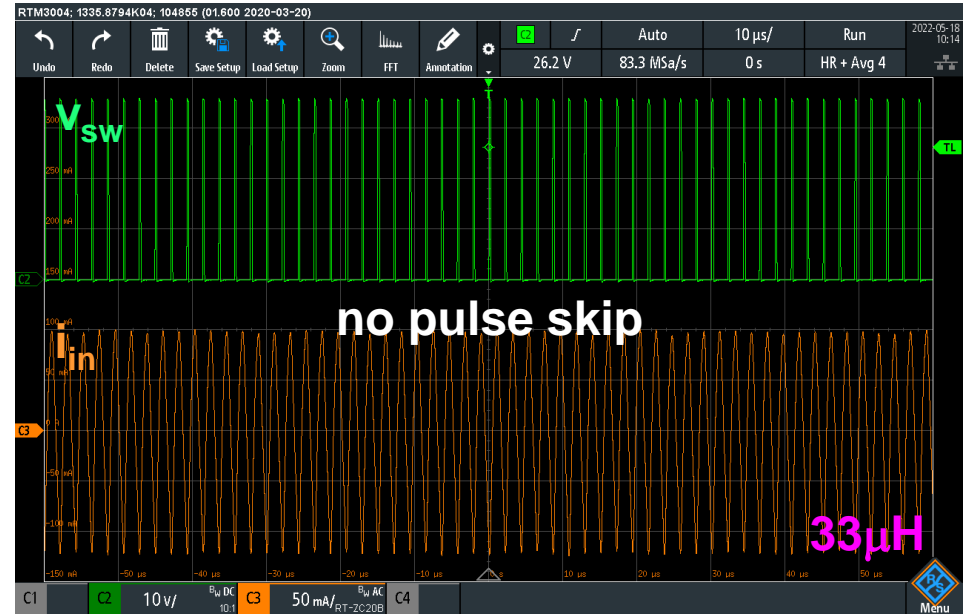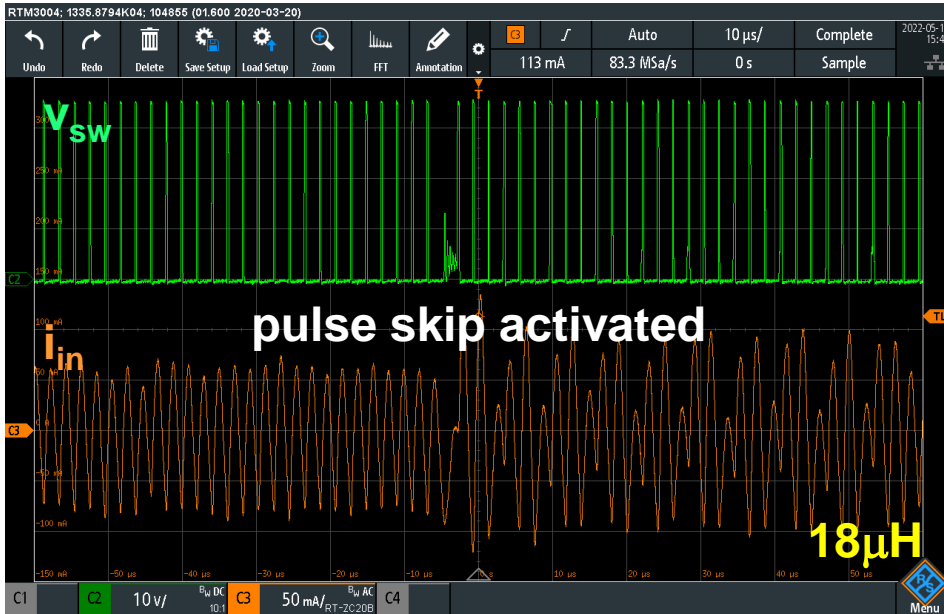

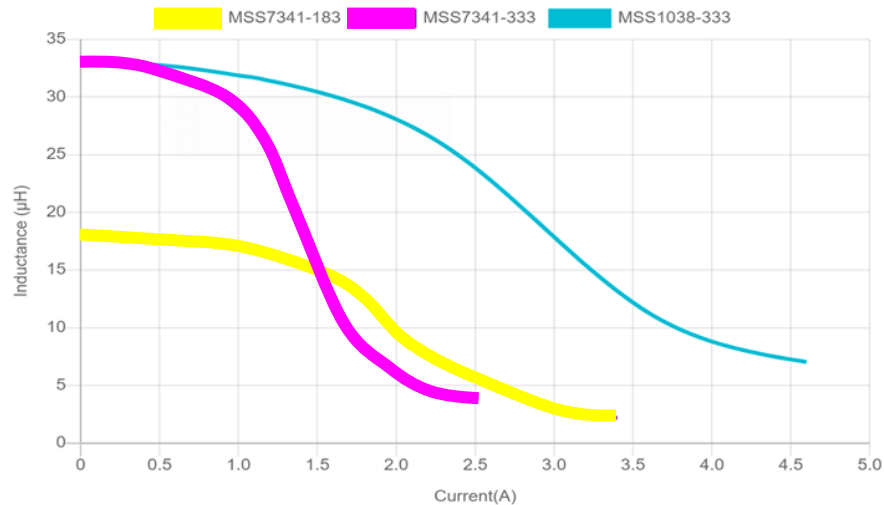**$V_{in} = 36V$**   
 **$V_{out} = 3.3 V$**   
 **$I_{out} = 0.27 A$**   
 **$f_s = 475 kHz$**



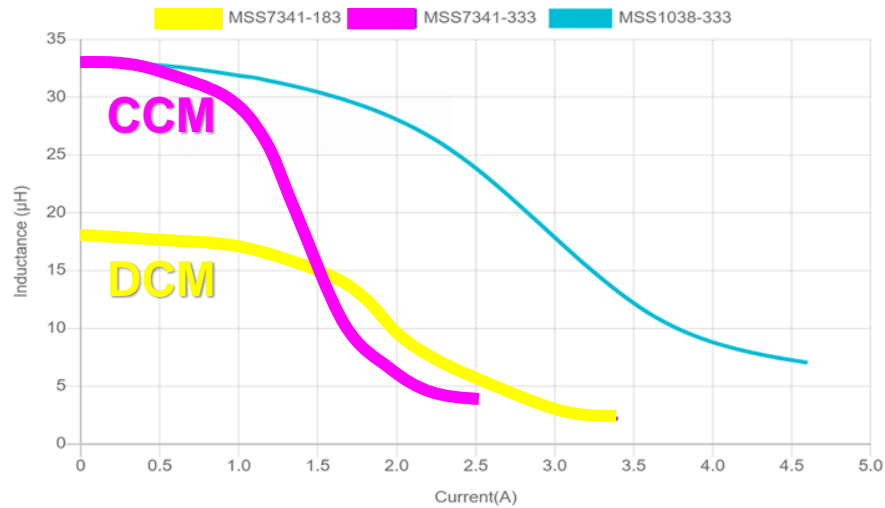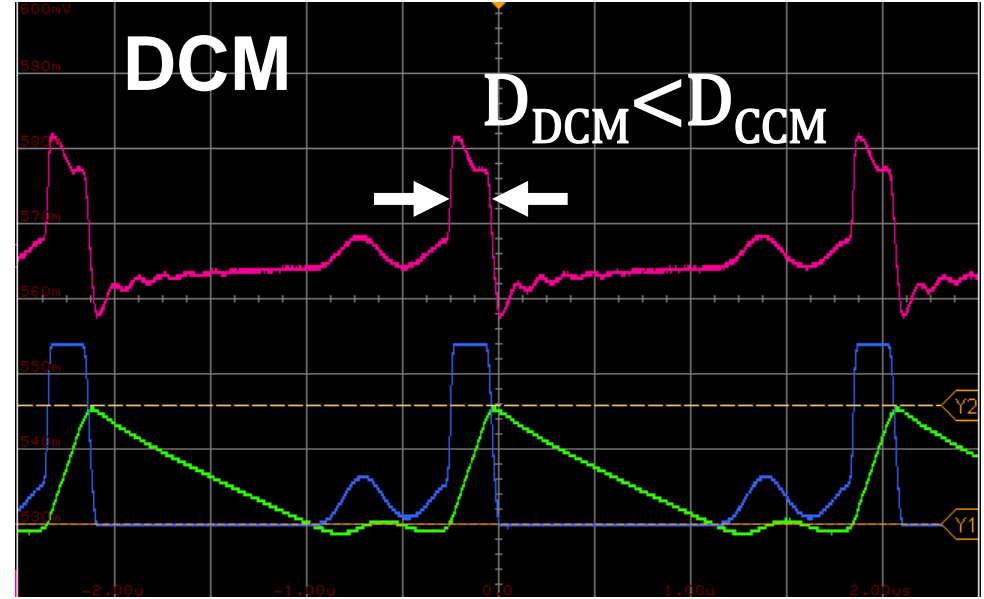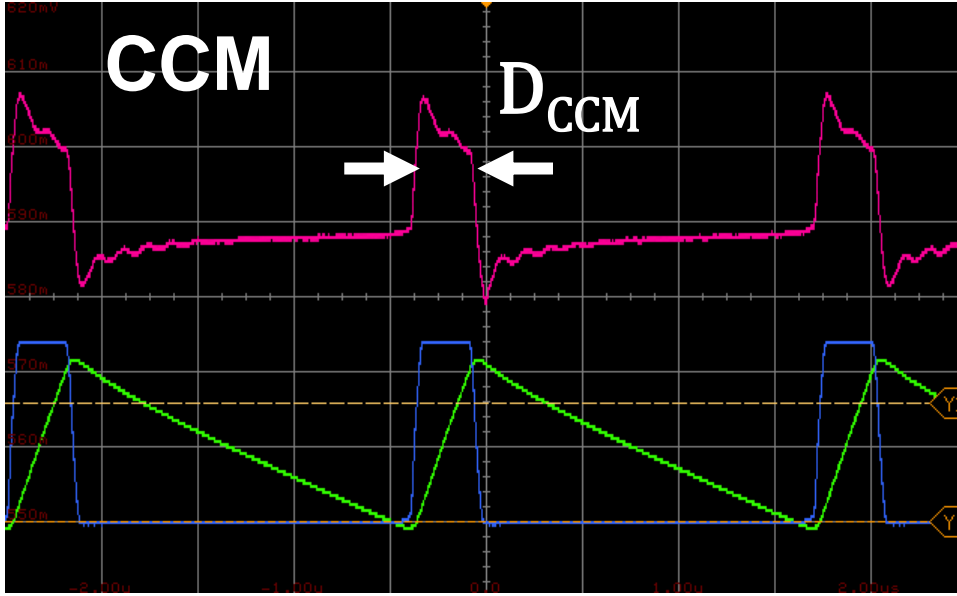

$$v_c = A_s I_o + D \left[ V_{ramp} + \frac{A_s (V_i - V_o)}{2L f_s} \right]$$

$$D_{CCM} = \frac{V_o}{V_i} \quad D_{DCM} = \frac{V_o}{V_i} \sqrt{\frac{2L I_o f_s V_i}{V_o (1 - V_o)}}$$





## INTERNATIONAL JOURNALS

1. K. Stoyka, N. Femia, G. Di Capua, **Power Inductors Behavioral Modeling Revisited**, IEEE Trans. on Circuits and Systems I: Regular Papers, vol. 0, no. 99, pp. 1-14, 2020 (10.1109/TCSI.2020.3002615).
2. **N. Femia, K. Stoyka, G. Di Capua, Impact of Inductors Saturation on Peak-Current Mode Control Operation**, IEEE Trans. on Power Electronics, vol. 0, no. 99, pp. 1-13, 2020 (10.1109/TPEL.2020.2974939).
3. A. Oliveri, G. Di Capua, K. Stoyka, M. Lodi, M. Storace, N. Femia, **A Power-Loss-Dependent Inductance Model for Ferrite-Core Power Inductors in Switch-Mode Power Supplies**, IEEE Trans. on Circuits and Systems I: Regular Papers, vol. 66, no. 6, pp. 2394-2402, June 2019.
4. **K. Stoyka, G. Di Capua, N. Femia, A Novel AC Power Loss Model for Ferrite Power Inductors**, IEEE Trans. on Power Electronics, vol. 34, no. 3, pp. 2680-2692, March 2019.
5. **G. Di Capua, N. Femia, K. Stoyka, Switching Power Supplies with Ferrite Inductors in Sustainable Saturation Operation**, Intern. Journal of Electrical Power and Energy Systems, pp. 494-505, vol. 93, December 2017.
6. G. Di Capua, N. Femia, K. Stoyka, **A generalized numerical method for ferrite inductors analysis in high current ripple operation**, Integration, the VLSI Journal, vol. 58, pp. 473-484, June 2017.
7. **G. Di Capua, N. Femia, A Novel Method to Predict the Real Operation of Ferrite Inductors with Moderate Saturation in Switching Power Supplies Applications**, IEEE Trans. on Power Electronics, vol. 31, no. 3, pp. 2456-2464, March 2016.



## INTERNATIONAL CONFERENCES

1. **G. Di Capua, L. Egiziano, N. Femia, A. Mayhugh, C. Latham, Exploiting the Benefits of Partially Saturating Inductors on Switch-Mode Power Supplies Electro-Magnetic Compatibility and Efficiency, IEEE APEC2022, Houston, TA**
2. K. Stoyka, G. Di Capua and N. Femia, **Coupled Inductors Analysis with Saturation and Thermal Effects**, 2020 27th IEEE International Conference on Electronics, Circuits and Systems (ICECS), Glasgow, UK, 2020, pp. 1-4.
3. **N. Femia, G. Di Capua and K. Stoyka, Saturation and Thermal Stability of Power Inductors, 2020 27th IEEE International Conference on Electronics, Circuits and Systems (ICECS), Glasgow, UK, 2020, pp. 1-4.**
4. K. Stoyka, G. Di Capua, N. Femia, **Normalized inductance modeling for ferrite power inductor families**, 2019 26th IEEE Int. Conference on Electronics, Circuits and Systems (ICECS 2019), Genoa, Italy, 27-29 Nov. 2019.
5. **G. Di Capua, N. Femia K. Stoyka, Impact of Inductors Saturation on DC-DC Switching Regulators, 2019 IEEE 5th Int. forum on Research and Technology for Society and Industry (RTSI 2019), Florence, Italy, 9-12 Sept. 2019.**
6. N. Femia, G. Di Capua, **On Buck-Boost Converter Power Inductor Matching**, 2019 IEEE International Symposium on Circuits and Systems (ISCAS 2019), Sapporo, Japan, 26-29 May 2019.
7. K. Stoyka, G. Di Capua, N. Femia, **Modeling of Stepped Air-Gap Ferrite Inductors in Switching Power Supplies**, IEEE Int. Conf. on Electronics Circuits and Systems (ICECS 2018), Bordeaux, France, 9-12 Dec. 2018.
8. **N. Femia, G. Di Capua, Hysteretic Regulators with Partially-Saturated Inductors, IEEE Int. Conf. on Electronics Circuits and Systems (ICECS 2018), Bordeaux, France, 9-12 Dec. 2018.**
9. G. Di Capua, N. Femia, K. Stoyka, **Loss Behavioral Modeling for Ferrite Inductors**, Int. Conf. on Synthesis, Modeling, Analysis and Simulation Methods and Applications to Circuit Design (SMACD 2018), Prague, Czech Republic, 2-5 July 2018.
10. K. Stoyka, N Femia, G Di Capua, **Optimizing power converters with partially saturated inductors by evolutionary algorithms**, 14th Int. Conf. on Synthesis, Modeling, Analysis and Simulation Methods and Applications to Circuit Design (SMACD 2017), Giardini Naxos, Italy, 12-15 June 2017.

INTERNATIONAL CONFERENCES

11. G Di Capua, N Femia, K. Stoyka, M. Lodi, A. Oliveri, M. Storace, **Ferrite inductor models for switch-mode power supplies analysis and design**, 14th Intern. Conf. on Synthesis, Modeling, Analysis and Simulation Methods and Applications to Circuit Design (SMACD 2017), Giardini Naxos-Taormina, Italy, 12-15 June 2017.
12. **G Di Capua, N Femia, K Stoyka, Validation of inductors sustainable-saturation-operation in switching power supplies design, 2017 IEEE Intern. Conf. on Industrial Technology (ICIT 2017), pp. 242-247, Toronto, Canada, 22-25 March 2017.**
13. G. Di Capua, N. Femia, M. Migliaro, K. Stoyka, **Genetic Programming Approach for Identification of Ferrite Inductors Power Loss Models**, 42nd Annual Conf. of IEEE Industrial Electronics Society (IECON 2016), Florence, Italy, 24-27 October 2016.
14. G. Di Capua, N. Femia, K. Stoyka, **Power Magnetics Volume and Weight Reduction in Aerospace Power Supply Units**, 2016 IEEE 17<sup>th</sup> Workshop on Control and Modeling for Power Electronics (COMPEL 2016), Trondheim, Norway, 27-30 June 2016.
15. G. Di Capua, N. Femia, K. Stoyka, **An Improved Algorithm for the Analysis of Partially Saturated Ferrite Inductors in Switching Power Supplies**, Intern. Conf. on Synthesis, Modeling, Analysis and Simulation Methods and Applications to Circuit Design (SMACD 2016), Lisbon, Portugal, 27-30 June 2016.
16. G. Di Capua, N. Femia, K. Stoyka, **Differential Evolution Algorithm-based Identification of Ferrite Core Inductors Saturation Curves**, 2015 IEEE Intern. Conf. on Industrial Informatics (INDIN 2015), pp. 1636-1641, Cambridge, UK, 22-24 July 2015.
17. K. Stoyka, G. Di Capua, A. Della Cioppa, N. Femia, G. Spagnuolo, **Identification of Ferrite Core Inductors Parameters by Evolutionary Algorithms**, 2015 IEEE Intern. Conf. on Industrial Informatics (INDIN 2015), pp. 1648-1653, Cambridge, UK, 22-24 July 2015.
18. G. Di Capua, N. Femia, **Switching Power Supplies operating with partially Saturated Inductors**, 2015 IEEE Intern. Conf. on Industrial Technology (ICIT 2015), pp. 1205-1210, Seville, Spain, 17-19 March 2015.



- inductors saturation does not yield negative effects on EMI, provided that the inductors are selected based on good practice fundamentals of power-design
- an intelligent power loss distribution in combination with saturating inductors enables reducing SMPS EMI filters size
- (de)saturating inductors help mitigating the noise generated by the combination of control chip special features, large BW feedback compensation and PCB crosstalk



- Power Design Hands-on Courses
  - high power density SMPS design based on semiconductor-to-passive devices optimal tuning
  - high dynamic performance SMPS design based on power-to-control optimal tailoring
  - EMC compliant SMPS design based on power-control-PCB optimal trading
- Low-Cost Inductors Testing Equipment
- Power Design Software