



以**Double Pulse Tester**協助寬能隙半導體於 電源轉換器功率級的設計及驗證

Using Double Pulse Tester to Assist in the Design and Verification of Wide Bandgap-Based Power Stage for Converter/Inverter

臺北科技大學 電機系

黃明熙

2023.11

□ Introduction

□ Key Components

□ DPT in Power Switch Applications

□ DPT in Power Stage Design and Verifications

□ DPT Demo

Traditional applications of the DPT

- ❑ Measure key parameters the power switch
- ❑ Measure voltage stress and loss for the power switch
- ❑ Investigate reverse characteristics for parasitic diode or diode
- ❑ Verify gate driver for the power switch


DPT applications for power stage design

- ❑ Measure stray inductance(s) of the main power flow path
- ❑ Measure the influence of stray inductance(s) on the turn-off voltage spike of power switch
- ❑ Investigate the current sharing phenomena among paralleled power switches
- ❑ Verify the Spice model of the power switch
- ❑ Investigate magnetic flux saturation of the transformer/choke


Power Stage Design for Converter/Inverter

□ Efficiency estimation and thermal design

 Estimate losses of power stage under required driving cycle and output power by Spice model using co-simulation for thermal design



Driving cycle

 

Virtual design

Power Stage Design for Converter/Inverter

□ Key issues and tools for the power stage design

- ✓ Q3D: extract the parasitic parameters
- ✓ Spice model: characteristics analysis of power switch
- ✓ Twin Builder/circuit simulation S/W: operation of the power stage (stress/current sharing) and losses estimation for thermal design
- ✓ Double pulse test: verify the simulation results

Simulation Tools
Verification

Power switch

- *stress analysis
- *characteristics of steady/transient state
- *losses

DC link capacitor

- *impedance vs. frequency
- *estimate losses

Thermal design


- *losses estimation
- *cooling methodologies

Busbar design

- *stray inductance
- *current sharing among capacitors

Power connection bar

- *current density distribution
- *loss


 


EMI/SI(Signal integrity)?


Paralleled operation of power switches
current sharing at steady and transient state

Fundamental of the DPT



□ Equivalent circuit and test pattern

  



Double Pulse Tester – Function Block

 

DPT Test Items

  

DPT Test Items

  

Double Pulse Tester Equipment

□ Dynamic power device analyzer/double pulse tester



Static

Output characteristics On-resistance Threshold voltage Transconductance
Junction, input, output and reverse transfer capacitance Breakdown voltage Gate charge

Dynamic

Turn-on characteristics Turn-off characteristics Dynamic on-resistance
Dynamic current and voltage Switching characteristics
Reverse recovery Gate charge Derived output characteristics

Ruggedness testing(at high voltages and high temperatures)

Short-circuit conduction time Short-circuit energy Avalanche energy

DPT Parameters

Group	Parameters	Description	Associated Standards
Turn-On Characteristics	$t_{d(on)}$, t_r , t_{on} , $e_{(on)}$, dv/dt , di/dt	Characterizes how quickly the transistor can turn on, the maximum di/dt and dv/dt , and the resulting energy loss. Contributes to switching loss characteristic.	FET – IEC 60747-9 IGBT - 60747-8
Turn-Off Characteristics	$t_{d(off)}$, t_r , t_{off} , $e_{(off)}$, dv/dt , di/dt	Characterizes how quickly the transistor can turn off, the maximum di/dt and dv/dt , and the resulting energy loss. Contributes to switching loss characteristic.	FET – IEC 60747-9 IGBT - 60747-8
Switching Characteristics	I_d vs. t , V_{ds} vs. t , V_{gs} vs. t , I_g vs. t , Clamped V_{ds} vs. t , e vs. t , I_d vs V_{ds} (switching locus)	These time-based parameters are waveforms retrieved directly from the oscilloscope. The I_d vs V_{ds} (switching locus) are derived from the waveforms.	
Reverse Recovery	t_{rr} , Q_{rr} , E_{rr} , I_{rr} , I_d vs. t	Characterization of reverse recovery of body diode in vertical FETs. Provides additional timing information regarding how quickly the transistor can switch between on and off.	IEC 60747-8
Gate Charge	V_g vs. Q_g , ($Q_{gs(th)}$, $Q_{gs(pl)}$, Q_{gd})	The voltage and the current of the gate are measured during a double pulse turn-on operation. The charge on the gate during different gate voltage transitions is characterized. This parameter is used to determine the driving loss of the transistor.	IEC 60747-8 IEC 60474-9
Derived Output Characteristics	I_d vs. V_g , I_d vs. V_d	Provides basic transfer characteristics for the semiconductor.	

Double Pulse Tester (Board Level)

□ Littelfuse

Electrical Specifications			
Parameter	Typical Value	Maximum Rating	Units
Input DC Link Voltage	800	1000	V
Input Control Voltage	12	13.2	V
Output Peak Current	-	100	A
Ambient Temperature	-	55	°C
Gate Driving Voltage	+20/-5	+22/-6	V




Source: Dynamic Characterization Platform-littelfuse

□ Cree



Source: Evaluation Board for Cree's SiC MOSFET in a TO-247-4 Package

□ VPEC


 


Source: High Temperature Characterization and Analysis of Silicon Carbide (SiC) Power Semiconductor Transistors

- Introduction
- **Key Components**
- DPT in Power Switch Applications
- DPT in Power Stage Design and Verifications
- DPT Demo

Double Pulse Tester – Sensors

□ Short ground pin/probe tip adapter

  


Source: Dynamic Characterization Platform-littelfuse

□ Fast response current sensor

	Current shunt resistor	Current transformer	Rogoski coil current probe
Pros	<ul style="list-style-type: none"> Best accuracy High bandwidth 	<ul style="list-style-type: none"> Isolated output 	<ul style="list-style-type: none"> Minimum insertion inductance Isolated output Smallest size
Cons	<ul style="list-style-type: none"> Large size Added loop inductance 	<ul style="list-style-type: none"> Large size Added loop inductance Lower bandwidth 	<ul style="list-style-type: none"> Low bandwidth Not suitable for switching energy measurement
Best Use	<ul style="list-style-type: none"> Eon/Eoff measurement 	<ul style="list-style-type: none"> Application where high bandwidth is not required 	<ul style="list-style-type: none"> High current measurement. e.g. Double pulse test
Equipment	T&M research co-axial current shunt <ul style="list-style-type: none"> SDN-414-10 (0.1Ω, 2GHz bandwidth) SSDN series for low insertion inductance 	Pearson 2877 current monitor <ul style="list-style-type: none"> 1V/A output 200MHz/100A 	PEM CWT Ultra Mini <ul style="list-style-type: none"> 9.2Hz-30MHz, 300A 

current sensor

Probe tip adapter for measuring voltage

 

Source: High Frequency Performance Delay, Rise-time and Peak di/dt

Double Pulse Tester – Current Sensor


□ Current sensor – coaxial resistor

BW=1200MHz, rising time $\leq 0.3\text{ns}$, w/o delay and limited thermal capacity

SDN - 414 Series

SDN-414- 2 Watt Units - 1 5/8 Inch Case

Model	Resistance ohms	Bandpass MHz.	Risetime nsec.	Emax joules
SDN-414-01	0,01	400	1	6
SDN-414-025	0,025	1200	0,3	3
SDN-414-05	0,05	2000	0,18	2
SDN-414-10	0,1	2000	0,18	1

 

ORDERING INFORMATION

When ordering specify model number, wattage, and tolerance. Example: SDN-414-10, 2 watts, 4%.

Please specify type of load terminals: standard wire=SDN - flat low impedance strips = TTSDN


Source: Investigation of the inductor's parasitic capacitance in the high frequency switching of the high voltage cascode GaN HEMT





	Bandwidth	Saturation	Linearity	Material Technology
Rogowski	0.1 ~ 100MHz	No	Very good	simple
CT	0.1Hz ~ 100MHz	Yes	Fair	simple
Hall	< 1MHz	Yes	Poor	complicated
GMR	DC ~ 5MHz	Yes	Fair	Very complicated
GMI	DC ~ 30GHz	No	Fair	Very complicated
Shunt	DC ~ 10MHz	No	Very good	simple
Coaxial Shunt	DC ~ 2GHz	No	Very good	simple

Double Pulse Tester – Current Sensor

 □ Calibration of the Rogowski probe by high BW coaxial shunt resistor and higher current.



  The distorted amplitude is still existed after de-skew, which will cause less accuracy in transient measured results.



Double Pulse Tester – Current Sensor

□ Calibration of the Rogowski probe by high BW coaxial shunt resistor



Specification	
Vdc	48V
Inductor	5.4 μ H
MOSFET	IPP041N41N3(120V 120A)



Part. No	Manufacturer	PEAK		Insulation voltage (kV)	BW -3dB(MHz)
		Current (kA)	di/dt (kA/us)		
CP9012S	Cybertek	0.12	8	1	30



  The de-skew time in both rising and falling time are near the same!



Double Pulse Tester – Voltage Probe

□ Measurement equipment – high voltage probe

GaN probe




P2000A GaN Probe	
Characteristic	Rating
System Bandwidth	700 MHz (-3 dB) typical
Attenuation Ratio (1)	100:1 ± 2 % at DC Connected to oscilloscope with an input impedance of 1 MΩ ± 1 %.
Absolute Maximum Voltage	< 1000V _{RMS}
Voltage Coefficient	0.00025 %/V %/V (typical)
Probe Rise Time	500 psec (10 % - 90 %) (typical)
Maximum Rated Input Voltage (2)	As defined in IEC 61010-031. Also see definitions in User Manual.
Measurement category I:	1000 V _{RMS} 4000 V transient overvoltage
Measurement category II:	1000 V _{RMS} CAT II
Input Resistance (System)	50 MΩ ± 1 %
Input Capacitance (System)	7 pF (typical)
Compensation Range	10 pF - 50 pF (typical)
Input Coupling of the Measuring Instrument	1 MΩ AC / DC
Weight (probe)	82g
Cable Length	1m
Probe Tip Diameter	5mm

item	SS-0170R	SS-0171R
Input enduring voltage	CATII6,000V(DC+AC peak)	CATII4,000V(DC+AC peak)
*Derating curve reference	CATII1,000V (DC+AC peak)	CATII1,000V (DC+AC peak)
Frequency bandwidth	DC to 400 MHz(±2 dB)	*Derating curve reference
Attenuation ratio	100:1±3.0 % 以内	



Voltage vs. frequency de-rating curve

 


Ref. https://www.iti.iwatsu.co.jp/en/products/accessories/Voltage_probe5_e.html

Double Pulse Tester - Inductor

□ Inductor – without magnetic core to provide linear characteristic




$$L = \frac{V_{dc}}{i_{max}} \Delta t$$

 

- Introduction
- Key Components
- DPT in Power Switch Applications**
- DPT in Power Stage Design and Verifications
- DPT Demo

Double Pulse Tester – Test Platform

Parameter	Specification
DC link voltage	300V
Inductor	70uH
Maximal current	40A
Gate driver UCC21520	Dual channels/ 4A source /6A sink
DUT	H1M065F050 and IKW75N60T

 

Compare Different Power Switches

□ DUT- key parameters of the SiC MOSFET and IGBT

SiC MOSFET

Parameter	Symbol	Test Conditions	Min.	Typ.	Max.	Unit
Turn On Delay Time	$t_{d(on)}$	$V_{DS}=400V, V_{GS}=-4/+20V,$ $I_D=20A, R_L=20\Omega,$ $R_{G(ext)}=2.7\Omega$		16		ns
Rise Time	t_r			17		
Turn Off Delay Time	$t_{d(off)}$			20		
Fall Time	t_f			10		
C_{oss} Stored Energy	E_{oss}	$V_{GS}=0V, V_{DS}=400V$ $f=1MHz, V_{AC}=25mV$		24		μJ
Turn-on Switching Energy	E_{on}	$V_{DS}=400V, V_{GS}=0/20V,$ $I_D=20A,$ $R_{G(ext)}=2.7\Omega$		21*		
Turn-off Switching Energy	E_{off}			28*		
Internal Gate Resistance	$R_{G(int.)}$	$f=1MHz, V_{AC}=25mV$		1.2		Ω

*Based on the results of calculation, note that the energy loss caused by the reverse recovery of free-wheeling diode is not included in E_{on} .


Parameter	Symbol	Test Conditions	Typ.	Unit
Inverse Diode Forward Voltage	V_{SD}	$V_{GS}=0V, I_{SD}=5A$	3.0	V
Continuous Diode Forward Current	I_S	$V_{GS}=-5V, T_C=25^\circ C$	36	A
Reverse Recovery Time	t_{rr}	$V_{GS}=0V,$	58	ns
Reverse Recovery Charge	Q_{rr}	$I_{SD}=30A, V_{DS}=400V,$	122	nC
Peak Reverse Recovery Current	I_{rrm}	$di/dt=300A/\mu s$	3.75	A

IGBT

Parameter	Symbol	Conditions	Value			Unit
			min.	typ.	max.	
IGBT Characteristic						
Turn-on delay time	$t_{d(on)}$	$T_J=25^\circ C,$ $V_{CC}=400V, I_C=75A,$ $V_{GE}=0/15V,$ $r_G=5\Omega, L_\sigma=100nH,$ $C_\sigma=39pF$	-	33	-	ns
Rise time	t_r		-	36	-	
Turn-off delay time	$t_{d(off)}$		-	330	-	
Fall time	t_f		-	35	-	
Turn-on energy	E_{on}	L_σ, C_σ from Fig. E Energy losses include "tail" and diode reverse recovery.	-	2.0	-	mJ
Turn-off energy	E_{off}		-	2.5	-	
Total switching energy	E_{ts}		-	4.5	-	
Anti-Parallel Diode Characteristic						
Diode reverse recovery time	t_{rr}	$T_J=25^\circ C,$ $V_R=400V, I_F=75A,$ $di_F/dt=1460A/\mu s$	-	121	-	ns
Diode reverse recovery charge	Q_{rr}		-	2.4	-	
Diode peak reverse recovery current	I_{rrm}		-	38.5	-	
Diode peak rate of fall of reverse recovery current during t_b	di_{rr}/dt		-	921	-	

Compare Different Power Switches


 
□ Switching loss comparison ($V_{dc}=300V$, $R_g=5\Omega$)



Switching loss of the SiC MOSFET and IGBT are 253.2 μ J and 1597.0 μ J, respectively.


Miller Effect

  □ Larger current spike at turn-on transient



Miller Effect

 
□ Miller effect at turn on transient (**Q2 OFF ->ON** and **Q1 OFF**)



- Introduction
- Key Components
- DPT in Power Switch Applications
- DPT in Power Stage Design and Verifications**
- DPT Demo


The Influence of Stray Inductance on Power Stage Design

 - Stray inductance may exist in power traces of PCB, leads of power switches (module), capacitor
- The stray inductance may induce voltage stress at turn-off transient, EMI, and imbalanced current sharing among paralleled power switches.




The Influence of Stray Inductance on Power Stage Design

 □ Extract and reduce stray inductance of main power flow path by Ansys Q3D in PCB design stage and use DPT to verify the design.



 
Minimize the stray inductance by Q3D to reduce turn-off voltage spike



Verify PCB Design

□ Stray inductance measurement by impedance analyzer (WK 6500B)

 
Valid method only for specified PCB shape



	1MHz	10MHz
Calculated inductance by Q3D(nH)	5.17	4.21
Measured inductance by WK 6500B(nH)	4.18	3.67
Error	23.68%	14.71%




The measured error may be induced by the WK 6500B.

Measured accuracy (WK 6500B)

 





Verify PCB Design

Three level LLC with SiC MOSFET (TO 247)

  
 


Verify PCB Design

Three level LLC with SiC MOSFET (TO 247)

    






Three level LLC with SiC MOSFET (TO 247)

  

	L_P	L_{O1}	L_{O2}	L_N
Q3D	11.1nH	22.4nH	18nH	8.9nH
DPT	10.2nH	20.4nH	16.6nH	9.5nH
Error	7.8%	8.9%	7.6%	6.7%

Investigate the Effect of MLCC in GaN-Based Power Stage

□ Power PCB layout

     

Initial design


Modified design

	Stray inductance (@30MHz)
Initial design	6.38nH
Modified design	1.34nH


Investigate the Effect of MLCC in GaN-Based Power Stage

□ Turn-off transient spike voltage measurement

Initial design

 



Modified design

 

Current Sharing Among Paralleled IGBTs

Power stack design with three paralleled IGBTs

  - ✓ DC link voltage: 1000V
- ✓ Maximum current: 7200A/phase, 2400A/IGBT module




Simulation-Assisted Design of a Power Stack for Improving Static Current Sharing Among Three IGBT Modules Connected in Parallel

ZHENG-FENG LI¹, (Student Member, IEEE), NOBUYA NISHIDA², HIROTOSHI AOKI³, HISASHI SHIBATA³, CHIH-CHIA LIAO¹, AND MING-SHI HUANG¹, (Member, IEEE)
¹Department of Electrical Engineering, National Taipei University of Technology, Taipei 106, Taiwan
²Mitsubishi Electric Corporation, Fikoko 810-8686, Japan
³TAMURA Corporation, Saitama 350-0214, Japan
 Corresponding author: Zheng-Feng Li (r94102@gmail.com)

Current Sharing Among Paralleled IGBTs

 
□ The influence factors of balanced current sharing



Internal circulation

To load

Influence factors	Dynamic	Static
Characteristic of power module	○	○
Gate driver	○	○
DC link busbar	○	○
Phase output bar (POB)	×	○

 

Improving static current sharing


Parameter extraction of IGBT module

Design POB, DC link busbar



Current Sharing Among Paralleled IGBTs

□ Stray inductance distribution

■ Initial design

 



■ Proposed design

  

MRID: The maximum ratio of inductance difference


$$MRID(\%) = \frac{|L_{POBC,1} - L_{POBC,2}|}{L_{POBC(Avg.)}} \times 100$$
  
$$L_{POBC(Avg.)} = \frac{\sum_{k=1}^3 L_{POBC,k}}{3}$$





Current Sharing Among Paralleled IGBTs

□ Test Setup


 


Inductance of the copper nut

  

Current Sharing Among Paralleled IGBTs

Co-simulation and measured results

  

- Introduction
- Key Components
- DPT in Power Switch Applications
- DPT in Power Stage Design and Verifications
- **DPT Demo**

Q and A