

4-SWITCH BUCK-BOOST CONVERTER VERIFICATION IN BATTERY APPLICATIONS

ROHDE & SCHWARZ

Make ideas real


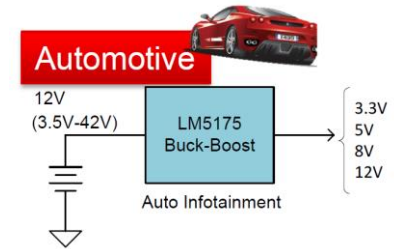


TABLE OF CONTENT


- ▶ Introduction - Applications And Key Requirements
- ▶ Evolution of Buck-Boost Converter
- ▶ Variants of Non-Inverting Step-Up/Step-Down Converter
- ▶ Operating Modes of 4-Switch Buck-Boost Converter
- ▶ Device Under Test - Verification and Measurements
- ▶ System Verification
- ▶ Conclusion

APPLICATIONS

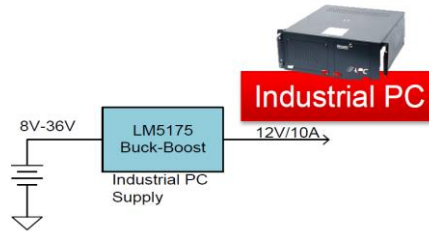- ▶ Automotive Battery Stabilization (Voltage Dips Due To Heavy Loads)
- ▶ Industrial Computers




- ▶ USB Power Delivery

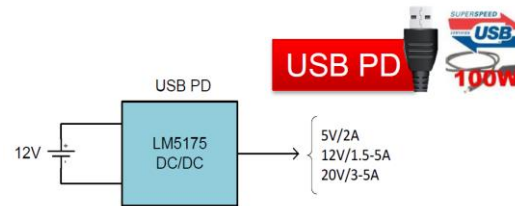

- ▶ Variable Supplies For Amplifier
- ▶ Local Energy Storage Systems (Bidirectional) E.g. USB Power Bank

KEY CHARACTERISTICS OF POWER CONVERTER IN BATTERY POWERED APPLICATIONS


- ▶ Input Voltage Variation In All Battery Supplied Application Exists
 - Step-Up/Step-Down Function Is Required (A Simple Buck or Boost Is Not Suitable)
 - In Some Applications, The Output Voltage Need To Be Programmable
- ▶ In Most Applications, Output Should Provide A Positive Voltage With Respect To Ground
- ▶ Some Applications Require Power Conversion Bidirectionally
- ▶ High Efficiency >95% And Power Levels Up To 250W
- ▶ Non-Isolated System
- ▶ Digital Control

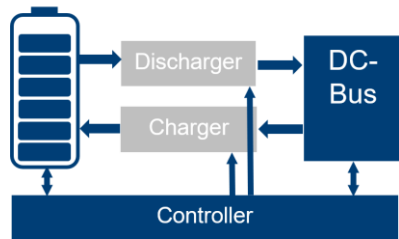

SINGLE SWITCH BUCK-BOOST CONVERTER

- ▶ The Magnitude of Output is Higher when Duty Cycle > 0.5
- ▶ The Magnitude of Output is Lower when Duty Cycle < 0.5
- ▶ Single Switch Topology Provides Negative Output Voltage


$$M = -\frac{D}{1-D}$$

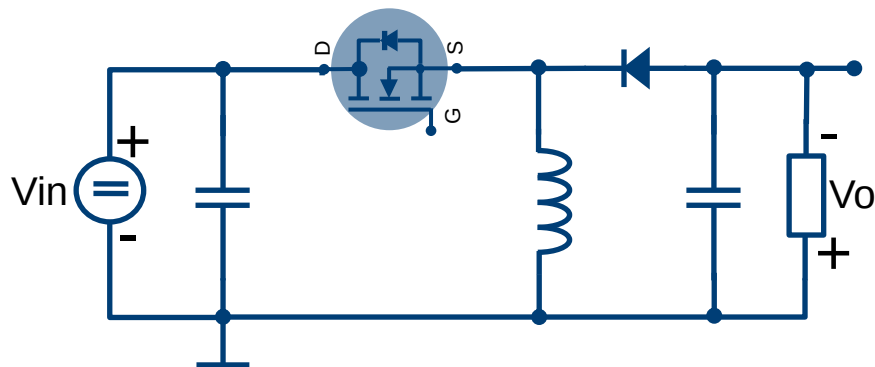


2-SWITCH BUCK-BOOST CONVERTER

- ▶ The Magnitude of Output is Higher when $D > 0.5$
- ▶ The Magnitude of Output is Lower when $D < 0.5$
- ▶ Non-Inverting Buck-Boost Solution
- ▶ Bidirectional Power Flow Is Not Possible

$$M = \frac{D}{1-D}$$

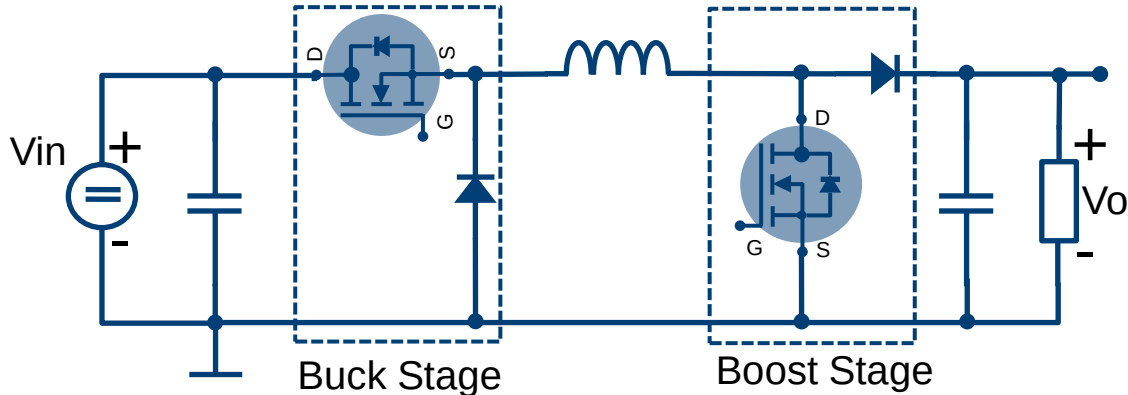


4-SWITCH BUCK-BOOST DERIVATION

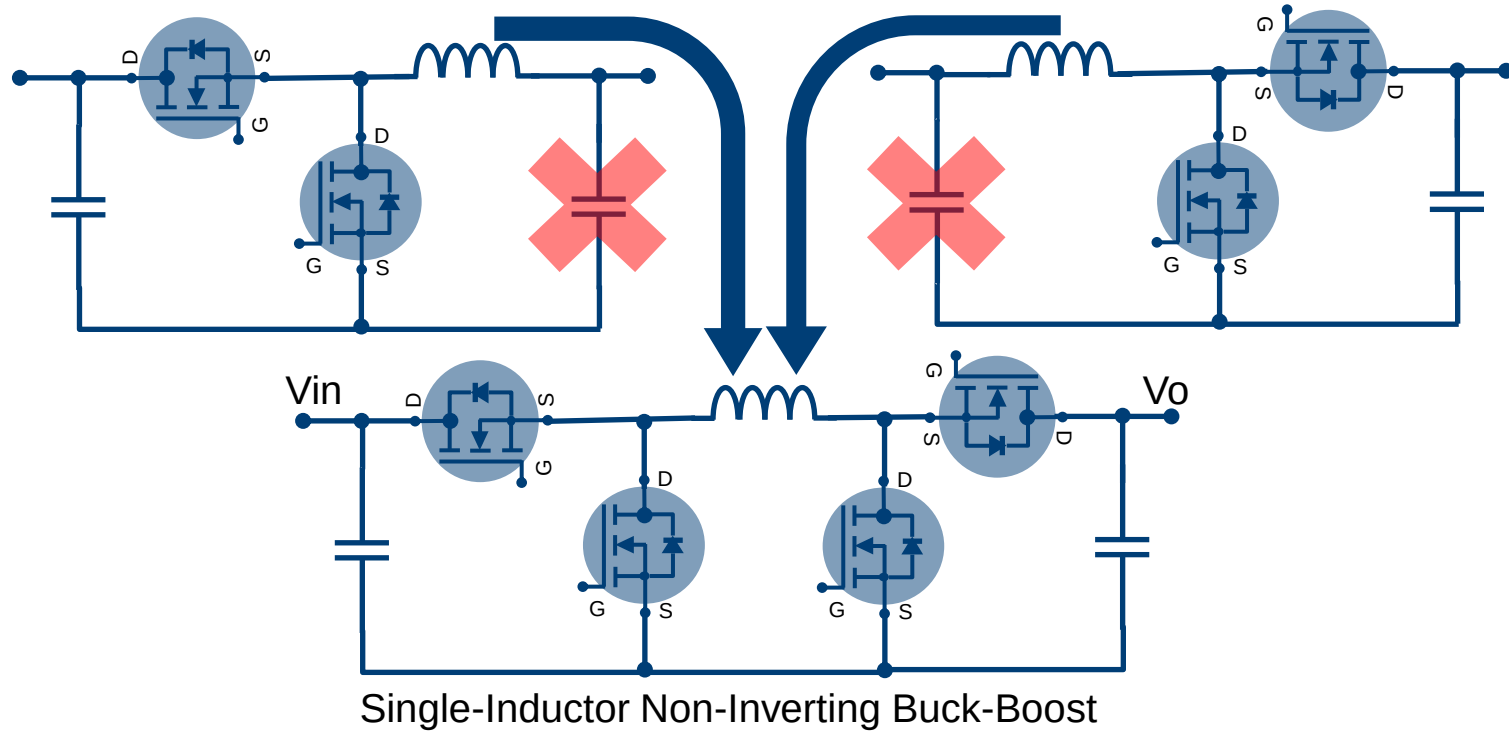

CASCADED BOOST AND BUCK CONVERTER

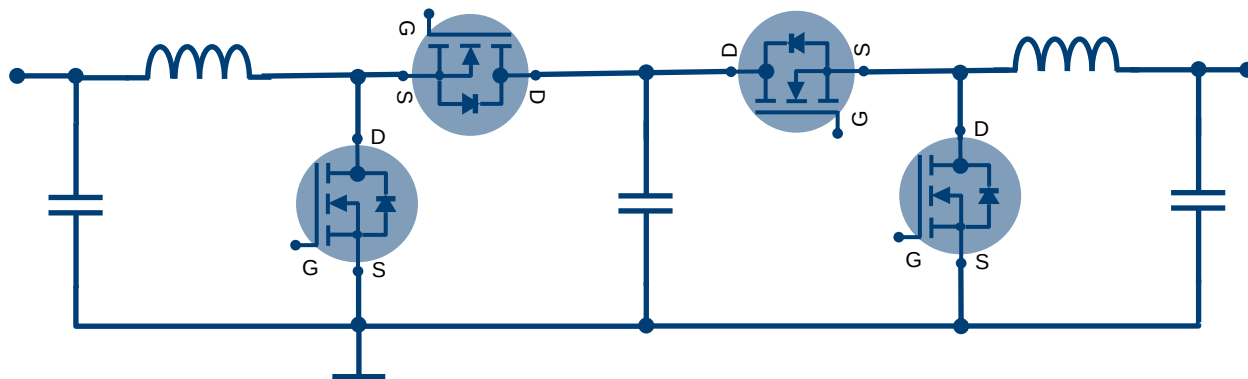
- ▶ Two Independent Controllers
- ▶ Two Inductors
- ▶ Bad Efficiency



SEPIC AND FLYBACK CONVERTER


SEPIC (Single Ended Primary Inductance Converter)

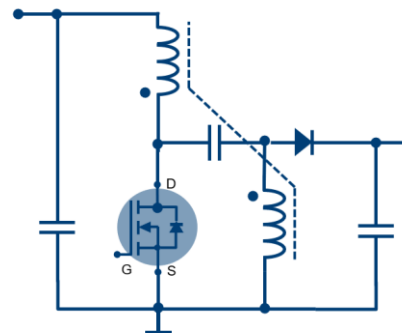- ▶ 2 Inductors
- ▶ Coupling AC-Capacitor



Flyback

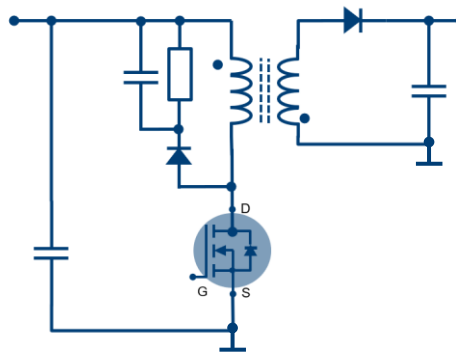- ▶ Coupled Inductors
- ▶ High Break Down Voltage





STEP-UP/DOWN TOPOLOGY COMPARISON

Topology	Strengths	Weaknesses	Power Level	Efficiency
Cascaded Boost-Buck	Low Input & Output Noise	Two Inductors Two Controllers	< 40W	85%
Sepic	Single Low Side Switch	Two Inductors High Switch Voltage	< 75W	90%
Flyback	Single Low Side Switch	Coupled Inductors High Switch Voltage	< 75W	88%
2-Switch Buck-Boost	Single Inductor	Diode Rectifier High Switch Current	< 25W	90%
4-Switch Buck-Boost	Single Inductor Synch Rectifier	Limited Controllers Compensation	25 - 250W	96%

4-SWITCH BUCK-BOOST OPERATION

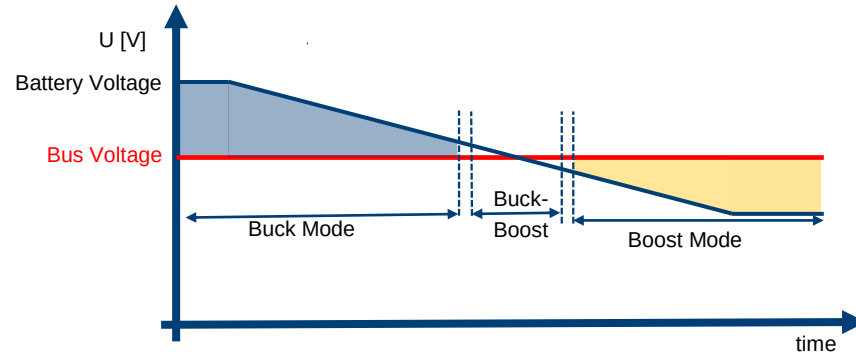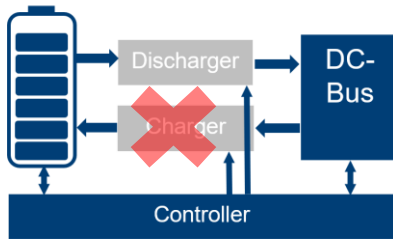- ▶ A Varying Input Voltage Drives The Converter Into 3 different Operating Modes (Unidirectional)
 - Buck Mode ($U_{in} \gg U_{out}$)
 - Boost Mode ($U_{in} \ll U_{out}$)
 - Buck-Boost/Transition Mode ($U_{in} \leq U_{out}$ & $U_{in} \geq U_{out}$)



- ▶ Battery Simulation Product Is Very Helpful To Simplify Your Validation


4-SWITCH BUCK-BOOST TOPOLOGY

► High-Side Switches

Provide Two Functions



► Low-Side Switches

Provide Only One Function

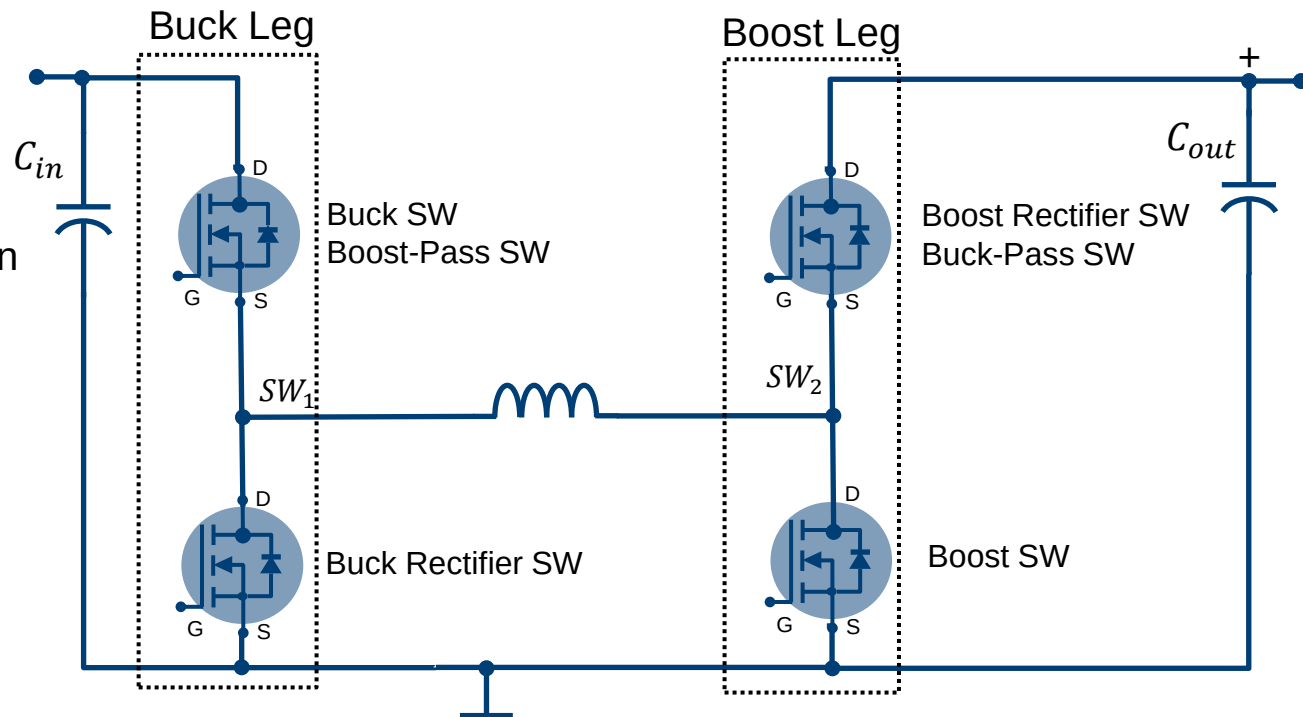



BUCK-MODE

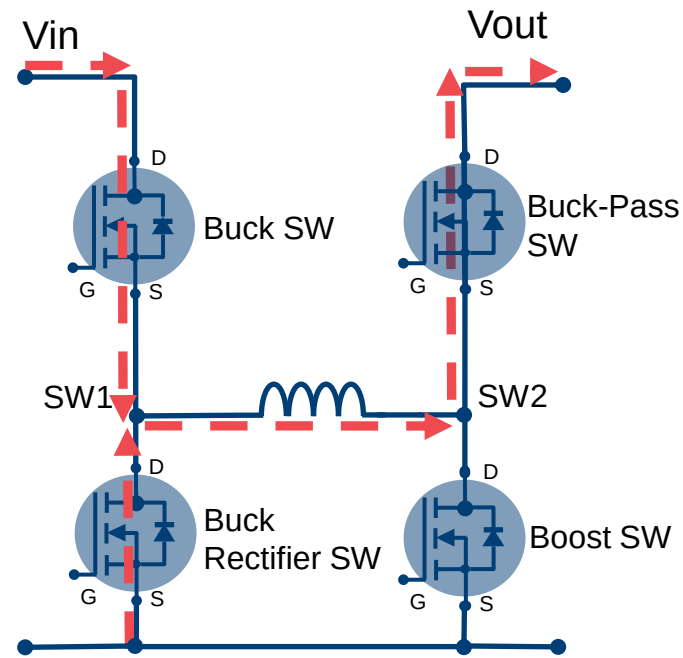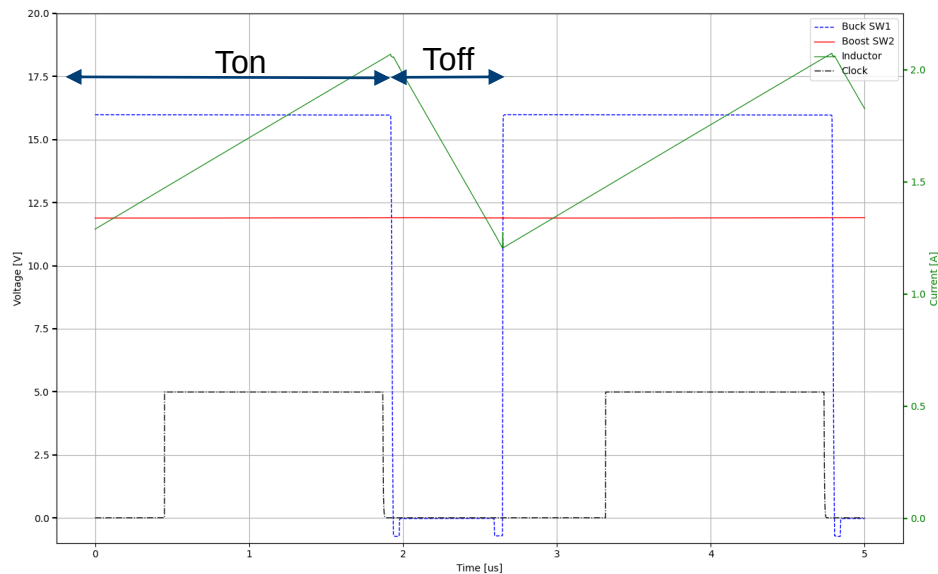- Condition $V_{in} \gg V_{out}$
- Switching Pattern Like Simple Buck





BOOST-MODE

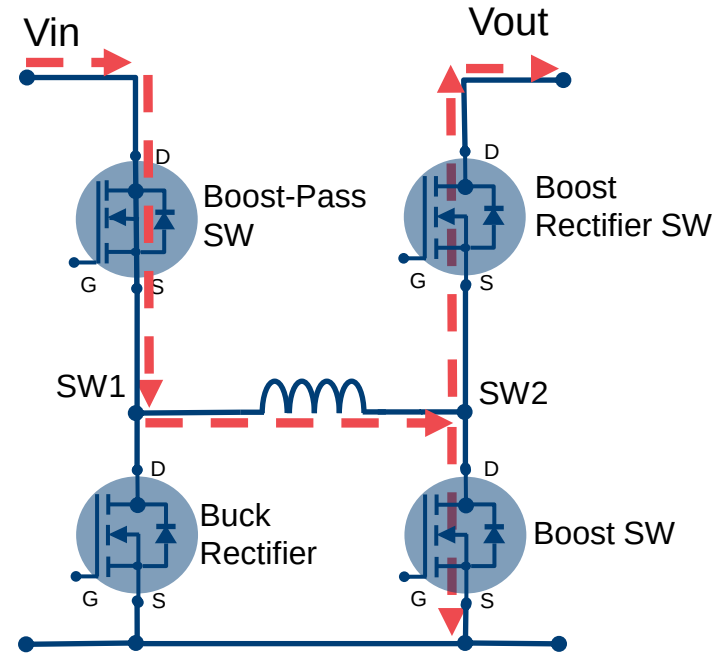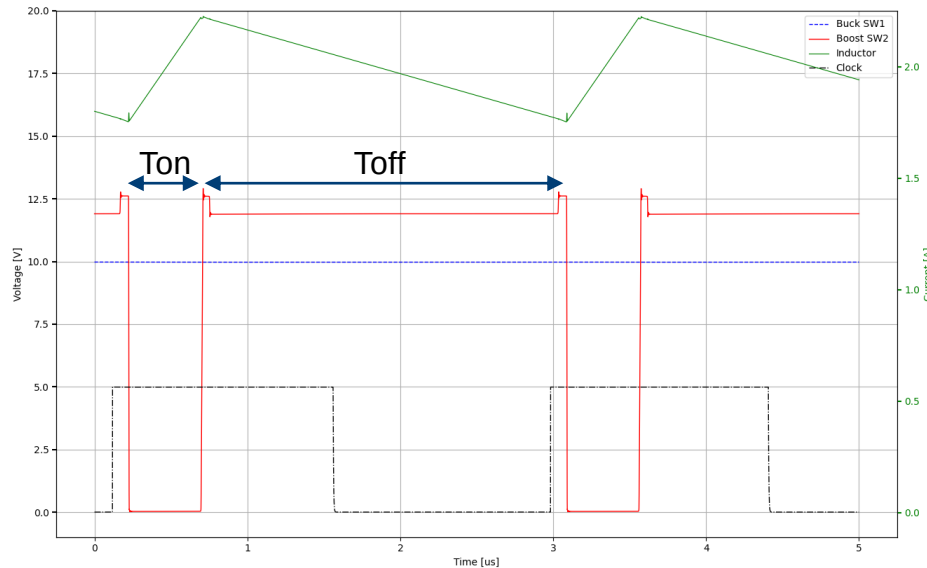- Condition $V_{in} \ll V_{out}$
- Switching Pattern like Simple Boost





BUCK-BOOST (TRANSITION MODE BUCK)

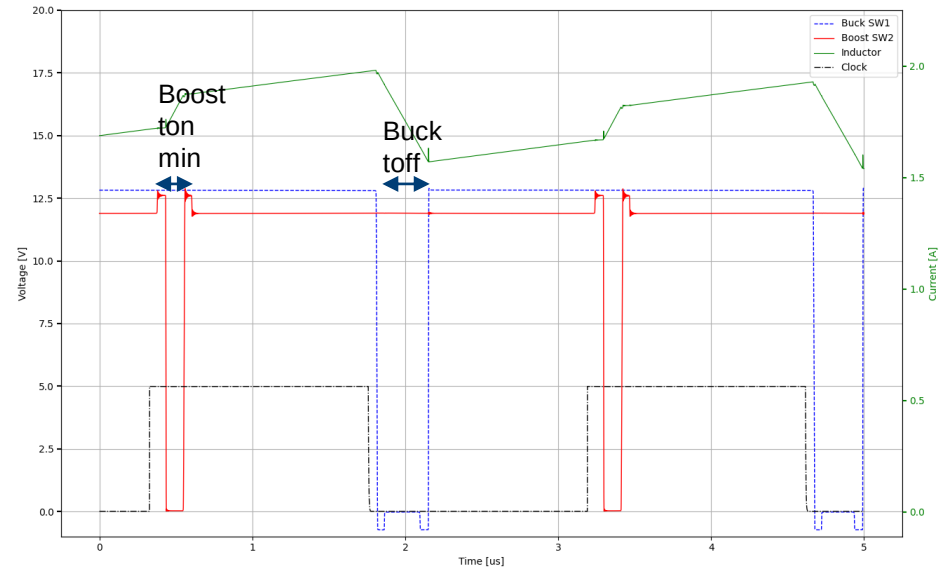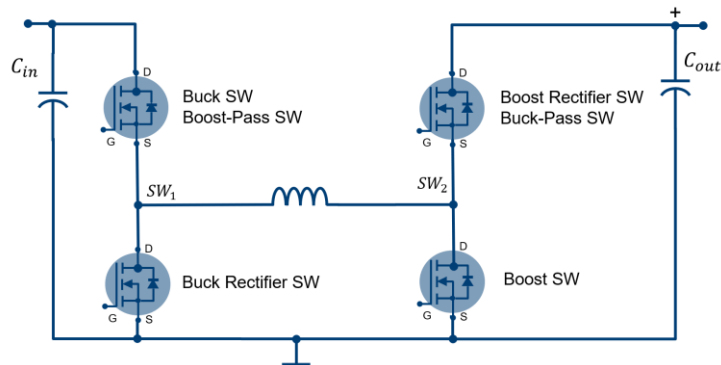- ▶ Transition Mode ($U_{in} \geq U_{out}$)
- ▶ Alternating Interleaved Buck and Boost Cycles
- ▶ Boost On Time Is Fixed At Minimum
- ▶ Buck Function Is Active




BUCK-BOOST (TRANSITION MODE BOOST)

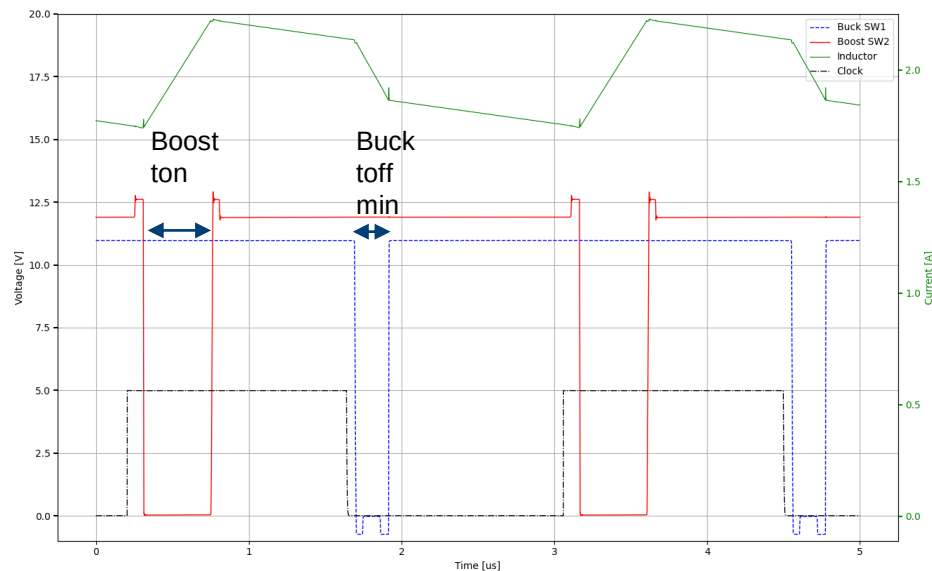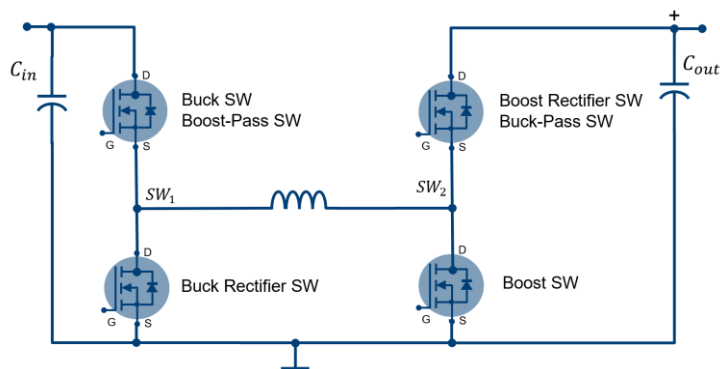- Transition Mode ($U_{in} \leq U_{out}$)
- Alternating Interleaved Buck and Boost Cycles
- Buck Off Time Is Fixed At Minimum
- Boost Function Is Active



4-SWITCH BUCK-BOOST DEVELOPMENT BOARD

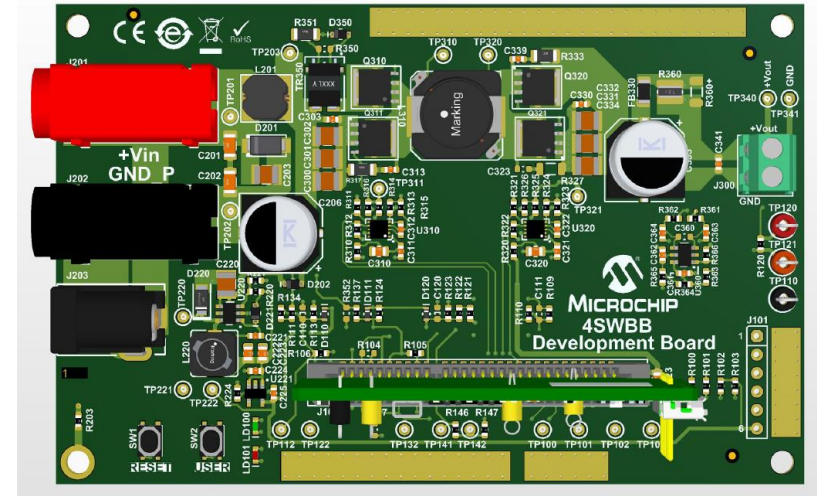- ▶ Nominal Operating Input Voltage: $8V < V_{in} < 18V$
- ▶ Output Power Max: 20W
- ▶ Output Current Max: 2A
- ▶ Output Voltage Max: 20V
- ▶ Typical Output Voltage: 12V
- ▶ Efficiency: 90% (Auxiliary Supply, EMI Filter)
- ▶ Protection Mechanism:
 - Over Voltage Detection
 - Under Voltage Detection
 - Over Current Detection
 - Etc.




www.microchip.com/en-us/development-tool/ev44m28a

Only Buck-Boost Mode Implemented In Firmware!!!


SWITCHING PATTERN VERIFICATION

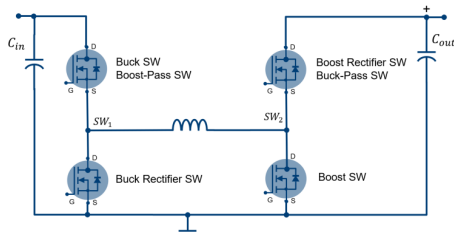- $U_{in} \approx U_{out}$
- $U_{in} > U_{out}$
- $U_{in} < U_{out}$




SWITCHING PATTERN ANOMALY

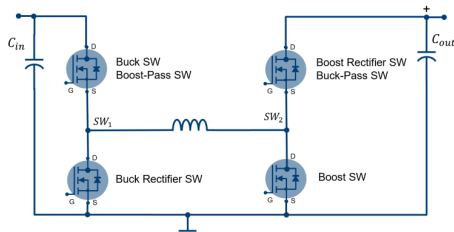- $U_{in} \approx U_{out}$
- Boost Rectifier Switch Does Not Switch
- It Happens At Smaller Output Current



PRE-RECORDED VIDEO OF SWITCHING PATTERN

 

SWITCH NODE ANALYSIS


► 2 x Switch Node (SW1 & SW2)

- Overshoot
- Ringing
- Rise and Fall Time

► 4 x Gate Source Measurements

- Ringing
- Gate Level
- Dead Time

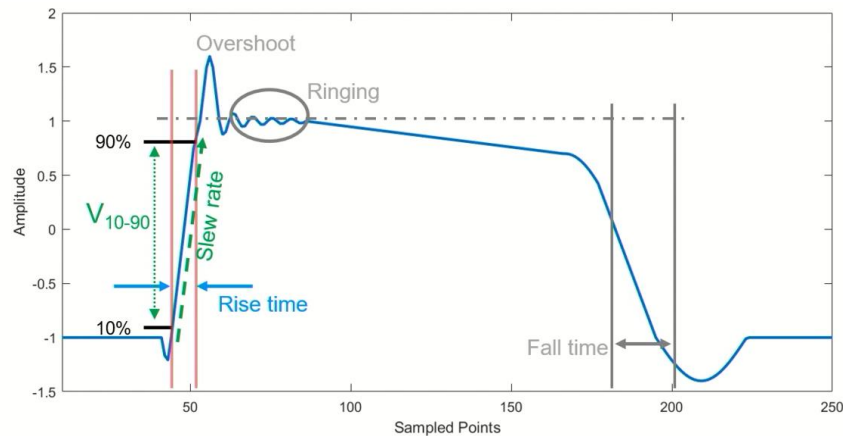► Correlation to Frequency Domain Can Be Useful





SWITCH NODE MEASUREMENTS

- Over and Undershoot At Switch Nodes
- Rise Time and Fall Time At Switch Nodes
- Switch Node Ringing Measured By Cursor
- Dead Time Between Buck & Boost Leg (Gates)



BATTERY MODEL CREATION

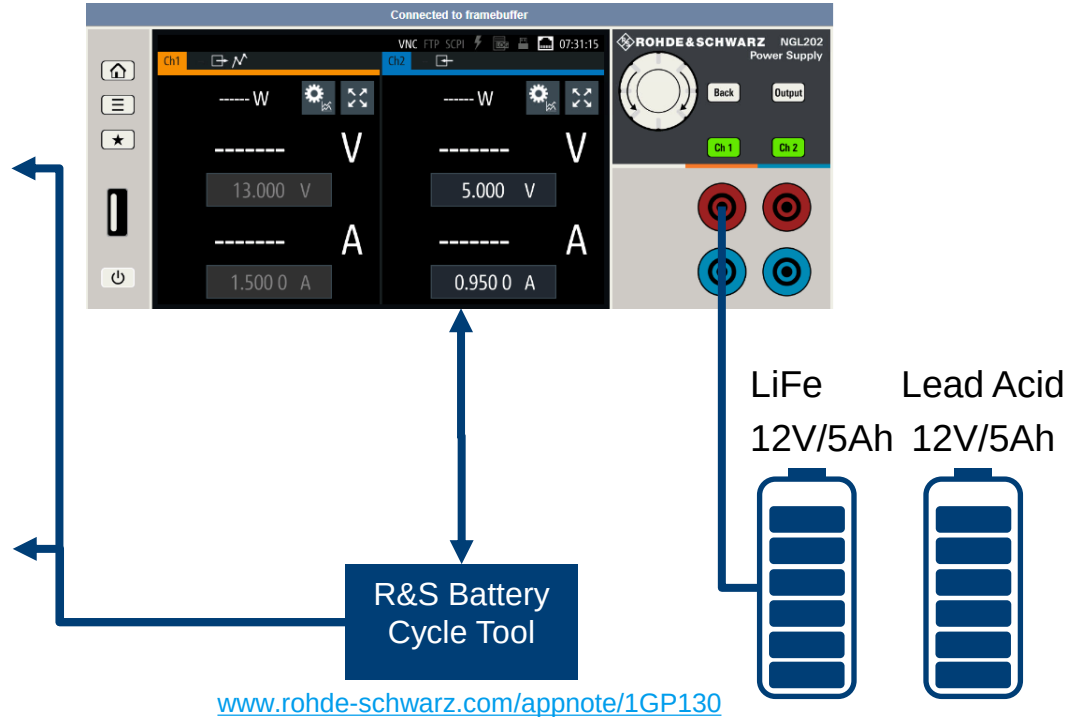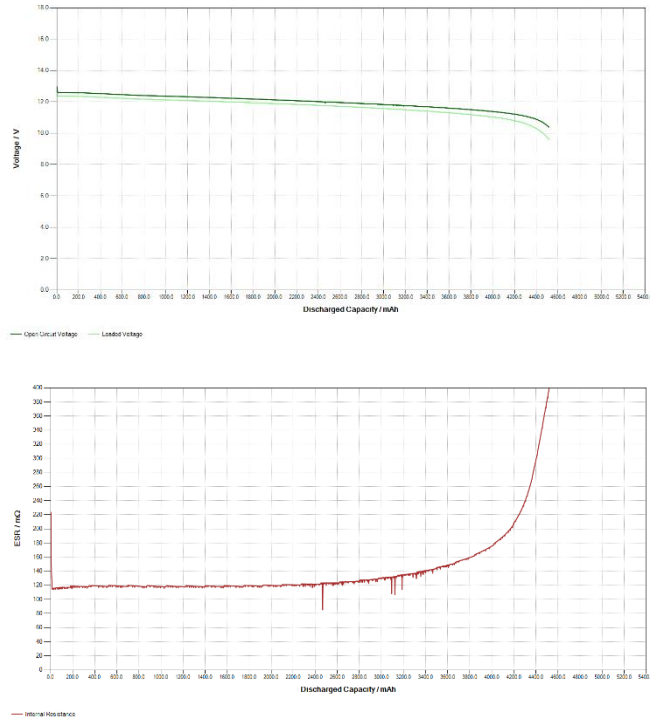

SYSTEM SETUP EXAMPLE




Verification That Output Voltage Is Stable Over The Complete Discharge Cycle

Window Trigger
(11,5V - 12,5V)

Trigger In
(Digital IO)

R&S
Battery
Model

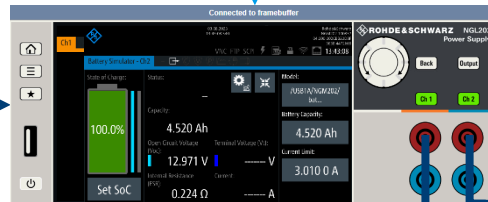

Vin
8V-14V

DUT
(Buck-Boost
Converter)

Vout
12V/1,7A

CONCLUSION

- ▶ 4-Switch Buck-Boost Is A Suitable Topology For Battery Applications, Where The Input Voltage Varies And A Bidirectional Flow Is Required
- ▶ An Oscilloscope Like the MXO58 Is A Great Tool To Verify The Converter Design Regarding Switching Pattern And Switching Analysis Efficiently
- ▶ An Instrument Like the NGM202 Can Create Battery Models And Simulate Batteries Avoiding Any Real Battery → Very Efficient And Reproducible Verification
- ▶ The NGM202 Can Be Use As Electronic Load To Program Any Load For The Converter
 - Including The Trigger In/Out Capability, This Enables The User To Verify The System Fully Automatically

ROHDE & SCHWARZ

Make ideas real

